RACTICAL
ELECTRONICS
ARCH 1975 30p

55¢

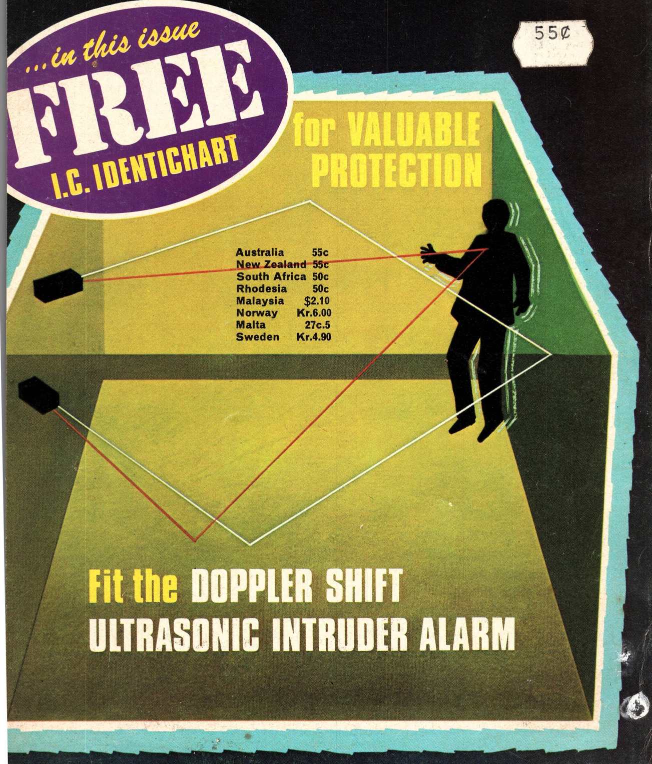

...in this issue

FREE

I.C. IDENTICHART

for VALUABLE PROTECTION

Australia	55c
New Zealand	55c
South Africa	50c
Rhodesia	50c
Malaysia	$2.10
Norway	Kr.6.00
Malta	27c.5
Sweden	Kr.4.90

Fit the DOPPLER SHIFT ULTRASONIC INTRUDER ALARM

NEW EDU·KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

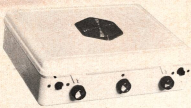

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN—PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3¼″ Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 55p (free with parts)

TOTAL BUILDING COSTS

£7·23 (+8% VAT 57p) **P.P. & Ins. 44p (Overseas Seamail P. & P. £2·35)**

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

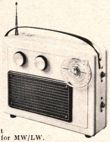

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½in × 7in × 2¾in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6·95** (+8% VAT 55p) **P.P. & Ins. 44p (Overseas Seamail P. & P. £2·35)**

POCKET FIVE

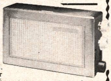

NOW WITH 3″ LOUDSPEAKER

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½in × 1½in × 3½in approx. Plans and parts price list free with parts.

Total Building Costs

£2·50 (+8% VAT 20p) **P.P. & Ins. 36p (Overseas Seamail P. & P. £1·70)**

TRANSONA FIVE NOW WITH 3″ LOUDSPEAKER

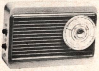

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list free with parts.

Total Building Costs

£2·75 **P.P. & Ins. 36p** (+8% VAT 21p) **(Overseas Seamail P.&P. £1·70)**

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, **and now with 3″ loudspeaker.** Attractive case with red speaker grille. Size 9in × 5¼in × 2¾in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£2·95** (+8% VAT 23p) **P.P. & Ins. 36p (Overseas Seamail P. & P. £1·70)**

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3″ loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£3·60** (+8% VAT 29p) **P.P. & Ins. 36p (Overseas Seamail P. & P. £1·70)**

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3″ Loudspeaker. Parts price list and easy build plans free with parts.

TOTAL BUILDING COSTS **£4·08** (+8% VAT 32p) **P.P. & Ins. 38p (Overseas Seamail P. & P. £2·00)**

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4″ 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6·98** (+8% VAT 56p) **P.P. & Ins. 47p (Overseas Seamail P. & P. £2·50)**

ROAMER TEN Mk. II

WITH VHF INCLUDING AIRCRAFT

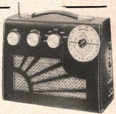

Now with free earpiece and switched socket.

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND

Latest 4″ 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in × 7in × 4in. Easy to follow instructions and diagrams. Parts price list and plans **50p** (FREE with parts).

TOTAL BUILDING COSTS **£9·50** (+8% VAT 76p) **P.P. & Ins. 52p (Overseas Seamail P. & P. £2·50)**

EDU-KIT

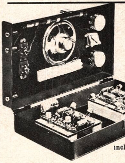

Build Radios Amplifiers, etc., from easy stage, diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3″ moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ½in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£5·50** (+8% VAT 44p) **P.P. & Ins. 40p (Overseas Seamail P. & P. £2·35)**

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

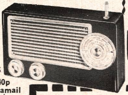

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW. and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

TOTAL BUILDING COSTS

£4·48 (+8% VAT 36p) **P.P. & Ins. 40p (Overseas Seamail P. & P. £1·25)**

ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT 6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Plans and parts price list free with parts.

TOTAL BUILDING COSTS

£3·98 (+8% VAT 32p) **P.P. & In. 40p (Overseas Seamail P. & P. £2·00)**

RADIO EXCHANGE LTD

*Callers side entrance "Lavells" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 ISA
Tel. 0234 52367 Reg. No. 788372

I enclose £ .... for ....

Name ....

Address ....

PE3

PRACTICAL
ELECTRONICS
VOLUME 11 No. 3 MARCH 1975

CONSTRUCTIONAL PROJECTS

ULTRASONIC DOPPLER SHIFT INTRUDER ALARM *by J. B. Dance*
Protect your home with this easy to construct security system 206

P.E. MINISONIC—5 *by G. D. Shaw*
This concluding article deals with making the most of the Minisonic 212

IN-CIRCUIT OHMMETER *by O. N. Bishop*
For measuring the resistance of a component without having to remove it from the circuit 228

ELECTRONIC THERMOSTAT *by R. A. Penfold*
An accurate temperature controller particularly suitable for photographic work 236

GEIGER COUNTER *by M. Plant*
Detect radioactive minerals with this portable pocket radiation monitor 242

GENERAL FEATURES

SWITCHING POWER SUPPLIES 223

INGENUITY UNLIMITED
Touch-Switch—Two-way Morse Trainer—Transistor Tester—Lighting Control Circuit 219

NEWS AND COMMENT

EDITORIAL—On Guard 205

SPACEWATCH *by Frank W. Hyde*
Pioneer 11—Red Spot—Radio Waves from Earth 216

POINTS ARISING
P.E. Orion—P.E. Minisonic 3—Digital Leaf—Marine Speedometer 220

NEWS BRIEFS
New Loudspeaker—New Year Award—Ipswich News 233

MARKET PLACE
Loudspeaker Kit, P.E. Orion, Digital Leaf and New Transistors 234

BOAT SHOW '75
Electronics for the mariner at this year's show 239

ELECTROMUSE *by Malcolm Pointon*
Setting-up and composing electronic music 241

INDUSTRY NOTEBOOK *by Nexus*
What's happening inside industry 245

PATENT REVIEW
Thought provoking ideas on file at the British Patents Office 248

READOUT
More on Boolean breakfast 249

SPECIAL FREE DATA SHEET INSIDE THIS ISSUE
I.C. IDENTICHART
An easy-to-read directory of over 450 integrated circuits

CEEFAX and ORACLE
Part 2 of this article will appear next month

Our April issued will be published on Friday, March 14, 1975

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year. Inland £3·85, Overseas £4·70. USA and Canada $13·00. International Giro facilities Account No. 5122007. State reason for payment, "message to payee".

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND – VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System – with a big plus over all the other kits – the PE Scorpio Kit is designed for *both* positive and negative ground automotive electrical systems. Not just +ve ground. Nor just —ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

★ Easier starting from cold ★ Firing even with wet or oiled-up plugs ★ Smoother running at high speed ★ Fuel saving ★ More power from your engine ★ Longer spark plug life ★ No more contact-breaker burn.

Electro Spares prices:
De luxe Kit only £10·85 inc. VAT and p & p.
Ready Made Unit £13.65 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components – pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results – or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price **only £28.50 inc. VAT and p & p.**

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is —3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from **£50 to £60 inc. VAT and p & p.**

★ All components as specified by original authors, and sold separately if you wish.

★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.

★ Price List only. Please send S.A.E. (preferably 9 × 4 minimum) for full details.

ELECTRO SPARES

The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888

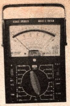

MULTIMETER Model C-7081 GN Range Doubler 50,000 ohm/volt High Sensitivity Meter **£14·40.** 20p P. & P.

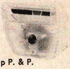

TAPE RECORDER LEVEL METER

500μA, **70p.** 5p P. & P.

CARDIOID DYNAMIC MICROPHONE

del UD-130. Fre-ency response 50–000c/s. Impedance al 50K and 600 ohms, 55. 11p P. & P.

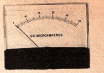

4¼in × 3¼in METER. 30μA, 50μA or 100μA, **£3·85.** 11p P. & P.

MULTI-METER

Model D62
20,000 ohm/volt, **£7·65.**
15p P. & P.

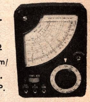

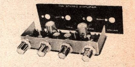

3 WATT STEREO AMPLIFIER

£4·30. 10p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ENGINEERS FREE YOURSELF FOR A BETTER JOB WITH MORE PAY!

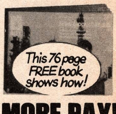

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This guide to success should be read by .y ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobdy will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

POST NOW

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Practical Radio and Electronics (Technatron) ☐
Electronic Engineering ☐
Television Maintenance and Servicing ☐
General Radio and TV Engineering ☐
Radio Servicing, Maintenance and Repairs ☐

C. & G. Radio, TV Electronics, Mechanics ☐
Radio Amateurs ☐
Practical TV ☐
Colour Television ☐
Computer Electronics ☐
C. & G. LI Radio TV Servicing cert. ☐
Post Master General 1st & 2nd class certs. ☐
C. & G. Electrical Engineering Practise ☐

C. & G. LI Installations and Wiring ☐
General Electrical Engineering ☐
Society of Engineers (Electrical Engineering) ☐
Electrical Installations and Wiring ☐
C. & G. Electrical Technicians (Primary) ☐
C. & G. Telecommunications ☐

To ALDERMASTON COLLEGE
Dept. EPE03, Reading RG7

NAME (Block Capitals Please) ....
ADDRESS ....
.... POSTCODE ....
Other subjects .... Age ....

Accredited by C.A.C.C.
Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

MAPLIN ELECTRONIC SUPPLIES

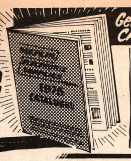

Get your 1975 CATALOGUE!

Includes dozens of useful and interesting circuits you can build: data: hundreds of pictures: transistor equivalents list and hundreds of new lines. Packed with information. ONLY 35p.

SUPERSONIC SAME-DAY-SERVICE – MEANS QUALITY COMPONENTS – FAST!

● RESISTORS

CARBON FILM

¼W 1Ω–1MΩ: 5%, 1MΩ–10MΩ: 10% E12.
½W 1Ω to 10Ω: 5%, IMΩ to 10MΩ: 10% E12
11Ω to 910kΩ: 5% E12 and E24 **1p** each.

METAL OXIDE

½W 10Ω to 1MΩ: 2% E12 and E24 **4p** each.

WIREWOUND

3W 0·22Ω, 0·27Ω, 0·33Ω, 0·47Ω: 10%: 1Ω: 5% **17p** each.
1·2Ω to 270Ω: 5% E12 **13p** each.
Other ranges stocked. See our catalogue for details.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades. E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

● POTENTIOMETERS

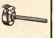

Rotary miniature carbon track ¼in spindle.
Values available: 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
Log. Single-gang **16p.** Lin. Single-gang (+1kΩ) **16p.**
Log. or Lin. Single-gang with switch **33p.**
Log. or Lin. Dual-gang without switch **49p.**

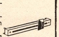

Slider 60mm track. Metal-cased: overall length 86·15mm (knob 7p extra).
Log. or Lin. Single-gang 1kΩ, 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, **36p** each.
Log. or Lin. Dual-gang 1kΩ, 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, **45p** each.

Presents: 0·1W vert. or hor. 100Ω, 220Ω, 470Ω, 1kΩ, 2.2kΩ, 4·7kΩ, 10kΩ, 22kΩ, 47kΩ, 100kΩ, 220kΩ, 470kΩ, 1MΩ **7p** each.

● CAPACITORS

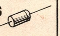

Sub-miniature
Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price	Mfd	V	Price
1	63	**6p**	47	63	**6p**	330	16	**14p**
1·5	63	**6p**	68	6·3	**6p**	330	63	**28p**
2·2	63	**6p**	68	16	**6p**	470	6·3	**6p**
3·3	63	**6p**	68	63	**14p**	470	10	**14p**
4·7	63	**6p**	100	4	**6p**	470	25	**16p**
6·8	40	**6p**	100	10	**6p**	470	40	**25p**
6·8	63	**6p**	100	25	**6p**	680	6·3	**14p**
10	25	**6p**	100	40	**6p**	680	16	**16p**
10	63	**6p**	100	63	**16p**	680	25	**25p**
15	16	**6p**	150	6·3	**6p**	680	40	**28p**
15	40	**6p**	150	16	**6p**	1000	4	**14p**
15	63	**6p**	150	25	**6p**	1000	10	**16p**
22	10	**6p**	150	40	**14p**	1000	16	**25p**
22	25	**6p**	150	63	**16p**	1000	25	**28p**
22	63	**6p**	220	4	**6p**	1500	6·3	**16p**
33	6·3	**6p**	220	10	**6p**	1500	10	**25p**
33	16	**6p**	220	16	**6p**	1500	16	**28p**
33	40	**6p**	220	25	**14p**	2200	6·3	**25p**
47	4	**6p**	220	40	**16p**	2200	10	**28p**
47	10	**6p**	220	63	**25p**	3300	6·3	**28p**
47	25	**6p**	330	4	**6p**	4700	4	**28p**
47	40	**6p**	330	10	**6p**			

● SWITCHES

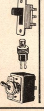

Rotary adjustable stop. 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way **36p** each. Slide Sub-min. DPDT **9p.** Slide min. DPDT **13p.** Push to make non-locking SPST **14p.** Push-on, push-off locking DPDT 250V 4A **48p.** Rocker white DPST 250V 10A **40p.** Rotary mains DPST 250V 2A **20p.** Toggle with on/off plate DPDT 250V 1·5A **25p.**

● TRANSISTORS AND DIODES

AC127	**18p**	BY126	**13p**
AC128	**18p**	BY127	**13p**
AC176	**17p**	BY164	**49p**
AD161/162MP	**93p**	BZY88 series	**13p**
BA100	**9p**	MPF102	**36p**
BA145	**22p**	OA91	**6p**
BC107	**10p**	OA200	**7p**
BC108	**10p**	OC71	**20p**
BC109	**13p**	SC146D	**88p**
BC109C	**15p**	T1S43	**28p**
BC142	**23p**	WOO5	**30p**
BC143	**26p**	WO4	**33p**
BC147	**10p**	1N914	**4p**
BC148	**10p**	1N4001	**6p**
BC149	**12p**	1N4002	**6½p**
BC168C	**12p**	1N4003	**7p**
BC169C	**12p**	1N4004	**7½p**
BC178	**17p**	1N4005	**8p**
BC182L	**10p**	1N4006	**8½p**
BC183L	**12p**	1N4007	**9p**
BC184L	**12p**	1N4148	**4p**
BC212L	**14p**	2N1302	**20p**
BC213L	**15p**	2N1303	**20p**
BC214L	**18p**	2N1304	**30p**
BCY71	**22p**	2N1711	**24p**
BD131	**45p**	2N2219	**25p**
BD132	**54p**	2N2646	**45p**
BD131/2MP	**£1·20**	2N2905	**33p**
BD135	**36p**	2N2926 Or, Ye, or Gn	**10p**
BD139	**49p**	2N3053	**18p**
BD140	**69p**	2N3055	**49p**
BF258	**35p**	2N3819	**22p**
BF259	**25p**	2N5459	**51p**
BFX29	**30p**	7400	**16p**
BFX30	**33p**	7413	**39p**
BFX84	**30p**	7447	**£1·10**
BFX85	**36p**	7473	**54p**
BFX87	**30p**	7474	**45p**
BFX88	**25p**	7490	**93p**
BFY50	**20p**	7493	**93p**
BFY51	**22p**	74121	**39p**
BFY52	**20p**		

L.E.D. RED

2mcd ¼in	**15p**
Panel mtg. clip	**5p**

(Other colours and 7-seg. displays in our catalogue)

● INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	**69p**
LH0042CH (TO99)	**£4·25**
MC1310P (14-pin DIL)	**£2·50**
MC1496 (14-pin DIL)	**95p**
MFC4000B	**59p**
MFC6040	**83p**
NE555V (8-pin DIL)	**65p**
SG1495 (14-pin DIL)	**£2·70**
SG3402 (14-pin DIL)	**£1·69**
µA741C (8-pin DIL)	**36p**
µA741C (14-pin DIL)	**45p**
µA747C (14-pin DIL)	**£1·05**
µA 748C (8-pin DIL)	**39p**
ZN414 (TO18)	**£1·20**

VOLTAGE REGULATORS

µA7805 5V 1·5A (TO3)	**£1·75**
µA7815 15V 1·5A (TO3)	**£2·30**
MVR 5V, 12V, 15V, 500mA (TO3)	**£1·60**
µA78M05 5V 500mA	**£1·30**
µA78M15 15V 500mA	**£1·30**
µA78L05 5V 100mA (TO92)	**60p**
µA78L15 15V 500mA (TO92)	**60p**
µA723C Variable 2 to 37V (TO99 or 14-pin DIL)	**75p**

Our catalogue contains application circuits and data for all the above I.C.s and many more.

DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

BCD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue **£1·38.**

● PLUGS AND SOCKETS

Din	Plug	Chassis Socket
2-pin	**8p**	**6p**
3-pin	**9p**	**7p**
4-pin	**10p**	**7p**
5-pin A (180°)	**10p**	**7p**
5-pin B (240°)	**10p**	**7p**
6-pin	**10p**	**9p**

JACK PLUGS

2·5mm Plastic Barrel	**9p**
2·5mm Metal Barrel	**15p**
3·5mm Plastic Barrel	**9p**
3·5mm Metal Barrel	**15p**
¼in Std. Mono Plastic Barrel	**13p**
¼in Std. Mono Metal Barrel	**24p**
¼in. Std. Stereo Plastic Barrel	**18p**
¼in Std. Stereo Metal Barrel	**30p**

JACK CHASSIS SOCKETS

2·5mm open-type metal	**9p**
3·5mm open-type metal	**9p**
¼in Std. Mono open-type metal	**10p**
¼in Std. Mono moulded with 2 break contacts	**14p**
¼in Std. Stereo open-type metal	**15p**
¼in Std. Stereo moulded with 3 break contacts	**18p**

In-line sockets of all above types.

PHONO

Plastic-topped plug	**5p**
Screened plug	**12p**
Chassis socket single	**4p**
Chassis socket twin	**6p**

● MAINS CONNECTORS

P360 3-pin 1·5A Chassis plug with line socket	**30p**
SA2190 3-pin 5A Chassis plug	**22p**
SA1862 Line socket for SA2190	**25p**
P437 3-pin 5A Chassis socket with line plug	**55p**

● TRANSFORMERS

LT700 min. output. Pri. 1kΩ; Sec. 5Ω 200mW **50p;** Sub-min mains 6–0–6V 100mA **95p,** 12–0–12V 50mA **95p** (Size both approx. 30 × 27 × 25mm).
Min. mains 0–6V 500mA, 0–6V 500mA **£1·36;** 0–12V 250mA, 0–12V 250mA **£1·36;** 0–20V 150mA, 0–20V 150mA **£1·36;** 0–24V 125mA, 0–25V 125mA **£1·36.**
Mains MT3AT: Sec: 12–15–20–24–30V 2A **£3·60.**
Mains MT206AT: Sec: 0–15–20V 1A, 0–15–20V 1A **£3·98.**

● ORGANS

A Full Scale Electronic Organ That You Can Build To Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS.

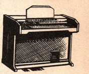

Leaflet MES51: Price **15p,** describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
Leaflet MES52: Price **5p** continues the description of the MES50 series organs and shows you how to add a second keyboard with lots more stops.

● THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4kΩ to 8kΩ (highest) or 2kΩ to 4kΩ or 1kΩ to 2kΩ, etc. right down to 16Hz to 32Hz! And this new compatible design is even smaller: only 3·5in × 3·7in including gold-plated edge connection.
DMO2T includes built in variable depth and rate frequency shift tremulant.
DMO2 **£12·25** DMO2T **£14·25**
SAJ110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. **£1·80** each or 6 for **£9·94** or 12 for **£18·16.**
Keyboards high quality, fully sprung.

Flat-front 48-note F to E	**£15·95**
Sloping-front 49-note C to C	**£15·95**
Sloping-front 61-note C to C	**£20·44**
Swell pedal with 10kΩ log. pot	**£5·93**
*Spring Line Unit (short)	**£3·05**
*Spring Line Unit (long)	**£7·59**
*Reverberation Driver Module	**£5·34**

*S.A.E. please for full details: leaflet MES24.

Gold-clad phosphor-bronze wire	**30p** per yd
Palladium earth bar	**15p** per octave length
Contact Blocks 2-make (GB2)	**22p**
Stop Tabs rocker type not engraved (white, red. grey or black) with DPDT switch	**49p**

SPECIAL OFFER

5W Audio Amp I.C. TBA810S with data and circuits.

Price £1·00

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESISER

We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.s, metalwork and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.A.E. please for price list and specification. We also stock all parts for the P.E. Synthesiser, and Minisonic.

P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea (0702) 44101

VAT Please add 8% to the final total. Post and Packing FREE in U.K. (15p handling charge on orders under £1)

First-class post pre-paid envelope supplied free with every order.

R T V C FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM

*

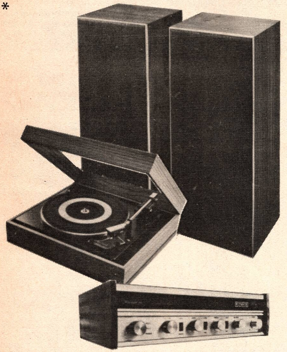

System 1. £51·00

40 Watt Amplifier. Viscount III – R102 now 20 watts per channel.
System I includes:
Viscount III amplifier – volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0·1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within + 1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: + 12dB to –17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble + 12dB to –12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) – 58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. $13\frac{3}{4}$″ × 9″ × $3\frac{3}{4}$″.

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers – Enclosure size approx. $17\frac{1}{2}$″ × $10\frac{3}{4}$″ × 6″ in simulated teak. Drive unit 13″ × 8″ with parasitic tweeter. 10 watts handling.

Complete System £51·00

System 2. £69·00

Viscount III amplifier (As System I)
Garrard SP 25 Mk III deck (As System I)
Two Duo Type III matched speakers – Enclosure size approx. 27″ x 13″ x $11\frac{1}{2}$″
Finished in teak veneer. Drive units 13″ x 8″ bass driver, and two 3″ (approx.) tweeters.
20 watts R.M.S., 8 ohms frequency range — 20 Hz to 18,000 Hz.

Complete System £69·00

PRICES: SYSTEM 1	
Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total: £59.20	
Available complete for only:	**£51·00 + £3.50 p & p**

PRICES: SYSTEM 2	
Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total: £84.20	
Available complete for only:	**£69·00 + £4.00 p & p**

STEREO 21 *QUALITY SOUND FOR LESS THAN £20·00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes:– **BSR 3 speed deck**, automatic, manual facilities together with stereo cartridge.
Two speakers with cabinets.
Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.
Specifications: For the technically minded:—
Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs – radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. $15\frac{1}{2}$″ × 8″ × 4″. Complete deck and cover in closed position approx. $15\frac{1}{2}$″ × 12″ × 6″.

Complete only **£19·95 + £1.60 p & p. Extras if required.** Optional Diamond Styli **£1.37.**
Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, **£3.85.**

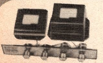

BUILD YOUR OWN * STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7·64+55p p & p Also available with 2 speakers (7″ × 4″) **£9·00** + 75p p. & p.

8 TRACK HOME CARTRIDGE PLAYER

*

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV Comparable unit sold eleswhere at £24.00 approx. **Yours for only**

£11.95 + 90p p & p.

PUSH BUTTON CAR RADIO KIT* ~ The Tourist II

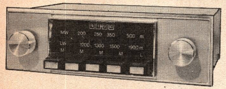

NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) **Integrated circuit** output stage, pre-built three stage IF Module. **Controls volume** manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4¾" deep approx **£7.70 + 55p. p & p.**

Speaker including baffle and fixing strip **£1.65 + 23p. p & p.**

Car Aerial Recommended—fully retractable **£1.37 + 20p. p. & p.**

The Tourist I Kit For the experienced constructor If you can solder on a printed circuit board you can build this model.
Same technical specification as Tourist II **Price £6.60 + 55p p & p.**

EMI SPEAKERS AT FANTASTIC REDUCTIONS

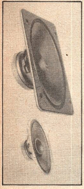

20 WATT SPEAKER SYSTEM ✱

System consists of a 13" × 8" (approx) eliptical woofer unit with a 8" × 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components. Circuit diagram.

Technical Specification:
Bass Unit
Flux density—100 K, speech coil—1½".
Cone, Triple laminated paper with P.V.C. surround.
Mid Range Unit
Flux density-33K, speech coil-1" with parasitic tweeter.
Power Handling
20 watts R.M.S., impedance—8 ohms, frequency response—20 Hz to 18,000 Hz.

OUR PRICE £6.60. Complete + 90p p & p.

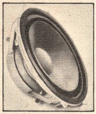

15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40·80.

OUR PRICE £18·70 + £1·50 p & p

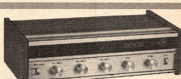

DISCO AMPLIFIER*

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.
Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).
Inputs *4 electrically mixed inputs. *3 individual mixing controls.
*Separate bass and treble controls common to all 4 inputs.
*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry.
*Attractive styling.

INPUT SENSITIVITIES –Input – 1.) Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).
–Inputs – 2), 3), 4). Medium output equipment – ceramic cartridge, tuner, tape recorder, organs, etc. – all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½"×6"×3½". **£15.00 + 60p. p & p**

PORTABLE DISCO CONSOLE *

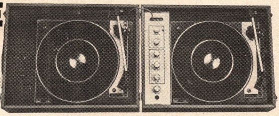

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.
The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:
Pre-amp – Output – 200mV.
Auxiliary inputs – 200mV and 750mV into 1 meg.
Mic input – 6mV into 100K. 240 volt operation.
Turntables capacity – 7", 10" or 12" records.
Rumble, wow and flutter
Rumble Better than –35dB. Wow Better than 0.2%.
Flutter Better than 0.06% (Gaumont kalee meter).
Finish – Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.
Console size –
Unit Closed – 17¾"×13¾"×8¾" (approx.)
Unit Open – 35¾"×13¾"×4⅜" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.

DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Jan. 1975 and subject to change without notice.
All prices include V.A.T. at 8% rate.

R T V C

Radio and TV Components (Acton) Ltd.

21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2

Personal Shoppers Edgware Road: 9a.m.–5.30p.m. Half day Thurs. Acton: 9.30a.m.–5p.m. Closed all day Wed.

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY

The famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed matt and brushed aluminium trim, and the Perspex cover has an easy "hinged-on, hinged-off" movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth, as above.

S.A.U.2 PICK-UP ARM

Recognised as one of today's most advanced pick-up arms it features

- Auto-bias Compensator
- Hydraulic Lowering Device
- Precision Balance
- Adjustable Head Shell

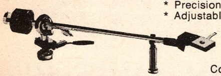

S.C.U.1 STEREO CARTRIDGE

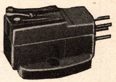

A quality cartridge designed specifically for the person who appreciates his equipment.

Contact your dealer for information or send stamp for a brochure.

A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoiseur, Brighouse

---

ERSIN

Multicore

5 CORE SOLDER

for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser

A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72

ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32

Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44

For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering tine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

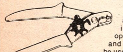

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B.80p

NEW SOLDER WICK

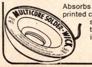

Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,
Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 15p P&P.
Prices and specifications subject to change without notice.

IP **I.L.P.** (Electronics) Ltd

SHEER SIMPLICITY!

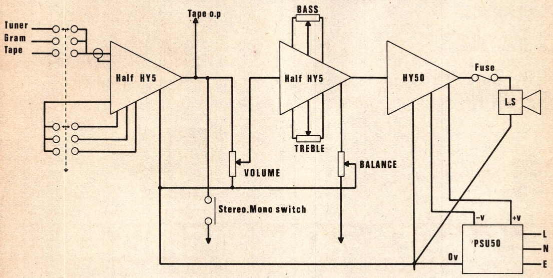

MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN

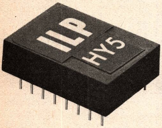

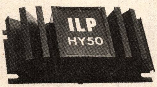

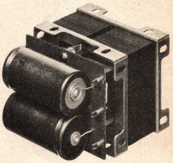

The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxillary 3–100mV; Input/impedance 47kΩ at 1kHz. **Outputs:** Tape 100mV; Main output 0db (0·775V RMS). **Active Tone Controls:** Treble ±12db at 10kHz; Bass ±12db at 100Hz. **Distortion:** 0·5% at 1kHz. **Signal/Noise Ratio:** 68db. **Overload Capability:** 40db on most sensitive input. **Supply Voltage:** ±16–25V.

PRICE £4·50 + 36p VAT
P. & P. free

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8Ω. **Load Impedance:** 4–16Ω. **Input Sensitivity:** 0db (0–775V RMS). **Input Impedance:** 47kΩ. **Distortion:** Less than 0·1% at 25W typically 0·05%. **Signal/Noise Ratio:** Better than 75db. **Frequency Response:** 10Hz–50kHz ± 3db. **Supply Voltage:** ±25V. **Size:** 105 × 50 × 25mm.

PRICE £5·98 + 48p VAT
P. & P. free

The **PSU50** incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: ±25V. **Input voltage:** 210–240V. **Size:** L.70, D.90, H.60mm.

PRICE £6 + 48p VAT
P. & P. FREE

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply ....
Total Purchase Price ....
I Enclose Cheque ☐ Postal Orders ☐ Money Order ☐
Please debit my Access account ☐ Barclaycard account ☐
Account number ....
Name and Address ....
Signature ....

If you're interested in electronics You'll like the NEW LITESOLD SUPER IRONS

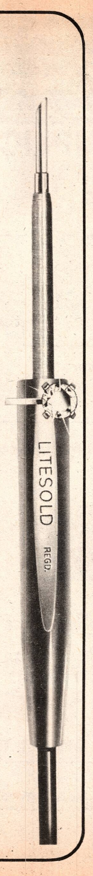

We've been supplying the electronics industry with soldering irons for many years and we have now put all our experience into an iron for the electronics enthusiast.

The new LITESOLD SUPER IRONS have all the features you have been looking for; a neon indicator which glows only when the supply is connected correctly and the iron is safely earthed, an unbreakable nylon handle, a burn-proof mains lead, a special oxydised binding, a long life element, a range of bit shapes to suit every job and a special bench stand.

There are three SUPER IRONS

the S90
12 watts for miniature jobs
at £4.77
the S142
20 watts for medium jobs
at £4.85
the S187
24 watts for heavy jobs
at £4.89
and the special spring stand at **£2.24**.

Get your LITESOLD SUPER IRON direct from

Light Soldering Developments Limited
97-99 Gloucester Road
Croydon Surrey
Telephone 01-689 0574

All prices include postage, packing and VAT but not the diamond ring.

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS

SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 5p for first transistor, 1p thereafter, over ten post free. INTEGRATED CIRCUITS 6p + 1p each added

	£p
1N21	0·17
1N23	0·35
1N85	0·88
1N253	0·50
1N256	0·50
1N645	0·16
1N725A	0·20
1N914	0·06
1N4007	0·12
1S113	0·25
1S202	0·23
2G371	0·40
2G381	0·22
2G414	0·30
2G417	0·25
2N404	0·22
2N697	0·16
2N698	0·30
2N706	0·12
2N706A	0·12
2N708	0·15
2N709	0·40
2N1091	0·55
2N1131	0·25
2N1132	0·24
2N1302	0·18
2N1303	0·18
2N1304	0·28
2N1305	0·22
2N1306	0·28
2N1307	0·28
2N1308	0·28
2N2147	0·78
2N2148	0·60
2N2160	0·78
2N2218	0·23
2N2219	0·25
2N2369A	0·16
2N2444	1·99
2N2613	0·28
2N2646	0·50
2N2904	0·20
2N2904A	0·25
2N2906	0·20
2N2907	0·23
2N2924	0·13
2N2925	0·15
2N2926	0·12
2N3054	0·48
2N3055	0·45
2N3702	0·11
2N3705	0·15
2N3706	0·11
2N3707	0·13
2N3709	0·10
2N3710	0·11
2N3711	0·11
2N3819	0·38
2N4289	0·30
2N5027	0·53
2N5088	0·33
2S301	0·59
2S304	1·15
2S501	0·75
2S703	1·00
AA129	0·20
AAZ12	0·75
AAZ13	0·12
AC107	0·51
AC126	0·25
AC127	0·25
AC128	0·15
AC187	0·21
AC188	0·20
ACY17	0·40
ACY18	0·27
ACY19	0·27
ACY20	0·22
ACY21	0·22
ACY22	0·16
ACY27	0·25
ACY28	0·25
ACY39	0·78
ACY40	0·22
ACY41	0·22
ACY44	0·32
AD140	0·50
AD149	0·50
AD161	0·44
AD162	0·44
AF106	0·30
AF114	0·25
AF115	0·25
AF116	0·25
AF117	0·24
AF118	0·57
AF119	0·20
AF124	0·30
AF125	0·30
AF126	0·30
AF127	0·30
AF139	0·41
AF178	0·55
AF179	0·65
AF180	0·55
AF181	0·50
AF186	0·48
AFZ11	1·15
AFZ12	2·00
ASY26	0·25
ASY27	0·33
ASY28	0·25
ASY29	0·30
ASY36	0·25
ASY50	0·20
ASY51	0·40
ASY53	0·20
ASY55	0·20
ASY62	0·25
ASY66	0·33
ASZ21	1·00
ASZ23	0·75
AU104	1·00
AUY10	1·00
BC107	0·14
BC108	0·13
BC109	0·14
BC113	0·15
BC115	0·20
BC116	0·20
BC116A	0·23
BC118	0·20
BC121	0·20
BC122	0·20
BC125	0·68
BC126	0·65
BC140	0·55
BC147	0·10
BC148	0·08
BC149	0·10
BC157	0·14
BC158	0·12
BC160	0·63
BC169	0·14
BCY31	0·45
BCY32	0·85
BCY33	0·38
BCY34	0·45
BCY38	0·55
BCY39	1·50
BCY40	0·80
BCY42	0·30
BCY70	0·18
BCY71	0·22
BCZ10	0·60
BCZ11	0·65
BD121	1·00
BD123	1·00
BD124	0·65
BDY11	1·45
BF115	0·20
BF167	0·25
BF173	0·28
BF181	0·35
BF184	0·22
BF185	0·22
BF194	0·10
BF195	0·13
BF196	0·15
BF197	0·15
BFS61	0·25
BFS98	0·25
BFX12	0·20
BFX13	0·26
BFX29	0·28
BFX30	0·28
BFX35	0·98
BFX63	0·50
BFX84	0·25
BFX85	0·28
BFX86	0·25
BFX87	0·25
BFX88	0·24
BFY10	1·00
BFY11	0·50
BFY17	0·40
BFY18	0·45
BFY19	0·55
BFY24	0·45
BFY44	1·00
BFY50	0·21
BFY51	0·20
BFY52	0·20
BFY53	0·17
BFY64	0·36
BFY90	0·81
BSX27	0·50
BSX60	0·93
BSX76	0·18
BSY26	0·17
BSY27	0·20
BSY51	0·50
BSY95A	0·12
BSY95	0·12
BT102/500R	0·75
BTY42	0·92
BTY79/100R	0·75
BTY79/400R	1·10
BY100	0·27
BY126	0·14
BY127	0·12
BY182	0·85
BY213	0·25
BYZ10	0·45
BYZ11	0·40
BYZ12	0·40
BYZ13	0·42
BYZ15	1·25
BYZ16	0·60
BZY88	0·10
C111	0·55
CRS1/05	0·30
CRS1/40	0·45
CS4B	1·90
CS10B	3·50
DD000	0·15
DD003	0·15
DD006	0·25
DD007	0·40
DD008	0·38
GD3	0·33
GD4	0·10
GD5	0·33
GD8	0·25
GD12	0·10
GET102	0·50
GET103	0·40
GET113	0·35
GET114	0·30
GET115	0·90
GET116	0·85
GET120	0·50
GET872	0·30
GET875	0·40
GET880	0·60
GET881	0·25
GET882	0·35
GET885	0·40
GEX44	0·08
GEX45/1	0·45
GEX941	0·45
GJ3M	0·50
GJ4M	0·50
GJ5M	0·25
GJ7M	0·50
HG1005	0·50
HS100A	0·20
MAT100	0·20
MAT101	0·25
MAT120	0·20
MAT121	0·25
MJE520	0·63
MJE2955	1·27
MJE3055	0·77
MJE340	0·47
MPF102	0·40
MPF103	0·36
MPF104	0·35
MPF105	0·36
NKT128	0·45
NKT129	0·30
NKT211	0·25
NKT213	0·25
NKT214	0·24
NKT216	0·40
NKT217	0·45
NKT218	1·13
NKT219	0·33
NKT222	0·30
NKT224	0·25
NKT251	0·24
NKT271	0·20
NKT272	0·20
NKT273	0·20
NKT274	0·20
NKT275	0·25
NKT277	0·20
NKT278	0·25
NKT301	0·85
NKT304	0·75
NKT403	0·70
NKT404	0·66
NKT678	0·30
NKT713	0·30
NKT773	0·25
NKT777	0·38
OA5	0·72
OA6	0·12
OA47	0·08
OA70	0·10
OA71	0·20
OA73	0·15
OA74	0·15
OA79	0·10
OA81	0·18
OA85	0·15
OA86	0·15
OA90	0·07
OA91	0·07
OA95	0·07
OA200	0·08
OA202	0·06
OA210	0·20
OA211	0·35
OAZ200	0·50
OAZ201	0·45
OAZ202	0·45
OAZ203	0·45
OAZ204	0·45
OAZ205	0·45
OAZ206	0·45
OAZ207	0·45
OAZ208	0·40
OAZ209	0·40
OAZ210	0·40
OAZ211	0·40
OAZ222	0·45
OAZ223	0·45
OAZ224	0·45
OAZ241	0·25
OAZ242	0·15
OAZ244	0·25
OAZ246	0·15
OAZ290	0·38
OC16	1·00
OC16T	1·00
OC19	0·50
OC22	1·00
OC23	1·25
OC24	1·10
OC25	0·40
OC26	0·40
OC28	0·66
OC29	0·65
OC30	0·40
OC35	0·55
OC36	0·60
OC41	0·35
OC42	0·40
OC43	0·70
OC44	0·20
OC44M	0·17
OC45	0·20
OC45M	0·18
OC46	0·27
OC57	0·60
OC58	0·60
OC59	0·60
OC66	0·50
OC70	0·18
OC71	0·18
OC72	0·28
OC73	0·50
OC74	0·30
OC75	0·30
OC76	0·30
OC77	0·54
OC78	0·25
OC79	0·30
OC81	0·29
OC81D	0·28
OC81M	0·20
OC81DM	0·18
OC81Z	0·45
OC82	0·23
OC82D	0·25
OC83	0·27
OC84	0·30
OC114	0·38
OC122	1·00
OC123	1·10
OC139	0·40
OC140	1·14
OC141	0·80
OC169	0·20
OC170	0·30
OC171	0·30
OC200	0·54
OC201	1·00
OC202	0·90
OC203	0·55
OC204	0·65
OC205	1·00
OC206	1·10
OC207	1·00
OC460	0·20
OC470	0·30
OCP71	1·20
ORP12	0·60
ORP60	0·55
ORP61	0·48
SX68	0·20
SX631	0·45
SX635	0·55
SX640	0·75
SX641	0·75
SX642	0·60
SX644	0·85
SX645	0·85
TIC44	0·29
V15/30P	0·75
V30/201P	0·75
V60/201	0·50
V60/201P	0·75
XA101	0·10
XA102	0·18
XA151	0·15
XA152	0·15
XA161	0·25
XA162	0·25
XB101	0·43
XB102	0·30
XB103	0·35
XB113	0·30
XB121	0·43
ZS170	0·10
ZS271	0·18
ZT21	0·25
ZT43	0·25
ZTX107	0·12
ZTX108	0·08
ZTX300	0·13
ZTX304	0·24
ZTX500	0·13
ZTX503	0·16
ZTX531	0·25
INTEGRATED CIRCUITS	
7400	0·16
7401	0·16
7402	0·16
7403	0·16
7404	0·26
7405	0·22
7406	0·42
7407	0·42
7408	0·28
7409	0·28
7410	0·16
7411	0·25
7412	0·30
7413	0·36
7416	0·36
7417	0·36
7420	0·16
7422	0·25
7423	0·37
7425	0·37
7427	0·37
7428	0·40
7430	0·16
7432	0·37
7433	0·37
7437	0·37
7438	0·37
7440	0·22
7441AN	0·92
7442	0·79
7450	0·16
7451	0·16
7453	0·16
7454	0·16
7460	0·16
7470	0·36
7472	0·38
7473	0·41
7474	0·42
7475	0·59
7476	0·45
7480	0·60
7482	0·87
7483	1·10
7484	1·00
7486	0·47
7490	0·55
7491AN	1·00
7492	0·70
7493	0·70
7494	0·80
7495	0·80
7496	0·95
7497	3·87
74100	1·89
74107	0·45
74110	0·58
74111	0·86
74118	0·90
74119	1·68
74121	0·50
74122	0·70
74123	1·00
74141	0·90
74145	1·26
74150	1·75
74151	1·00
74154	2·00
74155	1·00
74156	1·00
74157	0·95
74170	2·52
74174	1·57
74175	1·10
74176	1·26
74190	2·00
74191	2·00
74192	2·00
74193	2·00
74194	1·30
74195	1·10
74196	1·20
74197	1·20
74198	2·77
74199	2·52
Plug in sockets —low profile	
14 pin DIL	0·15
16 pin DIL	0·17

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only • Tel. 01-677 2424-7
All orders subject to V.A.T. at 8% rate. This must be added to the total order including postage.

Prices correct when going to press.

SAXON

Money saving high performance audio equipment

DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 **£5·45** Carriage free
35W RMS 25–50V
7 transistors, 7 diodes

SA50 **£6.90** Carriage free
50W RMS 25–65V
7 transistors, 7 diodes

SA100 **£12·50** Carriage free
100W RMS 45–70V
10 transistors, 7 diodes

- ★ 25Hz–25kHz
- ★ 0·2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4–16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components

120 watt module complete with built-in supply—extra heavy duty £22·50 Carr. 60p

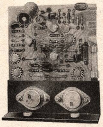

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED

PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	**£5·45**	Carriage 30p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	**£8·45**	Carriage 40p

STABILISED

PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	**£4·45**	Carriage free
MT45	Transformer for above	**£3·50**	Carriage 30p
PS70	Suits 2 SA100	**£5·45**	Carriage free
MT70	Transformer for above	**£4·90**	Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22·50

Carr. 30p

This well tried Pre-Amp mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in × 3in × 4in deep.

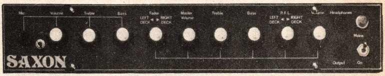

DISCO MODULE £9·50 Carr. 20p

Thousands sold of this extremely popular mono Pre-Amp. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12¾in × 3in × 2in deep.

3-CHANNEL SOUND-LITE £22·50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in × 3in × 2½in deep. Professional standards at a price you can afford!

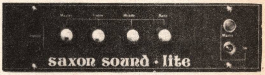

SINGLE CHANNEL VERSION £7·50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders

MULTI-PURPOSE MIXERS

M4HL **£19·50** Carr. 50p

M6HL **£29·50** Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed, The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3·50 Carr. free

This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9–100V)

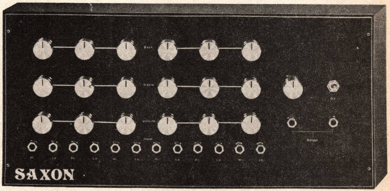

SAXON CSE 100

COMPLETE AMPLIFIER

£39·90
Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.

CSE 50
£29·50 Carr. free

NEW!!

SAXON MULTIMIX 100 £57 CARR. FREE

100W RMS **SLIDER** controls **PLUS** master slider.
Wide range bass and treble controls—fantastic value.
Ideal for complete Disco's, Groups, Clubs, etc.

SAXON MULTIMIX 50 EXACTLY AS ABOVE BUT 50W RMS **£45**

CALLERS AND MAIL ORDER:
SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS
(Please quote magazine when ordering)
SHOP HOURS: 9 a.m.–5 p.m. — LUNCH 12.30–1.30 p.m. MAIL ORDER DESK: 10 a.m.–3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.

TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p. for C.O.D.

Please include S.A.E. with all enquiries.

VAT at 8% must be added to all orders including carriage charges.

The largest selection

EX-COMPUTER STABILISED POWER MODULES

Complete with circuit diagrams, etc.
99p each plus 22p P. & P.

LOW COST CAPACITORS

0·01μF 400V.	**3p each**
500μF 50V. Elect.	**10p each**

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ × 4″ approx. 2 for **55p**

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen **99p** each

VEROBOARDS

Packs containing approx., 50sq. in. various sizes, all 0·1 matric **55p**

REPANCO CHOKES & COILS

RF Chokes
CH1. 2·5mH **29p** CH2. 5·0mH **30p**
CH3. 7·5mH **31p** CH4. 10mH **33p**
CH5. 1·5mH **28p**
COILS
DRX1 Crystal set **31p** DRR2 Dual range **45p**

COIL FORMERS & CORES

NORMAN ¼″ Cores & Formers **8p**
⅜″ Cores & Formers **10p**

SWITCHES

DP/DT Toggle **36p** SP/ST Toggle **30p**

FUSES

1¼″ and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1·5A, 2A
QUICK-BLOW **5p** each.

EARPHONES

Crystal 2·5mm plug **42p**
Crystal 3·5mm plug **42p**
8 ohms 2·5mm plug **22p**
8 ohms 3·5mm plug **22p**

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2·5mm and 3·5mm plugs **£1·85**

3-WAY STEREO HEAD-PHONE JUNCTION BOX

H1012 **£1·87**

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3bB **£1·21**

CAR STEREO SPEAKERS

(Angled) **£3·85** per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES

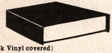

(Black Vinyl covered)

No.	Length		Width		Height	Price
BV1	8″	×	5¼″	×	2″	**£1·35**
BV2	11″	×	6″	×	3″	**£1·75**

ALUMINIUM BOXES

BA1	5¼″	×	2¾″	×	1½″	**49p**
BA2	4″	×	4″	×	1½″	**49p**
BA3	4″	×	2¾″	×	1½″	**49p**
BA4	5¼″	×	4″	×	1½″	**58p**
BA5	4″	×	2½″	×	2″	**49p**
BA6	3″	×	2″	×	1″	**42p**
BA7	7″	×	5″	×	2½″	**85p**
BA8	8″	×	6″	×	3″	**£1·10**
BA9	6″	×	4″	×	2″	**70p**

P. & P. 15p on each box

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen
Model 42 £1·95
Chrome Finish
Model 60 £1·50

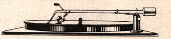

Ref. 36A. Record/Stylus Cleaning Kit **33p**
Ref. 43. Record Care Kit **£2·42**
Ref. 31. Cassette Head Cleaner **58p**
Ref. 32. Tape editing Kit **£1·68**
Model 9. Wire Stripper/Cutter **83p**
Ref. 46. Spirit Level **62p**
Ref. B. Stylus and Turntable Cleaning Kit **34p**
Ref. P. Hi-Fi Cleaner **31p**
Ref. 32A. Stylus Balance **£1·37**
Ref. J. Tape Head Cleaning Kit **62p**
Ref. 56. Hi-Fi Stereo Hints and Tips **42p**
Ref. 45. Auto Changer Groove Cleaner **£1·08**

ANTEX SOLDERING IRONS

X25. 25 watt **£2·05**
CCN 240. 15 watt **£2·48**
Model G. 18 watt **£2·26**
SK2. Soldering Kit **£3·25**
STANDS: ST3, suitable for all models **£1**
SOLDER: 18SWG Multicore 7oz **£1·61**
22SWG 7oz **£1·61.** 18SWG 22ft **51p**
22SWG Tube **33p**

ANTEX BITS and ELEMENTS

Bits No.		
102	For model CN240 $\frac{3}{32}$″	**42p**
104	For model CN240 $\frac{3}{16}$″	**42p**
1100	For model CCN240 $\frac{3}{32}$″	**42p**
1101	For model CCN240 ⅛″	**42p**
1102	For model CCN240 ¼″	**42p**
1020	For model G240 $\frac{3}{32}$″	**42p**
1021	For model G240 ⅛″	**42p**
1022	For model G240 $\frac{3}{16}$″	**42p**
50	For model X25 $\frac{3}{32}$″	**48p**
51	For model X25 ⅛″	**48p**
52	For model X25 $\frac{3}{16}$″	**48p**

ELEMENTS
ECN 240 **£1·30** ECCN 240 **£1·32**
EG 240 **£1·07** EX 25 **£1·16**

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0·54
C2	150	Capacitors mixed values approx. count by weight	0·54
C3	50	Precision Resistors 0·1%, 0·01% mixed values	0·54
C4	75	⅛th W Resistors mixed preferred values	0·54
C5	5	Pieces assorted Ferrite Rods	0·54
C6	2	Tuning Gangs, MW/LW VHF	0·54
C7	1	Pack Wire 50 metres assorted colours	0·54
C8	10	Reed Switches	0·54
C9	3	Micro Switches	0·54
C10	15	Assorted Pots & Pre-Sets	0·54
C11	5	Jack Sockets 3 × 3·5m 2 × Standard Switch Type	0·54
C12	30	Paper Condensers preferred types mixed values	0·54
C13	20	Electrolytics Trans. types	0·54
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0·54
C15	5	Mains Slide Switches	0·54
C16	20	Assorted Tag Strips & Panels	0·54
C17	10	Assorted Control Knobs	0·54
C18	4	Rotary Wave Change Switches	0·54
C19	2	Relays 6—24V Operating	0·54
C20	1	Pack Sheets of Copper Laminate approx. 20 sq. ins.	0·54

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)
Open Mon.–Sat. 9–5.30 p.m. Tel. 61593

PLUGS AND SOCKETS

PLUGS		
PS 1	D.I.N. 2 Pin (Speaker)	0·11
PS 2	D.I.N. 3 Pin	0·12
PS 3	D.I.N. 4 Pin	0·15
PS 4	D.I.N. 5 Pin 180°	0·16
PS 5	D.I.N. 5 Pin 240°	0·16
PS 6	D.I.N. 6 Pin	0·17
PS 7	D.I.N. 7 Pin	0·18
PS 8	Jack 2·5mm Screened	0·18
PS 9	Jack 3·5mm Plastic	0·12
PS 10	Jack 3·5mm Screened	0·18
PS 11	Jack ¼″ Plastic	0·15
PS 12	Jack ¼″ Screened	0·22
PS 13	Jack Stereo Screened	0·36
PS 14	Phono	0·10
PS 15	Car Aerial	0·22
PS 16	Co-Axial	0·15

INLINE SOCKETS		
PS 21	D.I.N. 2 Pin (Speaker)	0·14
PS 22	D.I.N. 3 Pin	0·20
PS 23	D.I.N. 5 Pin 180°	0·20
PS 24	D.I.N. 5 Pin 240°	0·20
PS 25	Jack 2·5mm Plastic	0·16
PS 26	Jack 3·5mm Plastic	0·16
PS 27	Jack ¼″ Plastic	0·30
PS 28	Jack ¼″ Screened	0·35
PS 29	Jack Stereo Plastic	0·30
PS 30	Jack Stereo Screened	0·38
PS 31	Phono Screened	0·18
PS 32	Car Aerial	0·22
PS 33	Co-Axial	0·22

SOCKETS		
PS 35	D.I.N. 2 Pin (Speaker)	0·08
PS 36	D.I.N. 3 Pin	0·11
PS 37	D.I.N. 5 Pin 180°	0·11
PS 38	D.I.N. 5 Pin 240°	0·11
PS 39	Jack 2·5mm Switched	0·12
PS 40	Jack 3·5mm Switched	0·12
PS 41	Jack ¼″ Switched	0·20
PS 42	Jack Stereo Switched	0·30
PS 43	Phono Single	0·08
PS 44	Phono Double	0·10
PS 46	Co-Axial Surface	0·10
PS 47	Co-Axial Flush	0·20

LEADS

LS 1	Speaker Lead 2 pin D.I.N. plug to open ends approx 3 metres long (coded)	0·20

CABLES

CP 1	Single Lapped Screen	0·07
CP 2	Twin Common Screen	0·11
CP 3	Stereo Screened	0·12
CP 4	Four Core Common Screen	0·23
PC 5	Four Core Individually Screened	0·30
CP 6	Microphone Fully Braided Cable	0·10
CP 7	Three Core Mains Cable	0·09
CP 8	Twin Oval Mains Cable	0·07
CP 9	Speaker Cable	0·05
CP 10	Low Loss Co-Axial	0·18

CARBON POTENTIOMETERS

Log and Lin
4·7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1	Single Less Switch	0·15
VC 2	Single D.P. Switch	0·28
VC 3	Tandem Less Switch	0·46
VC 4	1K Lin Less Switch	0·15
VC 5	100 K anti-Log	0·46

HORIZONTAL CARBON PRESETS

0·1 watt **0·06** each
100, 220, 470, 1K, 2·2K, 4·7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4·7M

SOLVE THOSE STI PROBLEMS!

with

CYANOACRYLATE C2

The wonder bond which works
bond plastic, rubber, metals,
components, permanently, imm

OUR PRICE ONL

for 2 gm. phia

BATTERY HOLDE

Takes 4, HP7's complete with
and lead. **34p.**

WORLD SC

JUMBO SEMICONDUCTOR

Transistors, Germ. and Silic
Diodes, Triacs, Thyristors, I.C
ALL NEW AND CODED.

APPROX. 100 PI

Offering the amateur a fantasti
and an enormous saving—iden
data sheet in every Pak.

Only £2 p. & p.

RECORD STOR CARRY CASE

7in EP. 18¾in × 7in × 8in (50

12in LP. 13¾in × 7⅜in × 12¾in

CASSETTE CASES

Holds 12, 10in × 3¾in × 5in. Loc

8-TRACK CART. CA

Holds 14, 13in × 5in × 6in **£1·95**
Holds 24, 13⅜in × 8in × 5⅜in **£2·**
Both with lock and handle.

SPECIAL PURCH

2N3055. Silicon Power Trans
Famous manufacturers out-of
free from open and short defect
able! 115W. TO3. Metal Case.
OUR SPECIAL PRICE 8

REPANCO TRANSF

240V. Primary. Secondary vo
able from selected tappings 4V,
14V, 15V, 17V, 19V, 21V, 25
40, 50 and 25V–0–25V.

Type	Amps	Pr
MT50/½	½	£1·
MT50/1	1	£2·
MT50/2	2	£3·

CARTRIDGES

ACOS
GP91-1SC 200mV at 1·2cm/sec
GP93-1 280mV at 1cm/sec
GP96-1 100mV at 1cm/sec
J-2005 Crystal/Hi Output
J-2010C Crystal/Hi Output Con
J-2006S Stereo/Hi Output
J-2105 Ceramic/Med Output
J-2203 Magnetic 5mV/5cm/s stylus
J-2203S Replacement stylus fo
AT-55 Audio-technica magne 4mV/5cm/sec

CARBON FILM RES

The E12 Range of Carbon Fi
⅛ watt available in PAKS
assorted into the following grou
R1 50 Mixed 100 ohms–820 o
R2 50 Mixed 1kΩ–8·2kΩ
R3 50 Mixed 10kΩ–82kΩ
R4 50 Mixed 100kΩ–1MΩ
THESE ARE UNBEATABL
JUST 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR LOW - NOISE CAS

C60, **36p**; C90, **48p**; C120, **60p.**

-the lowest prices!

PAK *QUALITY* COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

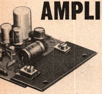

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.
The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
DISTORTION	Po = 3 WATTS f = 1KHz	0·25%
EDANCE	—	8–16 Ω
EDANCE	f = 1KHz	100 kΩ
CY RESPONSE —3dB	Po = 2 WATTS	50 Hz–25KHz
TY for RATED O/P	Vs=25V. R1=8Ω f=1KHz	75mV. RMS
NS	—	3″ × 2½″ = 1″

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
pply Voltage	25	30	30
or 2% T.H.D. f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AMPLIFIER ES

atts	**£2·50**
atts	**£2·85**
watts	**£3·20**

SUPPLIES

with AL10, AL20, AL30)	**95p**
Jse with AL60)	**£3·25**
NELS FP 12 with Knobs	**£1·00**

PRE-AMPLIFIERS

PA 12.	(Use with AL10, AL20 and AL30)	**£4·35**
PA 100.	(Use with AL60)	**£13·15**

TRANSFORMERS

T461 (Use with AL10) **£1·60** P & P 22p
T538 (Use with AL20, AL30) **£2·30** P & P 22p
BMT80 (Use with AL60) **£2·75** P & P 37p

PA12 PRE-AMPLIFIER SPECIFICATION

re-amplifier has been designed to match into
stereo systems. It is compatible with the
20 and AL 30 audio power amplifiers and it
plied from their associated power supplies.
o stereo inputs, one has been designed for use
ic cartridges while the auxiliary input will
Magnetic cartridges. Full details are given in
tion table. The four controls are, from left to
e and on/off switch, balance, bass and treble.
× 84mm × 35mm.

Frequency response—
20Hz–50KHz (—3dD)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV

Look for our
SEMICONDUCTOR ADVERTISEMENTS in
cal Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

STEREO 20

20" amplifier is mounted, ready wired and tested
chassis measuring 20 cm × 14 cm × 5·5 cm.
unit comes complete with on/off switch
ol, balance, bass and treble controls,
Power supply and Power amps.
printed front panel and match-
obs. The "Stereo 20" has been
it into most turntable plinths
fering with the mechanism or,
into a separate cabinet.
r 20w peak. Input 1 (Cer.)
1M. Freq. res. 25Hz-25kHz.
x.) 4mV into 30K. Harmonic
ass control ± 12dB at 60Hz
5% at 1 watt. Treble con.
kHz.

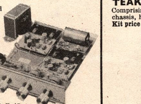

£14·45 P & P 45p

AK VENEERED CABINET

(front board undrilled) Size 10½″ × 8¾″ × 3″, **£3·95** plus 45p postage.

TEREO HEADPHONES

pedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume
5

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) *PLUS* THERMAL PROTECTION! The *NEW* AL60 Hi-Fi Audio Amplifier FOR ONLY £4·25

- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0·1% at 1KHz
- Supply voltage 15–50 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm × 105mm × 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1·5 amps at 35 volts. Size: 63mm × 105mm × 30mm.
These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available **10p** **PRICE £3·25**

TRANSFORMER BMT80 £2·15 p. & p. 40p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

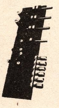

SPECIFICATION

Frequency Response	20Hz—20KHz ± 1dB
Harmonic Distortion	better than 0·1%
Inputs: 1. Tape Head	3·25 mV into 50K Ω
2. Radio, Tuner	75 mV into 50K Ω
3. Magnetic P.U.	3 mV into 50K Ω

All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.

Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than —65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm × 82mm × 35mm

ONLY £14·25

MK 60 AUDIO KIT

Comprising: 2 × AL60, 1 × SPM80, 1 × BTM80, 1 × PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. **Complete Price: £29·75** plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16¾″ × 11½″ × 3¾″, other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc. **Kit price: £9·95** plus 45p postage.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

*Postage and packing add **20p**. Overseas add extra for airmail.*
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

CHINAGLIA DINO – ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

CHINAGLIA

PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

CORTINA MINOR

33 RANGE POCKET MULTIMETER

- SENSITIVITY 20,000Ω/VOLT (D.C.), 4,000Ω/VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0–100mV, 1·5V, 5V, 15V, 50V, 150V, 500V, 1,500V. D.C. CURRENT 0–50μA, 5mA, 50mA, 500mA, 2·5A. A.C. VOLTS, 0-7·5V, 25V, 75V, 250V, 750V, 1,500V. A.C. CURRENT 0–25mA, 250mA, 2·5A, 12·5A. dB RANGES, −10 to +69. AF VOLTS RANGES 0–1,500V. RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF, IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2·5%. A.C. VOLTAGE AND CURRENT 3·5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 × 85 × 40mm. 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

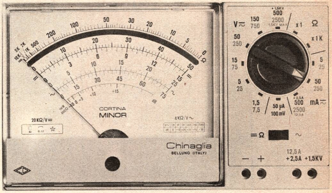

METER PRICE £16·30 (p & p 80p) PROBE £8·80 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone :—

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3. **Telephone 01-352 1897**

TRADE ENQUIRIES WELCOMED

I-N-T-E-R-L-O-C-K-I-N-G PLASTIC STORAGE DRAWERS

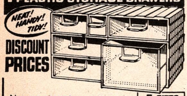

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2¼ins × 2¼ins). **£2** DOZEN.

DOUBLE UNITS (2D) (5ins × 4½ins × 2¼ins). **£3·50** DOZEN.

TREBLE (3D) £3·50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case **(6D2), £4·90** for 8.
EXTRA LARGE SIZE (6D1) £4·50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 8% V.A.T. to total remittance

FLAIRLINE SUPPLIES (Dept. PE3), 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back-up service to ensure your success.

VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coils, also available P.W. tele-tennis game. Send 5″ × 7″ S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS

124 Colne Road, Twickenham
Middlesex TW2 6QS
Telephone 01-898 1569
Telex 934642 Cadanac LDN

Use Access here

BARCLAYCARD welcome here

SET UP YOUR OWN HI-FI A BEGINNER'S GUIDE

by R. H. Warring Price **£1·90**

STEREO F.M. RADIO HANDBOOK by P. Harvey/K. J. Bohlman. Price **£2·70.**

RAPID SERVICING OF TRANSISTOR EQUIPMENT by G. J. King. Price **£2·05.**

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price **£2·05.**

ELEMENTS OF TRANSISTOR PULSE CIRCUITS by T. D. Towers. Price **£3·70.**

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price **£1·35.**

UNDERSTANDING SOLID STATE ELECTRONICS by Texas Instruments. Price **£1·35.**

ELECTRONIC SECURITY SYSTEMS by Leo G. Sands. Price **£3·30.**

PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES. Price **£2·80.**

SEMICONDUCTOR ELECTRONICS BY WORKED EXAMPLES by F. Brogan. Price **£2·70.**

TELEVISION RECEIVER THEORY I by G. H. Hutson. Price **£2·55.**

★ TOTAL PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
19-21 PRAED STREET
LONDON W2 1NP
Phone 01-723 4185
Closed Saturday 1 p.m.

ELECTROVALUE

Present a price-stabilizing policy for 1975

New revised catalogue ● attractive discounts ● free postage (U.K.)

A 100 OF THE BEST
out of our latest catalogue

2N1307	**47p**	AF200U	**40p**	BD132	**52p**
2N2646	**51p**	AF239	**60p**	BD135	**37p**
2N3053	**30p**	B1906	**36p**	BD136	**39p**
2N3054	**60p**	BA138	**31p**	BDY20	**83p**
2N3055	**70p**	BB103	**24p**	BF194	**15p**
2N3702	**11p**	BB105	**34p**	BFR39	**23p**
2N3703	**10p**	BB109	**43p**	BFR79	**23p**
2N3704	**11p**	BC107A	**18p**	BFX29	**33p**
2N3705	**10p**	BC107B	**18p**	BFX84	**27p**
2N3794	**18p**	BC108B	**15p**	BFY51	**23p**
2N3819	**25p**	BC108C	**15p**	BRY39	**50p**
2N4062	**11p**	BC109B	**18p**	BY164	**51p**
2N4443	**93p**	BC109C	**18p**	C106B1	**42p**
2N5062	**42p**	BC147A	**12p**	C106D1	**47p**
2N5163	**20p**	BC147B	**13p**	C1406	**78p**
2N5459	**35p**	BC148B	**12p**	MJ481	**£1·20**
40361	**48p**	BC149C	**14p**	MJ491	**£1·35**
40362	**44p**	BC158B	**15p**	MJ2955	**80p**
40602	**46p**	BC159	**15p**	MJE371	**89p**
40636	**£1·36**	BC167B	**13p**	MJE521	**81p**
40669	**£1·10**	BC168B	**12p**	MJE2955	**£1·12**
AC128	**17p**	BC169B	**12p**	MJE3055	**68p**
AC151R	**36p**	BC169C	**13p**	OA91	**6p**
AC153	**27p**	BC179B	**26p**	SD4	**8p**
AC153K	**37p**	BC182L	**12p**	TIP31A	**70p**
AC176	**24p**	BC184L	**10p**	TIP32A	**80p**
AC176K	**38p**	BC212L	**12p**	TIP41A	**80p**
AC187K	**31p**	BC214L	**14p**	TIP42A	**£1·00**
AC188K	**29p**	BC257A	**14p**	WO2	**30p**
AD133	**£1·92**	BC259B	**14p**	ZTX300	**14p**
AD136	**£1·11**	BCY58	**30p**	ZTX304	**23p**
AD149	**52p**	BD130	**70p**	ZTX500	**14p**
AD161	**42p**	BD131	**48p**	ZTX504	**45p**
AD162	**40p**				

ELECTROLYTIC CAPACITORS
Axial Lead

µF	3V	6·3V	10V	16V	25V	40V	63V	100V
0·47	—	—	—	—	—	—	**11p**	**8p**
1·0	—	—	—	—	—	**11p**	—	**8p**
2·2	—	—	—	—	**11p**	—	**8p**	**9p**
4·7	—	—	—	**11p**	—	**8p**	**9p**	**8p**
10	—	**11p**	—	—	**8p**	**9p**	**8p**	**8p**
22	—	—	**8p**	—	**9p**	**8p**	**8p**	**10p**
47	**8p**	—	**9p**	**8p**	**8p**	**8p**	**10p**	**13p**
100	**9p**	**8p**	**8p**	**8p**	**9p**	**10p**	**12p**	**19p**
220	**8p**	**8p**	**9p**	**10p**	**10p**	**11p**	**17p**	**28p**
470	**9p**	**10p**	**10p**	**11p**	**13p**	**17p**	**24p**	**45p**
1,000	**11p**	**13p**	**13p**	**17p**	**20p**	**25p**	**41p**	—
2,200	**15p**	—	—	**26p**	**37p**	**41p**	—	—
4,700	—	—	**36p**	**44p**	**58p**	—	—	—
10,000	**42p**	**46p**	—	—	—	—	—	—

RESISTORS

Code	*Watts*	*Ohms*	*1 to 9*	*10 to 99*	*100 up* (see note below)
C	⅓	4·7–470K	**1·3**	**1·1**	**0·9 nett**
C	½	4·7–10M	**1·3**	**1·1**	**0·9 nett**
C	¾	4·7–10M	**1·5**	**1·2**	**0·97 nett**
C	1	4·7–10M	**3·2**	**2·5**	**1·92 nett**
MO	½	10–1M	**4**	**3·3**	**2·3 nett**
WW	1	0·22–0·47	**16**	**14**	**11 nett**
WW	1	0·56–3·9Ω	**12**	**10**	**8 nett**
WW	3	1–10K	**9p**	**8p**	**6 nett**
WW	7	1–10K	**11**	**10**	**8 nett**

Codes:
C = carbon film, high stability, low noise.
MO = metal oxide. Electrosil TR5 ultra low noise.
WW = wire wound , Plessey.

Values: All E12 except C ½W. C ¾W and MO ½W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:
5% except WW 10% ± 0·05Ω below 10Ω and ½W MO 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only.

1975 is the year of challenge. Rather than sit back and wait for things to happen, we have produced our own policy to help stabilize price structure and maintain the services for which ELECTROVALUE are pre-eminent.

PRICES
as shown in our latest catalogue (No. 7, issue 3) will be maintained at least until March 31st next (except in cases of severe market fluctuation) and then held after review for further three month periods instead of making day to day price changes.

CATALOGUE 7 ISSUE 3
Is now ready with 108 pages of bargains and information. Price—30p post paid including 25p refund voucher for use on orders list value £5 or more.

DISCOUNTS
apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14·99; 10% on orders value £15 or more.

FREE POSTAGE AND PACKING
in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under, there is an additional handling charge of 10p.

QUALITY GUARANTEE
All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or substandard merchandise.

V.A.T. at 8%
must be added to total value of orders. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.

ANTEX Soldering Irons

C240	**£2·25**	Spare bits	**32p**
CCN240	**£2·65**	Spare bits	**42p**

WAVECHANGE SWITCHES
1 pole 12 way: 2 pole 6 way
3 pole 4 way: 4 pole 3 way each **33p**
TAG STRIP 28 way **11p**

NUTS, SCREWS, etc.
in lots of 100 each
4BA NUTS **21p**; 6BA NUTS **28p**; ½" 4BA Screws **30p**; ½" 6BA Screws **24p**; Threaded pillars 6BA, ½" hexagonal £1·38; Plain spacers ½" **£1·32.**

CAPACITORS
DALY ELECTROLYTIC *in cans, plastic sleeved*
1000mF/25V **34p**
5000/100 **£3·56**
5000 25V **75p**
2200/100 **£1·91**
1000/100 **£1·00**
1000/50 **50p**
2000/150 **70p**
5000/50 **£1·44**

POLYESTER TYPE C.280. *Radial leads for P.C.B. mounting. Working voltage 250V d.c.*
0·01, 0·015, 0·022, 0·033, 0·047 each **3p**
0·068, 0·1, 0·15 each **4p**
0·22 **5p**; 0·33 **7p**; 0·47 **8p**; 0·68 **11p**; 1·0 **14p**; 1·5 **21p**; 2·2 **24p.**

SILVERED MICA. *Working voltage 500V d.c. Tolerance 1% or 0·5pF.*
Values in pFs—2·2 to 250 in 26 stages each **6p.** 270–820 in 9 stages, each **7p.**
1000, 1500, 1800 **9p**; 2200 **10p**; 2700, 3600, 4700, 5000 **16p**; 6800, 8200, 10,000 **25p.**

TANTALUM BEAD
0·1, 0·22, 0·47, 1·0 mF/35V, 1·5/20V, 3·5/16V each **16p**
2·2/16V, 2·2/35V, 4·7/16V, 10/6·3V each **16p**
4·7/35V, 10/16V, 22/6·3V each **21p**
10/25V, 22/16V, 27/6·3V, 100/3V, 6·8/25V, 15/25V each **23p**

POLYCARBONATE
Type B42540 Working Voltage—250V. Values in mF:
0·0047, 0·0068, 0·01, 0·015, 0·22 each **4p**
0·018, 0·027, 0·033, 0·039, 0·047, 0·068, 0·082, 0·1 each **5p**
100 V, Values—0·1 **5p**; 0·12, 0·15 **6p**; 0·18, 0·22 **7p**; 0·27, 0·33 **9p**; 0·39, 0·47 **11p**; 0·56, 0·68 **16p.**

CERAMIC PLATE
Working voltage 50V d.c.
In 26 values from 22pF to 6800pF, each **2p.**

POTENTIOMETERS
ROTARY, CARBON TRACK

Double wipers for good contact and long working life
P.20 SINGLE linear 100 ohms to 4·7 megohms. each **14p**
P.20 SINGLE log. 4·7 Kohms to 2·2 megohms. each **14p**
JP.20 DUAL GANG lin. 4·7 Kohms to 2·2 megohms each **48p**
JP.20 DUAL GANG log. 4·7 Kohms to 2·2 megohms. each **48p**
JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only each **48p**
JP.20 DUAL GANG antilog 10K only **48p**
2A DP mains switch for any of above **14p** extra
Skeleton Carbon Presets, Decades of 10, 22 and 47 only available within limits in ranges above.
Type PR, horizontal or vertical 100Ω–10MΩ each **6p**

SLIDER
Linear or log mono 4·7K to 1 meg. in all popular values each **30p**
STEREO, matched tracks, lin. or log. in all popular values from 4·7K to 1 meg. **60p**
Escutcheon plates, mono, black or grey each **10p**
Control knobs, blk/wht/red/yel/grn/blue/dk. grey, lt. grey each **7p**

MINITRON DIGITAL INDICATORS
3015F Seven segment filament compatible with standard logic modules. 0–9 and decimal point; 9mm characters in 16 lead DIL **£1·20**
Suitable BCD decoder driver 7447 **£1·15**
3015G showing + or − & 1 & dec. pt. **£1·20**
LEDS (Light Emitting Diodes) **25p**
Photo Cells cadmium sulphide, each **40p**

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address. Dept. PE3. S.A.E. with enquiries requiring answers.

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9–5.30 daily; Sat. 9–1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9–1 p.m. 2–5.30 daily; Sat. 9–1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA. P O Box 27, Swarthmore PA 19081.

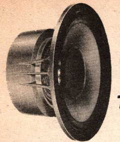

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7·75
Baker Group 35 3, 8 or 15 ohm	£8·50
Baker Group 50/12 8 or 15 ohm	£12·50
Baker Deluxe 12in d/cone	£10·75
Baker Major 12in d/cone	£8·50
Baker Regent	£7·75
Baker Superb	£14·50
Baker Auditorium 12	£12·50
Celestion MH1000, 8 or 15 ohm	£10·95
Celestion PST8 for Unilex	£3·25
Celestion G12M 8 or 15 ohm	£12·00
Celestion G12H 8 or 15 ohm	£15·00
Celestion G15C 8 or 15 ohm	£24·00
Celestion G18C 8 or 15 ohm	£33·00
Coral 6½in d/cone roll surr. 8 ohm	£2·50
Coral 8in d/cone roll surr. 8 ohm	£3·25
EMI 13in × 8in 3, 8 or 15 ohm	£2·25
EMI 13in × 8in 150 d/c 8 ohm	£2·50
EMI 13in × 8in 450 t/tw. 3, 8 or 15 ohm	£3·75
EMI 13in × 8in type 350 8 or 15 ohm	£8·25
EMI 13in × 8in 20W bass	£6·60
EMI 6½in 93850 4 or 8 ohm	£3·00
EMI 5in 14A/7030 mid range 8 ohm	£2·50
EMI 8 × 5 d/cone, roll surr. 10W	£2·50
EMI 2½in tweeter 97492AT	£0·65
Eagle DT33 30W tweeter	£5·45
Eagle HT15 horn tweeter	£3·80
Eagle CT5 cone tweeter	£1·75
Eagle CT10 tweeter 8 or 16 ohm	£2·55
Eagle MHT10 horn tweeter	£3·80
Eagle crossover CN23, CN28, CN216	£1·50
Eagle FR4	£5·30
Eagle FR65	£8·35
Eagle FR8	£10·65
Elac 9 × 5 59RM109 15 ohm, 59RM114 8 ohm	£2·80
Elac 6½in 6RM171 d/c roll surr.	£3·50
Elac 6½in 6RM220 d/cone	£2·65
Elac 4in tweeter TW4	£1·50
Elac 10in d/cone 10RM239 8 ohm	£2·65
Elac 8in 8CS175 3 ohm	£2·50
Fane Pop 15W 12in	£5·25
Fane Pop 25T 30W 12in	£7·25
Fane Pop 50W 12in	£12·00
Fane Pop 55 60W 12in	£12·50
Fane Pop 60W 15in	£13·25
Fane Pop 100W 18in	£24·50
Fane Crescendo 12A 100W 12in	£29·00
Fane Crescendo 12B bass	£29·00
Fane Crescendo 15in 100W	£36·00
Fane Crescendo 18in 150W	£51·95
Fane 801T 8in d/c roll surr.	£7·00
Fane 807T 8in d/c roll surr.	£3·85
Fane 808T 8in d/c	£2·75
Fane 701 twin ribbon horn	£35·00
Fane 910 horn	£12·75
Fane 920 horn	£33·00
Goodmans 8P 8 or 15 ohm	£5·00
Goodmans 10P 8 or 15 ohm	£5·30
Goodmans 12P 8 or 15 ohm	£12·95
Goodmans 12P-D 8 or 15 ohm	£16·75
Goodmans 12P-G 8 or 15 ohm	£15·75
Goodmans Audiomax 12AX 100W	£36·50
Goodmans Audiomax 15AX	£40·25
Goodmans 15P 8 or 15 ohm	£21·00
Goodmans 18P 8 or 15 ohm	£36·00
Goodmans Midax 750	£16·00
Goodmans Axent 100 tweeter	£7·25
Goodmans Audiom 100 12in	£12·00
Goodmans Axiom 401 12in	£17·25
Goodmans Twinaxiom 8	£8·25
Goodmans Twinaxiom 10	£9·00
Kef T27	£5·25
Kef T15	£6·00
Kef B110	£7·25
Kef B200	£8·25
Kef B139	£14·25
Kef DN8	£2·00
Kef DN12	£4·95
Kef DN13	£3·30
STC4001G super tweeter	£6·19
Richard Allan CG8T 8in d/c r/surr.	£6·35
2½in 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£0·65
2½in 75 ohm	£0·50
7in × 4in 3 or 8 ohm	£1·40
8in × 5in 3 or 8 ohm	£1·50
10in × 6in 3, 8 or 15 ohm	£2·30

SPEAKER KITS

Baker Major Module	each £10·75
Goodmans Mezzo	each £45·00
Goodmans DIN 20	each £9·75
Helme XLK25	pair £22·00
Helme XLK30	pair £14·95
Helme XLK50	pair £39·95
Kefkit 1	each £20·95
Kefkit 3	each £36·75
Richard Allan Twinkit	each £8·95
Richard Allan Triple 8	each £13·75
Richard Allan Triple	each £19·95
Richard Allan Super Triple	each £23·75
Wharfedale Linton 2 kit	pair £19·25
Wharfedale Glendale 3 kit	pair £34·50
Wharfedale Dovedale 3 kit	pair £52·50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)

Baker Major 100 watt	£49·75
Linear 30/40	£30·00
Linear 40/60	£35·00
Linear 80/100	£58·95
Linear 100 watt slave	£44·00

Eagle PA range in stock—ask for catalogue.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1·50 pair), tweeters and crossovers 20p.

Send stamp for free booklet "Choosing a Speaker"

ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.

Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.

Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C60 C90 C120	1 37p 50p 63p	5 £1·80 £2·48 £3·10	10 £3·50 £4·95 £6·20
AGFA HIGHDYNAMIC SUPER	C60 + 6 C90 × 6 C120	1 50p 68p 99p	5 £2·40 £3·35 £4·90	10 £4·70 £6·60 £9·80
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C60 C90	1 85p £1·08	5 £4·20 £5·35	10 £8·30 £10·60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO
(DEPT. PE)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

CALCULATORS

BUY FROM THE SPECIALISTS

UP TO 45% OFF RRP

All guaranteed 1 year. Money refunded on goods returned within 7 days.

VATMAN £14·91 + VAT

Model	Our Price	Functions
Decimo Vatman	14·91	P, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, B, N.
Decimo Vatman	16·91	P, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, BM, N.
Decimo Memory	23·88	P, M, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, BM, N, [W].
Decimo Slide rule	25·88	P, M, [A], R, G, 8D, E, F, K4, [H], [X], [J], I, C, L5, BM, N.
Decimo 9202	39·83	S, M, [A], R, G, 8D, E, F, K2, H, I, J, L5, BM, N.
Anita 811	39·95	P, M, [A], R, 8D, E, F, K4, H, I, C, B, N.
Bohn Omnitrex*	44·95	T, M, [A], R, G, 8D, E, F2, K4, H, I, C, BM, M.
Bohn Omnitrex SQ1*	50·95	T, M, [A], R, G, 8D, E, F7, K2, G, [H], [X], [J], I, C, M, V, U.
JUST OUT		
Bohn Metric*	59·22	T, W, [A], R, G, 8D, E, F, K2, H, I, M, C, V also 12 conversions ins/cms, ft/metres, yds/metres, miles/km, ozs/ccs, qts/litres, gals/litres, F°/C°, ozs/grams, lbs/kg, area measurement, cubic measurement.
Bowmar MX75*	39·97	T, M, [A], R, 8D, E, F, K4, H, I, J, C, V.
Bowmar MX100*	65·99	T, M, 8D, E, F, K4, C, V, J, true scientific 20 functions for algebra, geometry, logs, calculus, integrals, etc.
Special Import	19·90	P, M, [A], R, 8D, E, F/2/4, K4, M, I, J, C, V, N
		Print-Outs
Ricomac 1000P	81·97	2 colour print-out, A, 10D, F/S, K4, M, sub total, acc ÷ X buffer
Ricomac 1220	121·19	Ditto, plus 12D, [A], 2M, rounding, [W] silent.

Code

A = percentage, B = battery (mains adaptor extra), BM = battery (mains adaptor incl.), C = carrying case, D = digits, E = + − × ±, F = floating decimal point, F/S = floating point and select, F2 = floating point and 2 places, F7 = floating point and 7 places, G = green display, H = x^2, I = x , J = x, K^2 = constant X ÷, K^4 = constant × ÷ + −, L5 = 50 hr. battery life, L10 = 100 hr. battery life, M = memory, N = negative entry, P = pocket, R = prorating, S = desk model, T = hand and desk, U = display blanking, V = rechargeable, W = exchange, X = √x, [ ] = extra separate keys, * = positive feel.

50p P. & P. and please add 8% VAT on all total prices.

BARCLAY ELECTRONICS
STANLEY HOUSE, 1115 FINCHLEY ROAD
LONDON, NW11

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110–200/220/240V
30W, **£2·10;** 50W, **£2·70;** 75W **£3·45;** 100W, **£4;** 500W, **£12;** 750W, **£16·50;** 1000W, **£20·25,** etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6·3V 1·5A, **£1·45;** 3A, **£1·80;** 6A, **£3·60;** 12V 1·5A, **£1·80;** 3A, **£3·30;** 6A CT, **£4·50;** 18V 1·5A CT, **£3·30;** 24V 1·5A CT, **£3·30;** 3A CT, **£4·50;** 5A, **£6·75;** 8A, **£8·70;** 12A, **£12·40;** 40V 3A CT, **£6;** 50V 6A CT, **£15·75;** 25V 2A + 25V 2A, **£6·40;** 12V 4A + 12V 4A, **£6·40.**

LT TRANSFORMERS TAPPED SEC, Prim 200/240V
0–10–12–14–16–18V 2A, **£3·30;** 4A, **£4·50.**
0–12–15–20–24–30V 2A, **£4·20;** 4A, **£6.**
0–5–20–30–40–60V 1A, **£4·20;** 2A, **£6.**
0–40–50–60–80–90–100–110V 1A, **£6·40.**

MIDGET RECTIFIER TRANSFORMERS
For FW rect., 200/240V a.c. 6–0–6V 1·5A or 9–0–9V 1A **£1·65** each; 12–0–12V 1A or 20–0–20V 0·75A or 9-0-9V 0·3A or 12–0–12V 0·25A or 20–0–20V 0·15A or 6V 0·5A + 6V 0·5A or 9V 0·35A + 9V 0·35A or 12V 0·25A + 12V 0·25A or 20V 0·15A + 20V 1·5A, **all at £1·90 each.**

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425–0–425V 500 MA, 6·3V CT 6A, 6·3V CT 6A, 0–5–6·3V 3A **£18·75;** TX1 425–0–425V 250 MA, 6·3V CT 4A, 6·3V CT 4A, 0–5–6·3V 3A, **£11·25;** MT3 Prim. 0–110–240V, sec., 250V 100 MA, 6·3V 2A, E/S, **£3·75.**

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec., tapped 3–8–15 ohms, A–A 6·6kΩ 30W **£6·75;** A–A 3kΩ 50W **£10·15;** 100W (EL34 KT88, etc.), **£17·25;** MRT/10, tapped multi O/P 10W **£4.**

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W **35p.**

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, **£7·60;** 35W **£8·40;** Hi-Fi Major Module 20W w/tweeter crossover, **£11·80.** Baker Speaker Lists. FANE 60W **£13·50;** EMI 13 × 8in, 8Ω, **£2;** 5in 8Ω, **£1·15;** 7 × 4in 15Ω, **£1·60;** 8 × 5in 3, 8, 15 or 80Ω, **£1·75 each.**

LOUDSPEAKERS
2½in 8 or 75Ω, 2½in 8 or 25Ω, 3in 3, 8, 25 or 35Ω, 3½in 8 or 80Ω, **95p** each; 5in 3, 8 or 25Ω, 5 × 3in 3 or 8Ω, **£1·15;** 7 × 4in 3 or 15Ω, 6½in 3Ω, **£1·30;** 10 × 6in 3Ω, **£1·50.**

SPEAKER AUTO MATCHING TRANSFORMER
12W 3 to 8 or 15Ω up or down, **£1·50.**

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads, 200/240V a.c., **£3·75.**

SYNCHRONOUS GEARED MOTORS, 200/240V a.c.
Brand new, Smiths. Built-in gearbox, 2r.p.h., **75p each.**

Carriage and VAT extra on all orders
S.A.E. ENQUIRIES, LISTS. MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

BARGAINS FROM OUR FREE CATALOGUE

6th edition. 20 large pages filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy by return. Meanwhile, for prompt delivery order from our ad. this month NOW.

B.P.P. TRANSISTOR PACKS ALL AT 50p EACH

TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic
B81	10	Reed Switches, 1in long ⅛in dia. Highspeed P.O. type
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked
H38	30	Short lead Transistors, NPN Silicon Planar types Ex-equipment
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945
H41	2	BD131/BD132 Complementary Plastic Transistors
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65

UNMARKED AND UNTESTED

B1	50	Germanium Transistors PNP, AF and RF
B66	150	Germanium Diodes Min. glass type
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202
B86	100	Sil. Diodes sub. min. IN914 and IN916 types
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
H67	10	3819N Channel FET's plastic case type

PLASTIC POWER TRANSISTORS—2 ranges

In NPN or PNP at shatteringly low prices under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15	*1–12*	*13–25*	*26–50*
40 watt	**20p**	**18p**	**16p**
90 watt	**24p**	**22p**	**20p**

Range 2. VCE. Min 40. HFE Min 40	*1–12*	*13–25*	*26–50*
40 watt	**30p**	**28p**	**26p**
90 watt	**35p**	**33p**	**30p**

Please state NPN or PNP on order.

X-HATCH GENERATOR MK.2

Four patterns—essential for colour TV alignment. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3in × 5¼in × 3in. Operates from three U-2-type batteries (extra).

Ready built unit only **£9·93**

Complete kit **£7·93**

OVER 1,000,000 TRANSISTORS

of all most-needed types in stock including power, diode, rectifier, etc. Marked, tested and guaranteed. Hundreds of worthwhile bargains are to be found in our FREE CATALOGUE (6th edn.). Also zener diodes, I.C.s, etc.

SUNDRY

Metrication Pocket Charts **12p.** 8 assorted relays **£1.** Rev. counter device (for cars) **£1.** UHF/TV Tuner Unit **£2·50.** LM380 Audio I.C. **£1.** Technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 15p for postage and packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—*Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.*

CHALLENGING VALUES!

Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatch and include well printed instructions.

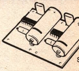
SS.103-3

AMPLIFIER MODULES

Pre-amplifiers; tone control

SS.100 Active tone control unit to provide bass, treble, balance and volume controls **£1·60**

SS.101 Pre-amp for ceramic cartridge, tape and radio **£1·60**

SS.102 Pre-amp for low output magnetic cartridge tape and radio. With R.I.A.A. correction ±1dB at 1kΩ **£2·25**

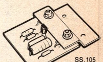
SS.105

POWER AMPLIFIERS

SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6–22. Size 3in × 2in. **£1·75**

SS.103–3 Stereo version of above using one I.C. on each channel **£3·25**

SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2½in × 1¾in. **£1·95**

SS.110 Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26–32V. **£2·40**

SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. T.H.D. better than 0·2%. Power requirements—45V d.c. With 0·15in centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms **£3·60**

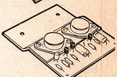
SS.140

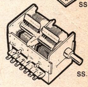
SS.201

TUNER MODULES

SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88–108MHz. With A.F.C. facility. Operates from 6–16V **£6·25**

SS.202 I.F. stage (with I.C.). Pre-tuned. A.F.C. connection. Operates from 4·5–14V **£5·25**

SS.203 Stereo Decoder. Designed essentially for use with SS.201 and SS.202, this module can also be used on most mono F.M. tuners. A L.E.D. may be attached. Operating voltage 9–16V d.c. **£5·62**

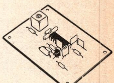
SS.202

POWER SUPPLY STABILISER

SS.300 Add this to an unstabilised supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable. **£3·25**

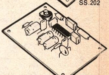
SS.203

- * ALL MODULES TESTED AND GUARANTEED
- * WITH WELL PRINTED INSTRUCTIONS
- * FULL RANGES OF ANCILLARY COMPONENTS AVAILABLE—SEE CATALOGUE

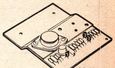
SS.300

BI-PRE-PAK LTD

Co Reg No 820919
222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.
TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF NECESSARY

Have you had your FREE CATALOGUE?

To BI-PRE-PAK, 222–224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send ....

for which I enclose .... inc. V.A.T.

NAME ....

ADDRESS PE3

'BIG' Discounts

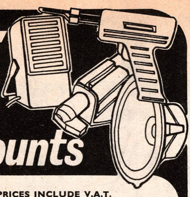

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS	£
EMI 13in × 8in 3, 8 or 15 ohm	
Plain	2·05
With Co-Axial Tweeter	
8 ohm only	2·20
Twin Tweeter 8 ohm only	3·95
Type 350, 8 ohm, 20W	7·95
6½in, 8 ohm, 10W	2·40
8in, 8 ohm, 10W	3·75
12in, 8 ohm, 20W	6·70
8in × 5in, C/Mag. 5W	1·40
8in × 5in, Dual cone 8 ohm, 10W	2·55
ELAC 6½in 8 ohm Dual cone	2·15
ELAC 8in 8 ohm Dual cone	2·30
ELAC 10in 8 ohm Dual cone	3·50
GOODMANS 6½in 8 ohm Dual cone	2·15
FANE, 7in × 4in, 3 or 8 ohm	1·00
ADASTRA 10in, 8 or 15 ohm, 10W	3·55
BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7·95
P. & P.	0·40
5in, 8 ohm, C/Mag.	0·85
2½in, 8 ohm or 64 ohm	0·55
P. & P.	0·15

TWEETER AND CROSSOVER	
EMI 3½in, 3 or 8 ohm C/Mag.	1·30
Cone Tweeter 8 or 15 ohm, 10W	2·60
Cone Tweeter 8 ohm, 3W	1·45
Horn Tweeter 8 ohm, 20W	6·40
Dome Tweeter 8 ohm, 30W	5·60
Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1·30
P. & P.	0·15

KIT FORM CABINETS, TEAK VENEER.	
12in × 12in × 6in with 8in, 8in × 5in or 6½in and 3½in cutout	3·40
17in × 10in × 9in with 8in or 13in × 8in cutout	4·25
18in × 11in × 9in with 13in × 8in cutout for EMI 350	4·75
P. & P. each	0·50

MICROPHONES	
CM70 Planet stick metal, switch crystal	1·55
DM160 Dynamic omni-dir, ball metal	4·90
UD130 50K/600 ohm, uni-dir, ball metal	6·40
TW209	5·75
CONDENSER MIKE 600 ohm, uni-dir	9·35
Cassette Stick Mike with R. Control on/off switch (2·5 and 3·5mm J/Ply)	1·50
P. & P.	0·30

SOLDERING IRONS	
ANTEX CN240 15W	2·00
SK1 Kit (15 watt iron, 2 spare Bib, etc.)	3·40
X25 25W (low leakage)	2·00
P. & P.	0·15

CARTRIDGES AND STYLII	
ACOS GP91/2SC or 3SC Stereo comp.	1·00
GP93/1 or 95/1 Stereo crystal	1·35
GP94/1 or 96/1 Stereo ceramic	1·75
GP101 Crystal comp.	0·80
GP104 Stereo ceramic	1·65
BSR X5M or5XH Crystal comp.	1·70
SX6M or SX6H Crystal comp.	1·90
SC5M Stereo ceramic	2·60
SONOTONE 9TAHC or 9TAHC/G diam.	1·80
3509 Stereo ceramic diam.	1·90
GOLDRING G850	2·95
G800	3·95
G800E	6·90
P. & P.	0·15
D. Diamond Stylii for above	1·25
G800/G850	1·95
G800E	3·95
P. & P.	0·05

BATTERY ELIMINATORS	
240V input 6, 7·5 or 9 300mA	2·95
12V (please specify output) 300mA	2·30
P. & P.	0·15

TAPES	Stnd.	LP	DP
5in	50p	65p	1·25p
5¾in	65p	80p	1·45p
7in	80p	1·10p	1·80p

PLASTIC LIBRARY CASES

5in Reels **18p**. 5¾in. **22p**. 7in. **25p**.

P. & P. 1–3 9p each. 4 or more lot 35p

LOW NOISE CASSETTES	1–5	6–10	11–20
C60	35p	33p	30p
C90	65p	43p	40p
C120	75p	52p	50p

Cassette Head Cleaner	0·35
P. & P. 1–5 each	0·05
6–10 lot	0·20
11–20 post free	

BIB ACCESSORIES	
Tape Editing Kit, Ref. 23	1·35
Recording Tape Splicer, Ref. 20	1·15
Cassette Tape, Editing, Ref. 24	1·50
Cassette Salvage Kit, Ref. 29	0·45
12's Cassette Case, Ref. 34	1.50
Stylus Balance, Ref. 32A	1·20
Spirit Level, Ref. 46	0·50
Hi-Fi Stereo Test Cassette	2·10
Groove-Kleen Record Cleaner	1·90
P. & P.	0·15

CALCULATORS	
SINCLAIR Cambridge	£19·95
Scientific	£29·95

WHARFEDALE SPEAKER BARGAINS		P & P
Linton 2 Kit (pr.)	19·00	1·50
Glendale 3 Kit (pr.)	33·50	2·00
Dovedale 3 Kit (pr.)	52·00	2·00
Denton 2 Speaker (pr.)	30·00	2·50
Linton 2 Speaker (pr.)	39·50	2·50
Dovedale 3 Speaker (each)	42·00	2·50
Glendale 3 Speaker (pr.)	57·00	3·50
Kingsdale 3 Speaker (each)	59·95	4·00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE3
P.O. Box 470, Manchester M60 4BU

CJL PRICES INCLUDE P&P AND V.A.T.

☐**AERIAL**, telescopic, 15-120cm.	£1.20
☐**AERIAL**, telescopic, h and v swivel, 15-80cm. .	£1.78
BIB HI-FI ACCESSORIES	
☐CASSETTE TAPE RECORDER CARE KIT . .	£1.95
☐CASSETTE SPLICING AND EDITING KIT . .	£1.50
☐HI-FI STEREO TEST CASSETTE	£2.10
☐¼" TAPE EDITING KIT	£1.35
☐GROOV-KLEEN RECORD CLEANER	£1.85
☐**EARPHONE**, stethoscope style, 8 ohm dynamic .	£1.00
☐**HAND DRILL**, (Leytool), compact precision drill, 5/16"chuck. Gears totally enclosed. S/L bearings.	£2.99
INTEGRATED CIRCUITS	
☐AUDIO POWER AMPLIFIER (National) LM380	£1.00
☐A.M. RADIO RECEIVER (RCA) CA3123E	£1.40
☐F.M. STEREO DECODER (Motorola) MC1310P	£2.80
☐TIMER (Signetics) NE555V	£0.78
☐VOLTAGE REGULATOR (Fairchild) uA7805	£1.70
☐VOLTAGE REGULATOR (Signetics) NE550A	£0.80
☐D.I.L. SOCKETS (Pk of 3) 8 or 14 pin	£0.50
☐**KEYNECTOR**. rapid connect to mains-single/multiple leads. Built-in piano switches, neon & 13A fuse	£3.20
☐**LOCKFLEX RULE** (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/½"wide steel tape. Blade length lockable-power return. A superb rule	£0.93
☐**MICROPHONE**, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output .	£1.80
☐**MULTIMETER**, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k .	£4.95
☐**SIGNAL INJECTOR**, audio through video signals, excellent for servicing amplifiers, radio & tv . .	£3.92
☐**SOLDERING IRON, 25 WATT**, (Antex), X25, 240V, Very low leakage, 1/8"long life bit (interchangeable)	£1.85
☐3/32"bit £0.45 ☐3/16"bit £0.45 ☐Element	£0.95
☐**STAND**, ST3, High grade base, chrome plated spring, sponges and accomodation for spare bits .	£0.95
☐**SPEAKER**, miniature, 75mm dia, 8 ohms. . .	£0.80

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

London College of Furniture

Department of Musical Instrument Technology

Full-time Courses

HIGHER DIPLOMA COURSE:

Advanced studies for those who are 19 years of age or over and who have suitable educational or industrial qualifications.

Higher Diploma in Musical Instrument Technology. (Subject to approval).

CERTIFICATE COURSES IN:

Piano Tuning, Construction, Repair and Maintenance, Early Stringed Keyboard Instrument Construction, Harpsichord, Clavichords, Fretted Instruments, Guitars, Lutes, Violas and Cellos, Electronics for Musical Instruments.

PART-TIME COURSES:

Block Release or Day Release.

Stringed Keyboard Instrument Design and Manufacture, Violin Making, Early Fretted Instrument Making, Piano Tuning and Maintenance, Woodwind Instrument Maintenance.

ilea

Further information from Senior Administrative Officer, London College of Furniture, 41 Commercial Road, London E1 1LA. Tel. 01-247 1953

Europe's Largest Hi-Fi Retailers

LASKYS

give you the greatest choice

MK 200 MULTIMETER KIT

uild yourself a
uality 20000 opv.
ultimeter and
ve money.
omplete kit with
eter scale,
ovement and
tary range
elector ready
ounted in
binet. All parts,
tteries, test prods and
structions. Ranges: 0/0.6/6/30/
20/600/1200V D.C. 0/6/30/120
00/1200V A.C. Current: 0/0.6/6/
)/600mA. Resistance: 0/10/
00K/1/10 Meg ohms. Decibels:
20 to +63db. Size: 90 x 150 x
5mm

UR PRICE £7.95 P&P 30p.

UDIOTRONIC Model ATM1

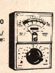

op value 1,000
v pocket multi-
eter. Ranges: –
10/50/250/1,000
lt AC and DC.
C current 0-1mA/
00mA. Resistence:
150k ohms.
ecibels: –10 to
22dB. Size 90 x
) x 28mm.
omplete with
st leads.

UR PRICE £3.25 P&P 15p

UDIOTRONIC Model ATM5

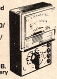

wel movement,
tractively moulded
se with edgwise
ms adjustment.
anges: 0-3/15/150/
00/1200V AC,
500 opv). 0-6/30/
00/600V DC,
000 opv). 0-300
A/0-300mA DC.
esistance: x 10 &
100. –10 to +16dB.
pplied with battery
st leads and data
ooklet. Size: 121 x 73 x 29mm.

UR PRICE £3.95 P & P 20p

IOKI 720X VOM

versatile,
curate measur-
g instrument.
,000 opv. 0/
25/100/500/
00V DC. 0/10/
/250/1000V
C. 0–50uA/
0mA. 0–20k/
Megohms.

**UR PRICE
5.97**
&P 30p

IODEL C7202EN

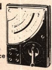

,000 o.p.v. DC.
,000 o.p.v. AC
lirror Scale.
25/50/250/500/
00/2500 V. DC.
/50/100/500/1000
. AC. DC Resistance
10. ×1000 (30Ω
entre scale) DC
urrent 50uA/
5mA/250mA. –20
+68 dB.

UR PRICE £6.95 P & P 30p

IODEL PL436

,000 opv DC.
000 opv AC.
lirror scale
/3/12/30/120/
00V DC. 3/30/
20/600V DC.
0/600μA/60/
00mA.
0/100K/1 Meg/10 Meg Ohm.
20 to 46 dB.

UR PRICE £6.97 P&P 30p.

HIOKI 730X

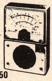

30,000 opv. Overload protection.
6/30/60/300/600/
1200V DC. 12/60/
120/600/1200V AC.
60/μA/
30mA/300mA.
2K/200K/
2 Meg Ohm.
–10 to 63 dB.

OUR PRICE £7.50
P&P 30p.

U4323 MULTIMETER

20,000opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x 10, x 100, x 1,000, x 10,000 (50Ω. 500Ω, 5kΩ, 50kΩ centre scale) Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.

OUR PRICE £7.70 P&P 30p

U435 MULTIMETER

20,000opv. Ranges:

75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.

OUR PRICE £8.75 P&P 30p

MODEL C7208FM

30,000 opv DC.
15,000 opv AC.
·6/3/15/60/300/600/
1200 V. DC. 6/30/
120/600/1200 V. AC./
DC Resistance ×1,
×10, ×100, ×1000
(50Ω centre scale)
DC Current 30uA/
3/30/600mA. –20 to +63dB.

OUR PRICE £8.95 P & P 30p

U4324 MULTIMETER

High sensitivity, overload protected. 20,000opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistence: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: –10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

OUR PRICE £9.25 P&P 30p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.

OUR PRICE £13.50 P&P 30p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6/15/150/60/600mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.

OUR PRICE £10.25 P&P 50p

HIOKI 750X VOLT-OHM-MILLIAMETER

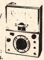

43 ranges: 0–0.3/0.6/1.5/3/6/12/30/60/150/300/600/1,200V DC. 0–3/6/15/30/60/120/300/600/1,200V AC. Current: 0–30/60uA/1.5/3/15/30/150/300 mA/6/12A. Resistence: 0–3/300k/3/30Mohms. Decibels: –10 to +17dB. Output: – 0–3/6/15/30/60/120/300V. Accuracy ± 3% DC, ± 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.

OUR PRICE £11.95 P&P 40p

TMK MODEL TW50K

46 ranges, mirror scale. 50k/V DC 50k/V AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts 1.5/3/5/10/25/50/125/250/500/1000. DC current 25/50uA/2.5/5/25/50/250/500mA/5/10A. Resistence: 10k/100k/1 Meg/10 Meg ohms. –20 to +81.5dB.

OUR PRICE £12.50 P&P 20p

MODEL C7080EN

Giant 6" mirror scale. 20,000 opv. 0/0.25/1/2.5/10/50/250/1000/5000V DC. 0/2.5/10/50/250/1000/5000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. –20 to +50dB.

OUR PRICE £19.95 P&P 35p

MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.

OUR PRICE £13.95 Carr. paid

HIOKI MODEL 700X

100,000opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/500mA/6/12A DC. 2k/200k/2M/20MOhms. –20 to +63dB.

OUR PRICE £14.95 P&P 30p

MODEL AS.100D VOM

100,000 opv.
Mirror scale.
Built-in meter
protection. 0/3/
12/60/120/300/
600/1200V DC.
0/6/30/120/300/
600V AC. 0/10μA/
6/60/300mA/
12 Amp. 0/2K/
200K/2M/200 Meg
Ohm. – 20 to 17 dB.

OUR PRICE £17.50 P&P 30p.

KAMODEN HM720B FET VOM

Input impedence 10 Megohms. Ranges: – 0/.25/1/2.5/10/50/1000V DC. 0/2.5/10 50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms

**OUR PRICE
£21.00** P & P 40p

KAMODEN 360 MULTIMETER

High sensitivity, DC 100kohm/V AC 10kohm/V 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0,5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. Decibels –20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with, test leads etc.

OUR PRICE £17.50 P & P 40p

Model HT100B4 MULTIMETER

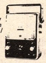

Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1-/50/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistence' 0–20/200k/2/20 Meg. ohms. DC current: – 10/250uA/2.5/25/250 mA/10A. AC current: –0–10A. –20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.

OUR PRICE £17.50 P&P 40p

370WTR MULTIMETER

Features AC current ranges. 20,000opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: –20 to +62dB.

OUR PRICE £19.95 P&P 30p

U4317 MULTIMETER

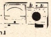

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm. mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000 V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: –5 to +10dB Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

OUR PRICE £16.50 P&P 40p

KAMODEN 72.200 Multitester

High sensitivity tester. 200,000 opv Overload protected. Mirror scale. Ranges: –0/.06/.3 3/30/120/600/1200V DC. 0/3 12/60/300/11200 V AC. 0/6uA/1.2mA/120mA/600mA/12A DC 0/12A AC. –20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.

OUR PRICE £22.50 P&P 30p

MODEL AF.105 VOM

50,000 opv. Mirror
scale. Meter
protection.
0/·3/3/12/60/120/
300/600/1200V DC.
0/6/30/120/.
300/600/1200V DC.
0/30μA/6/
60/300 mA/
12 Amp. 0/10K/
1m/10m/100
Meg Ohms. 20 to 17 dB.

OUR PRICE £12.50 P&P 30p.

TMK MODEL 117 FET ELECTRONIC VOLTMETER

Battery operated. 11 Meg input, 26 ranges. Large 4¼" mirror scale. Size: 149 x 117 x 60mm. 0.3–12000V DC. 3–300V RMS AC. 8–800V P-P. DC current 0.12–12mA. Resistence up to 2000MOhms. Decibels: –20 to +51dB. Supplied complete with leads and instructions.

OUR PRICE £18.50 P&P 20p

TMK 100K LAB TESTER

100,000opv. 6½" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC. 5k/V AC DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current 10/100uA/10/100/2.5/10A. Resistence: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: –10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.

OUR PRICE £19.95 P&P 30p

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.

**OUR PRICE
£4.50** P&P 20p

KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.

OUR PRICE £17.50 P & P 40p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.06/0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.

OUR PRICE £10.50 P&P 30p

S100TR MULTIMETER TRANSISTOR TESTER

100,000opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/600uA/12/300mA/6/12A DC 0/10k/1 Meg/100 Meg. –20 to +50dB. 0.01–0.2 MFD Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.

OUR PRICE £19.95 P&P 25p

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedence 52' Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.

OUR PRICE £4.25 P&P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1–25; HOR. AMP. Bandwidth: 500kHz. Sensitivity ay 100kHz VRMS/mm: 0.3–25 Preset triggered sweep 1–3000usec. Free running 20–200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115–230V AC.

OUR PRICE £43.00 Carr. paid

ALL PRICES EXCLUDE VAT

Also see following pages

SINCLAIR DM2 DIGITAL MULTIMETER

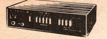

Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

RANGES:
DC VOLTS: 1v, 10, 100v, 1000v.
AC VOLTS: 1v, 10v, 100v, 1000v.
DC CURRENT: 1mA, 10mA, 100mA, 1000mA.
AC CURRENT: 1mA, 10mA, 100mA, 1000mA.
RESISTANCE: 1k, 10k, 100k, 1000k

OUR PRICE £59.95 P & P 50p

RUSSIAN CI16 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usec. to 100 milli-sec/cm. Free running time base, 50Hz–1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.

OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorbtion Wave Meter and Oscillating Detector. Frequency range 440kHz–280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £17.50 P&P 30p

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE

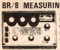

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pf-1110 mfd ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 ± 1% Bridge Voltage at 1,000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7⅜" x 5" x 2"

OUR PRICE £27.50 P&P 30p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.

OUR PRICE £8.97 P&P 30p

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly callbrated. Variable R.F. attenuator audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

OUR PRICE £19.95 P&P 50p

MODEL TE20 RF SIGNAL GENERATOR

Six bands. 120kHz–260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105–125V, 220–240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.

OUR PRICE £18.95 P&P 50p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sinewave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £37.50 P&P 50p

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz Sine Wave 19–100,000 Hz Square Wave. Output Sine or Square wave 10v. P. to P. Size 180 x 90 x 90mm. Operation 220/240v. A.C.

OUR PRICE £19.95 P&P 50p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedence 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.

OUR PRICE £24.95 P&P 50p

BELCO AT201 Decade ATTENUATOR

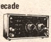

Frequency range 0–200kHz. Attenuator 0–111dB, 0.1dB steps. Impedence 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 55mm.

OUR PRICE £12.50 P&P 50p

DT 124 POWER UNIT

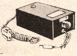

220–240V AC. Input–Output 6, 7.5 or 9V DC 400 mA.

OUR PRICE £2.20 P&P 50p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5–20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95 P&P 50p

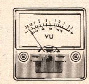

VU METER TYPE 3

Size: 33mm 20mm.

£1.25 P&P 15p

SDH8V MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedence. Frequency response 20Hz–18kHz. Complete with 10ft. coiled lead and jack plug.

OUR PRICE £4.97 P&P 30p

BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphone impedence 16 ohms. Microphone impedence 200 ohms.

OUR PRICE £5.95 P&P 30p

UNIPEX NT 100A

The unipex NT100A is a compact portable transistorised PA amplifier. This versatile unit has a maximum output of 10 watts RMS and operates on any 10-16V DC source, negative or positive ground and uses only 1.5A at rated output. Supplied complete with mounting brackets etc, plus full installation and operating instructions.

OUR PRICE £21.75 P&P 50p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Beau-walnut cabinet. 184 x 77 x 108mm.

OUR PRICE £7.50 P&P 30p

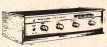

RANK AUDIO RA 210T STEREO AMPLIFIER

7½ 7½ watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate base, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer.

OUR PRICE £17.50 P&P 50p

VHF 105

This unit will give instant reception of the ground-to-air, air-to-ground waveband. Simply place beside any AM or FM Radio, covering 535–1605 kHz, 88–108 MHz – no conversion or connection required. This converter is self powered by one 9-volt (PP3 Type) battery and comes complete with a full set of instructions and battery.

OUR PRICE £3.50 P&P 50p

Just arrived – the sensational

WIEN ET1008 CASSETTE! RECORDER

A highly recommended cassette recorder at this really low Laskys price.

FANTASTIC VALUE!

ONLY £8.95 P&P 50p

SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 4D SOUND

 

This clever unit enables you to add 4D sound to your existing system. Complete with simple connection details. Use this converter (together with 2 extra speakers) to achieve the fantastic 4D quadrophonic sound! The effect of being immersed within the music becomes a thrilling new experience (2 year guarantee).

OUR PRICE £3.95 P&P 50p

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88–108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £8.95 P&P 20p

Stereo Multiplex Adaptor £5.95 extra

WALKIE TALKIES

SKYFON NV7
Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna.

OUR PRICE £31.50 per PAIR P.&P 50p.

NOT LICENSABLE IN THE U.K.

ELECTRONIC CALCULATORS

We carry a tremendous range of both pocket and desk calculators from as little as **£8.90** Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

MINIATURE ORGAN MUSIC MASTER AM100

Spanning nearly two octaves, including semitones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.

OUR PRICE £7.95 P&P 50p.

BINATONE DIGITAL CLOCK

Attractive ivory case. Large clear numbers for hours, minutes and seconds. A.C. 240V operation. Size approx. 6¼ x 3 x 3½ inches.

OUR PRICE £4.50 P&P 50p.

SINCLAIR ICI2 INTEGRATED CIRCUIT AMPLIFIER

complete with printed circuit mounting board.

OUR PRICE £1.50 P & P 15p.

SINCLAIR Project 80 Modules

Z40 Power Amp.	£5.95	P & P 15p
Z60 Power Amp.	£7.45	P & P 15p
Stereo 80 Pre-Amp.	£13.95	P & P 15p
Active Filter Unit	£7.45	P & P 15p
FM Tuner	£13.95	P & P 15p
Stereo Decoder	£8.95	P & P 15p
PZ5 Power Supply	£5.95	P & P 30p
PZ6 Power Supply	£8.95	P & P 30p
PZ8 Power Supply	£8.45	P & P 30p
Transformer for PZ8	£4.05	P & P 50p

SINCLAIR Project 80 Packages

2xZ40/Stereo 80/PZ5	£25.44	P & P 35p each
2xZ40/Stereo 80/PZ6	£27.84	
2xZ60/Stereo 80/PZ8	£29.84	

TE1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls, speakers on–off slide switch, stereo headphone socket.

OUR PRICE £2.25 P&P 15p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.57	£3.00	£7.08
C90	£2.24	£4.25	£10.00
C120	£2.73	£5.17	£12.24

P&P 3p each. 10 and over Post Free

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.

OUR PRICE £8.97 P&P 20p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £8.50 P&P 30p

JOSTY KIT

HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT Oxford Street, 42 & 257 Tottenham Court Road, 34 Lisle Street, 152, Fleet Street, 311 Edgware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

AF20 Mono amplifier	£5.61
AF25 Mixer	£3.29
AF30 Mono pre-amplifier	£3.20
AF35 Emitter amplifier	£2.42
AF80 0.5W mic. amplifier	£4.86
AF305 Intercom	£7.67
AF310 2 Mono Amplifier	£7.55
M160 Multi-vibrator	£2.18
M1302 Transistor tester	£8.33
M191 VU Meter	£5.37
M192 Stereo balance meter	£5.93
LF380 Quadraphonic device	£ 8.42
AT5 Automatic light control	£3.75
AT30 Photo cell switch unit	£6.68
AT50 400W triac light dimmer/speed control	£5.18
AT56 2,200W triac light dimmer/speed control	£6.75
AT60 1 channel light control	£10.82
AT65 3 channel light control	£16.52
GU330 Tremolo unit	£8.10
HF61 Diode detector	£3.87
HF65 FM transmitter	£3.21
HF75 FM receiver	£3.66
HF310 FM tuner	£16.32
HF325 Deluxe FM tuner	£26.33
HF330 Decoder (HF310/325)	£10.55
GP310 Stereo pre-amplifier for use with 2 x AF310	£22.98
GP312 Circuit board	£10.02
GP304 Circuit board	£5.33
HF380 lw/vhf aerial amplifier	£6.02
HF395 broadband aerial amp.	£2.10
NT10 Stabilised power supply 100mA, 9V	£6.27
NT300 Stabilised p. supply	£13.16
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2 amps	£5.64
NT305 Voltage converter	£5.64
NT315 Power supply 240V AC to4,5/15V DC, 500mA	£12.0

Amateur Electronics by Josty-Kit, the professional book for the amateur —covers the subject from basic principals to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.

OUR PRICE £3.30 (No VAT)
P&P 25p plus VAT.

AE1 100mW output stage	£1.55
AE2 Pre-amplifier	£1.32
AE3 Diode receiver	£2.05
AE4 Flasher	£1.26
AE5 Astable multi-vibrator	£1.14
AE6 Monostable multi-vibrator	£1.11
AE7 RC generator	£1.08
AE8 Bass filter	£1.05
AE9 Treble filter	£1.05
AE10 CCIR filter	£1.05

Also see previous page

ALL PRICES EXCLUDE VAT

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR 3 LISLE ST., 311 EDGWARE RD., & 152 FLEET ST., BRANCHES or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIG MODEL SD640
Size: 85 x 64mm

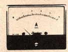

50uA	£3.90
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-50uA ..	£3.85
100-0-100uA ..	£3.80
1mA	£3.75
5mA	£3.75
10mA	£3.75
50mA	£3.75
100mA	£3.75
500mA	£3.75
1A DC	£3.75
5A DC	£3.75
10A DC	£3.75
5V DC	£3.75
10V DC	£3.75
20V DC	£3.75
50V DC	£3.75
300V DC	£3.75
15V AC	£3.85
300V AC	£3.85
VU Meter ..	£4.00

CLEAR PLASTIC MODEL SW100
Size: 100 x 80mm

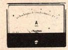

50uA	£4.70
100uA	£4.60
500uA	£4.40
50-0-50uA ..	£4.60
100-0-100uA ..	£4.55
1mA	£4.40
1A DC	£4.40
5A DC	£4.40
20V DC	£4.40
50V DC	£4.40
300V DC	£4.40
150V AC	£4.55
300V AC	£4.55
VU Meter ..	£5.00

EDGWISE MODEL PE70
Size: 90 x 34mm

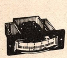

50uA	£4.25
100uA	£4.20
200uA	£4.15
500uA	£4.00
50-0-50uA ..	£4.20
100-0-100uA ..	£4.15
1mA	£3.95
300V AC	£4.05
VU Meter	£4.40

MODEL ED107 EDUCATIONAL METER
Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

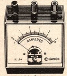

50uA	£8.70
100uA	£8.10
50-0-50uA ..	£8.10
1mA	£7.80
1-0-1mA	£7.80
1A DC	£7.80
5A DC	£7.80
5V DC	£7.80
10V DC	£7.80
15V DC	£7.80
20V DC	£7.80
50V DC	£7.80
300V DC	£7.80
500mA/5A DC	£8.80
5V/50V DC ..	£8.80
5V/15V DC ..	£8.80
1/5A DC	£8.80

CLEAR PLASTIC MODEL MR 85P
Size: 120 x 110mm

50uA	£5.60
100uA	£5.55
200uA	£5.50
500uA	£5.40
50-0-50uA ..	£5.55
100-0-100uA ..	£5.50
500-0-500uA ..	£5.35
1mA	£5.35
1-0-1mA	£5.35
5mA	£5.35
10mA	£5.35
50mA	£5.35
100mA	£5.35
500mA	£5.35
1A DC	£5.35
5A DC	£5.35
15A DC	£5.35
30A DC	£5.55
10V DC	£5.35
20V DC	£5.35
50V DC	£5.35
150V DC	£5.35
300V DC	£5.40
15V AC	£5.45
300V AC	£5.45
S Meter 1mA ..	£5.35
VU Meter	£5.70
1A AC	* £5.35 *
5A AC	* £5.35 *
10A AC	* £5.35 *
20A AC	* £5.35 *
30A AC	* £5.35 *

240° Wide Angle
1mA METERS

MW1-6 60 x 60 mm
£6.50 P & P 15p
MW1-8,80 x 80mm
£6·90 P&P 15p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0—260V.
MODEL S260 BENCH MOUNTING

		P&P
1A	£10.50	50p
2.5A	£12.00	50p
5A	£17.50	50p
8A	£30.35	£1.00
10A	£33.75	£1.00
12A	£35.40	£1.00
20A	£85.00	£1.50
25A	£95.00	£1.50
40A	£120.00	£1.50

ALL PRICES EXCLUDE VAT

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830
Size: 110 x 83mm

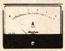

50uA	£4.40
100uA	£4.35
200uA	£4.30
500uA	£4.25
50-0-50uA ..	£4.35
100-0-100uA ..	£4.30
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
10A DC	£4.20
5V DC	£4.20
10V DC	£4.20
20V DC	£4.20
50V DC	£4.20
300V DC	£4.20
15V AC	£4.30
300V AC	£4.30
VU Meter	£4.50

CLEAR PLASTIC MODEL MR 45P
Size: 50 x 50mm

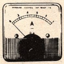

50uA	£3.30
100uA	£3.25
200uA	£3.20
500uA	£3.10
50-0-50uA ..	£3.25
100-0-100uA ..	£3.20
500-0-500uA ..	£3.05
1mA	£3.05
5mA	£3.05
10mA	£3.05
50mA	£3.05
100mA	£3.05
500mA	£3.05
1A DC	£3.05
5A DC	£3.05
10V DC	£3.05
20V DC	£3.05
50V DC	£3.05
300V DC	£3.05
15V AC	£3.15
300V AC	£3.15
S Meter 1mA ..	£3.05
VU Meter	£3.50
1A AC	* £3.05 *
5A AC	* £3.05 *
10A AC	* £3.05 *
20A AC	* £3.05 *
30A AC	* £3.05 *

CLEAR PLASTIC MODEL MR 38P
Size: 42 x 42mm

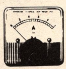

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£2.90
50-0-50uA ..	£3.15
100-0-100uA ..	£3.10
500-0-500uA ..	£2.85
1mA	£2.85
1-0-1mA	£2.85
2mA	£2.85
5mA	£2.85
10mA	£2.85
20mA	£2.85
50mA	£2.85
100mA	£2.85
150mA	£2.85
200mA	£2.85
300mA	£2.85
500mA	£2.85
750mA	£2.85
1A DC	£2.85
2A DC	£2.85
5A DC	£2.85
10A DC	£2.85
3V DC	£2.85
10V DC	£2.85
15V DC	£2.85
20V DC	£2.85
50V DC	£2.85
100V DC	£2.85
150V DC	£2.90
300V DC	£2.90
500V DC	£2.95
750V DC	£2.95
15V AC	£2.95
50V AC	£2.95
150V AC	£2.95
300V AC	£2.95
500V AC	£3.10
S Meter 1mA ..	£2.85
VU Meter	£3.30

CLEAR PLASTIC MODEL SD460
Size: 59 x 46mm

50uA	£3.60
100uA	£3.55
200uA	£3.50
500uA	£3.45
50-0-50uA ..	£3.55
100-0-100uA ..	£3.50
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
5V DC	£3.40
10V DC	£3.40
20V DC	£3.40
50V DC	£3.40
300V DC	£3.40
15V AC	£3.55
300V AC	£3.55
VU Meter	£3.75

POSTAGE & PACKING 15p

CLEAR PLASTIC MODEL MR 65P
Size: 86 x 78mm

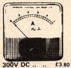

50uA	£4.05
100uA	£3.95
200uA	£3.90
500uA	£3.85
50-0-50uA ..	£3.95
100-0-100uA ..	£3.90
500-0-500uA ..	£3.80
1mA	£3.80
1-0-1mA	£3.80
5mA	£3.80
10mA	£3.80
50mA	£3.80
100mA	£3.80
500mA	£3.80
1A DC	£3.80
5A DC	£3.80
10A DC	£3.80
15A DC	£3.80
20A DC	£3.90
30A DC	£3.95
50A DC	£4.15
5V DC	£3.80
10V DC	£3.80
15V DC	£3.80
20V DC	£3.80
50V DC	£3.80
150V DC	£3.80
300V DC	£3.80
15V AC	£3.90
50V AC	£3.90
150V AC	£3.90
300V AC	£3.90
500V AC	£4.00
S Meter 1mA ..	£3.90
VU Meter	£4.20
1A AC	* £3.80 *
5A AC	* £3.80 *
10A AC	* £3.80 *
20A AC	* £3.80 *
30A AC	* £3.80 *
50mA AC ..	* £3.80 *
100mA AC ..	* £3.80 *
200mA AC ..	* £3.80 *
500mA AC ..	* £3.80 *

BAKELITE MODEL S80 Enlarged Window
Size: 80 x 80mm

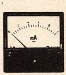

50uA	£4.60
100uA	£4.55
500uA	£4.30
50-0-50uA ..	£4.55
100-0-100uA ..	£4.50
1mA	£4.30
1A DC	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30
300V AC	£4.40
VU Meter ..	£4.80

CLEAR PLASTIC MODEL MR 52P
Size: 60 x 60mm

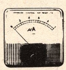

50uA	£3.80
100uA	£3.60
500uA	£3.45
50-0-50uA ..	£3.60
100-0-100uA ..	£3.45
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10V DC	£3.40
20V DC	£3.40
50V DC	£3.40
300V DC	£3.40
15V AC	£3.50
300V AC	£3.50
S Meter 1mA ..	£3.40
VU Meter	£3.90
1A AC	* £3.40 *
5A AC	* £3.40 *
10A AC	* £3.40 *
20A AC	* £3.40 *
30A AC	* £3.40 *

BAKELITE MODEL MR 65 Size: 80 x 80mm

25uA	£5.40
50uA	£4.10
100uA	£4.05
500uA	£3.75
50-0-50uA ..	£4.05
100-0-100uA ..	£4.00
500-0-500uA ..	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
2A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
30A DC	£3.70
50A DC	£3.90
5V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70
300V DC	£3.90
30V AC	* £3.70 *
50V AC	* £3.70 *
150V AC	* £3.70 *
300V AC	* £3.70 *
500V AC	* £3.70 *
VU Meter	£4.20
1A AC	* £3.70 *
5A AC	* £3.70 *
10A AC	* £3.70 *
20A AC	* £3.70 *
30A AC	* £3.70 *
50A AC	* £3.70 *
500mA AC ..	* £3.70
50mV DC ..	£3.85
100mV DC ..	£3.85

ASK LASKYS about Hi fi

CALL INTO YOUR NEAREST LASKYS BRANCH OR SEND COUPON BELOW FOR NEW 32 PAGE HI-FI PRICE LIST

CENTRAL LONDON

481 OXFORD ST	01-493 8641
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833
10 TOTTENHAM CT. RD.	01-637 2232
27 TOTTENHAM CT. RD.	01-636 3715
33 TOTTENHAM CT. RD.	01-636 2605
42/45 TOTTENHAM CT. RD.	01-636 0845
257/8 TOTTENHAM CT. RD.	01-580 0670

ESSEX

86 SOUTH ST. ROMFORD	20218
205/206 CHURCHILL WEST, VICTORIA CIRCUS, SOUTHEND	0702 612241

GLOUCESTERSHIRE

16/20, PENN ST. BRISTOL 0272-20421

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS
0892-23242

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER
0533-537678

NORTHAMPTONSHIRE

73 ABINGTON STREET,
NORTHAMPTON 0604-35753

STAFFORDSHIRE

30 WULFRUM WAY, WOLVERHAMPTON
0902-23384

SURREY

1046 WHITGIFT CENTRE, CROYDON	01-681 3027
38/40 EDEN ST., KINGSTON	01-546 1271
32 HILL ST. RICHMOND	01-948 1441

WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM
021-236 3503

ALL BRANCHES OPEN FROM 9am to 6pm MON TO SAT

OUR CUSTOMER SERVICES DIVISION at head office will answer all your enquiries – just ring **01-200 1321**

EXPORT Personal exports arranged for overseas visitors. Goods specially packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.

BARCLAYCARD & ACCESS

Phone your order to 01-200 0037 or call into any branch

NO DEPOSIT TERMS available on most goods for personal callers

CHEQUES TO THE VALUE OF £30. ACCEPTED FROM PERSONAL SHOPPERS WITH BANKERS CARD. IN OTHER CASES AND FOR AMOUNTS IN EXCESS OF £30. PLEASE ALLOW TIME FOR CLEARANCE. BANKERS DRAFTS ACCEPTED.

All prices correct at 13/1/75
subject to change without notice E.&O.E.

A member of the Audiotronic Group of Companies

FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 8% VAT to total value of goods including post and packing.

TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ. Tel:01-200 1321

Please send me the following items ______________________

TOTAL PURCHASE PRICE ______________ (inc. P&P and VAT)

32 Page HI-FI PRICE LIST	TICK HERE
	☐

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is ☐

NAME ______________________

ADDRESS ______________________

Signature ______________________

Registered in England No. 347947 at 12 Lower Grosvenor Place. London SW1 0EX PE3

Whether your project is electrical or electronic, SCS Components have a complete professional service for the non-professional. We are franchised distributors of Mullard components and Motorola, Ferranti, Signetics, G.I. and Monsanto, too. Our Trade Counter can supply you with all you need, including first-class technical advice. Or simply send cash with your order.

Never before have you been able to get top quality, guaranteed components so quickly, so inexpensively. Send for a free copy of our latest price list. Try us; we think you'll notice the difference.

SCS Components,
Northfield Industrial Estate,
Beresford Avenue, Wembley,
Middlesex HA0 1SD
Tel: 01-903 3168

PLEASE SEND ME ____ COPIES OF YOUR
FREE PRICE LIST
NAME
ADDRESS

PE

ON GUARD

WHILE technology continually advances, bringing many improvements at the material level, human nature on the other hand seems to undergo little change with the passage of time. For instance, the struggle waged between occupier and trespasser, and between owner and would-be purloiner goes on just as relentlessly today as it did in times long past.

The odds against the criminal have not altered much either, it seems, despite the increasing involvement of electronic and other technical aids. In fact electronics is probably responsible to some extent for the greater abundance of valuable, and often portable, loot that tempts today's criminals. The villains also have access to advanced technology and can, if they are sufficient determined, surmount or otherwise render innoxious many of the security systems created to deter or defeat them. The safest intruder detection systems obviously are those that do not advertise their presence, or at any rate their vital sensing elements. For in the final reckoning it is immunity from hostile action that makes a security system really 100 per cent. effective.

In this regard security systems relying upon invisible radiations have considerable advantages. Both infra-red and radio frequencies are used in security applications. Some of the more advanced commercial systems employ microwaves and exploit the Doppler shift effect to detect the presence and movement of a body within a protected area. But the use of radio transmitters does bring both the equipment and the intended user within the jurisdiction of the official licensing authority (currently the Home Office, Radio Regulatory Division). The complications involved (which include obtaining design approval for the apparatus concerned) are not likely to be worthwhile for the average person who wishes to build and install his own intruder detection system without fuss or bother. Such needs however are likely to be fully met by a Doppler shift system using ultrasonic radiations. This method can be highly effective in detecting the slightest of movements within the area under surveillance and presents none of the problems of licensing which are associated with radio frequency versions.

This month's design for an Ultrasonic Doppler Shift Intruder Alarm has been fully tested and has proved highly sensitive and consistent in performance in rooms of varying size. Undoubtedly this project will be the answer in many cases where effective monitoring of an enclosed area is required. The equipment can be installed unobtrusively so that its presence (or purpose) is not suspected by unauthorised persons, thus saving it from malicious attentions of technically knowledgeable anti-social types. The importance of this aspect cannot be over-stressed. Electronic techniques can be used for defensive or offensive purposes, and the technical capabilities and resources of today's criminal classes must not be underestimated in any degree.

INCREASE IN COVER PRICE

With effect from this month, the cover price of PRACTICAL ELECTRONICS is increased by 5p to 30p. Further substantial rises in the cost of paper are chiefly responsible. We naturally regret the need for this increase but trust our readers will understand that it is unavoidable.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

ULTRASONIC INTRUDER

A SIMPLE ultrasonic intruder alarm can be made in which the alarm is triggered when the intruder breaks the ultrasonic beam. Unfortunately such a simple arrangement is not very satisfactory since it may be impossible to ensure that an intruder will always pass through the beam. In addition, this type of equipment must be set up very carefully or a sufficient part of the ultrasonic signal will reach the receiver even when the intruder is in the beam and his presence will remain undetected.

This article describes an ultrasonic intruder alarm based on the Doppler shift principle. It can detect the movement of any object within a room when the object has dimensions of not less than a few cms. For example, it has been found that if a person inside the protected area breathes in, the movement of his chest can trigger the alarm. The movement of a person's hand at a speed exceeding about one inch per second can trigger the alarm.

Whilst there is some variation in sensitivity from one point to another the equipment is usually effective throughout most of the volume of a room and there is no necessity for a burglar to be in any particular region of the room for detection to take place.

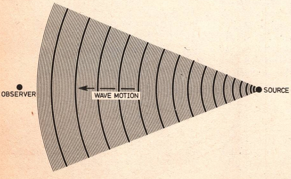

Fig. 1. Wave motion from source to observer, showing how Doppler effects can be observed

DOPPLER SHIFT

The basics of Doppler shift are familiar to everyone who has detected a fall in the frequency of the note received as a fast moving noisy object passes by him. This fall is very apparent in the case of low flying aircraft or when a car passes close to the observer with its horn sounding.

Similarly, if an observer moves towards a stationary source of sound, the frequency he observes will be higher than that emitted by the source.

THEORY

Let us imagine that the stationary source shown in Fig. 1 emits waves at a frequency of fHz. If the observer is stationary, f waves will pass him per second and he will therefore observe this frequency. If, however, the observer moves towards the source, he will meet more waves per second, since these additional waves are distributed in the space through which he is moving.

The wavelength, λ, of the waves is equal to v/f metres where v is their velocity in metres/second. If the observer moves towards the source with a velocity of b metres/second, he will meet an additional $b/\lambda = bf/v$ waves per second. Thus he meets a total of $(f + bf/v) = f(1 + b/v)$ waves per second. In other words, the movement of the observer towards the source causes the frequency he receives to be raised from f to $f(1 + b/v)$ Hz.

If the observer moves towards the source with a velocity of 1% of the velocity of sound (namely about 3 m/s), the received frequency will be raised by 1%. If the waves are reflected from the observer back towards the source, a person at the source will find that the reflected waves are raised in frequency by twice this amount (that is, by 2%). This is because the observer is reflecting the waves at the

DOPPLER SHIFT ALARM

By J. B. DANCE M.Sc.

frequency he is receiving them, but these reflected waves occupy a shorter distance in space owing to the movement of the observer towards the source.

A similar change will occur when the observer moves away from the source, but the frequency of the reflected waves will then be lower than the transmitted frequency.

ULTRASONICS

Let us consider the Doppler effect in ultrasonics when a transducer is employed which emits waves at the typical frequency of 40kHz. If a reflecting object moves at 3m/s, the reflected waves reaching the transducer will have a frequency shift of about 2% of 40kHz, namely 800Hz.

In the case of an intruder moving about in a room, the major components of the velocity of parts of his body are more likely to be in the range 20 mm/s to 1 m/s. The reflected waves therefore reach the transmitter with a frequency shift of roughly 5Hz to 300Hz.

In the present project the transmitting transducer and the receiver of the reflected waves are not in the same position. This will cause the frequency shift to be somewhat reduced (depending on the relative position of the reflecting object), but nevertheless the frequency change will be of the same order. The equipment must therefore be designed to detect shifts in the low audio and sub-audio frequency ranges.

POSSIBLE TECHNIQUES

Various techniques can be employed to detect the frequency shift. All depend on the detection of the frequency difference between the emitted and received frequencies and not on measurement of the frequencies themselves.

It is possible to employ a single ultrasonic transducer to transmit ultrasonic pulses and during the intervals between the pulses, use the transducer as a receiver of the reflected signals. This would complicate the circuit so much that it would outweigh the saving in the cost of an extra transducer.

BEAT NOTE

In order to keep the project as simple as possible a system which will detect the beat note developed when the transmitted frequency and the Doppler shifted reflected frequency reach the receiver simultaneously is used.

The signal from the receiver transducer is greatly amplified at 40kHz before it is fed to a diode pump circuit. By a suitable choice of time constant, most of the 40kHz signal can be filtered out to leave the audio or sub-audio beat note. This is used to drive a level detector circuit which, in turn, operates a relay.

TRANSMITTER

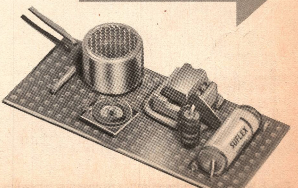

TRANSMITTER CIRCUIT

The circuit of the transmitter is shown in Fig. 2. A 555 integrated circuit is employed so that the circuit can be as simple as possible.

The output at pin 3 continually switches between potentials slightly above that of the negative line and slightly below that of the positive line. This square voltage waveform drives the transducer. The frequency is set by VR1.

THE TRANSDUCERS

The output of the 555 is used to operate a new type of miniature ultrasonic transducer, the 96D-40. This is available in "T" and "R" types for the transmitter and receiver respectively. Optimum results will be obtained only if the "T" type is used in the transmitter and the "R" type in the receiver, although results may be obtained if these units are interchanged.

TRANSMITTER

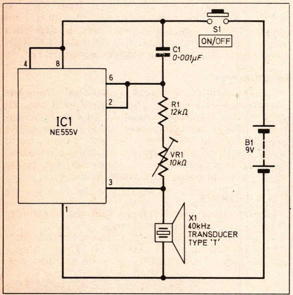

Fig. 2. The transmitter circuit

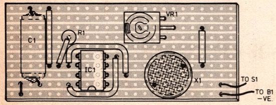

Fig. 5. Component layout and Veroboard cuts for the transmitter of Fig. 2

These transducers contain small piezo-ceramic "bimorph" plates sealed in a small aluminium cylinder slightly over ½in in diameter. There are two connecting pins on the back and the one connected to the aluminium case should be earthed. The ceramic plates resonate at about 40kHz and cannot be used at frequencies which are more than about 1kHz from this frequency.

When the square wave voltage from the 555 circuit is applied to the transmitter transducer, the ceramic plate resonates and emits an ultrasonic pressure wave into the air through the metal grille at the front of the device.

COMPONENTS . . .

TRANSMITTER

IC1	NE555V timer i.c.
C1	0·001μF, 15V, 10% mica or polystyrene
R1	12k Ω, 10%, 0·1W
VR1	10k Ω preset trimmer
X1	40kHz transducer type T, 96D–40 (Hall Electronjcs)
S1	SPST on/off switch
B1	9V battery or suitable p.s.u.

RECEIVER

Resistors

R1	6·8k Ω
R2	100 Ω
R3	100k Ω
R4	390k Ω
R5	10k Ω
R6	10k Ω

All 10%, 0·1W or larger.

Capacitors

C1	25μF (Fig. 3), 8μF (Fig. 4), 15V elect.
C2	8μF 15V elect.
C3	8μF 15V elect.
C4	8μF 15V elect.
C5	47pF polystyrene or mica
C6	0·01μF 63V polyester
C7	10nF (Fig. 3), 0·1μF (Fig. 4)
C8	0·1μF (Fig. 3), 1·0μF (Fig. 4)
C9	500μF (Fig. 3), 0·01μF (Fig. 4)
C10	1μF
C11	0·1μF

Semiconductors

IC1	TAA930 (Phoenix Electronics Ltd., 139 Havant Rd., Portsmouth, PO6 2AA)
IC2	LM380N audio power amplifier
TR1	C450, BC109, etc.
TR2	D40C1 Darlington device (Jermyn Industries Ltd., Vestry Estate, Sevenoaks, Kent)
D1-5	HG1011, OA95, OA81, 1N914, 1S914, etc. (5 off)

Miscellaneous

Transducers, 96 D–40 types T and R for transmitter and receiver respectively (Hall Electronics, 48 Avondale Rd., Leyton, London, E.17.). 8Ω loudspeaker. Relay RLA, 12V with 2 pair changeover contacts, e.g. GPR100 (Pye TMC Components, Roper Rd., Canterbury, Kent). 8- and 14-pin d.i.l. sockets if required. Veroboard to suit. Die-cast boxes or cases made to suit. Batteries or power supply, wire, solder, etc.

BASIC RECEIVER

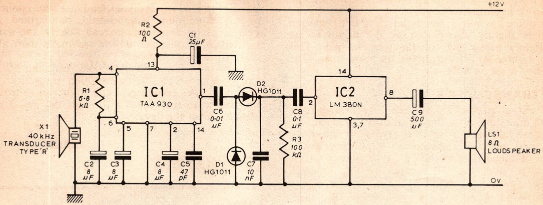

Fig. 3. Circuit diagram of the basic ultrasonic receiver

THE RECEIVER

When an ultrasonic signal strikes the transducer in the receiver a 40kHz signal appears across the transducer terminals. The amplitude of this signal may be of the order of 100µV. One can amplify this signal by using discrete transistors, but a TAA 930 integrated circuit has been used in this project since it greatly reduces the number of components required.

One of the first circuits used by the writer to detect the beat frequency is shown in Fig. 3. The 40kHz signal from the transducer is first amplified by the TAA 930.

This integrated circuit is actually intended for use in the sound section of television receivers as a 5·5MHz i.f. amplifier/limiter and demodulator. It contains four cascaded differential amplifiers coupled by emitter followers and allows a high gain to be obtained with stability.

The 40kHz output of the amplitude limiter at pin 10 is just over 1V peak-to-peak when the input to pin 4 exceeds the threshold value of about 50µV. However, the signal at pin 10 is internally connected to the section of the TAA 930 intended for use as an f.m. demodulator. It was found that a low impedance 8V peak-to-peak 40kHz signal could be obtained from pin 1 (which is the audio output when the device is used in television receivers).

In the circuit shown, the output from pin 1 is fed to a diode pump which has a load with a 1 ms time constant. The audio beat note is developed across this load and in Fig. 3 is fed to an LM380N audio power amplifier which drives a loudspeaker.

IN USE

The transmitter is placed a few feet from the receiver and VR1 of Fig. 2 is adjusted until a maximum voltage is obtained across C7 of Fig. 3. Whenever a person moves his hand or any other object fairly rapidly in the room, the beat note is heard in the loudspeaker. If the movement is very slow, the beat note frequency becomes too low to be heard, as would be expected from the theory.

RELAY DRIVE

The circuit of Fig. 4 is used with the transmitter of Fig. 2 as a true intruder alarm.

As in the circuit of Fig. 3, a low amplitude beat note is formed across C7 of Fig. 4. This is amplified by TR1. This transistor may be any low cur-

RECEIVER ALARM CIRCUIT

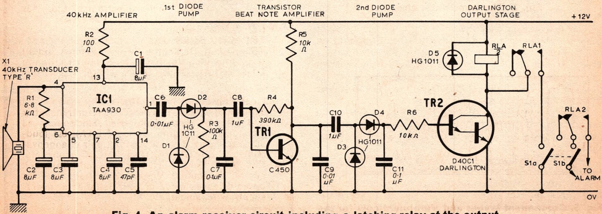

Fig. 4. An alarm receiver circuit including a latching relay at the output

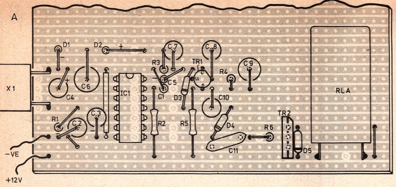

Fig. 6. Component layout and Veroboard cutting details for the receiver of Fig. 4. Note the mounting of the transducer and the extra board space which may be used for power supply or other items

rent, high gain *npn* transistor. Large coupling capacitors are used so that the circuit will be sensitive to the low (sub-audio) frequency beat notes which occur when the intruder moves slowly.

The output from TR1 is fed to a second diode pump, D3 and D4. This converts the beat note into a steady voltage. When this steady voltage across C11 exceeds about 1·1V, it drives the D40C1 Darlington device into conduction and the relay closes.

The diode D5 across the relay merely removes the transient reverse voltages which appear across the relay coil when the current falls. If D5 is omitted, these transients may damage the D40C1 device. Whilst the writer employed HG1011 diodes, any small low power germanium (or silicon) diodes should be satisfactory in this application. OA95 and OA81 are suitable.

LATCH-ON

When the switch S1 is open, the relay will open and close as the amplitude of the beat note rises and falls. The circuit should be tested with S1 open so that one can ascertain how much movement is required to close the relay without having to open S1 in order to de-energise the relay for the next test.

When S1 is closed, the relay will be energised by the beat note as before, but a current will now continue to flow through the relay coil and the contacts RLA1 even when the beat note has ceased. The relay will therefore remain latched on. Contacts RLA2 remain closed after the alarm has been triggered until the equipment is reset by opening the switch S1.

CONSTRUCTION

The transmitter and the final form of the receiver may be made up to suit individual requirements on Lektrokit, p.c.b. or on Veroboard. The transmitter layout is not at all critical but it would be wise with the receiver to keep the input leads as short as possible as the high amplification used can make the unit sensitive to external stimuli.

The prototypes shown in Figs. 5 and 6 are mounted on Veroboard for convenience and component layouts and board cutting details are shown in the figures.

Both models were constructed with a view to mounting in fairly confined spaces both because they are in any case not very large anyway and because this aids concealment if it is not wished to advertise the presence of security equipment. Each unit could be mounted in a false book back made from an old book from which the "heart" had been cut. The aperture required in the book spine can be covered with fine muslin and painted or dyed to suit the rest of the book.

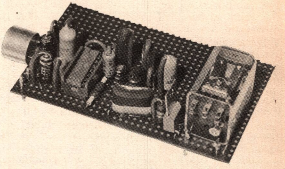

As can be seen, the receiver is mounted on a larger than needed piece of Veroboard so that, if required, a power supply or, for that matter, batteries, can be mounted on the same board.

If the constructor wishes to mount the units in plain boxes this is equally simple and 6 B.A. holding bolts can be used to secure the boards in place in any suitable die-cast or plastic box without trouble. Of course an aperture would have to be provided in one box wall to which the transducer is presented.

The switch S1 is not mounted on the receiver board as its operation "arms" the system when the transmitter is operating. If set-up by someone in the same room who then leaves, obviously the alarm will be actuated. Under normal circumstances one would house this set/reset switch outside the area to be protected.

ADJUSTMENTS

When each power supply is first connected the current consumption should be checked. It should be about 8mA for the transmitter and about 15mA for the receiver with the relay not operated.

The units should be placed so that the transducers are close together and facing each other. A high impedance voltmeter is placed across C7 of Fig. 4. VR1 of Fig. 2 is adjusted for a maximum reading on this meter. The units are then separated by a few feet and rotated so that the transducers no longer face one another as shown in Fig. 7. A fine adjustment is made to VR1 for maximum reading on the meter connected in the relay unit.

This frequency adjustment ensures that the 555 oscillator frequency matches the resonant frequency of the two transducers.

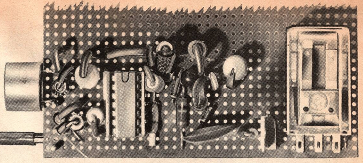

PRACTICAL POINTS

When the prototype units were close together with the transducers facing one another, it was found that the relay always remained closed even when no movement was occurring within the room. Presumably enough of the 40kHz signal then reaches TR1 for it to operate the second diode pump. Variations will occur with the gain of the components used in the relay unit, but the equipment should be set up so that swamping of the receiver transducer by the transmitted frequency does not occur.

Variations of the arrangement shown in Fig. 7 seem to be best. The two transducers point away from one another towards opposite walls of the room. The reflected signal from an intruder and the reflected signal from the walls of the room will then have amplitudes of the same order and optimum sensitivity will be obtained.

As shown the area immediately in front of the transducers is the most sensitive. Regions well away from the front of the transducers are less sensitive, whilst the areas behind the equipment are least sensitive of all. When testing the equipment, remember that one cannot always expect to obtain a beat note if one moves so that one keeps the same distance from the equipment. In practice this is virtually impossible in the most sensitive areas but it may be possible by moving one's hand above the transducers.

CONCLUDING COMMENTS

The circuit is sensitive to movement over almost the whole of the room containing the equipment. It is virtually impossible for an intruder to enter the room without triggering the system when the equipment is working.

Obviously the equipment has room size limitations but it has been tested successfully in rooms up to 17 × 17ft. Clearly, in a large room some thought should be given to the placing of the equipment in relation to the doors and windows of the room and in relation to any valuable objects requiring special protection.

Remember to shut all windows in the protected room before the equipment is switched on. Otherwise a curtain blowing in the breeze or a bird entering the window can easily trigger the alarm and someone may be aroused from his bed in the early hours of the morning!

If one wishes to have very complete protection, one may arrange that the alarm sounds when either the normally closed contacts of RLA open or when the normally open contacts close. If the intruder cuts the wires to RLA or joins them, the alarm will then sound.

The intruder alarm can, incidentally, form a useful party game where one has to move out of the room extremely slowly without triggering the alarm. In order to give people a reasonable chance, the gain may be reduced by including a resistor in the emitter circuit of TR1.

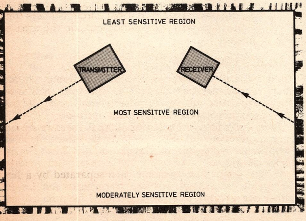

Fig. 7. Locations of the transmitter and receiver in a room for best general effect showing, in general terms, the variations in sensitivity

CRITICAL SETTINGS

The basic circuit does not include the gain control mentioned above and readers may find that in use the receiver is sometimes too sensitive, reacting constantly. A simple way of avoiding this is to detune the transmitter slightly by adjusting VR1.

Further, the receiver will not operate with a reduced power supply and operation will in any case be erratic if supply variations are allowed. So good batteries or a stabilised supply are needed.

The manufacturers' tolerances for the transducers used dictate the final maximum voltages used. As this is 7V the transmitter line voltage should not exceed 9V.

The larger board used in the prototype receiver was selected specifically to accept a small power supply suitably stabilised and set to give the required rail voltages. If the two units are positioned close together, as perhaps in a pair of book ends, then it is not difficult to envisage interconnection and of course supply of the mains voltage.

Output could be along a three-core cable carrying both the connections for S1 and the output switched with a common wire. Thus the system can be wired into an existing system as a simple switch if required. ★

PE MINISONIC

By G. D. SHAW

PART FIVE

- **Making the most of the MINISONIC**

IN THIS the final part of the Minisonic series we will look at some of the ways in which the units of the Minisonic can be connected to produce some interesting effects. These are only suggestions, since the ways in which the Minisonic can be used are limited only by the imagination of the user.

THE VOLTAGE CONTROLLED FILTER

There are three principal ways in which the filter may be used as a sound treatment, of which two have been examined during the check-out procedure. Before going into these in any detail however let us look for a moment at what exactly it is that the filter does to the sawtooth waveform.

Fig. 5.1 illustrates a number of waveforms with the filter control voltage at different levels. In stage one the control voltage is very low i.e. with the frequency control just off the minimum end stop. If the sawtooth signal is around 1kHz say, the effect of the filter is to remove virtually all the upper harmonics leaving the fundamental which is almost of sine form.

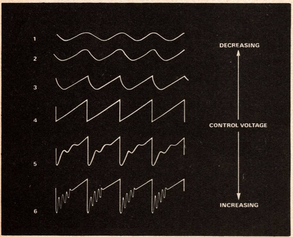

Fig. 5.1. These waveforms illustrate the effect of the VCF on a sawtooth waveform with varying control voltages. The control voltage increases from a minimum at 1 to a maximum at 6

Stage two and three illustrate the situation which occurs when the control voltage is increased successively; in each case the output waveform is assuming more of the sawtooth characteristic albeit still severely rolled off.

In stage four the control voltage is such as to allow the filter to admit the whole of the sawtooth without any roll-off.

Q CONTROL

The degree of roll-off of the filter is affected very largely by the amount of feedback admitted to the ladder network by means of the Q control. With Q at minimum the roll-off is much less accentuated and, indeed, the signal level from the filter is significantly greater than when the Q is at maximum.

Thus, with the Q at minimum the filter can act very much in the same way as a tone control i.e. passing all those frequencies lying below that set by the control voltage and rolling-off all those which lie above the set value at around 6dB per octave.

Increasing the feedback above a critical point will induce the filter to commence self oscillation. Similarly when operating at high Q the filter will also begin to oscillate when the control voltage is advanced beyond a point where the input signal is wholly accepted. This situation is illustrated in stages five and six of Fig. 5.1, the frequency of oscillation being proportional to the increase in ladder current.

What applies, in general terms, to the changes occurring in a sawtooth waveform also applies to other waveforms which are rich in harmonics. In the case of a sine wave input however the effect of the filter is simply to cause a variable degree of attenuation to the signal in a manner dependent on the input frequency, control voltage and Q control settings.

USING THE FILTER AS A VCA

Fig. 5.2 illustrates schematically the method of patching to enable the filter to act as an automatic Waa-Waa or as a voltage controlled amplifier.

In this case the negative output of the CONTROL ENVELOPE INVERTER is patched into the control input (jack socket) of the filter. The VCA level control on channels 1 and 2 should be turned to minimum level and the output of the filter patched into either one of the PA stages.

Set the INVERTER level control about midway with the attack and decay controls of ES1 set about one third of their full rotation.

Place the stylus momentarily on the keyboard and when the resultant sound has decayed away—say in four or five seconds—adjust the frequency control of the filter so that the VCO signal is just barely audible.

The keyboard may now be played in the normal way during which time the attack, decay and control envelope controls may be adjusted to achieve the desired effect. Note that the greater the level of the control envelope the harsher will be output signal when the envelope is at its peak.

An inverted Waa-Waa effect can be achieved by setting the filter frequency control to maximum and using the positive going envelope to programme the filter. In this case the output of the filter should be patched into VCA1 external input with VCO1 level control set to minimum.

TRACKING THE VCO's

With the arrangement of patching as shown in Fig. 5.3 the filter may be used to track the frequency of the VCO's. This is because the control input of the filter is directly linked to the output of the HOLD circuit and thus variations in this level will adjust the passband of the filter.

This method of operation is particularly useful if the instrument is being used in an imitative sense or if the constructor wishes to achieve a softer, harmonically reduced output signal. With this mode, the keyboard should be played at the same time adjusting the filter frequency and Q controls until the desired sound is achieved.

It will be found that a number of acoustic instruments can be effectively imitated using this method. For example, wind instruments such as the horn and trombone, string instruments such as the violin and cello and a clarinet tone have all been successfully synthesised with the prototype Minisonic.

THE FILTER AS A TONE CONTROL

In the previous method of operation the passband of the filter was continuously being adjusted as the keyboard was being played such that the proportion of harmonic roll-off was effectively constant regardless of the frequency of the input signal.

If an open circuit jack plug is now placed into the control input socket of the filter the passband is now entirely dependent on the setting of the frequency control. With this at maximum the filter will pass frequencies up to 15kHz (−6dB) more, in fact, than the Minisonic would normally produce in a strictly musical sense.

With the frequency control near its minimum setting the −6dB passband is only 3Hz and thus the greater part of any filtered musical signal from the VCO's would not reach the power amplifier stages.

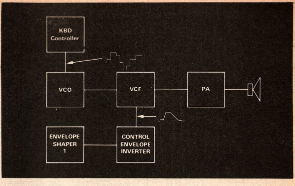

Fig. 5.2. Diagram showing the patching arrangement to use the voltage controlled filter as a Waa-Waa

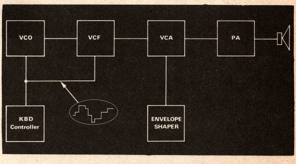

Fig. 5.3. With the patching arrangement shown here the VCF will track the frequency of the VCO's

The filter is now acting as a treble cut system with the degree of cut obtainable being varied by the Q control. With this at minimum the roll-off is about 6dB per octave and at maximum about 15dB per octave.

THE RING MODULATOR

The overall function of the RING MODULATOR has been described elsewhere in this series but it might perhaps be useful to consider some of the uses to which it can be put. In a musical sense the RING MODULATOR can be used to create very rich chord structures.

For example, with both VCO's tuned apart by the interval of a fifth, i.e. the frequency of one oscillator is 1·5 times the frequency of the other, the output from the ring modulator will be, in the case of the sum frequency, 2·5 times, and in the case of the difference, 0·5 times, the frequency of the oscillator producing the lowest pitch.

If the output of this latter oscillator is taken as being the fundamental then the output of the RING MODULATOR may be said to comprise the sub-octave and twelfth with respect to the fundamental.

If this signal is now mixed with the outputs of the VCO's originating the signals then the end result is a four note, musically concordant chord.

Similar effects may be obtained when the VCO's are in unison, an octave apart or tuned to other recognisable musical intervals. In all cases the richness of the resultant sound quite belies the size and complexity of the instrument producing it.

Two methods of patching in the RING MODULATOR to give composite chords are illustrated in Fig. 5.4a and 4b.

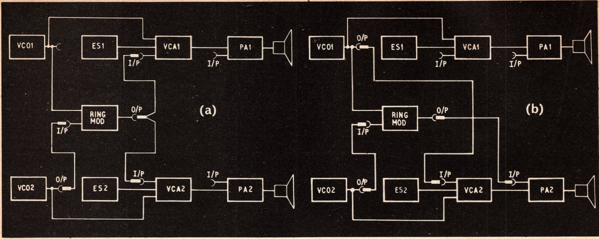

Fig. 5.4a and b. Two methods of patching to give chord effects. In (a) PA1 gives VCO1 + RING MODULATOR output and PA2 gives VCO2 + RING MODULATOR output. In (b) PA1 output is silent and PA2 gives VCO1 + VCO2 + RING MODULATOR. In this case ES1 must be disabled by placing an open circuit jack plug in its control input

OTHER RING MODULATOR EFFECTS

Apart from its musical possibilities the RING MODULATOR may be used extensively in the production of sound effects. For example with white noise patched into the uncommitted input and with VCO1 running at low frequency—say around 10Hz—the reset point of the sawtooth will be differentiated by the RING MODULATOR input decoupling capacitor such that the output of the RING MODULATOR will comprise a series of staccato cracks akin to machine gun fire. Filtering the output of the modulator can ring the changes quite widely over this one, very simple sound.

Dalek type voices can be produced by the patching arrangement shown in Fig. 5.5. The microphone should be of the ceramic cartridge variety having a fairly substantial output of 100mV or so.

Remember to connect the screen of the microphone lead to the body of the DIN socket. A range of effects may be achieved by varying the frequency of VCO1 between about 20Hz and 1kHz bearing in mind that the greater part of the resultant audio signal will be derived from this oscillator.

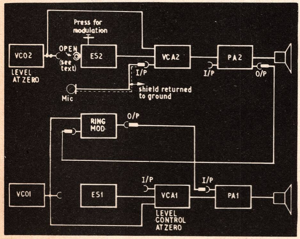

Fig. 5.5. Patching arrangement to give "Dalek" voices. Place open circuit jack plug in ES2 jack socket

If the microphone output appears to be insufficient to fully drive the RING MODULATOR a tape recorder can be employed by first of all taping the required speech and replaying through the Minisonic from the external speaker or earphone output.

NOISE GENERATOR

Other forms of sound effects may be derived from the NOISE GENERATOR in conjunction with the filter. With VCO2 level control at zero and the NOISE GENERATOR patched into the audio input of the VCF, set the Q control to maximum and manually swing the frequency control between half and full rotation. The resultant sound will be closely akin to that of howling wind.

Resetting the Q control just off its zero point and swinging the frequency control within its lower half rotation will simulate the sound of heavy, squally rain.

Another interesting experiment with the NOISE GENERATOR and filter combination is to play the passband of the filter from the keyboard. Set Q to a maximum and adjust the keyboard span control so that there is a wider than normal voltage span between consecutive notes. Patch the output of the filter into VCA1 and set VCO1 level control to zero.

While playing the keyboard adjust the filter frequency control and keyboard span control until there are distinct pitch changes in the audio signal resulting from the playing of successive keys. Pure tones cannot be achieved of course but the ability to change the noise pitch rapidly and predictably comes in very useful when creating say a brush accompaniment line to a pre-recorded melody.

SIMPLE "MULTI-TRACKING"

Those fortunate owners of reel-to-reel recorders with "sound-on-sound" facilities will need no introduction to the methods whereby so-called "multi-tracking" may be employed to produce composite recordings. It is not generally realised however that the humble cassette recorder can also be employed in this way if a second recorder is available.

Fig. 5.6 shows schematically how the "hook-up" may be accomplished bearing in mind that with the

2mm input socket on the PA stage it will be necessary to connect the screen of CR1 output lead to either the DIN socket casing on the Minisonic or to the jack plug shield of the input lead to CR2.

Let us assume that the composite recording is to comprise a simple melodic line punctuated by sound effects of various kinds. The method is as follows:

1. Set the recording level of CR2 and switch to "Record."
2. Play the melodic line as required and check the recording by replaying.
3. If satisfactory, rewind the cassette and transfer to CR1.
4. Set up the patch for the required sound effect and check it.
5. With a fresh cassette in CR2 switch to "Record". Switch CR1 to replay and, at the appropriate time, bring in the required sound effect. This is not as difficult as it might seem because, in order to get the sound effect on to the tape in CR2, the PA level control has to be set fairly high and thus the signal coming from CR1 can be quite clearly heard on the Minisonic loudspeaker. (Remember to set the replay level on CR1 to zero).
6. Repeat steps three to five as necessary until all the required effects have been recorded.

The number of transfers which can be made in the above manner with a cassette recorder is fairly limited due to the generally poor signal to noise ratio of these machines. Nevertheless, if the operation is carried out with care and with regard to recording levels and so on the results are likely to surprise even the most cynical.

ELECTRONIC REVERBERATION

Reverberation in an acoustic sense implies the presence of a series of multiple echoes each following rapidly on the heels of the other, each with a phase difference relative to the other and each, on successive returns, having a diminished intensity.

While the Minisonic does not possess any of the accoutrements normally associated with the production of artificial reverberation, it is nevertheless possible to utilise the long decay characteristic of the ENVELOPE SHAPERS together with the filter to provide a kind of reverberant quality which can be quite pleasing.

REVERBERATION PATCHING

One possible method of patching to achieve this effect is illustrated in Fig. 5.7. Two acoustic channels are used. Channel 2 carries the output from VCO2 together with that of the VCF and has a relatively short envelope decay period. Channel 1 carries the output of VCO1 and the output of the VCF and has a prolonged decay.

If the oscillators are tuned nominally in unison but with a slow beat between them the effect at the VCF is that when the outputs of both oscillators are in phase the total input signal level at the VCF is greater, and therefore more harmonically enriched than when the signals are in antiphase.

Thus when the outputs of the Minisonic are played through the domestic hi-fi system which has the loudspeakers placed reasonably far apart the effect is for the onset of the sound to be central to the listener with a sighing decay to one side or the other.

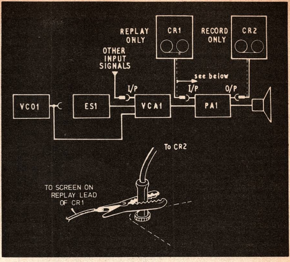

Fig. 5.6. Using two cassette recorders to obtain "multi-tracking". The inset shows how the screen of the replay load can be earthed to the lead from CR2 if metal jack plugs are used

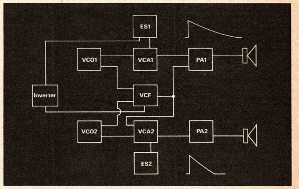

Fig. 5.7. A suggested patching arrangement to give a reverberation effect

With some adjustment to the controls the reverberant quality and spatial movement of the sound can be strikingly effective.

PLAYING THROUGH POWER AMPLIFIERS

The recorder outputs of the Minisonic can be considered to be compatible with the high level inputs to almost all makes of domestic power amplifier. In fact, the playing of the instrument through the domestic system is preferable to using the small monitoring speakers which only have a poor low frequency response. ★

ERRATA:

In Fig. 2.8 (*December 1974*), breaks shown in column 40 should be repeated in column 21

In Fig. 3.10 and 3.11 a 470μF 16V electrolytic should be connected between +9V rail and 0V. It may be conveniently placed on the Veroboard panel between the two power amplifiers

In Figs. 3.5 and 3.11 (HF DETECTOR), the cathode of D1 should go to −9V not ground

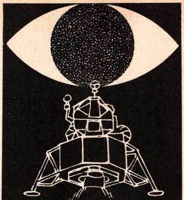

SPACEWATCH

BY FRANK W. HYDE

PIONEER II

The second look at Jupiter, a close look, was achieved by *Pioneer 11* early in December. The spacecraft passed inside the proton belt where it was subjected to contact with high energy protons. *Pioneer 10* passed inside the outer shell only. Normally it was to be expected that the spacecraft might have suffered considerably in this passage but the speed of *Pioneer 11*, over 100,000 miles an hour, enabled a safe flight through the proton belt. This remarkable flight took *Pioneer 11* within 26,000 miles of the cloud tops of the planet.

Many of the results from the encounter of Jupiter by *Pioneer 10* were confirmed by *Pioneer 11*. In particular, the very energetic electron emissions into space, modulated in intensity due to the rapid rotation of Jupiter, were encountered when the spacecraft was at the 100,000 mile distance.

It was found that Jupiter is radiating both protons and electrons. This is a puzzle that the teams are attempting to solve. These are found both at the edge and inside the magnetosphere. The extent of this magnetosphere has been confirmed by *Pioneer 11* to be as much as 40 Jupiter radii in the plane of the planet's orbit and as much as 80 radii in the vertical direction. The decametric radiations suggest that the electrons with energies above 3·5MeV existed as a cause of the radiations. *Pioneer 11* has shown that the flux, deduced from the earthbound observations of radio waves, is rather less than the actual value.

These findings could have far reaching consequences because the level of flux from other sources are usually calculated from the level of radiations that are received. There are some objects, such as the Crab Nebula, that may need a rechecking. On the other hand the synchroton theory of the radiations, that is the decametre radiations, may need a reappraisal.

Since the fluxes that have been observed at Jupiter are some ten times greater than those calculated from the groundbased observations, there arises very important questions in astrophysics.

JUPITER FINDINGS

The results from *Pioneer 11* are already giving still another possible model of Jupiter. It would appear to be a planet with an extended large magnetosphere which is greatly disturbed by the solar wind and stirred up by the passage of the satellites Amalthea, Io, Ganymede, Callisto and Europa. There appear also to be some special effects of the magnetic fields. For example the electron densities appear not at the equator of the magnetic field but to the north and to the south.

The convective model suggested by the *Pioneer 10* results is confirmed. Also confirmed is the drop in cloud level towards the poles. The fluid nature and hydrostatic equilibrium of the planet seems to be established beyond doubt.

RED SPOT

The red spot observed by *Pioneer 10* has changed somewhat now. A large white spot has appeared and caught up with the red spot. The tail of the spot seems to be extending. The small red spots that were previously observed have disappeared. The great red spot projects above the surface of the general cloud level by about 5 miles.

The bands at the various latitudes north and south of the planet's equator are in fact the clouds of gas rising from the interior. Because the rotation of Jupiter has a surface velocity of the order of 22,000 miles an hour the clouds are stretched out round the planet to form the bands. This is strikingly different from the clouds on Earth which are formed in circular cyclonic or hurricane patterns.

Other points from the preliminary data refer to the density of the four Galilean satellites. Io is shown to have a density of 3·5 grammes/cubic centimetres, Europa 3·4, Ganymede 1·8 and Callisto 1·5. The meteoroid particles which were detected around Jupiter by *Pioneer 10* have been confirmed by *Pioneer 11* as being infalling to the planet. The experiments to detect such particles have been continued by *Pioneer 11* after leaving the Jovian orbit and suggest that these meteoroids originate from comets.

SATURN FLYPAST

Pioneer 11 has left Jupiter and is on its way to Saturn. Certain resetting of the track of the spacecraft has been made and it seems that the path will take it through the rings as was hoped. The actual passage should be from above the rings between the gap bounded by the inner rings and the crepe ring.

At the point of "fly through" the spacecraft will be in the shadow of the planet. However, the angle of approach and the angle of departure will be such that the mystery of the rings will be finally settled. The spacecraft will, it is hoped, have a favourable position to take pictures of Titan.

So far calculations point to the date of the encounter of the spacecraft and the planet as being about September 3, 1979.

Pioneer 11 will leave for its journey out of the Solar system in the opposite direction to *Pioneer 10*. Also *Pioneer 11* will be the first of the spacecraft to chart the region above the plane of the ecliptic.

RADIO WAVES FROM EARTH

Since 1970 it has been known that the Earth radiates in a manner similar to the Sun and Jupiter. It was first observed when *OS1* carried very low frequency detectors in orbit. This work has been continued on later satellites, one in 1971 and another in 1973. A team from Iowa University have now made a special study of this part of the radio spectrum.

The radiation is very intense and lies between the frequencies of 50 and 500kHz. It would seem that the level of intensity lies around 10^9W, as compared with 2×10^7W of the radiations from Jupiter. The Earth radiation occurs at an altitude of under three earth radii. This is the region of high auroral activity.

The team from Iowa have compared the radio storms with auroral photographs from the US Airforce satellite and there seems to be a significant correllation between the pictures and the time of the radio emissions. Usually the radio bursts last for about half an hour to several hours.

The amount of energy which is dissipated during the auroral activity is about 10^{11}W. This suggests that there is 1 per cent dissipated as radio noise. Donald Gurnett, the leader of the Iowa team, thinks that the radiation may originate from a cyclotron process.

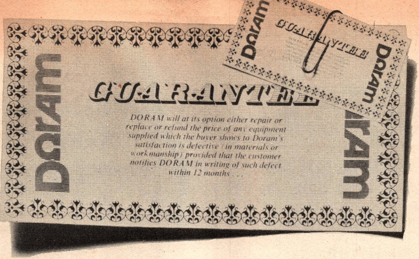
Doram
Doram
Doram
GUARANTEE
GUARANTEE
Doram

DORAM will at its option either repair or replace or refund the price of any equipment supplied which the buyer shows to Doram's satisfaction is defective (in materials or workmanship) provided that the customer notifies DORAM in writing of such defect within 12 months . . .

Vith the Doram catalogue, even the guarantee is guaranteed.

Doram is an entirely new
y of buying electronic
nponents.

So, to succeed, it's got
nave something going for
ght?

We agree with you.
d where Doram scores is in
security it gives the amateur
/er.

We'll give you peace of
d three ways.

-quibble guarantee.

Firstly, we guarantee to
lace any component which
ves faulty. Absolutely free
harge.

And secondly, our
rantee is backed by the
gest electronics distribution
oup in Britain.

day service.

Thirdly, we guarantee
'll have your components
hin 7 days from our receipt
our orders.

We're so confident of our
ice that if we can't supply the part you want within 7 days we'll give you an immediate refund.

So you'll never get a tedious wait.

You know just where you stand with Doram.

All branded goods.

All goods supplied by Doram are made by big-name manufacturers. And they're all to manufacturer's specifications. They're the best money can buy.

In fact, Doram gives the amateur the sort of service only professionals have enjoyed before.

Millions of components.

All in all, we're big enough to offer you stocks of millions of components, on over 4,000 product lines.

All you do is buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager) and then take your pick from it.

Use the coupon now. Send today for the first-ever Doram catalogue. It can take a lot of worry out of amateur components buying.

And for 25p that's not bad, is it?

I ENCLOSE 25p.* PLEASE SEND ME THE NEW DORAM CATALOGUE.

Name..

Address..

....

....

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PE/3/75

hurst

ELECTRONICS

92 Warwick Road, Ealing, London · W5 5PT
Telephone: 01-567 0424

HE 100
100 WATT POWER AMP
MODULE

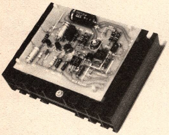

- ★ Includes large black anodised heatsink—no further heatsinks required.
- ★ Top grade glass-fibre P.C.B.
- ★ Uses high quality components.
- ★ Fully protected—short/open circuit proof.
- ★ Only 5 external connections.
- ★ Fully guaranteed.

TECHNICAL SPECIFICATIONS

★ Power output : 106W R.M.S. into 8Ω
★ Distortion : 0.8% at full O/P. Typ. 0.4%
★ Frequency response : 15 Hz–23kHz
★ Signal to noise : Better than–96dB
★ Input sensitivity : OdB (0.775V)
★ Input impedance : 10kΩ
★ Supply volts : 45–0–45V

Price **£15.12** inc. VAT. (ready built)

Enclose 50p postage & packing.
Power supply for HE 100 (including transformer, capacitors, rectifier) **£8.95** inc. VAT. Postage & packing 85p.

Pre-amps etc., also available.
SAE for details.

Enough books are written about crime, this one stops it.

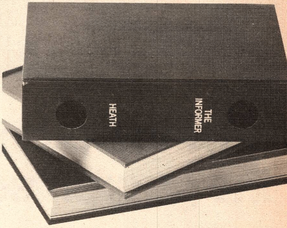

Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar.

For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

Heath (Gloucester) Limited,
Dept. PE35. Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.

The GD-39
Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PE35. Gloucester GL2 6EE. Please send me a free Heathkit catalogue.

Name____________________
Address____________________
____
____________ Postcode________

Remember easy terms are available with the Heathkit Monthly Budget Plan.

HEATH
Schlumberger

INGENUITY UNLIMITED

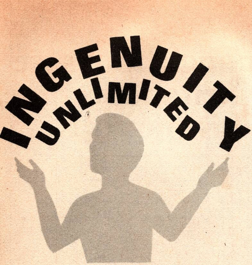

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit **YOUR IDEA**?

SIMPLE TOUCH SWITCH

THE circuit shown in Fig. 1 was developed as a simple switch for a hand torch. In basic form it will switch itself off after a given delay dependent on the value of C1.

The three transistors form one effective very high gain device and each conducts in turn when a resistance, in this case a finger-tip, is placed between the "on" touch plates. The bulb lights up when the "on" plate is touched and then slowly goes out at a rate set by C1 once the finger is removed.

An off touch plate could be added as shown dotted so that immediate switching can be effected.

The battery voltage and final transistor selection depends on the bulb used and this in turn depends on the application but in the prototype a BFY51/52 was used. Provided low leakage silicon devices are used no switch is required as the standing current should drop to below 0·5μA.

The switch S1 is used to keep the torch alight without holding it if this feature is required.

Of course there are other applications for this simple circuit including room lighting and indeed the lamp could be replaced by a triac or relay and be used to give locked switching if required.

P. Sanhen
Sutton, Surrey.

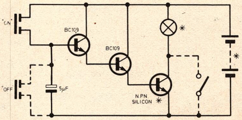

* RATING TO SUIT APPLICATION

Fig. 1.

TWO-WAY MORSE TRAINER

THIS simple circuit (Fig. 1) using one i.c., consists of a relaxation oscillator formed by gates G1 and G2 of a 7400 with timing components C1, C2, R1 and R2. The outputs are gated through gates G3 and G4 to the loudspeakers LS1 and LS2 when associated morse keys MK1 and MK2 are operated.

Whilst the frequency may be varied by choice of the capacitors and resistors mentioned, it is probably advisable to stick to the values given since there can be problems with the circuit not starting.

A number of loudspeakers were tried, as well as headphones and all worked well. Although the recommended logic supply voltage is 5V, a 6V lantern battery has been used over a long period with no trouble. Drain in use is about 20mA so battery life is good.

The resistors R5 and R6 are included as current limiters and the loudspeakers may be replaced by l.e.d.s if visual display is required as for example with deaf operators.

A. Ward,
Jersey.

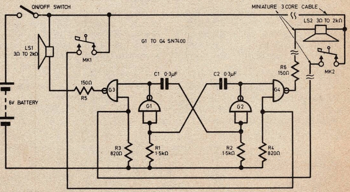

Fig. 1.

TRANSISTOR TESTER

With a view to holding costs at a reasonable level and using ex-equipment devices where possible the circuit of Fig. 1 was developed to test transistors.

Used as a plug-in extension to an existing multimeter, the tester will measure I_{coe} from 0 to 30μA and 0 to 300μA and β from 0 to 120 and 0 to 300 at 5mA. The values of the components given are for a multimeter with a 30μA, 1kΩ movement, but calculations for other instruments are quite straightforward.

Heart of the unit is the constant current source, R3, R4, R5, D1, D2, which feeds a known I_b to the transistor under test. The choice of voltage for D1 and D2 is fairly restricted as it has to be high enough to overcome V_{be} variations but sufficiently low to allow a reasonable use of the battery supply. In the event, 6V seems a good compromise.

Neglecting a small I_{coe}, β is given by I_c/I_b which gives

$$R_{base} = \frac{V_{effective}}{I_b} \text{ or } \frac{V_{eff} \times \beta}{I_c}$$

The voltage across the base resistance R_b is only the effective voltage V_{eff} of one diode as the forward voltage of the other is approximately equal to V_{be}. R3 is chosen such that it allows I_b to flow even at a low battery voltage but does not consume excessive power.

As constant alteration of meter setting is not attractive in such an application the flexibility is accommodated in the circuit of Fig. 1 and the meter is used on its most sensitive range. R9 protects overcurrent from flowing in the event of a shorted device. R10 shunts the still protected meter up to 300μA.

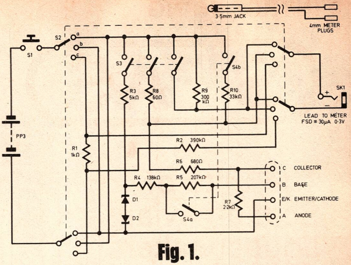

Fig. 1.

For leakage measurements S3 is open circuit and even though the base is connected to ground via D1 and D2 it is effectively open circuit.

R9 must be shorted for β measurements and R8 is used to shunt the meter to 5mA. In this position R6 gives some protection, limiting the current to about 15mA on short circuit. For a diode test R7 limits the current to 3mA.

For reliable operation the battery voltage should be greater than 7V and the battery should be capable of supplying 6mA.

For a transistor holder I used half an 8-pin d.i.l. socket soldered on a piece of Veroboard which in turn was Araldited to the top of a box containing the circuitry and switches.

S4 is connected so that with S4a open and S4b closed both h_{fe} and leakage measurements are at their least sensitive. The meter is less likely to be overloaded if S4 is kept in this state and switched if needed.

S2 gives *npn* in position a, *pnp* in position b and battery test in position c. For diode testing the device to be tested is inserted in the anode and cathode sockets. If it conducts on *npn* then the anode and cathode terminals indicate actual terminations, if the reverse then the opposite connections apply.

The unit is not intended to be accurate beyond about 10 per cent but devices can be matched to about 2 per cent.

N. E. Thomas,
Oxford.

LIGHTING CONTROL MODIFICATIONS

Some readers may find that the circuit used in the "Lighting Control Unit" (July 1973 issue) is not entirely suited to some salvaged components. In particular the transistor TR1.

If a silicon device is used in this position there is a danger of base-emitter breakdown due to reverse bias and this indeed occurred with two BC169C's used in the writer's circuit.

The insertion of protection diodes in the base leads has served to cure the problem quite easily and readily available OA81 devices were used. Equally, OA71 could be used.

A further modification to this useful circuit, shown in Fig. 1, is to include two controls for the original VR1 so as to obtain greater control over some of the effects.

J. Adams,
Oxford.

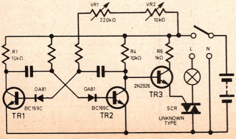

Fig. 1.

POINTS ARISING

P.E. ORION ***(January and February 1975)***

In the components list the case was quoted as being GB3, this should be GB1.

The mains transformer SL8 can be obtained direct from Gardners Transformers Ltd. see Market Place page 234.

P.E. MINISONIC—3 ***(January 1975)***

In the components list, for the H.F. Detector transistor, TR1 was not listed. This should be type BC184.

DIGITAL LEAF ***(January 1975)***

See Market Place page 234.

MARINE SPEEDOMETER ***(February 1975)***

Due to poor reproduction of Fig. 3 it is impossible to identify the breaks in the copper strips of the Veroboard. Assuming the board is annotated from the top left corner, strips *A* to *NN* and holes *1* to *46*, the breaks should be made at the following points: *26G, 9J, 12T, X38, CC10, DD10, EE10, FF10, HH19, II19, LL38.*

INTRODUCING

SEAS by Macel

The Elite of Scandinavian Loudspeakers

High Quality High Fidelity Loudspeaker Kits

INTRODUCTORY OFFER INCLUDES VAT AT 8% AND POSTAGE (UK ONLY)

(ALL KITS INCLUDE FULL WIRING DIAGRAM AND CABINET DRAWING)

(8 ohms impedance)

Improve your Disco, P.A. and Guitar sound by using these Hi-Fi Kits in recommended compact enclosure designs. These are Hi-Fi speakers of rugged construction capable of withstanding the high power used in the Music Industry and yet the Kits have good sensitivity giving more acoustical power out for a given electrical power input.

Kit 35 illustrated here is particularly recommended for the Music Industry. The recommended enclosure size is 24″ × 14″ × 10″.

Naturally all Kits are ideal for Hi-Fi at home.

Kit 35 (60 watts)

PRICE LIST

The following include High Compliance Bass Units and Cone Middle/Treble Units.

Kit 91H: 2 way and crossover (1 × 6½″ plus 1 × 3½″) (8–18 litre box) 10 watts 60–20,000 c/s. £7·35 each.
KIT 94H: 3 way and crossover (1 × 11″ × 6½″ plus 1 × 3½″ plus 1 × 2″) (25–40 litre box) 25 watts 45–20,000 c/s. £13·25 each.

The following include Neoprene Edge Bass Units and Dome Middle/Treble Units. Outer connecting lead and all internal wiring with mechanical push-on connectors.

KIT 10-2: 2 way and crossover (1 × 6½″ plus 1″ dome) (8–12 litre box) 20 watts 45–20,000 c/s. £15·35 each.
KIT 18: 2 way and crossover (1 × 8″ plus 1½″ dome) (15–20 litre box) 30 watts 35–20,000 c/s. £16·30 each.
KIT 30: 2 way and crossover (1 × 10″ plus 1½″ dome) (25–35 litre box) 35 watt 30–20,000 c/s. £16·95 each.
KIT 35: 3 speakers and crossover (2 × 8″ plus 1½″ dome) (30–40 litre box) 60 watts 30–20,000 c/s. £23·30 each.
KIT 60: 4 speakers and crossover (2 × 10″ plus 1 × 6″ × 4″ plus 1½″ dome) (50–70 litre box) 25–20,000 c/s. £34·95 each.

To **MACEL ELECTRONICS LTD**

P.O. Box 64, 14 High Street, Ipswich IP1 3LR.
Tel. 0473 215465
I enclose cheque/postal order

£.......... for..

NAME ....
ADDRESS ....
....

*Please debit my *Barclaycard/Access account. Account number

☐☐☐☐☐☐☐☐☐☐☐☐

BRITAIN'S FASTEST SERVICE!

A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	7p
AC107	68p
AC126	25p
AC128	22p
AC128/AC176	51p
AC151	26p
AC152	40p
AC153	42p
AC176	29p
AC153/176K	71p
AC187K	40p
AC188K	36p
AC187/188K	76p
ACY17	41p
ACY18	28p
ACY19	32p
ACY20	26p
ACY21	30p
ACY22	10p
AD140	80p
AD149	70p
AD161	64p
AD162	64p
AD161/162	£1·28
AF106	40p
AF114	46p
AF115	40p
AF116	58p
AF117	40p
AF124	38p
AF125	38p
AF126	39p
AF139	64p
AF186	30p
AF239	69p
AF279	74p
ASY26	70p
ASY27	72p
BA138	35p
BB103	27p
BB104	50p
BB105	37p
BC107	16p
BC107/BC177	46p
BC108	14p
BC108/BC178	49p
BC109	16p
BC109/BC179	44p
BC109C	18p
BC140	52p
BC147	16p
BC148	16p
BC149	16p
BC157	17p
BC158	15p
BC159	17p
BC147/157	33p
BC148/158	31p
BC149/159	33p
BC167	15p
BC168	14p
BC169	14p
BC169C	15p
BC177	30p
BC178	35p
BC179	28p
BC182	15p
BC182L	15p
BC183	14p
BC183L	14p
BC184	16p
BC184L	13p
BC212	19p
BC212L	19p
BC238	14p
BC238/308	28p
BC257	16p
BC258	15p
BC259	16p
BC307	17p
BC308	14p
BCY70	22p
BCY71	33p
BCY72	19p
BD241A	54p
BD242A	60p
BD243A	72p
BD244A	78p
BD124	£1·00
BDY20	96p
BF115	30p
BF167	29p
BF180	50p
BF194	18p
BF195	18p
BF196	18p
BF200	46p
BF254	17p
BF255	17p
BFX29	39p
BFX84	34p
BFX85	41p
BFX86	35p
BFX87	33p
BFX88	30p
BFY50	33p
BFY51	30p
BFY52	31p
BFY53	28p
BFY90	£1·35
BPX29	£1·62
BR100	22p
BRY39	66p
BSX19	26p
BSX20	25p
BSY27	27p
BSY95A	12p
BT106	£1·26
BTY79/400R	£2·52
BY100	20p
BY127	12p
BZY88C3V3 to BZY88C30V	10p
BZX61C7V5 to BZX61C30V	28p
BZY93C9V1	80p
BZY93C12V	80p
BZY93C15V	80p
BZY93C18V	80p
CA3005	£1·35
CA3011	83p
CA3013	£1·17
CA3014	£1·37
CA3018	72p
CA3018A	83p
CA3020	£1·39
CA3028A	79p
CA3035	£1·37
CA3043	£1·57
CA3046	70p
CA3048	£2·11
CA3052	£1·62
CA3053	47p
CA3065	£1·28
CA3088E	£1·24
CA3089E	£1·94
CA3090AQ	£4·20
CA3123E	£1·40
CR1/051C	65p
CR1/401C	86p
CZ6	17p
D10 (NTGD10)	50p
IR2160	82p
IRC20	60p
JA424	£2·08
LD30A	29p
MC1303L	£1·59
MC1305P	£1·99
MC1307P	£1·38
MC1310P	£2·80
MC1330P	88p
MC1352P	90p
MC1466L	£3·50
MC1468L	£2·41
MC4024P	£1·84
MC4044P	£1·84
MFC4000B	50p
MFC6030	£1·21
MFC6040	£1·15
MFC8010	£1·44
MFC8040	£1·24
MFC9020	£1·56
MJE371	94p
MJE520	70p
MJE521	82p
MJE2955	£1·49
MJE3055	87p
MJ480	£1·15
MJ481	£1·45
MJ491	£1·84
MJ802	£3·65
MJ802/MJ4502	£7·65
MJ900	£1·88
MJ1000	£1·50
MJ4502	£4·00
MLM309K	£2·08
MPF102	49p
MPF103 (2N5457)	45p
MPF104 (2N5458)	61p
MPF105 (2N5459)	45p
NE555V	78p
NKT0033	92p
NKT211	32p
NKT212	32p
NKT271	22p
NKT274	22p
NKT275	29p
NKT279A	36p
NKT281	22p
NKT401	88p
NKT402	96p
NKT403	82p
NKT404	78p
NKT405	£1·00
NKT406	79p
NTGD10	50p
OA10 (NTGD10)	50p
OA47	10p
OA79	6p
OA90	6p
OA91	6p
OA95	9p
OA200	8p
OA202	8p
OC25	72p
OC28	87p
OC29	88p
OC35	78p
OC36	78p
OC41	57p
OC44	20p
OC45	20p
OC71	20p
OC72	20p
OC75	20p
OC76	46p
OC77	62p
OC81	32p
OC81D	29p
OC83	32p
OC84	32p
OC170	44p
OC171	47p
OCP71M	42p
ORP12	50p
PM7A2	£1·98
PM7A6	£2·62
PN70	13p
PN71	13p
PN107	9p
PN108	9p
PN109	9p
PN3819 (2N3819)	24p
SL103A	54p
SL403A (Rectifier)	71p
SL803A	94p
ST2	22p
T2700D	£1·01
T2800D	90p
T2800M	£1·33
TAD100	£1·97
TAD110	£1·97
TBA810S	£1·32
TIL112	£2·00
TIL209	30p
TIS43	36p
TR1	22p
VA1039	15p
VA1040	15p
VA1066s	15p
VA1077	17p
W005	25p
W01	26p
W02	26p
W04	27p
W06	32p
W08	40p
ZTX107	14p
ZTX108	11p
ZTX300	19p
ZTX302	24p
ZTX303	15p
ZTX304	30p
ZTX314	18p
ZTX320	40p
ZTX500	20p
ZTX501	22p
ZTX502	25p
ZTX503	20p
ZTX504	60p
1N914	4p
1N3754	18p
1N4001	4p
1N4002	4p
1N4003	5p
1N4004	7p
1N4005	7p
1N4006	8p
1N4007	9p
1N4148	4p
1N5400	16p
1N5404	22p
1N5408	33p
1S44	4p
1S920	10p
2N404	58p
2N697	26p
2N706	25p
2N706A	27p
2N708	20p
2N914	25p
2N918	54p
2N930	25p
2N1303	61p
2N1305	65p
2N1307	69p
2N1309	73p
2N1613	26p
2N1711	30p
2N1893	46p
2N2218	34p
2N2218A	48p
2N2219	43p
2N2219A	50p
2N2368	26p
2N2369	23p
2N2369A	25p
2N2484	48p
2N2646	58p
2N2904	32p
2N2904A	35p
2N2905	38p
2N2905A	40p
2N2924	23p
2N2925	27p
2N2926	10p
2N3053	30p
2N3054	60p
2N3055	65p
2N3228	88p
2N3391A	40p
2N3525	£1·04
2N3702	14p
2N3703	14p
2N3704	14p
2N3705	14p
2N3706	14p
2N3707	14p
2N3708	14p
2N3709	14p
2N3710	14p
2N3711	14p
2N3773	£3·20
2N3819	35p
2N3866	82p
2N3904	20p
2N3906	24p
2N4058	15p
2N4060	16p
2N4061	16p
2N4062	16p
2N4441	70p
2N4444	£2·20
2N4871	48p
2N4990	54p
2N4991	46p
2N5245	68p
2N5457 (MPF103)	45p
2N5458 (MPF104)	61p
2N5459 (MPF105)	45p
2N5756	£1·00
2N5777	54p
2N6027 (D13T1)	58p
3N128	74p
3N140	92p
3N141	82p
3N152	92p
741/T05	50p
741/8DIL	34p
747/14DIL	85p
748/T05	41p
3015F	£1·40
3015G	£2·00
7400	24p
7401	24p
7402	24p
7403	24p
7404	30p
7405	30p
7408	30p
7409	30p
7410	24p
7413	36p
7420	24p
7425	36p
7430	24p
7440	29p
7442	£1·39
7443	£1·74
7444	£1·74
7445	£2·47
7446	£1·74
7447	£1·50
7450	24p
7451	24p
7453	24p
7454	24p
7460	24p
7470	54p
7472	36p
7473	54p
7474	55p
7475	54p
7476	54p
7480	80p
7482	£1·04
7483	£1·58
7486	39p
7490	84p
7491A	£1·54
7492	£1·02
7493	90p
7494	£1·36
7495	96p
7496	£1·78
74100	£1·97
74107	62p
74121	51p
74141	£1·20
74150	£4·02
74151	£1·32
74153	£1·62
74154	£2·40
74155	£1·86
74156	£1·86
74190	£2·16
74191	£2·16
74192	£2·09
74193	£2·09
74196	£1·80
74197	£1·80
40250	58p
40310	56p
40312	56p
40360	40p
40361	38p
40362	40p
40406	44p
40407	34p
40408	50p
40409	52p
40410	52p
40430	£1·01
40468A	44p
40575	£1·13
40576	£1·31
40602	46p
40673	52p

COSMOS LOGIC

CD4000AE	46p	CD4017AE	£2·27	CD4030AE	89p
CD4001AE	46p	CD4018AE	£2·27	CD4035AE	£2·23
CD4002AE	46p	CD4019AE	£1·04	CD4040AE	£2·70
CD4007AE	46p	CD4020AE	£2·53	CD4042AE	£1·80
CD4009AE	91p	CD4022AE	£2·23	CD4043AE	£2·02
CD4010AE	91p	CD4023AE	46p	CD4044AE	£2·02
CD4011AE	46p	CD4024AE	£1·62	CD4049AE	72p
CD4012AE	46p	CD4025AE	46p	CD4050AE	72p
CD4013AE	83p	CD4026AE	£3·04	CD4051AE	£2·36
CD4014AE	£2·27	CD4027AE	£1·35	CD4056AE	£1·80
CD4015AE	£2·27	CD4028AE	£1·97	CD4060AE	£3·56
CD4016AE	86p	CD4029AE	£3·06	CD4069AE	46p

MULLARD MODULES

LP1185 FM IF Module	£4·69
LP1186 FM Tuner Module with Diode Tuning	£6·00
LP1400 High performance stereo decoder module using frequency multiplex system	£6·08

ORDER AS TYPE NO. + "MULLARD MODULES"
DATA AND APPLICATION CIRCUIT FREE WITH MODULE UPON REQUEST
N.B. SEE BELOW FOR SPECIAL DISCOUNT ALLOWANCE

LOGIC PROBE

Powered by 5v DC supply of circuit under test, this device gives instant indication of Logic High (Red) "1" and Logic Low (Green) "0". L.E.D. Indicators.

Leaflet on request **£9·30 each**

See below for special discount allowance

LIGHT DIMMER BY ANCO

For exciting lighting from "Off" to full brilliance controlling up to 250 watts. Designed to fit in place of standard wall switches. (Not suitable for Fluorescent Lighting.) **£3·85**

CA3401 QUAD OP. AMP.

Interchangeable with MC3401 **65p**

INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder, break off frame holders—your DIL mounting is complete!!

Pin Sockets	**1,000 pieces**	**£7·00**
Pin Sockets	**100 pieces**	**£1·00**

NE555V TIMER I.C.

As used in magazine articles including July Practical Wireless. **78p**

DATA AND CIRCUITS **15p**

CA3123E I.C.

Superhet System with RF Amp. IF Amp. Mixer, OSC. g.c. Detector and Voltage Regulator. Ideal for car radio applications. **£1·40**

APPLICATION SHEET AND DATA **15p**

SEVEN WATT AUDIO AMP. I.C.

TBA810S **£1·32**

Featuring thermal protection. Ideal for car radio applications.

APPLICATION SHEET AND DATA **15p**

ARROW SPECIALISE IN EDUCATIONAL AND GOVERNMENT ORDERS

—See catalogue for further details.

ARROW SERVICE PLUS

10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN

COMPREHENSIVE CAT. →

Important Notice "All prices are *exclusive* of V.A.T. Please add V.A.T. to the final total of your order *after* deducting any discount which may be due" VAT. REG. 246062672

ARROW ELECTRONICS LTD.

DEPT. PE 12, 7 COPTFOLD ROAD
BRENTWOOD
ESSEX CM14 4BN

I enclose PO/Cheque for 10p
Name ……………………
Address ……………………

Arrow Electronics Limited
Dept. PE 12
7 Coptfold Road
Brentwood
Essex
CM14 4BN

REGISTRATION No. 1062424

SWITCHING POWER SUPPLIES

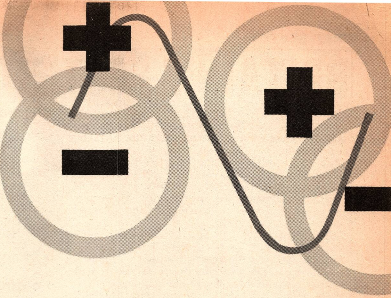

IN THE majority of power supplies, the mains transformer and the smoothing and reservoir capacitors account for most of the bulk and weight. This situation, although unavoidable in the past, is unfortunate because the mains transformer, which contributes a major part of the weight, plays no vital part in the functioning of the power supply, its only real purpose being to isolate the mains from the output of the power supply. In practice the main transformer is also used to step down the input voltage to a convenient level, but this could easily be achieved by other means.

The basic concepts behind transformerless, or switching, power supply units have been known for some considerable time. Unfortunately, until two or three years ago, components capable of putting the ideas into practice were not available.

Switching regulators dispense with bulky 50Hz transformers and smoothing components, yet achieve isolation between the mains and power supply output. The reduction in size and weight achieved is in the order of 8 : 1 but as with everything else, one does not get something for nothing. However, in the vast majority of cases, the trade-off is extremely worthwhile. In some cases the performances may not be as high as with linear techniques. This point will be dealt with in more detail later in the article.

OPERATING PRINCIPLES

Transformerless or switching power supplies achieve isolation between mains and output by employing a high-frequency transformer as against the conventional 50Hz transformer and herein lies the secret of the small size of switching power supplies. It is a fundamental fact that the higher the frequency employed the smaller a transformer can become to handle a given amount of power.

The basic principles of switching regulator operation are illustrated in Fig. 1. The mains input is converted to d.c. by a bridge rectifier and smoothing circuit after high frequency filtering. This d.c. is applied to a pair of switching transistors which are driven at tens of kHz by the control circuitry. The square wave output of the switching transistors is applied to a small h.f. transformer, the output of which is rectified and smoothed to provide the output of the power supply. This voltage is compared with a reference voltage and, if a difference exists, an error signal is generated and fed to the control circuitry. The control circuitry adjusts the mark-space ratio of the signal applied to the switching transistors in such a way as to reduce the error signal to zero. Another method relies on a frequency variation. This ensures that the output of the power supply remains constant.

It will be noted that two small high-frequency transformers are employed, one in the main current path and one in the feedback loop, to ensure that the output is isolated from the mains.

The two high-frequency filters stop spurious voltages at the switching frequency and its harmonics from being fed back into the mains wiring and into equipment powered by the power supply.

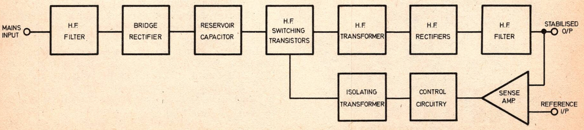

Fig. 1. Block diagram of switching regulator

FIRST SYSTEM

Several circuits have been developed which give a variety of different advantages. The first (see Fig. 2) used a conventional inverter circuit working at 20kHz. This was driven from a multivibrator, the main transistors TR1 and TR2 being alternately on and off.

The output from the transformer is a square wave, which is rectified by fast recovery rectifiers and then smoothed.

The input voltage to the inverter is 150V, thus limiting the peak voltage on the transistors to 300V. To generate this 150V rail, the 240V mains supply is rectified and smoothed to give 340V, which is fed to a switching regulator that reduces the voltage to 150V.

This regulator is a constant frequency circuit with the "on" time of the switching transistor TR3 controlled to keep the rectified output constant via the 150V rail. The two circuits are driven from the same oscillator so that they do not beat together.

Such a unit has four active loss stages and three passive. To remove one of these active loss stages the switching regulator and the inverter must be combined. The normal inverter has alternate stages fully on or fully off, and at all times one stage is on.

The output is set by the turns ratio of the transformers which is fixed, and the input voltage. In the next inverter (Fig. 3) a variable off time is injected between each on period by controlling the ratio of the on and off pulses, thus controlling the output.

The secondary output is a series of pulses of variable mark-space, so that it is now only necessary to filter those pulses to get a mean output, which can then be varied.

CIRCUIT VARIATIONS

Two variations of the circuit are possible depending on the manner in which the mark-space ratio is varied. We can have either a constant on pulse with a variable off time, or a fixed frequency with variable on and off times.

Fixed pulse width gives a system that is free of restraints and is thus more able to overcome sudden overloads interference or mains loss. Since the pulse width determines the ripple voltage for a given choke and output capacitance value, the ripple will remain constant against line and load variations. Also the circuit can give very large swings of output voltage and input voltage without unlocking. The main disadvantages are that since it operates near the audio range it can, under light load conditions, break into the audio range. Furthermore, as the ripple frequency is variable, it is more difficult to filter out.

Transformerless 4½ to 6V, 50A power supply

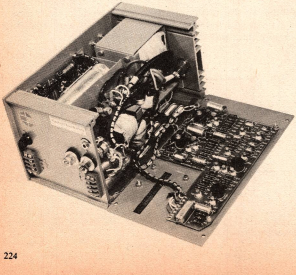

The other system (constant frequency) offers an almost exact complement to the fixed pulse width. It is completely quiet under normal working conditions, and filters used external to the equipment can be tuned to give maximum attenuation at this frequency.

It cannot be used over such a wide range of input and output variations, however, and is more prone to jump into an uncontrolled frequency mode of operation.

Both systems are currently in use, depending upon the application.

COMPONENT CONSIDERATIONS

In these two circuits, the components under most danger are the inverting transistors. By using the series type of inverter to limit the peak transistor volts, we have both transistors in series across the line. Control circuits must ensure that both transistors are not turned on at the same time, or a short circuit would be placed across the line, thus destroying one or both of the transistors.

Also, the pulse widths supplied to both transistors on alternate cycles must be identical, or the energy drawn from the series capacitors will be unbalanced. If this happens, the centre voltage will move towards the greater pulse width and the transformer will tend towards saturation.

The output voltage of one side will then fall, and if it falls too low it will not bring its rectifier into conduction. Such a condition is much easier to control in the constant pulse width system.

CONTROL

All control in these systems is by non-dissipating elements apart from saturated switches. Thus the highest dissipation is in the high current output rectifiers. Fast recovery rectifiers have been used for some years with proven reliability, but their saturation voltage is of the order 1 to 1·2V at the currents being used.

Schottky diodes offer an answer to the high dissipation problem in that they have a forward voltage drop of only 0·4V at very high currents and thus considerably reduce dissipation. At present, they only offer an increase in efficiency and not a reduction in size of the heat sink required. This is because their maximum junction temperature is 100°C, so they have to be kept extremely cool.

Transformerless supplies, examples of which are shown in the accompanying photographs, offer three major advantages that are very difficult to provide with linear units. They can operate from mains voltages of from 200 to 264V without tap changes; they can maintain their output voltage at full load with a mains interruption of 30ms, and they can be used over a 0V to 6V range at full current with no tap changes.

In fact they run cooler with lower output voltages, and a 250A 2V unit could easily be produced if it were required. They are thus ideal for use as constant-current units or as bench variables.

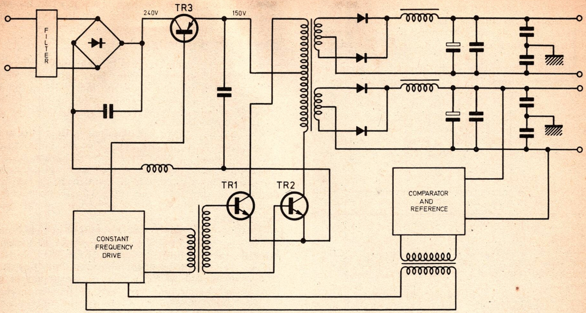

Fig. 2. Conventional inverter circuit diagram

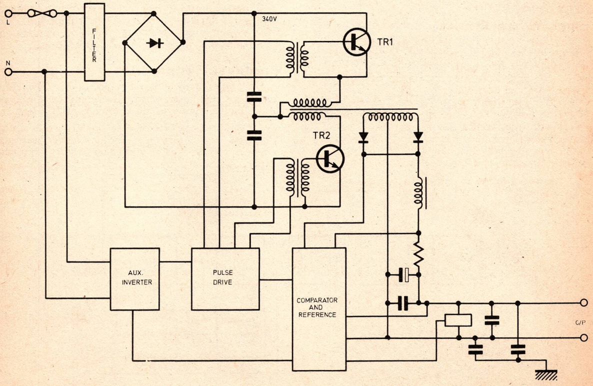

Fig. 3. Variable output inverters

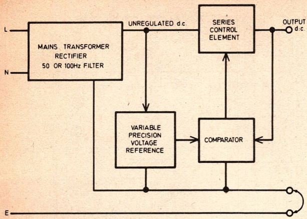

Fig. 4. Linear regulator block diagram

The output specification of these units is satisfactory for TTL circuits, and their use in lightweight desktop equipment is advantageous because of their size and weight.

If any communications equipment is used with these power units, additional screening will probably be required; but even with a large amount of screening their size will prove most attractive.

LIMITATIONS

For highly critical applications, the switching regulator would not normally be used because, inevitably, a small amount of ripple at the switching frequency appears on the output and the transient response is not up to the best that can be achieved by good linear regulators.

However, for many purposes these factors are of no consequence and then the switching regulator really comes into its own. From the equipment manufacturer's point of view, the space and weight savings enable more compact equipment to be produced at a lower cost.

ONE STEP FURTHER

Having looked at the relative advantages and disadvantages of the switching regulator when compared with the linear regulator, it is now necessary to look at one of the disadvantages of the conventional linear regulator. A block diagram of a typical linear regulator appears in Fig. 4.

The output voltage is compared with a precision voltage reference. If the two differ the comparator either increases or decreases the impedance of the series control transistor to correct the output voltage. To allow the series control element to do its job, the unregulated d.c. from the transformer and rectifier assembly must always be of a higher voltage than the output voltage.

If the power supply had an output which could be varied from 0 to 50V at 10A then the unregulated d.c. supply must be around 55V. At 1V, 10A output, 54V would be dropped across the series control element and 540W would be dissipated in it. This problem is usually overcome by having a range switch which varies the output of the unregulated section so as to limit the power dissipation in the series control element to a reasonable value.

However, large efficient heat sinks are needed for the series control transistor which add to the bulk of the power supply. Due care must be taken with cooling air-flow through the power supply, further adding to the size and weight problems.

A new approach has been recently announced which was developed by APT Electronics Ltd. This involves combining switching and linear regulators in an attempt to achieve the best of both worlds.

COMBINED TECHNIQUES

A number of the disadvantages of both switching and linear regulators can be overcome or minimised by a new technique which combines both linear and

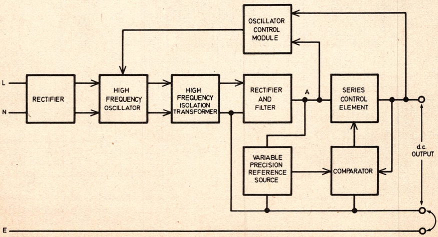

Fig. 5. Power unit incorporating both linear and switching principles

switching regulators in a single unit. A block diagram of a laboratory bench power supply, currently being manufactured by APT, is shown in Fig 5.

Operation of the system is best described by imagining that the unit is switched on and is supplying an output, say 40V, to a load. Point A on the circuit must be at a potential of more than 40V for the series control element to function. For reasons which will become clear later we will state that point A is at 45V.

If the voltage reference source output is deliberately lowered to 30V the comparator will provide an output which will increase the impedance of the series control transistor so as to reduce the output of the power supply to 30V. As this is taking place the voltage drop across the series control element would tend to rise. The oscillator control module senses this increase and lowers the duty cycle of the oscillator so the input voltage to the series element falls. Circuit values are such that the voltage across the series element is maintained at 5V.

With 30V now at the output, therefore, point A will be at 35V. The technique ensures that even for a 0 to 50V 10A power supply, power dissipation in the series control element is limited to 50W even at the normal worst case condition of 1V output at 10A.

The main advantages of the technique are therefore the elimination of the 500W mains transformer and bulky 100Hz smoothing components, and a considerable reduction in internal power dissipation allowing smaller heat sinks to be used.

Such a power supply does not perform as well as a good quality series linear regulator but is much better than a straight switching regulator. For a 50V, 10A power supply the relative advantages of the linear series, switching and combined switching series regulators are summarised in Table 1.

Table 1.

Parameter	Linear	Switching	Linear/ Switching
Regulation	Excellent	Good	Good
Transient response	Excellent	Poor	Fair
Ripple and noise	Excellent	Poor	Good
Ease of output voltage adjustment	Fairly easy	Fairly difficult	Easy
Size	Very large	Very small	Small
Weight	Very heavy (90lb)	Very light (10lb)	Very light (16lb)

A photograph of the combined switching and linear regulator is shown.

THE FUTURE

Power supply performance will continue to improve and will be assisted by monolithic integrated circuit and thick film hybrid microcircuit developments.

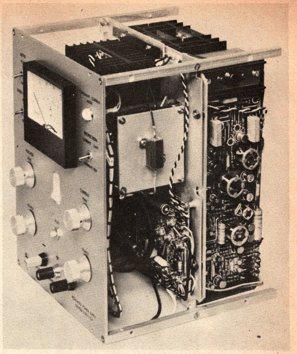

The SSU 10-50, 0 to 50V, 500W laboratory power supply from APT Electronics

Thick film microcircuits consists of a substrate (or base material) on which the circuit to be manufactured is printed. Conductors are printed with palladium, or similar ink and resistors will be formed by printing with one of the many inks available for this purpose. The printed substrate is "baked" in a furnace and then active components such as transistors and integrated circuits are added.

Hybrid microcircuits are very reliable, much more reliable than the printed circuit board with separate components, and can be designed to have a uniformity of performance very difficult to achieve by other means.

This last point is very important in power supply manufacture and indeed complete regulator control circuits using monolithic chips and discrete components are manufactured in hybrid microcircuit form at Coutant's Ilfracombe factory.

Any improvement in the monolithic results in an improvement in the hybrid. The two techniques are therefore complementary. ★

P.E. STAFF VACANCY

There is a vacancy for a technical sub-editor on the staff of Practical Electronics. An interesting and satisfying job for an electronics enthusiast. Sound technical knowledge and practical experience more important than journalistic experience.

Write with brief personal details to The Editor, Practical Electronics, Fleetway House, Farringdon Street, London EC4A/4AD.

...IN CIRCUIT OHMMETER

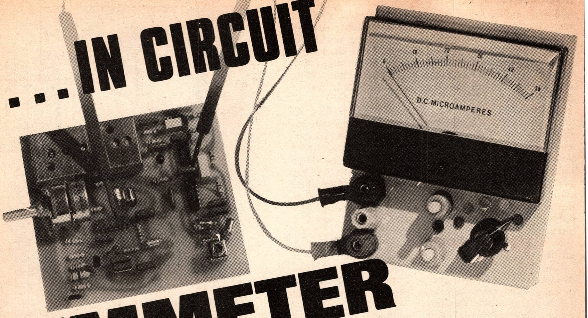

By O.N. BISHOP

This instrument can be used for measuring the resistance of a component without the need to disconnect it from its circuit. This facility can save a lot of time in circuit checking, particularly when working with miniature components on circuit boards. It may also be used in the normal manner for checking unconnected components.

Like a conventional ohmmeter, it can be used for discovering short-circuits and checking continuity—again without removing components from the board.

Utilising a 50μA meter, it covers five ranges with full scale deflections of 500Ω, 5kΩ, 50kΩ, 500kΩ and 5MΩ respectively. Scaling is linear with an accuracy of ± 1 per cent. This means that the meter face does not have to be calibrated.

Other applications include go/no-go checks for semiconductors and capacitors.

HOW IT WORKS

The action of this ohmmeter depends on a special property of the operational amplifier, when connected as shown in Fig. 1. Here, the potential at the inverting input is automatically held at zero, with respect to negative potential. We sometimes say that the inverting input is a "virtual ground".

The non-inverting input (+) is at negative potential simply because it is wired to the negative rail. But the inverting input has a current (I_r) flowing to it. To keep the potential at zero, the amplifier detects this current and almost instantaneously adjusts its own output voltage (E_o) to cause a current (I_x) to flow in its feedback loop. This current is just sufficient to keep the potential of the inverting input at ground, or zero. In other words, the current I_x is equal in magnitude to I_r, but opposite in sign. It flows away from the inverting input. Mathematically we can say that

$$I_x = -I_r$$

The input, or reference current, comes from a reference cell, of voltage E_r and before reaching the inverting input flows through a reference resistor, R_r, so that

$$I_r = \frac{E_r}{R_r}$$

Similarly for the current in the feedback loop:

$$I_x = \frac{E_o}{R_x}$$

Since I_x is equal but opposite to I_r, we can combine these two equations and get

$$\frac{E_o}{R_x} = -\frac{E_r}{R_r}$$

which by rearrangement of terms gives:

$$R_x = -\frac{R_r}{E_r} \cdot E_o$$

This is the basis of resistance measurements by the ohmmeter. R_x is the unknown resistance which we want to measure. R_r and E_r are known and are constant. For different values of R_x we obtain different values of E_o, and E_o is linearly though inversely related to R_x. If we place a voltmeter between the output of the amplifier and the ground rail we can measure E_o, and use this value to derive the value for R_x. In practice we do not have to do any actual calculation; we simply calibrate the meter scale of the voltmeter to read "Ohms" instead of "Volts".

IN-CIRCUIT OPERATION

Fig. 2 shows R_x as part of a complex network of resistors. Some of the "resistors" in the diagram might be other components with some degree of electrical resistance, such as diodes, transistors, inductances or capacitors. To operate the ohmmeter in these circumstances the distant terminals of all resistors adjacent to R_x must be grounded. In the diagram, points C, D, E and F would need to be grounded.

Terminal A of R_x is at ground potential owing to the nature of the amplifier circuit, as explained above. Points C and D are also grounded. Since both ends of R_c and R_d are at ground potential, no current can flow through these resistors—they might just as well not be there. We can ignore them. Terminal B has a potential E_o provided by the output of the amplifier. Within very wide limits of load this potential is constant. So current flows from ground through R_f and R_e, but without affecting E_o. In this way the meter reads the resistance R_x, and is entirely unaffected by the network around.

The only circumstance in which this circuit will not ignore other resistors is when another resistor is wired in parallel with R_x. Then it is not possible to ground its distant terminal without also grounding either point A or B. The meter will indicate the parallel resistance of R_x and the second resistance, but not the resistance of R_x alone. If the second resistor should be a variable resistor there is no problem, for by grounding the wiper of the resistor we can treat it as two separate resistors.

CIRCUIT DETAILS

The practical circuit is shown in Fig. 3. The current I_r comes from B1, which also powers part of the amplifier IC1. The Zener diode D1 gives a regulated 5·1 volts and the resistors R2 and VR1 connected across D1 act as a potential divider. By adjustment of VR1 a voltage of 0·1 volts can be obtained at the wiper. This is E_r.

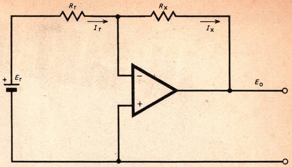

Fig. 1. Basic op. amp. circuit

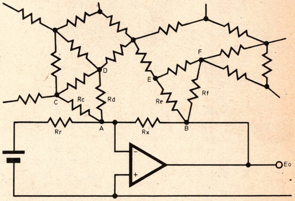

Fig. 2. In-circuit measurement

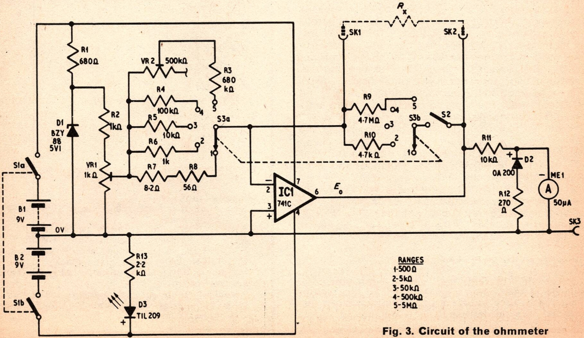

Fig. 3. Circuit of the ohmmeter

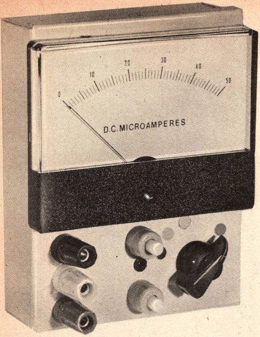

To provide a number of ranges any one of the resistors or resistor combinations R3/VR2, R4, R5, R6, or R7/8 can be switched into circuit, to act as R_r of Fig. 1. The output from the amplifier is fed out to the resistor to be measured through a terminal SK2 and back through SK1 to the inverting input of the amplifier. The voltmeter for output is a microammeter in series with resistor R11. So connected, the meter will give full-scale deflection for $E_o = -0{\cdot}5$ volts. Inserting these working values of E_r and maximum E_o in the equation, we can calculate that for any range the maximum resistance measurable is:

$$R_{x(max)} = -\frac{R_r}{0{\cdot}1}(-0{\cdot}5)$$
$$= 5R_r$$

So, when R6 is in circuit, f.s.d. of meter indicates R_x = 5kΩ; similarly, when R5 is in circuit, f.s.d. indicates 50kΩ and with R4, f.s.d. indicates 500kΩ. For a f.s.d. of 500Ω one might think that R7 and R8 should total 100Ω, but in practice they total only 64Ω. This is because such a low resistance draws a heavy current from the potential divider, and the potential (E_r) of the wiper falls. A corresponding reduction of R_r from theoretical 100V to practical 64V restores the balance of the equation, and gives f.s.d. at 500Ω. At the highest range, 5MΩ at f.s.d., the amplifier output does not reach the theoretical level, so the reference current has to be increased by using a reference resistor less than 1MΩ. This is provided by R3, with VR2 in series for adjustment to the correct total value.

CONTINUITY CHECKS

On all ranges short-circuiting of SK1 and SK2 puts R_x at zero, so E_o falls to zero. So this instrument can be used for checking continuity. When the terminals are unconnected, R_x is infinite and E_o is infinite too, at least theoretically, though the characteristics of the amplifier limit it to about −7 volts. Such a high voltage across a meter rated at 0·5 volts would damage the winding so D2 and R12 are wired in parallel to the meter to limit meter current to about 75μA. At low potentials the diode is non-conducting, but with increasing potentials the meter exceeds f.s.d. and the diode begins to conduct in its forward direction so that excess current is shunted through it.

The l.e.d. indicator is important for, unlike an ordinary ohmmeter which uses current only when actually connected to a resistor, this ohmmeter uses current as long as it is switched on. It draws about 7mA from B1 and, with the indicator l.e.d. in the B2 circuit, draws about 4·5mA from B2. These are low requirements, so small PP3 batteries can be used.

INTERNAL RESISTORS

By closing S2, one of two internal resistors (R9, R10) can be connected across the sockets, if the meter is also switched to range 2 (5kΩ f.s.d.) or range 5 (5MΩ f.s.d.). The purpose of these is threefold. They provide a simple check on battery condition and meter adjustment. They are used when checking capacitors or when measuring resistances greater than 5MΩ. The calculation for this is given later.

COMPONENTS . . .

Resistors

R1	680Ω
R2	1kΩ
R3	680kΩ
R4	100kΩ 2%
R5	10kΩ 2%
R6	1kΩ 2%
R7	8·2Ω
R8	56Ω
R9	4·7MΩ
R10	4·7kΩ
R11	10kΩ
R12	270Ω
R13	2·2kΩ

All 5% ¼ W carbon unless stated otherwise

Potentiometers

VR1	1kΩ
VR2	500kΩ
VR3	100Ω (optional, see text)

Semiconductors

D1	BZY88 Zener 400mW, 5·1V
D2	OA200
D3	TIL209, l.e.d.

Integrated circuit

IC1	741C op. amp.

Miscellaneous

ME1	Microammeter, 50μA f.s.d. SEW SD830 or similar
S1	Push-switch or toggle switch, DPST
S2	Push-switch or toggle switch, SPST
S3	Rotary wave-change switch, 2-pole, 6-way
SK1–3	Terminals, yellow, green, black

Veroboard, 0·1 in matrix, 24 holes × 24 strips (half a 5″ × 2½″ board)
Veropins; knob for S3, battery connectors.
1% or 2% resistors for calibration (470Ω, 4·7kΩ, 47kΩ, 470kΩ, 4·7MΩ.)

OHMMETER WIRING DETAILS

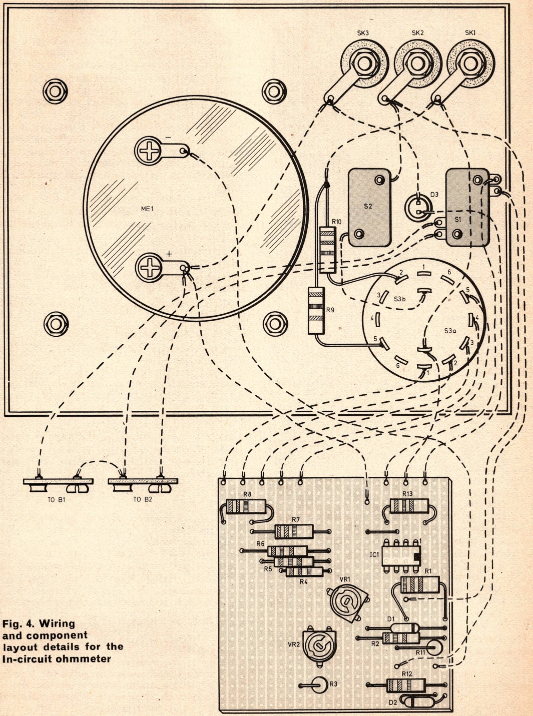

Fig. 4. Wiring and component layout details for the In-circuit ohmmeter

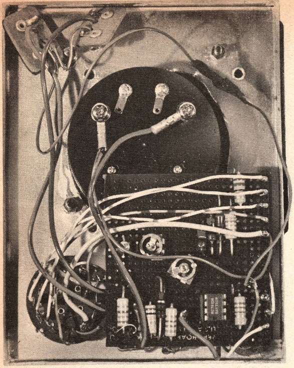

CONSTRUCTION

This presents few problems. Details of layout of circuit board are given in Fig. 4, and are not critical.

The lid of a 10·5cm × 13·5cm × 4cm box was drilled for meter, terminals, switches and l.e.d., and the connections between these were completed before wiring to the circuit board. Fairly long leads were routed to these components, ready for making connections to the Veropins on the circuit board. For convenience the circuit board, with components ready mounted on it, was stuck to the back of the meter case, using contact adhesive; connections to the board then being made.

Apart from marking switch positions for S3, no panel labelling was thought to be necessary. The switch positions were indicated by coloured discs stuck in position on the panel. In order from low to high range these discs were brown, red, orange, yellow and green. This corresponds to the resistor colour code, being the third colour of a resistor corresponding to f.s.d. on each range. Coloured self-adhesive spots sold as colour-slide spots were used for red, yellow and green, and the other discs were punched from coloured card.

SETTING UP

Make sure S2 is open, then connect a 4·7kΩ resistor across terminals SK1 and SK2. If possible, use a 1% or 2% resistor but, if not, try with several 5% resistors. Switch to the 5kΩ range and switch on the batteries. The needle may rest anywhere on the scale, or even swing violently beyond 50. Adjust VR1 until the needle comes to 47 (corresponding to 4.7kΩ on this range). It can now be seen why a precision resistor is not required for R11. Any inaccuracy in R11 is compensated for by adjusting VR1. The value of E_r is only nominally 0·1V and f.s.d. is only nominally 0·5V, but the ratio between them remains the same (1 : 5) and the equation still applies.

Now check the 50kΩ and 500kΩ ranges, using 47kΩ and 470kΩ external resistors. These should give correct readings (47 on the scale in each case) without further adjustment of VR1. If not, check wiring—particularly correct connections on the rotary switch, and also that R10 really was out of circuit when you set the 5kΩ range!

Now put a 4·7MΩ resistor across the terminals and switch to the 5MΩ range. Adjust VR2 until the meter reads 47. Finally switch to the 500Ω range, with a 470Ω resistor across the terminals; the needle should read 47. If it reads low, reduce the value of R8; if it reads high, increase R8. Some constructors may prefer to use a 100Ω preset in place of R7 and R8 and adjust this to get the correct reading.

Check the internal resistors by closing S2. The needle should read 47 on the 5kΩ and 5MΩ ranges, with no resistors connected externally to the terminals. Battery condition can also be assessed by this.

USING THE METER

Individual components are connected across SK1 and SK2. Components in circuit are tested by first disconnecting any power supply from the circuit and discharging any capacitors. Then the device under test is connected to SK1 and SK2. The distant terminals of any devices which are joined to the device under test are grounded by connecting them to SK3. A number of leads with crocodile clips will be found useful for this.

When measuring resistances, be sure to have S2 open, or there will be false readings on the 5kΩ and 5MΩ ranges.

The internal resistor of the 5MΩ range can be made use of for measuring resistances higher than 5MΩ. The formula for such resistances in series is:

$$\frac{1}{R} = \frac{1}{R_x} + \frac{1}{4{\cdot}7}$$

Where R is the resistance measured as shown on the scale, R_x is the unknown external resistor, and all values are expressed in megohms. This equation can be rearranged to give:

$$R_x = \frac{4{\cdot}7 \times R}{4{\cdot}7 - R}$$

So if R is measured, R_x can be calculated. If scale reading is 46 (normally equivalent to 4.6MΩ on this range), this would indicate a value of $R_x = (4{\cdot}7 \times 4{\cdot}6)/(4{\cdot}7 - 4{\cdot}6) = 21{\cdot}62/0{\cdot}1 = 216$MΩ. So by using the internal resistor one can estimate very high resistances, though with reduced accuracy, for with high resistances the difference between 4·7 and R is only a few scale-divisions, which cannot be estimated to a high percentage accuracy. Still, one is no worse off than when measuring high resistances at the crowded end of the scale of an ordinary ohmmeter.

Diodes and transistors can be tested for shorts and open-circuit—often a sufficient means of confirming that a component is useless. Switch to the 5MΩ range for these tests. Terminal SK1 is positive to SK2, and by connecting a diode first one way round then the other it can soon be found if it passes negligible reverse current (equivalent to high resistance—often in excess of f.s.d.). Similarly an *npn* transistor will conduct from base to emitter and

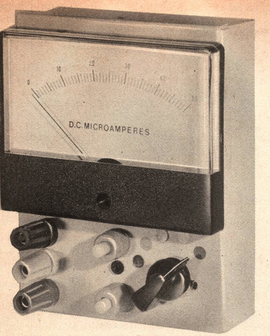

from base to collector, but not in reverse or from collector to emitter. A *pnp* transistor will conduct only from emitter or collector to base. When connected for conduction, the meter will indicate some resistance less than f.s.d. When otherwise connected, a greater resistance (usually greater than f.s.d.) will be shown.

CAPACITORS

To test capacitors, switch to either the 5kΩ range (for capacitors of 1μF or more) or the 5MΩ range (for capacitors less than 1μF). Close switch S2. Without the capacitor in place, the needle should read 47. When a capacitor is connected across SK1 and SK2, the needle kicks sharply toward zero, then steadily returns to 47. The higher the capacitance the greater the swing, and the longer time taken to return to 47. It is important to discharge the capacitor before testing and re-testing. With electrolytic capacitors observe correct polarity (positive to SK1). Take care not to charge the capacitor unknowingly; if you touch one terminal of the capacitor with one hand, and have the other hand in contact with a lead from the instrument, a current can pass through your body sufficient to charge the capacitor appreciably, and give a false reading—possibly *no* kick, which would be taken to indicate a useless open-circuit capacitor.

It is worth remembering this point too when measuring high resistances. The resistance of the human body from hand to hand is about 1–2MΩ. If this is shunted across a high resistor under test a very false reading will be obtained.

Readers may observe that the time taken for the needle to fully return to its starting point (47) is proportional to the capacitance of the capacitor. This could be the basis of a simple and rough way of estimating capacitance. Similar capacitance testing can be done with an ordinary ohmmeter, but usually a barely perceptible kick is obtained below 10,000pF. With this ohmmeter a useful check can be made on capacitors as low as 30pF. ★

NEWS BRIEFS

New Loudspeaker

THE application of modern technology to a loudspeaker concept proposed over 30 years ago has resulted in the development of a new loudspeaker construction which promises to overcome many of the mechanical drawbacks associated with normal cone-construction driver units.

The innovator, Mr Josef K. Manger, a German radio retailer, has used modern materials to produce a so-called resistive diaphragm driver which was demonstrated to the I.E.E. and the Technical Press last month using pre-production models and normal disc records.

Whilst all such demonstrations are subjective, this one indicated that the new units will bear close watching in the near future since, to the writer, they seemed to come closer to representing the actual sound experienced when standing in, for example, an orchestra, than anything heard so far.

This is perhaps an exaggerated claim but certainly the units are capable of reproducing a square wave as such which (again to the writer's limited knowledge) no other equipments seem able to do.

Currently the units are to be made in Germany in the near future on a commercial scale and it is understood that Mr Manger is looking for a possible British manufacturer to make here under licence.

World's Best Timekeeper Goes On Show

WHAT is claimed to be the world's most accurate wristwatch will soon be on display at the Science Museum in London. The Omega "Marine Chronometer" has a guaranteed accuracy of within one second per month which is achieved by using a quartz crystal vibrating at 2359296Hz as the reference.

A special feaure of this watch is that the hour and second hands can be set independently without affecting the accurate timekeeping.

Before each watch is put on the market it is sent to an independent laboratory where a certificate is awarded confirming the watch's performance.

Complete with stainless steel case and bracelet the Marine Chronometer sells for £680.

New Year Award For Radar Executive

THE New Year Honours List included the name of Dr K. Milne who has been awarded the OBE for outstanding work as Research Executive with Plessey Radar.

A recognised authority in microwave antenna research and design, Dr Milne has been responsible for many major projects including advanced radar, satellite communications and navaid systems. He is an active member of the Electronics Research Council and of international committees, contributing to the recognition of Britain's high status in microwave technology.

Ipswich News

A LECTURE entitled "Sound Synthesis for the Amateur" will be given by Douglas Shaw at The School of Engineering Technology, Rope Walk, Ipswich, on **February 26** at 7 p.m.

This lecture is part of a Hi Fi course, currently running at the Civic College, but P.E. readers in the Ipswich area who have an interest in sound synthesis are cordially invited to attend by the course tutor, P. B. Broadribb Esq.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

P.E. ORION

Good news for P.E. Orion amplifier builders, the manufacturers of the cabinet used in the prototype unit, H.M. Electronics Ltd, have recently informed us that they hope to be able to produce a pre-drilled cabinet with a self-adhesive anodised aluminium front panel as an optional extra.

H.M. Electronics have also informed us that we have quoted the wrong type number for the cabinet in our components list. The correct type number for the case is the GB1 and not GB3 as stated in the article.

Full details and a price list of their complete range of equipment cabinets can be obtained from **H.M. Electronics Ltd., 275a Fulwood Road, Sheffield, S10 3DB.**

We have been informed that some readers have experienced difficulty in obtaining the mains transformer. This transformer, type SL8, can be purchased from **Gardners Transformers Ltd., Christchurch, Hants., BH23 3PN,** for £10·23 including postage and VAT.

Alternatively, the transformer for the P.W. Texan amplifier can be used in the P.E. Orion. This has a lower current rating and will give a slightly reduced output power, but it should be entirely satisfactory for speech and music. This transformer is available from **Henry's Radio Ltd., 303 Edgware Road, London, W2 1BN,** for £5·94 including postage and VAT.

LOUDSPEAKER KIT

Readers who have completed or nearing completion of the P.E. Orion, and are shopping around for a reasonable speaker system that they can build for themselves, may find the range of SEAS hi-fi loudspeaker kit now being marketed by Macel Electronics worth investigating.

Designed for sealed enclosures, there are five kits available, capable of handling outputs ranging from 20W to 70W. The frequency response of the units ranges from 25 to 20,000Hz, according to speakers used and size of enclosure. Each kit includes a tweeter, main driver(s), crossover unit and connecting wire with a din plug. The speaker impedance is 4 to 8 ohms.

A feature of the systems is that each kit contains a recommended enclosure design with full measurements and constructional guidance notes.

Further information and full details of their complete range of SEAS hi-fi loudspeaker kits can be obtained from **Macel Electronics Ltd., P.O. Box 64, 14 High Street, Ipswich, Suffolk.**

DIGITAL LEAF

Suitable inexpensive valves for use with the "Digital Leaf" greenhouse automatic moisture system, described in our January issue, are available from Concordia Automation Components.

Several types are available with $\frac{1}{8}$in, $\frac{1}{4}$in, $\frac{3}{8}$in and $\frac{1}{2}$in B.S.P. connections for mains or low voltage supplies at prices from £6 each. This is approximately half the figure quoted in the article.

Further information on these valves can be obtained from **Concordia Automation Components Ltd., 6 Central Park, Worcester Park, Surrey, KT4 8HZ.**

NEW LITERATURE

Recently formed to market p.c.b. hardware, heat sinks and modules manufactured by Assmann KG, Germany, Dieter Assmann Electronics announce the availability of a new catalogue.

The catalogue contains 50 pages of detailed information covering the whole of the Assmann product line. Dual-in-line sockets, for example, can be supplied with from 8 to 40 pins, including the popular 14- and 16-pin units. Sockets and mounting pads for transistors are also available in most of the popular configurations.

The range additionally includes p.c.b. connectors, and bread boards for experimental and development work. Details of jumper links, terminal pins, u-pins, eyelets and insulated terminals form a complete section in the catalogue. A very broad range of heatsinks is also covered, including extruded and cast aluminium, and staggered finger types.

Copies of the catalogue can be obtained from **Dieter Assmann Electronics Ltd., Victoria Works, Water Lane, Watford, Herts.**

SEAS hi-fi loudspeaker kit from Macel Electronics

SEMICONDUCTORS

High Speed 741

In many areas of application engineers need a higher slew rate from their operational amplifiers than can be obtained from the everyday 741 chip.

Motorola have provided the answer to this problem with a plug-in alternative designated MC1741-SCP1.

The new device, available ex-stock from Jermyn at a 1-off price of £0·92 each, boasts a slew rate of 10V per microsecond, suiting it to digital-to-analogue converters and amplifiers where bandwidth from d.c. to over 100kHz is important.

Further details available from **Jermyn Industries, Vestry Trading Estate, Sevenoaks, Kent.**

HIGH SPEED '741' OP. AMP.

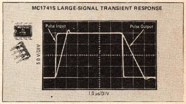

Audio Transistors

Five new complementary pairs of silicon epi-base, epi-collector power transistors designed for a complete voltage range have just been announced by SGS/ATES.

The first pair, BD433 and BD434, have been developed for in-car entertainment applications with power requirements up to 12W. The second and third pairs BD435 and BD436, and BD437 and BD438, are particularly suited to hi-fi audio amplifiers up to the 15/20W range.

All types in the range are suitable for industrial applications such as power drivers, switching circuits and current regulators up to 4A and, of course, for automotive applications such as flashing lights, lamp dimmers and direction indicators.

All the devices are rated at 36W P_{tot}, 4A I_c and an f_t of 3MHz, whilst the V_{ceo} values for pairs are as follows: BD433/34, 22V; BD435/36, 32V; BD437/38, 45V; BD439/40, 60V and BD441/42, 80V.

Further details available from **SGS/ATES (U.K.) Ltd., Planar House, Walton Street, Aylesbury, Bucks.**

NEXT MONTH...

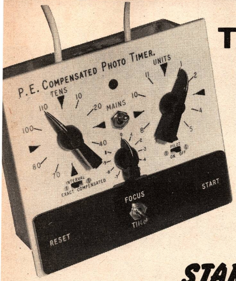

THE PE COMPENSATED PHOTO TIMER

The P.E. compensated photo timer not only provides simple selection of time interval from 0·1s up to 120s with controls designed specifically to suit darkroom conditions, but additionally provides for exposure compensation of mains voltage variation effects on enlarger lamp light output.

STARTLE YOUR FRIENDS WITH THIS MUSICAL DOORBELL

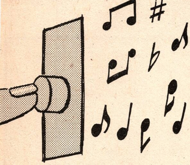

Capable of playing a tune of welcome (or rejection!) dependent on the choice of programme you put in. Integrated circuitry and state-of-the-art logic make for simplicity of construction.

STARTING NEXT MONTH...

INTRODUCTION TO TRANSDUCERS

An important and informative series on Transducers, their operation, types, uses and technical features. Make certain not to miss any of this in-depth study of these important tools in the art of measurement.

TEMPERATURE
HEAT LIGHT WEIGHT
DISTANCE SOUND
FREQUENCY DEPTH

PRACTICAL
ELECTRONICS

APRIL 1975 ISSUE ON SALE MARCH 14, 1975—PRICE 30p

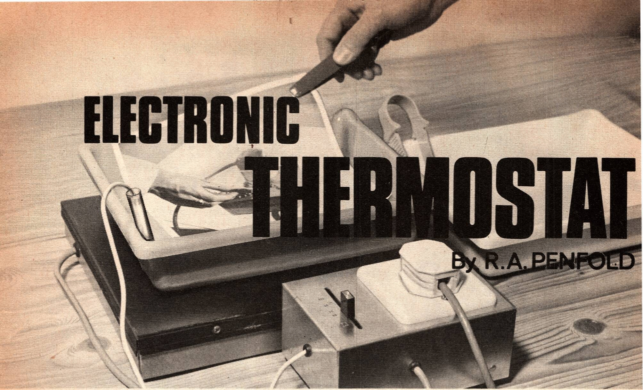

ELECTRONIC THERMOSTAT

By R.A. PENFOLD

In photographic work it is often necessary to keep solutions at a constant temperature during the printing process. The situation is especially critical when it comes to colour printing, where it may be necessary to maintain the temperature of the solutions to within a fraction of a degree.

The normal method of achieving this is to place the dishes containing the photographic chemicals on a thermostatically controlled dish warmer. However, many devices of this type use mechanical thermostats which are far too insensitive for accurate temperature control, and can often only keep the solutions to within a couple degrees of the required temperature.

PRECISE CONTROL

The device which forms the subject of this article was built to give a much more precise control over a system such as that just described, and has proved to be very successful in use. Exactly how accurately it will maintain a given temperature will depend to a certain extent on the apparatus with which it is employed, and also on the efficiency of the sensor. It should however, be able to maintain a temperature to an accuracy of about plus or minus 0·2 degrees.

It can of course be used for any similar purpose where it is necessary to maintain a liquid at a constant temperature. The range covered by the unit is from slightly below 50°F to a little more than 100°F.

Circuits of this type can be rather complicated, but in this design the utilisation of an i.c. operational amplifier enables a very simple and straightforward circuit to be used.

THE CIRCUIT

A complete circuit diagram of the electronic thermostat is shown in Fig. 1. The unit is designed around the 741C i.c., which is used here as a differential amplifier.

COMPONENTS . . .

Resistors

R1, R2	5·6Ω (2 off)
R3	33kΩ
R4	27kΩ
R5	10kΩ
R6	4·7kΩ
R7	430Ω
R8	220kΩ

All ½W 10% carbon

Potentiometer

VR1	10kΩ linear slider

Capacitors

C1, C2	220μF 16V elect. (2 off)

Semiconductors

TR1	BC109
D1–D4	1N4001 (4 off)
D5, D6	BZY88 C10 10V 400mW Zener (2 off)
D7	OA200 or any general purpose silicon diode
IC1	741C 8-pin d.i.l.

Thermistor

TH1	VA1066S

Miscellaneous

SK1	Surface mounting mains socket
RLA	Miniature 12V relay (Omron 1051, 465 Ω Home Radio)
T1	Mains primary, 9–0–9V 80mA secondary (Osmor MT9, Home Radio)
S1	Single pole on/off
FS1	500mA with holder

0·1in matrix Veroboard 35 × 15 holes

6in × 4in × 2½in aluminium chassis with base plate

Screened cable, hardware for sensor

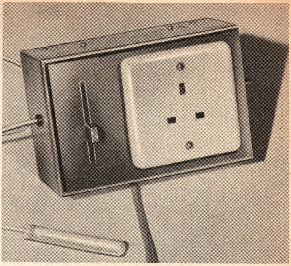

The completed Electronic Thermostat showing layout of controls on the front panel

As the name suggests, this amplifies the difference between the two input voltages. The output will be near ground if the inverting input is at a higher potential than the non-inverting input. On the other hand the output will be near the supply rail if the non-inverting input is at a higher potential than inverting one.

The gain of the i.c. is extremely high, and the voltage difference required at the inputs to cause the output to swing fully one way or the other is only a fraction of a millivolt. This tends to give the circuit built-in triggering, as there is such a restricted range of voltages which will give an intermediate state at the output.

BRIDGE CIRCUIT

At the inputs to the i.c. there is a bridge circuit. One arm of this is formed by R3, VR1, and R4, and the other by R5, R6, TH1. The supply is connected to the input of the bridge.

Thermistor TH1 is mounted in a probe which is immersed in the liquid to be controlled. Its resistance will therefore increase if the temperature of the liquid drops, and decrease if the temperature increases. This change in resistance will cause the voltage at the non-inverting input to change also, a positive change in temperature causing a negative change in voltage.

The output from IC1 is coupled via R8 to TR1, which has the relay in its collector circuit. The contacts of the relay are taken to a mains socket, into which the dish heater is plugged. When the output of IC1 is high (+20V) the relay is energised. R7 is required in order to reduce the supply to a more suitable level to power the relay. Diode D7 is the normal protective diode. Even when the output of the i.c. is low there is an output potential of about two volts. R8 is therefore required to prevent the relay from being permanently held on.

CALIBRATED SCALE

In practice VR1 is marked with a scale calibrated in degrees. If, for example, this is set to 100°F, at the start the liquid will probably be at about room temperature, and considerably less than 100°F. The voltage at the non-inverting input will be high in comparison to that set at the other input by VR1. The output of IC1 will thus be high and the heater will be turned on. As the liquid warms up the voltage at the non-inverting input will decrease, until eventually when the liquid reaches 100°F, this voltage being equal to that at the other input, will cause the output of IC1 to go low, and the heater to be turned off.

The liquid will now of course begin to cool, but will not be allowed to cool much, as this cooling will be sensed by the thermistor, which will unbalance the input voltages resulting in the heater being turned on again. The circuit will continue to oscillate in this way, thus stabilising the temperature of the liquid.

POWER SUPPLY UNIT

A simple stabilised mains power supply is used. This consists of two full wave supplies, each providing 10V, connected in series to give 20V, which is

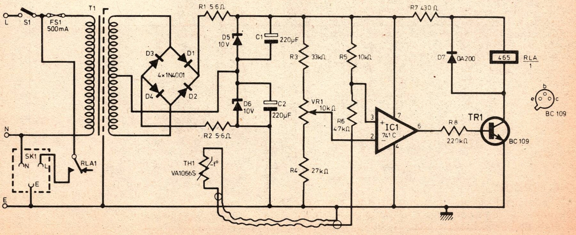

Fig. 1. Complete circuit diagram of the Electronic Thermostat

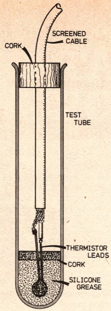

Fig. 2. Construction of the sensor using a small test tube and some silicone grease

adequate for the 741C. D5, and D6 in conjunction with R1 and R2, and the relatively high secondary impedance of T1 give the stabilisation. C1 and C2 provide the necessary smoothing.

SENSOR CONSTRUCTION

The thermistor must be contained in a watertight compartment, and it must also be in good thermal contact with the outer surface of the container. Fig. 2 illustrates the construction of the sensor used with the prototype. The outer casing is a small glass test tube. The thermistor is mounted at the bottom of the tube, and is immersed in silicone grease to ensure a good thermal contact with the test tube.

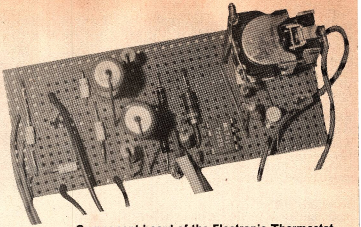

Component board of the Electronic Thermostat

The small slice of cork above this helps to keep the thermistor firmly in place, and also helps to prevent its leads from shorting together. Also, the silicone grease is rather thick, and needs to be pushed to the bottom of the tube. The slice of cork is very good for this task. Thin microphone cable is used to connect the sensor to the main body of the instrument.

CASE CONSTRUCTION

A suitable case for the unit consists of a 6in × 4in × 2½in aluminium chassis fitted with a base plate. Four rubber cabinet feet are bolted to the base. The general layout of the case can be seen from the photographs. The mains socket is mounted on top of the case on the right hand side. This mounted by two 4BA ¾in bolts.

A large part of the socket fits behind the panel, and a large cut out must be made for this to fit through. This is easily made by drilling a string of ⅛in holes around the perimeter of the cut out, and then using a ⅛in "Abrafile" to join the holes.

The slider potentiometer is mounted on the left of the mains socket, and it is glued into position. The cut out for this can be made in a similar way as that for the mains socket. A nail file can be used to smooth up the edges of the slot.

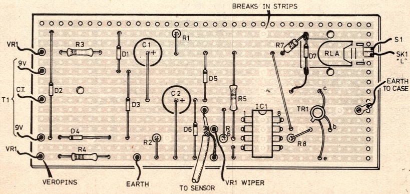

Fig. 3. Layout of components on the Veroboard. The diode D7 is connected directly across the coil contacts of the relay

The on/off switch is mounted on the centre of the right hand side panel. The lead from the sensor enters the case opposite this on the left hand side, and the mains lead enters on the lower edge of the case. The holes for both these leads must be fitted with rubber or p.v.c. grommets.

COMPONENT PANEL

Most of the components, including those of the p.s.u. (except T1), are mounted on a 0·1in matrix Veroboard panel. Fig. 3 shows the layout of this.

The mounting holes for the relay are ⅛in diameter. The mounting screws and washers are supplied with the relay. There are two mounting holes for the board, and these are for 6BA clearance. The outer braiding on the lead from the sensor is too large in diameter to go through the holes in the Veroboard, and is therefore taken to a pin.

When completed, the board is mounted on the upper side of the case by two 6BA ½in bolts. Two stand off insulators are required to hold the board a little way clear of the case.

ADDITIONAL WIRING

T1 is glued to the inside of the case opposite the Veroboard panel. Unfortunately the lead out wires of this are too short to reach the Veroboard panel. The leads from T1 are taken to a miniature three way connector block, and three insulated wires are taken from this to the component panel. The mains input is also taken to one side of a three-way connector block, and from here the connections are made to the various parts of the circuit.

Only the two connections to the relay contacts at the top, and middle of the relay are used, the lower one being ignored. Up to five amps at 250V can be handled by the specified relay.

It is essential that the negative supply is earthed, as if this is not done the relay will not switch over cleanly. For reasons of safety the case must also be earthed. A solder tag on one of the mounting bolts of the component panel is used to make the connection to the case. The two connector blocks can be bolted to the case, but on the prototype these were left supported only by the leads connected to them.

CALIBRATION

A scale is marked along the run of VR1. The various points along this are easily found. If for example it is required to find the setting which corresponds to 100°F, the sensor is placed in some water which has been heated to precisely this temperature. Once the sensor has had time to adjust to the temperature of the water, the slider of VR1 is brought as far down the scale as possible without the relay turning off. This point is then marked 100°F.

The scale is rather broad, as a fairly wide range of temperatures is covered. If absolute accuracy is required, it is advisable to initially use a thermometer to monitor the temperature of the liquid, and then if necessary, small adjustments can be made to the setting of VR1 to bring the temperature to exactly that required. ★

21st London International BOAT SHOW 75

Once again the annual International Boat Show has brought forward a variety of new and interesting developments in electronics associated with the sea. One of the most important and significant innovations on display this year was the Lucas Marine safety buoy. The buoy is automatically released from a sinking vessel and remains anchored to the vessel at depths up to 3,000ft. It sends out a distress signal at 121·5 and 243MHz, emits a high intensity flashing light, releases a 50ft floating line with light to act as a rallying point for survivors and releases an automatically inflating four to six man life-raft. Other facilities are also available, such as marker dye and calming oil.

The electronics are powered by lithium batteries which have a recommended replacement life of four years. The transmitted distress signal has been satisfactorily received at a range of 180 miles.

Another new device to aid safety at sea is the G.H.T. Gas Safety Unit. Using solid state gas sensors and electronic control, this unit not only senses the presence of dangerous gases, but turns off the gas at source. The unit is fitted with voltage failure protection and has to be reset once triggered or if the supply fails.

One of the most popular ranges of instruments among the racing yachtsmen, Brookes and Gatehouse, has this year been increased and modified. A new unit, the Halycon—they must run out of names soon—is a repeating compass with dead reckoning indicator providing information on position in two co-ordinates. This year B. and G. have introduced a quartz crystal controlled chronometer and l.e.d. internal lighting for their repeater instruments.

Baron Instruments have introduced a Square Mk. 2 range—re-designed housings and dials. Two versions of the log are available (0–15 knots and 0–35 knots) and three versions of the depth sounder 0–30, 0–60ft/fathoms and 0–10/100 metres.

Decca were showing the 36 mile 110 Radar for the first time; this equipment employs a 4ft scanner and therefore is not likely to be seen on anything but the largest private yachts. This set is basically an improved version of the 101 Radar that has proved itself over the years.

Space Age Electronics were displaying a doppler speedometer with audible output for dingy tuning—the transducer is inserted in the centre board case and an increase in speed increases the frequency of the output. However, at £40 it may not be very popular.

Also from Space Age a portable echo sounder for fishermen; using l.e.d. output it is claimed that fish can be easily recognised. Can be used in a boat or from the river bank.

Finally, two points concerning EMI. The first is rather sad—The Electrascan radar will soon be discontinued, presumably competition from others, the servicing requirements and the general financial situation have all taken their toll. The second item—looking ahead to next year's Boat Show—the CCTV Division of EMI Sound and Vision Equipment Limited, is providing additional security in the form of an automatic closed circuit TV alarm system.

The system is in no way intended to inhibit normal movement through the entrances and exits, but it is intended to assist the existing security services to prevent the unauthorised entrances of people into the show halls.

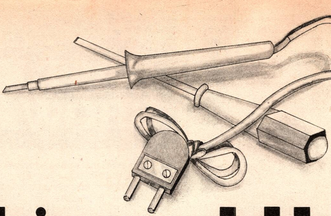

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

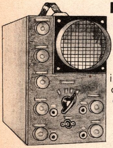

1

Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you willneed not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

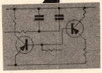

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

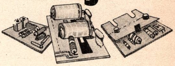

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

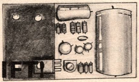

FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EL35
P.O. Box 156, Jersey, Channel Islands.

NAME ....

ADDRESS ....

....

(Block caps please)

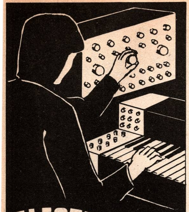

ELECTROMUSE

By Malcolm Pointon

THE time has come to introduce a few practical projects in the production of taped music. In the coming months it is hoped to bring out some hints on the creative use of the P.E. Minisonic Synthesiser, but for the moment it seems advisable to get into practice with tape manipulation, to perform a short composition and settle on the kind of equipment required to get the best out of the Minisonic—or any other sound source destined to be frozen on tape.

Firstly the equipment. It is generally advisable to have two tape machines available, although both need not necessarily be sophisticated stereo (or quadrasonic) units. Preferably both should be reel-to-reel machines (for ease of editing) though one can get along quite well with one stereo reel-to-reel machine and a cassette deck. In the interest of increased versatility a choice of tape speeds should be available (19, 9·5, and 4·75cm/s being normal on domestic equipment).

If one or both machines are stereo with track-to-track dubbing (so-called multi-play) one can extend the number of superimposed recordings without unduly affecting the final quality. Personally, however, I tend to ignore this facility and use two stereo machines through a mixer in order to produce a stereo result.

Basic set-up

The mixer unit need not be an elaborate affair. A very workable battery-powered stereo unit can be built around a couple of 741 op.amps with as many input and output connections as required. For the coming projects, including this month's, I recommend at least eight inputs, individually switchable from left to right channels, and three-plus-three outputs.

Any stereo amplifier will serve in the set-up since it is to be used only for monitoring purposes; one of the stereo outputs from the mixer will be permanently connected to its Auxiliary, Tape, Radio or Phono socket.

The final piece of equipment for this month's project is a short-wave radio receiver, see Fig. 1.

Method of composing

As a student some years ago I felt the urge to attempt some electronic music, spurred on by the apparent simplicity of the sound material in Stockhausen's "Study II". Without the mass of equipment necessary I had to rack my brains to find an alternative sound source. The problem was partially solved by a domestic four-waveband a.m. radio set. After hours of patient (and enjoyable) knob-twiddling I managed to find a selection of "electronic" sounds which promised to be of use. Armed with a splicing block, razor blade, splicing and leader tape and a four-speed mono tape recorder I spent a fortnight's spare time producing a two-minute piece.

The project outlined below works along these lines, but since stereo is pretty commonplace nowadays I have decided to compose a two-channel work. Those who may only have access to mono machines could still, with a bit of juggling, produce a mono version of it.

PELORIA

I have called my piece "Peloria"* which is laid out in time, the numbers 1 to 20 across the top and bottom of the score referring to equal time intervals chosen by the performer, see Fig. 2.

Each channel has three imprecisely laid out pitch bands—high, medium and low. The dynamic levels are similarly imprecise: *pp*=very soft, *p*=soft, *mf*=moderate level, *f*=loud, *ff*=very loud. The short-wave sound material, chosen by the performer, is shown largely in rectangular blocks, variously shaded; blocks containing horizontal lines indicate a rich or busy sound with no discernible melodic or rhythmic consistency; similar vertical narrow bands represent a very short event.

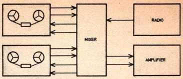

Fig. 1. Simple tape effects set-up

The areas shaded with dots represent fleeting pitches which may be discernibly rhythmic or melodic yet move at great speed. The blocks shaded with short curved lines represent melodic and rhythmic patterns of a moderate-to-quick speed. Horizontal broken lines signify a decrease in level towards silence if placed after continuous lines, an increase if they appear before.

The sound material for "Peloria" is available, from my experience, all year round. I suggest that all the sounds required for the piece be recorded at some length and at all speeds available on your tape machine; this gives sufficient length to cut out unwanted blips and to ensure an increased variety of pitch bands. Decide on the length of your time interval—you may do this roughly with the seconds hand of a watch or more precisely by measured lengths of tape. Those events which require an increase or decrease in level should be re-recorded using the level controls on the mixer.

From the material you now have snip out the measured lengths for channel one, not forgetting the periods of silence. Record the whole of the sequence on to the left-hand channel of your stereo machine. Now edit the tape for channel two, placing leader tape between events; this will allow you to pause during the gaps and come in on time for the final transfer to the right-hand channel of your stereo machine. Absolutely exact synchronisation is not necessary in this piece.

*Peloria: The regularity in a normally irregular flower (Chamber's Twentieth Century Dictionary).

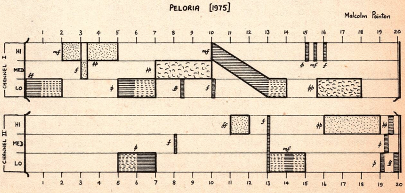

Fig. 2. Mr. Pointon's method of composing electronic music for his piece called "Peloria"

THE Geiger counter described in this article is small enough to be slipped into the pocket and taken out into the country to look for radioactive minerals. Quarries and old mine workings are good hunting grounds, particularly if geologically old rocks are being uncovered. Unfortunately, your search is not likely to be very rewarding in this country.

Nevertheless, the instrument will show that we are being exposed continually to a natural background radiation made up of cosmic rays and the emissions from radioactive materials in the ground and air around us and over which we have very little control. The instrument can also be used to locate sources of radioactivity should these be mislaid in the workshop and laboratory.

The instrument is quite sensitive, it will count by producing a click in an earpiece, a single beta particle (an electron) whose mass is about one million billion billionth of a kilogram (10^{-30}kg) and which could be moving at about 800 million kilometres per hour!

GEIGER COUNTER

By M. PLANT M.Sc.

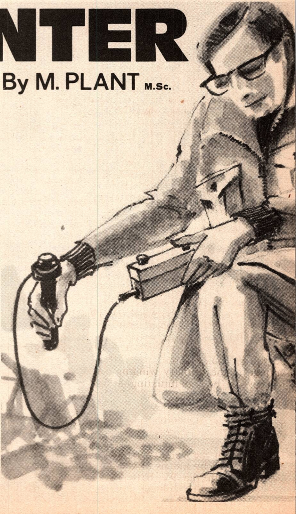

The accompanying photographs show one form of the completed Geiger counter with the electronics housed in a plastics slide box. In use the box is held close to the ear, the thumb holding the push-button switch down.

THE GEIGER TUBE

The Geiger counter tube is the part which is sensitive to the atomic radiations which are emitted from radioactive sources and which make up cosmic rays. The type of tube shown in the photographs is fairly common and consists of a central anode surrounded by the cathode. Photos show the kind of tube which has an end window to allow it to respond to alpha particles (the nuclei of helium atoms) and to low energy beta particles, both of which are most easily absorbed by the material through which they pass. The less sensitive tube shown in the model responds to the very penetrating radiation of gamma rays and high energy beta particles.

Geiger tubes (strictly called Geiger-Muller or GM tubes) are available on the government surplus market for a few pounds and are often advertised in the pages of this journal or are available from suppliers of Mullard equipment.

The tube selected should have an operating voltage of about 400V. An important feature of the counts per minute versus voltage across the anode-to-cathode of a geiger tube is the so-called plateau of operating voltage which is shown in Fig. 1. The sensitivity of the tube increases gradually over this plateau and it is important to operate the tube within this range of voltage; the midpoint of the plateau is usually chosen and the present instrument can be adjusted to operate the tube at this voltage. Geiger-Muller tubes have commonly a two-pin base requiring a special holder, but some have an octal base although just two of these pins actually make connection to the tube.

THE CIRCUIT

Fig. 2 shows the circuit which consists essentially of three parts, an inverter or d.c.-to-d.c. converter, a voltage doubler, and an amplifier. The inverter and voltage doubler enable a 9V battery to provide up to 500V to operate the GM tube, and the amplifier is required to amplify the voltage pulses obtained across a resistor in series with the tube when the tube responds to the effect of a particle passing through it.

THE INVERTER

The inverter is a simple resistance-coupled oscillator which gives about 250V across the secondary of the 9-0-9V/250V transformer at a frequency of about 40Hz.

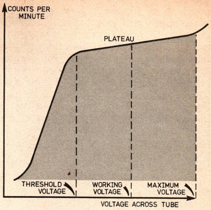

Fig. 1. The characteristic curve of a GM tube

Up to 250V a.c. is available across the secondary winding of the transformer and this is doubled and rectified by the diodes D1 and D2 and the capacitors C2 and C3 to provide about 500 V d.c.

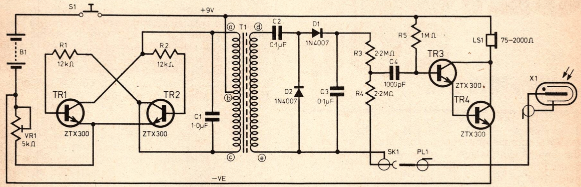

Fig. 2. Circuit diagram of the power supply, GM tube and amplifier

TR1 starts to conduct when the circuit is switched on and current increases in the associated half of the primary winding of the transformer, induces a voltage in the other primary half which rapidly drives TR1 into saturation via the base coupling resistor R1 and thus biases TR2 off.

Flux increases in the core of the transformer until saturation is reached when the positive feedback provided by the induced primary voltage falls to zero. TR1 is returned to the off state and this ends the first half cycle of the period of oscillation. The collapsing flux in the transformer core induces a voltage in the primary winding associated with TR2 to drive it on, so initiating a second similar half-cycle.

Capacitor C1 across the collectors of the transistors eliminates the possibility of high frequency oscillation and makes for reliable starting of the inverter. The actual primary voltage being switched by the two halves of the primary winding of the transformer can be varied by means of the variable resistor VR1 in series with the 9V battery so that the voltage available from the voltage doubler can be varied to suit the characteristics of the tube used.

The output from the supply is applied across the GM tube via R3 and R4. The passage of a radioactive particle through the gas filling the tube causes some of the gas to be ionised. Under the high voltage between the anode and cathode, a rapid avalanche of ionisation occurs and ions are collected by the electrodes resulting in a very small current through the external resistors R3 and R4. This pulse of ionisation is short-lived and the tube is quickly ready to respond to another ionising particle passing through it. The voltage change across the external resistors is coupled to a two-transistor amplifier by the coupling capacitor C4 so that a loud click is heard in the earpiece.

ASSEMBLY

A piece of Veroboard was selected for assembling the circuit, the precise dimensions depending on the physical size of the components to hand and the case used. In the present instance the case used in the prototype was a Kodak slide box measuring 108 × 32 × 52mm and the Veroboard measured 46 × 54mm.

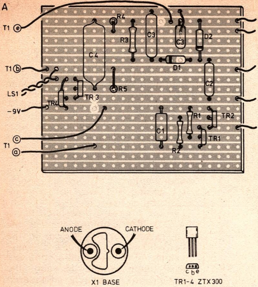

Fig. 3. Component layout and Veroboard cutting details for the counter

COMPONENTS . . .

Resistors

R1, R2	12kΩ, 2 off
R3, R4	2·2MΩ, 2 off
R5	1MΩ

All ¼W, 10%

Potentiometers

VR1	5kΩ skeleton pre-set

Capacitors

C1	1μF, 250V
C2	0·1μF, 250V
C3	2 off 0·22μF, 250V to make up 0·1μF, 500V
C4	1,000pF mica

Semiconductors

TR1, 2, 3 & 4	Silicon *npn* ZTX300 or similar, 4 off
D1, 2	1N4007, 2 off

Switches

S1	Push-to-make button switch or slide switch

Miscellaneous

T1	Transformer, 9–0–9V primary, 240V secondary. Midget mains type such as Osmor MT9
LS1	Small earphone, 75Ω or above (to 200Ω)
X1	Mullard MX168 or similar low voltage type GM tube. Possible sources Henry's Radio, 20th Century Electronics Ltd., New Addington, Croydon, Surrey
B1	9V, PP3 or PP6 suits
	Tube holder; co-ax cable; co-ax plug and socket; Veroboard; wire; solder; suitable box.

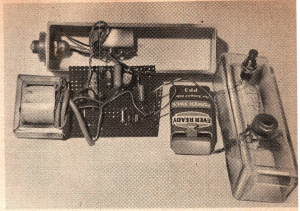

Completed Geiger Counter ready for installing in a photographic slide case

Fig. 3 shows the component layout of the prototype circuit in which C3 is made up of two 0·22μF, 250V capacitors connected in series to give, effectively, a 0·1μF, 500V capacitor. However, a suitable single capacitor may be obtained for this circuit, although physical size may preclude use. The main precaution to be taken is to ensure that the high voltage cannot be inadvertently connected to the low voltage side of the circuit, otherwise damage to the transistors and C1 may result.

SETTING-UP

After assembly and before connecting the Geiger tube, switch on the circuit and listen for a faint low frequency hum coming from the earpiece which indicates that the inverter is working. Rotate the high-voltage-adjust variable resistor VR1 and the hum should change in intensity and frequency slightly.

Next, use a high impedance voltmeter to measure the voltage available at the socket for the GM tube and adjust this voltage to that required to drive the tube. Sometimes this voltage is marked on the side of the tube.

If the voltage is not marked and you are unsure of the correct operating voltage, connect the tube and increase the voltage slowly by means of VR1 until the tube begins to respond to the background radiation and clicks are heard. Increase the voltage by about 20V and then leave VR1 alone. The counting rate due to the background depends upon your locality, the operating voltage of the tube and the volume of the gas in the tube as well as its construction.

Using a gamma-ray sensitive tube, a background count rate of about 45 clicks per minute should be obtained.

Bring up a luminous watch or clock face to the tube and the count rate will increase. The Geiger counter is now ready for use. From time to time it will be necessary to adjust VR1 to compensate for the fall with use of the terminal voltage of the battery. Never operate the tube at too high a voltage so that it breaks into continuous discharge for this will decrease its useful life markedly. ★

INDUSTRY NOTEBOOK

By Nexus

SMALL IS BEAUTIFUL

From time to time I have been criticised for writing too often about the smaller enterprises in the electronics industry. But there's a lot to be said in favour of the homely neighbourhood store compared with the supermarket. Both have their role to play in our complex world. The same with electronics where there is still plenty of room for the small man in among the giants. And it is still demonstrable that for sheer profitability in the electronics industry the optimum size of the workforce is about 300 people. This is the maximum size where the boss still knows everyone and everyone knows the boss. Where people know what's going on, feel appreciated, have some job satisfaction.

It's the sort of size, too, where a company is still flexible. Reaction times are less and response is quicker. Product lines can be switched quickly to meet changing conditions. There is no multi-million pound investment in a single product line that might, and often does, go sour when brought to the market place.

A good example of what I mean is Brandenberg Ltd. which celebrated its 21st anniversary recently. It's a comfortable little unit employing 160 people in a 25,000ft^2 plant at Thornton Heath.

Turnover is running at over £1 million with £100,000 going for export. The company makes high voltage power supplies. Buy one of those super Cambridge 'Stereoscan' scanning electron microscopes and you'll find the high voltage supply made by Brandenberg.

The lethal punch in Rentokil electronic fly-killers comes from another Brandenberg unit and radar displays, photocopiers, nuclear physics, all are grist to the Brandenberg mill for EHT assemblies. Anything up to 100,000 volts—more if a "special" is required.

BUT GROWTH NECESSARY

Having said all that, it still has to be admitted that growth remains a prime business objective, even with companies like Brandenberg. Nearly all managing directors are dedicated to growth as a desirable end in itself. The challenge is to keep growth profitable. With present rates of inflation it is natural that turnover should increase by, say, 20 per cent a year from the same volume of business, but if running cost increases are in excess of 20 per cent then the company is slipping behind. So you need greater efficiency.

GDS Sales Ltd., the Slough-based component distributors, have now implemented a computerised inventory management and order processing system based on an IBM 3/10 with disk file and video display terminals. The system is the result of over a year of planning and it really does its job. It gives a quicker order turnround for the customer but, equally important, it spins off all the management information needed for true efficiency, especially in stricter control of the £400,000-worth of components stored in the main warehouse. GDS, in one of the most hotly competitive areas of electronics, has doubled turnover in two years and is keeping ahead of the game. In the same period the company has opened distributor operations, though as yet on a smaller scale, in Holland, Switzerland and Denmark.

TOP SECRET

High-flying Racal Electronics Group is still showing the rest how to conduct a profitable world-wide business. Last published figures show increased turnover at £34·62 million and almost £3 million profit. And 1975, despite the prevailing gloom, is again forecast as a record year. Racal chairman Ernest Harrison is one of the most forthright men in the industry. But even he keeps mum over what Racal is up to in the speech privacy market. Last year a new company was formed called Racal-Datacom based in Salisbury. It is manufacturing equipment for speech scrambling—all rather hush-hush and we are told only that "the speech privacy market will grow in the next two years".

Harrison is a firm believer in small companies where people are well-motivated. As soon as a Racal company gets too big for real efficiency it is split and a new company formed. There are acquisitions, too, such as British Physical Laboratories who recently joined the Group.

THE BIG LEAGUE

Of course you've got to be big and have huge resources to cope with projects of great magnitude. Satellites, for example.

This year sees Marconi getting its teeth into MAROTS, the European marine communications satellite due for launch in the Autumn of 1977. Marconi is prime contractor for the satellite payload with a contract price of £11 million.

Hawker Siddeley Dynamics has a budget of £9 million for the spacecraft. And MAROTS itself is only the experimental and pre-operational unit paving the way for a more advanced system.

British Aircraft Corporation has a £1·25 million contract for satellite sub-systems for the ISEE-B in the International Sun Explorer Satellite System. All these satellite contracts have been placed through the European Space Research Organisation.

BAC will also be busy this year working through the backlog of orders for the Rapier low-level air defence missile in which quite a number of electronics companies are engaged on sub-contracts. BAC took orders last year for a staggering £100 million of Rapier systems, the bulk of them from the Middle East. Total Rapier sales are now well over £200 million.

NORTH SEA ELECTRONICS

And whatever the dividends from North Sea oil in the years ahead, there's certainly plenty of business there today. The Post Office, for example, is spending a cool £8 million on quadruple diversity troposcatter systems out to the rigs operated by the Total, Mobil and Occidental Groups. Marconi gets £1·5 million of the work for the shore terminals. Marconi is also supplying huge quantities of other equipment including the privately owned troposcatter links run by BP and Phillips Petroleum.

Nobody has yet worked out the cost of defending the rigs once they become operational. Certainly there will be a need for patrol vessels and aircraft fitted with radar, sonar and communications. It's a whole new world of opportunity for the electronics industry.

Just in case anyone gets the idea that the giants can only move slowly, let me recount a story out of the £200 million a year turnover Pye of Cambridge Group. Pye TVT did a rush job for Australia to get colour TV outside broadcast vans delivered in time for the opening of the colour service on March 1, 1975. By working round the clock a twelve week installation and testing procedure was telescoped to four weeks.

NEW LOW PRICES!

Sinclair Scientific kit

(Was £19.95 - save £5!)

£14.95
(INC. VAT)

Britain's most original calculator now in kit form
The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range – features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables!
With the functions available on the Scientific keyboard, you can handle *directly*

sin and arcsin,
cos and arccos,
tan and arctan,
automatic squaring and doubling,
$\log_{10}$, antilog_{10}, giving quick access to x^y (including square and other roots),
plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?
No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer – they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

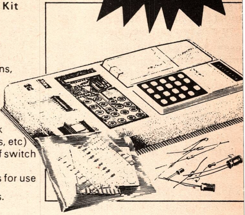

Features of the Sinclair Scientific

● **12 functions on simple keyboard**
Basic logs and trig
functions (and their
inverses), all from a k
board as simple as a
normal arithmetic cal
culator's. 'Upper and
lower case' operation
means basic arithmet
keys each have two e
functions.

● **Scientific notati**
Display shows 5-digi
mantissa, 2-digit exp
nent, both signable.

● **200-decade rang**
10^{-99} to 10^{+99}

● **Reverse Pol**
logic Post-fixe
operators allow c
calculations of unlin
length – eliminate ne
for an = button.

● **25-hour battery**
4 AAA manganese al
line batteries (e.g.
MN2400) give
hours continuo
use. Complet
independe
from exter
power.

● **Genuin**
pocketable
4 1/3" x 2" x 11/16".
Weight 4 oz. Attractiv
styled in grey, blue ar
white.

EW LOW PRICES!

Sinclair Cambridge kit

(Was £14.95-save £5!)

Now only £9.95 (INC. VAT)

its new low price, the
ginal Sinclair Cambridge
remains unbeatable value.

ess than a year, the
mbridge has become
tain's most popular pocket
culator.

not surprising. Check the
tures below – then ask
urself what other pocket
culator offers such a
werful package at such a
sonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this money-back, no-risk offer today
The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question.
All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific
Price in kit form £14.95 inc. VAT
Price built £21.55 inc. VAT.
Cambridge
Price in kit form £9.95 inc. VAT.
Price built £13.99 inc. VAT.

eatures of the Sinclair Cambridge

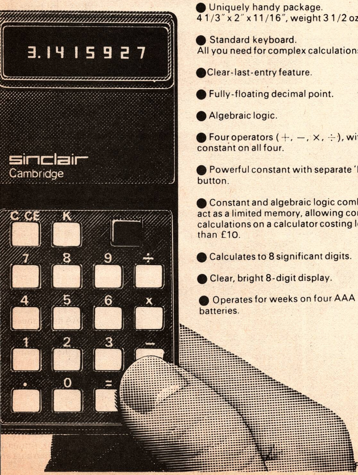

- Uniquely handy package. 4 1/3" x 2" x 11/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, –, ×, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £10.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
FREEPOST St Ives,
Huntingdon, Cambs. PE17 4BR

Please send me
☐ Sinclair Scientific kit at £14.95
☐ Sinclair Scientific built at £21.55
☐ Sinclair Cambridge kit at £9.95
☐ Sinclair Cambridge built at £13.99

All prices include 8% VAT.

*I enclose a cheque for £................., made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/ Access account. Account number

*Delete as required.

Signed

Name

Address

Please print. FREEPOST – no stamp needed.

sinclair

Sinclair Radionics Ltd,
FREEPOST St. Ives,
Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

PATENTS REVIEW...

BANISHING THE STEREO SEAT

Domestic stereo systems suffer from the disadvantage that a good stereo image is obtainable only at that part of the room where the axes of the two speakers intersect. Omni-directional speakers are less critical over listening position, but are unable to produce a truly firm stereo image anywhere in the world. In BP 1 368 070 Andrei Vladimirovich Borisenko, of Leningrad, has a proposal which could well enable a good solid stereo image to be obtained over a wide area of a listening room.

As the inventor points out, image localisation depends on the intensity of sound heard from each loudspeaker and the time at which it arrives at the listener's ears. As the listener varies his position in a room, so both the relative level heard at each ear and the relative arrival time sensed at each ear also varies. The proposal is to use acoustic focusing devices to ensure that the intensity and arrival time of sounds heard by a listener are effectively constant over a wide area of the listening room.

As in conventional systems, two loudspeaker cabinets are used, each with three types of transducer (woofer, tweeter and mid-range) are used. But two mid-range units are arranged in each cabinet as a horizontal pair and they beam their sound into the room via a laminar acoustic lens. This takes the form of a number of vertical parallel plates, see Fig. 1.

BP 1 368 070

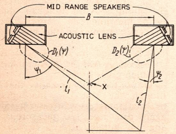

Fig. 1.

The plates are made from wood or plastic, are arranged vertically, and are of varying length. When the listener stands at position X the plates have virtually no influence or effect on the sound waves from the mid-range speakers. But as the listener moves away from the position X towards one side, the nearest speaker's plates both diminish the level of sound to that ear and delay it in dependence on how close and thus how far off the axis of the plates he is standing.

Obviously, the dimensions and angling of the plates will be critical and the patent suggests that, with the speakers 2·4 metres apart, each should have between six and eight plates, set at 40 degrees to a straight line drawn between the speakers.

PHASE CONVERSION

Single phase supplies may be converted into multi-phase supplies either by using a single phase motor driving a multi-phase alternator or by phase shifting the single phase supply in advance and retard by passive networks.

In BP 1 362 195 Raymond Russell of Newcastle-upon-Tyne claims that accurate phase shift results may be obtained from simpler passive networks, than those usually recommended. He suggests taking as a starting point the observation that a single phase supply can be regarded as an unbalanced three phase system.

In Fig. 1 three identical arms are arranged in delta configuration. Each arm has a resistor R and a capacitive impedance Z_c. The reactive component X_c of the impedance Z_c is such that current leads voltage by 60 degrees. A single phase supply is connected across any two of the junction points 1, 2, 3 and the resulting three phase supply is taken off across the three star-connected windings T. The windings are connected between neutral point a and junction points, b, c, d between the resistors R and impedance Z_c.

The inventor specifies that it is essential to arrange for R to be equal in magnitude to the 60 degree capacitive impedance Z_c. A null method of achieving this is described by way of example. The first step is to take three nominally equal capacitors and, by putting trimmers in parallel with the two smallest, match them accurately with parallel resistors they are connected at Z in Fig. 2.

The next step is to provide, from a balanced three phase supply, three voltage outputs, V_A, V_B and V_C. This is achieved by connecting the supply to 1, 2 and 3 via three adjustable load resistors arranged in star configuration, connecting voltmeters across points 1, 2; 2, 3 and 3, 1 and adjusting the resistors to balance the system. Voltmeters V can then be located between a and b, c and d, and null deflections obtained with trimmers, see Fig. 2.

It is claimed that a very high order of accuracy can be achieved.

BP 1 362 195

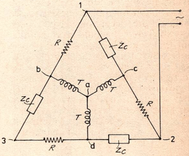

Fig. 1.

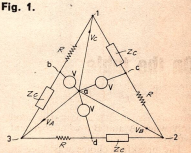

Fig. 2.

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 25p each

Readout—

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

"Wee Morag"

Sir—With regard to Mr Parfitt's etter January issue, I was astounded o discover that "wee Morag" from he local hamburger stall has at last made good, and is serving Boolean Breakfasts, incognito, in a Croydon hotel.

I met the lady under much the same unfortunate circumstances. I had occasion to ask her for "one hamburger with onion, and one without". Imagine my chagrin when I was served with one salt and one pepper, one tomato ketchup and one bill for 45p, but no hamburger and certainly no onion.

I questioned Morag, inquiring as to the whereabouts of the food, only to be told that, according to Boolean Algebra "hamburger and onion and hamburger and no onion, equals nothing", and was shown a truth table to verify that remarkable statement. The column of zeros at he end of the analysis somewhat overcame me, I must confess, and was therefore too perplexed to see hrough the deception. Had I been ess staggered, I would have pointed out that a hamburger is neither true nor false; it is instead merely present or absent; and that Boole is correct when his A's and B's are ogical statements, and wrong when hey are hamburgers and onions (or for that matter, eggs and bacon).

Alistair C. Thompson,
Lanarkshire.

On the table

Sir—The fallacy lies in the use of $A + A.B = A$ to describe Mr Parfitt's breakfast, see *Readout*, January issue. This equation is good only when A and B are independent events.

The breakfast choice was "egg or egg and bacon". The "egg and bacon" is really "bacon if and only if egg and bacon together", which is not A.B (in Mr Parfitt's notation) but $B \equiv A.B$. Thus we have to consider two breakfasts (mutually exclusive)

Egg (A) or
Egg and bacon ($B \equiv A.B$)
in an enclosure OR relationship.

Mr M. J. Hughes dealt with this in "Logic Tutor", Part 5 (P.E. Sept. 1973) and gives the equation

$$Q = A\overline{B} + B\overline{A}$$

with truth table

A	B	Q
0	0	0
1	0	1
0	1	1
1	1	0

No one can say that some P.E. readers are guilty of not doing their homework.

C. F. Tozer,
Dorset.

Misconception

Sir—There is a very simple answer to Mr Parfitt's problem (*Readout*, January 1975).

By applying his own brand of mathematical analysis, he should have seen that he had only to walk out of the hotel or walk out and pay his bill. He would then argue that both courses of action are equivalent to the first, and he would never notice that he had paid his bill in full.

To be more serious, the apparent paradox comes from a misconception of the nature of Boolean variables. In the expression: $A + (AB) = A$, "A" and "B" are statements which may be "true" or "false". The expression should be read "If A, or both A and B are true, then A is true."

When written in this manner the validity of the expression is patently obvious.

The paradox of the "Boolean bed and breakfast" arises because Mr Parfitt has thought of Boolean variables as objects instead of as statements.

I hope this letter may serve to clarify the thoughts of any non-mathematically-minded P.E. readers, especially those who run hotels, and have found unexpected losses on their December balance sheets.

J. Dickson,
Rochester, Kent.

Bacon and eggs

Sir,—One of the wonderful attractions of mathematics is how easily confusion can arise. Confusion is wonderful because it is the opposite to "Blue Peter": it can be resolved only by going into it more deeply, providing great pleasure and satisfaction.

In mathematics many different algebras use the same symbols for different meanings, + and . vary according to whether they are applied to numbers, vectors, matrices, sets, truth statements, switching circuits or whatever. Mathematicians deliberately introduce this joyous confusion in order that it should be resolved *by comparing the different algebras.* If this comparison is not done, you may as well have different symbols for each different algebra (as in O-level SET algebra which use ∪ and ∩ instead, reducing the depth to superficial levels).

If we were in the algebra of numbers, then given

$$A.B + A = A$$

we could deduce $A.B = 0$ by subtracting A from both sides or by adding $-A$ to both sides. But in Boolean algebra, + does not mean number or quantity addition, and subtraction does not exist.

If comparison is not acceptable, the alternative is to put more depth into the Boolean algebra: + meaning "either one or other or both" and "=" also not being straightforward. In the eggs and bacon situation, the algebra should be interpreted as "Given Bacon and Eggs or Eggs, necessarily implies being given Eggs." The nearest to the number $-A$ in Boolean algebra is $\overline{A}$ meaning the opposite of A (no eggs or maybe the rest of the menu).

If $\overline{A}$ is used the $A.B + A = A$
gives $\overline{A}.A.B + \overline{A}.A = \overline{A}.A$
which gives $0 = 0$

Translated this means that although the study of mathematics, or breakfasts or waitresses or managers can give 1/0 pleasure, staying in hotels always leaves one penniless.

M. Everett,
Saltdean,
Sussex.

P. B. PRODUCTS LTD.

ELECTRONIC · SCIENTIFIC · INSTRUMENTS
57 HIGH STREET · SAFFRON WALDEN · ESSEX CB10 2DP · ENGLAND
Telephone: Saffron Walden 22876 Telex: 817201

FREE RESIST COATED CIRCUIT BOARD
For every order placed for any of the products listed below, each order will receive a piece of fibre glass circuit board, approx. size 6in × 6in, coated with negative resist.

DRILLING MACHINES AND DRILL KITS
Specially designed for engineers, lab workers, jewellers, engravers, sculptors, model makers and hobbyists. These powerful, low power, drilling machines are capable of drilling holes up to 3mm in diameter in any material. They will DRILL, SAW, GRIND, BURR, BRUSH AND POLISH.
Reliant Drill with 3 collets, 9,000 r.p.m. **£3·68** (50p).
Reliant Drill Kit, 3 collets, 20 tools £8·34 (97p).
Drill Stand, used horizontally or vertically for drilling, sawing, buffing, or as a miniature lathe for turning small components between centres **£8·34** (97p).
MAJOR DRILL KIT "for the man with everything". Contains 9,000 r.p.m. super drill, power unit, drill stand, 40 assorted tools, presentation box, normally £34·76 only **£27·81** (£3·22).

SOLDERLESS MODULAR BREADBOARDS
These DEC breadboards are used throughout the world for making prototype and production working circuits. The patented contact allows components to be inserted over and over again without soldering.

S DEC. Discrete components only. Normally £1·98 only **£1·32** (25p).
T DEC. Station for one integrated circuit normally £3·63 only **£2·43** (39p).

U DEC A. Discrete and I.C. components normally £3·99 only **£2·67** (40p).
Each Dec is boxed and has instructions, carriers, plugs, coloured leads are also available.

COPPER CLAD GLASS-FIBRE CIRCUIT BOARD
$\frac{1}{32}$in Single sided normally 85p per sq. ft. only **55p** per sq. ft. (29p).
$\frac{1}{32}$in Double sided normally 93p per sq. ft. only **60p** per sq. ft. (30p).

$\frac{1}{32}$in Single sided normally £1·52 per sq. ft. only **75p** per sq. ft. (31p).
$\frac{1}{32}$in Double sided normally £1·60 per sq. ft. only **80p** per sq. ft. (31p).

RESIST COATED CIRCUIT BOARD
Positive or negative resist, single or double sided copper clad fibre glass circuit board. State which required.

Size		$\frac{1}{32}$in	5/64in or $\frac{1}{8}$in or $\frac{3}{32}$in		1·00mm or 1·19mm or $\frac{1}{16}$in paper	
inch	SS	DS	SS	DS	SS	DS
3 × 4in	**6p**	**7p**	**10p**	**12p**	**8p**	**9p**
6 × 8in	**24p**	**25p**	**46p**	**48p**	**26p**	**27p**
8 × 10in	**40p**	**41p**	**78p**	**80p**	**42p**	**43p**
12 × 12in	**72p**	**73p**	**98p**	**£1·00**	**74p**	**75p**

Please add 8% VAT and 20p postage to all above orders.

Example positive or negative coated 4 × 3in **12p** each + VAT & post. 5 × 5in **25p** each + VAT & post. Please quote if positive or negative coated and size. Ferric chloride 5 litre etchant mix **£1·50** (35p). Temperature controlled, air agitated etching tank **£85·00** (£6·96).
Please add to the sum shown in brackets after the price to cover the cost of post and VAT.

SPARKRITE Mk II

Electronic Ignition... Better on all points

Because you keep your points!

The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly – with **all** the advantages and **none** of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

●Fitted in 15 minutes. ●Up to 20% better fuel consumption. ●Instant all weather starting. ●Cleaner plugs – they last 5 times longer without attention. ●Faster acceleration. ●Faster top speeds. ●Coil and battery last longer. ●Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.
WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!

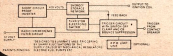
SHORT CIRCUIT PROOF INVERTER
400 VOLTS
ENERGY STORAGE NETWORK
OUTPUT TO IGNITION COIL
FEED BACK
THYRISTOR ELECTRONIC SWITCH
TRIGGER CIRCUIT* WITH SWITCH-OFF CLAMP AND CB BOUNCE SUPPRESSION
TRIGGER FROM CONTACT BREAKER
RADIO INTERFERENCE FILTER CIRCUIT
12 VOLT SUPPLY
*DESIGNED TO ELIMINATE MISS-TRIGGERING BY SHARP FLUCTUATIONS OF THE SUPPLY CAUSED BY MECHANICAL REGULATORS, ELECTRIC FUEL PUMPS ETC
R.P.M. LIMIT UNIT
(OPTIONAL)
PATENTS PENDING

Sparkrite MK II – full capacitive discharge electronic system – not just a transistorised inductive discharge booster.

PRICES

D.I.Y. Kit only £10·93 incl. VAT and P & P
Ready Built Unit £13·86 incl. VAT and P & P
(Both to fit all cars with coil/distributor ignition up to 8 cylinders).
We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition.
Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
(Dept PE 2) 82 Bath Street
Walsall WS1 3DE Phone 33652

Please supply:
Sparkrite Mk. 2 D.I.Y. Kit(s) at £10·93 each incl. VAT and P & P (Will make pos. or neg. earth). ☐
Sparkrite Ready Built Neg. Earth Unit(s) at £13·86 each incl. VAT and P & P ☐
Sparkrite Ready Built Positive Earth Unit(s) at £13·86 each incl. VAT and P & P ☐

NAME ________________
ADDRESS ________________

I enclose cheque/P.O. for £________
Send SAE for brochure.

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A *must* for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11·49
8 channel component set (excl. thyristors)	£20·32
Power supply component set	£4·78
PCB for 4 frequency channels	£2·50
PCB for power supply and 8 lamp drivers	£1·25

P.E. CCTV CAMERA
Details in List

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work, or for home-movie shows.

Component set, incl. PCB	£2·95

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:	
Set of resistors, capacitors and presets	£5·96
Stereo printed circuit board	£1·28
Pre-Amplifier:	
Sets of resistors, capacitors, potentiometers and switches—	
Standard Tolerance Set	£10·57
Superior Tolerance Set	£16·04
Stereo PCB (as Published)	£2·20
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4·58
Printed circuit board	72p

HI-FI TAPE LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter)	£22·05
Mono component set (excl. panel meter)	£13·31
Power supply component set	£3·72
Stereo main PCB	£2·50
Stereo sub-assembly PCB	86p

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB)	£2·30
Regulated power supply (including PCB)	£3·71

PROJECT Q4 (P.W. Oct. 73/Jan. 74)

Multi-system Quadraphonic Decoder.

Decoder component set	£13·74
Power supply components	£3·22
Printed circuit board	£2·60

SEMICONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB	£6·56

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB)	£2·20

PHASING CONTROL UNIT (P.E. Oct. 74)

(for use with above Phasing Unit)

Component set (including PCB)	£3·50

P.E. SOUND SYNTHESISER

The well-acclaimed and highly versatile Synthesiser published in P.E. Feb. 1973 to Feb. 1974.

Component sets and printed circuit boards. List shows full details including discounts.

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

Component set	£3·41
Printed circuit board	£1·10

RHYTHM GENERATOR (P.E. Mar./Apr. 74)

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures. See list for discount.

Tempo, Timing and Logic Circuit	
Component set (excl. switches)	£17·25
Double-sided PCB for above	£2·30
Mixer, Pre-amp and Effects Circuits	
Component set	£12·70
Printed circuit board	£2·67
Monitor Amplifier	
Component set and PCB	£3·10
Power Supply	
Component set and PCB	£5·65

ULTRASONIC TRANSMITTER-RECEIVER

A highly sensitive and long range "invisible beam" detection circuit with numerous applications.

Component set with PCBs, but excluding transducers	£4·40

P.E. RONDO

PCB details in List

POWER SLAVES

PCB details in List.

P.E. ELECTRONIC PIANO

Details in List.

HOME INTERCOM

Details in List.

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency doubler.

Component set	£5·83
Printed circuit board	£1·44

REVERBERATION UNIT (P.W. Nov./Dec. 72)

A high-quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit)	£6·44
Printed circuit board	£1·40

P.E. MINISONIC
Details in list
(inc. discounts)

8W AMPLIFIER (P.W. Nov. 72)

A moderately powered amplifier of more than average performance. (While stocks last.)

Main Amplifier	
Mono component set	£4·18
Stereo component set	£8·36
Mono printed circuit board	72p
Pre-Amplifier	
Mono component set	£2·50
Stereo component set	£6·46
Stereo printed circuit board	£1·66
Power Supply	
Component set	£3·90

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module	
Component set and PCB	£3·48
Basic Output Circuits	
Combined component set with PCBs, for alpha-phone, cardiophone, frequency meter and visual feed-back lamp driver circuits	£4·96
Audio Amplifier Module	
Type PC7	£5·50

PHOTOPRINT PROCESS CONTROL (P.E. Jan./Feb. 72)

For colour and B. & W. an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter)	£8·85
Printed circuit board	£1·60

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)

Dual-purpose dark-room unit with good accuracy.

Component set with PCB, but excluding meter	£4·00

WIND AND RAIN UNIT (P.E. Oct. 73)

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB	£2·40

PCB LAYOUT AND CIRCUIT DIAGRAMS SUPPLIED WITH ALL PCBs DESIGNED BY PHONOSONICS

LIST
Send S.A.E. for free list giving fuller details of kits, PCBs, and other components.

P. & P.
Add 18p to all orders

VAT
Add 8% (or current rate if different) to total order cost including P. & P.

OVERSEAS
P. & P. will be charged at cost. VAT does not currently apply. List gives fuller details including kit weights. Charge for list: Europe 10p, other countries 20p.

COLOUR CODE IDENTIFICATION SUPPLIED WITH MOST KITS AND AS PART OF LIST

Semiconductors

AC128	20p
AC176	20p
BC107	13p
BC108	13p
BC109	13p
BC147	12p
BC148	12p
BC149	12p
BC157	13p
BC158	13p
BC159	13p
BC182L	12p
BC184	12p
BC204	14p
BC209C	14p
BC212L	15p
BC213	15p
BC478	29p
BCY71	22p
BF178	40p
BFY50	22p
BFY51	22p
BFY52	24p
BSY95A	22p
MJE2955	110p
MJE3055	75p
NKT0033	112p
OC28	60p
OC71	14p
OC72	14p
OC84	25p
ORP12	60p
ZTX107	12p
ZTX503	15p
ZTX531	23p
2N706	13p
2N914	22p
2N1304	22p
2N2219	27p
2N2905	27p
2N2907	22p
2N3054	66p
2N3702	12p
2N3703	12p
2N3704	12p
2N3819	35p
2N3823E	39p
2N4060	12p
2N4871	36p
2N5245	51p
2N5777	45p

Diodes

1N914	4p
1N4001	6p
1N4002	7p
1N4004	8p
1N4005	8p
1N4007	10p
OA91	7p
OA200	8p
OA202	8p
1GP7	12p
1SJ50	11p
ZIJ	70p

Integrated Circuits

709 8-pin DIL	40p
709 TO5	40p
723 TO5	95p
741 8-pin DIL	40p
747 14-pin DIL	115p
748 TO5	63p
748 8-pin DIL	63p
748 14-pin DIL	63p
7400	20p
7402	20p
7410	20p
7420	20p
7447	175p
7473	44p
7489	425p
µ7815 TO220	250p
CA3046	69p
MFC6040	95p
PA263	169p
SG3402N	169p

Zeners

3·3V 400mW	12p
3·9V 400mW	15p
4·7V 1W	25p
5·1V 400mW	15p
5·6V 400mW	15p
5·6V 1·3W	20p
6·2V 400mW	15p
9·1V 400mW	15p
11V 1W	25p
12V 400mW	15p
12V 1·3W	20p
18V 400mW	15p
18V 1W	20p
20V 400mW	15p
20V 1·3W	23p
27V 400mW	15p

Thyristors

1A 400V	75p

Electrolytic Capacitors (µF/V)

0·47/63V	8p
1·0/63V	6p
1·5/63V	6p
2·2/63V	6p
4·7/63	6p
6·8/40	6p
10/25	6p
10/63	6p
15/40	6p
22/10	6p
22/25	6p
33/6·3	6p
33/16	6p
33/40	6p
33/50	6p
47/10	6p
47/25	6p
47/40	6p
47/63	7p
100/4	6p
100/10	6p
100/25	6p
100/40	7p
100/63	13p
150/16	6p
150/63	13p
220/10	6p
220/16	7p
220/25	11p
220/40	14p
220/63	21p
330/10	6p
470/6·3	6p
470/10	12p
470/25	16p
470/40	20p
500/64	46p
680/6·3	10p
680/25	20p
680/40	25p
1000/10	14p
1000/16	25p
1000/25	30p
1000/40	54p
2200/25	45p
2200/40	63p
2800/100	360p
3300/63	133p
3300/100	360p
4700/16	60p
4700/25	75p
4700/40	93p

Polyester (µF)

0·01	3p
0·015	3p
0·022	3p
0·033	3½p
0·047	3½p
0·068	3½p
0·1	4p
0·15	5p
0·22	5½p
0·33	7p
0·47	9p
0·68	11p
1·0	14p
2·2	24p

Tantalum (µF/V)

0·1/35	12p
0·22/35	12p
0·47/35	12p
1·0/35	12p
1·5/35	16p
2·2/35	12p
4·7/35	12p
10/16	12p
10/25	16p
15/6·3	16p
22/16	16p
47/6·3	16p
47/16V	25p
100/3	16p

PRICES ARE CORRECT AT TIME OF PRESS. E. & O.E. DELIVERIES SUBJECT TO AVAILABILITY.

PHONOSONICS, DEPT. PE33, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY

DON'T FORGET VAT!

TRANSISTORS

AC107	0·16	BC159	0·13	C111E	0·55	T6217	0·30
AC126	0·13	BC171	0·16	CV5441	0·27	V405A	0·25
AC127	0·13	BC172	0·16	CV7464	0·10	V10-50	0·40
AC128	0·12	BC173	0·16	CV7594	0·25	Y25	0·10
AC138	0·20	BC184	0·18	CV7648	0·30	Z116	0·75
AC141	0·20	BC208	0·12	CV8762	0·40	ZTX107	0·12
AC142	0·20	BC209	0·13	MDS33	0·30	ZTX302	0·17
AC153	0·22	BC212L	0·14	ME4102	0·12	ZTX502	0·17
AC176	0·15	BC301	0·30	NKT162	0·25	2G106	0·21
AC176	MP	BC336	0·15	NKT164	0·25	2G306	0·44
AC128	0·25	BC337	0·15	NKT212	0·20	2G345A	0·18
AC178	0·25	BCZ11	0·28	NKT221	0·17	2G402	0·25
ACY17	0·28	BD131	0·40	NKT224	0·15	2N526	0·46
ACY19	0·22	BD132	0·40	NKT270	0·15	2N697	0·15
ACY20	0·22	BD131	MP	NKT278	0·15	2N715	0·35
ACY21	0·22	BD132	0·75	OC22	0·50	2N726	0·25
AD161	0·38	BD139	0·60	OC28	0·50	2N753	0·55
AD162	0·38	BD140	0·60	OC35	0·46	2N1304	0·19
AD161	MP	BF167	0·24	OC36	0·55	2N1305	0·19
AD162	0·75	BF194	0·12	OC45	0·14	2N1309	0·25
AF115	0·26	BF196	0·15	OC70	0·11	2N1754	0·20
AF116	0·26	BF197	0·16	OC71	0·11	2N2484	0·30
AF178	0·50	BF274	0·39	OC72	0·15	2N2926	0·14
ASY52	0·22	BFX29	0·30	OC81	0·17	2N3055	0·50
BC107	0·09	BFX85	0·33	OC201	0·30	2N3702	0·12
BC108	0·09	BFY50	0·20	OC445K	0·25	2N3703	0·12
BC109	0·09	BFY51	0·20	SGS26920	0·15	2N3704	0·14
BC142	0·30	BFY52	0·20	SGS26942	0·14	2N3710	0·10
BC143	0·30	BFY81	0·65	SGS26949	0·15	2N3711	0·10
BC147	0·10	BSY38	0·20	SGS27022	0·18	2N3713	0·20
BC148	0·10	BSY39	0·20	SU203	0·65	2N4047	0·25
BC149	0·10	BSY40	0·31	TK100	0·75	2S322	0·46
BC157	0·11	BSY41	0·31	TIS90M	0·33	2S712	0·46
BC158	0·11	C111	0·50	TIS91M	0·33	2S745	0·46

DIODES

				OA202	0·08	IN4003	0·05
AA119	0·06	BY100	0·16	IN34A	0·08	IN4004	0·06
2 AALL9	0·18	BY127	0·16	IN202	0·10	IN4005	0·07
AAZ15	0·11	BY164	0·55	IN252	0·10	IN4006	0·08
BA90	0·10	BYX38 300	0·46	IN984B	0·10	IN4007	0·09
BA111	0·20	BYZ13	0·28	IN1124	0·10	IN4151	0·06
BA112	0·20	BZY95	0·15	IN3064	0·12	IN4148	0·04
BAY31	0·15	OA81	0·08	IN4001	0·05	IN4244	0·07
BAY74	0·16	OA200	0·07	IN4002	0·05	IS3036A	0·15

ZENER DIODES

400mW 2-33V	all **0·07** each	BZY91 C12 STUD TYPE	3·00
1W/1·5 2-33V	all **0·16** each	BZY91 C33R STUD TYPE	3·00
		BZY91 C43 STUD TYPE	3·00

TESTED S.C.Rs

50 PIV 3A TO-66 CASE	0·25
100 PIV 3A TO-66 CASE	0·25
200 PIV 3A TO-66 CASE	0·30
400 PIV 3A TO-66 CASE	0·40
600 PIV 3A TO-66 CASE	0·50
800 PIV 3A TO-66 CASE	0·60

ZENER DIODES

CV7204 11V STUD TYPE 0·60

THYRISTOR BT 109

CON/BRI 0·75

OPTOELECTRONICS

ORP 12 0·48 OCP 71 0·48

LOGIC I.C.s

TYPE			
MC930	0·15	MC946	0·14
MC932	0·15	MC948	0·25
MC933	0·15	MC962	0·15
MC944	0·16	MC9093	0·40
MC945	0·30	MC9097	0·40

74 SERIES I.C.s

SN741	0·45	SN7400	0·18
SN7400	0·18	SN7405	0·18
SN7401	0·18	SN7406	0·39
SN7402	0·18	SN7490n	0·74

JETs SUPER BARGAIN PACKS

No	Qty	Contents	Price
J1	1	Pre-amp component kit plus data	0·55
J2	3	Transistors AF115 new and marked	0·55
J3	10	Transistors Y25 new and marked	0·55
J4	4	Transistors 2N726 new and marked	0·55
J5	8	Zener diodes top hat type 75 volt	0·55
J6	75	Diodes mixed new and marked	0·55
J7	50	Metres con/wire mixed colours	0·55
J8	25	Metres con/wire, 4 metres solder	0·55
J9	100	Resistors hi/stab ½W mixed values	0·55
J10	100	Resistors hi/stab ¼W mixed values	0·55
J11	45	sq inches approx. copper clad veroboard	0·55
J12	250	Resistors mixed values	0·55
J13	100	Polystyrene capacitors 10pF to 300pF	0·55
J14	100	Capacitors miniature mixed values	0·55
J15	5	Terminal blocks 12 way brand new	0·55
J16	4	Toggle switches assorted	0·55
J17	10	Switches 5 push to make off/on	0·55
J18	12	Standard crocodile clips	0·55
J19	12	Screwdrivers 5 inches in length	0·55
J20	1	Pack nuts and bolts, solder tags, etc., etc.	0·55
J21	2	Solenoids 24 volt pull ex-new equipment	0·55
J22	20	Volume controls mixed lin and log	0·55
J23	75	Syn/rubber grommets mixed sizes	0·55
J24	1	Component board full BC107-8-9, etc	0·55
J25	20	Screw on rubber feet ½ inch dia. approx	0·55
J26	1	Pack marker sleeve mixed rod	0·55
J27	5	Lengths of ferrite rod	0·55
J28	20	Tag strips assorted lengths	0·55
J29	4	Micro switches brand new	0·55
J30	2	Sets of 5 bank push switches new	0·55
J31	20	Pre-set pots lin and log mixed	0·55
J32	20	Capacitors can type mixed	0·55
J33	50	Ceramic plate capacitors mixed	0·55

BONANZA

½ MILLION CAPACITORS

WE CANNOT NAME THE WELL KNOWN MAKER DUE TO THE LOW PRICE. THEY ARE OF THE VERY LATEST DESIGN AND TYPE. 100 MIXED VALUES AND TYPES VALUED AT OVER £5. YOURS FOR ONLY £1·50. NO MORE TO PAY (WHAT A BARGAIN).
Electrolytics 6·8µF at 40V, 100µF at 63V, 680µF at 16V, etc.
Polyester 1500pF at 400V, 0·0015pF at 400V, 0·0068pF at 400V.
Miniature Metallized Film 0·22nF at 250V, 47nF at 250V, etc.
Ceramic Plate 82pF at 100V, 22000pF at 40V, 4700pF at 40V, etc.
etc. . . .etc. . . .etc. . . .etc. . . .etc. . . .etc. . . .etc. . . .etc. . . .etc.

SPECIAL OFFER I.C.s

BULK PURCHASE BRAND NEW 14 PIN DECADE COUNTER SN 7490 2 FOR ONLY **£1·00**

SPECIAL OFFER

BULK PURCHASE BRAND NEW BC 337 TRANSISTORS NPN TO 84 case 20 FOR **£1·00**

SPECIAL OFFER RESISTORS

CARBON FILM CR 25 TYPE 1m2 2m2 10% 10 120 470kΩ 5% etc . . . etc . . . . etc . . .
200 MIXED FOR ONLY **£1·00**

SPECIAL OFFER DIODES

IN4148 BRAND NEW
40 FOR ONLY **£1·00**

SPECIAL OFFER 1.C 1TT

TCA270b ONLY **£3·00**

MAINS TRANSFORMER 240V INPUT 12V 8A 25V 1·1A 30V 1·5A C CORE **£2·50** P. & P. **25p.**
PAPST TAPE MOTOR 220V 50Hz **£2·50** P. & P. **25p.**
AMPLIFIER 9V 500MW **0·95p.** P. & P. **5p.**
P. A. R. BISTABLE RELAY LATCHING 24V DC4 C/O CONTACTS **0·65p.**
RELAY KEYSWITCH 24V 1 POLE 2 WAY NEW AND BOXED **0·55p.**
RELAY T.M.C. MINIATURE 3,300 ohms 2 POLE 4 WAY **0·55p.**
TELEPHONE DIALS BRAND NEW £1·00 EACH P. & P. FREE.
ELECTROLYTICS 0·1µF 250V **9p.** 25µF 50V **8p.** 40µF 16V **4p.** 16-16µF 500V CAN TYPE **35p.** 32-32µF 450V CAN TYPE **35p.**
CAPACITORS 0·047µF 400V **8p.** 125µF 10V **7p.** 100µF 10V **8p.**

FREE OFFER ONE J PACK OF YOUR OWN CHOICE WITH ALL ORDERS VALUED AT £5·00 AND OVER.

PLEASE ADD 10% TO ALL TOTAL ORDERS FOR POST AND PACKAGE.

MAIL ORDER DEPT. ONLY

(Callers by appointment)

J.E.T. ELECTRONICS

90a Mawney Road, Romford, Essex RM7 7DA
Telephone: Romford 61486

SPECIAL OFFERS ARE AVAILABLE ONLY WHILE STOCK LASTS

PC ETCHING KIT

Contains 1lb ferric chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner, dish for etching and instructions. **£3·30.**

RESISTORS and CAPACITORS

500 asstd. resistors **£1·40**, 2500 **£5**, 15 different trimmers, air-spaced and compression up to 1250pF **£1**.

VEROBOARD

100 sq ins assorted sizes and pitches, about 8 bits **£1·10.**

8 PIN DIL 741's

FULL SPEC. OF COURSE

10+26p 25+23p

100+21p 250+20p

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb **80p**, 3lb **£1·65**, 10lb **£4·45**, 100lb **£35.**

P.O. AMPLIFIER UNIT

Contained in steel case 5¾ × 5 × 3¾" are 2 × GET116 transistors on heat sinks, 3 pot cores, 2 30V zeners, 4 audio transformers, 1% R's & C's. With circuit **£1.**

SEMICONDUCTORS

All new full spec devices; AC127 AC128 AC176 AC177 AC187 AC188 all **20p**; BC107, 8, 9 **10p**; 723C **75p**; 741C **35p**; IN914 **4p**; IN4001 **6p**; IN4004 **8p**; IN4007 **12p**; 800V 1½A **10p**; 400mW zeners **10p**; 400V 6A triac **£1.**

7lb BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, plus PC boards with transistors and diodes. Also loads of odds and ends. Contents always changing as new goods come in. Amazing value at **£2·30.**

COMPUTER PANELS

Always thousands in stock, all sizes, shapes and prices from **5p.** 3lb assorted **£1·40**, 7lb **£2·65**, 56lb **£15.** 12 high quality panels with power transistors, IC's, trimpots etc **£2·50.** Pack containing about 500 components including at least 50 transistors **95p.** Pack of boards with 50 14 pin DIL DTL IC's **£1.**

TRANSFORMERS

All mains primary, 6-0-6V @ 100mA **85p**; 9-0-9V @ 100mA **90p**; 12-0-12V @ 100mA **95p**; 16-0-16V with 9V tap @ 1½A **£2**; 24-0-24V @ 500mA **£1·85**; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V @ 1A **£1·45**; The following are ex-equip: 22½-0-22½V @ 1A **£2**; 12V @ 15A **£3·50**; 18V @ 5A **£3**; 55V @ 5A **£4.**

MULTIMETERS

LT101; 0-10-50-250-1000V AC & DC, 0-1-100mA DC, 0-150KΩ Only **£3·60.** IT12; 20,000 Ω/V, 0-5-25-50-250-500-2500V DC, 0-10-50-100-500-1000V AC, 0-50µA-2·5-250mA, 0-60k-6MΩ, −20 to +22dB. Protected meter movement **£6·20.**
Computer equipment: Ampex TM2 8 track ½" tape decks **£27** (Callers only). Also paper tape punches, readers, etc.

POWER SUPPLIES

G101. Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1·7–10·5V output with 2 extra capacitors (provided) **£1·20.** G102. These are stabilized power supplies giving 7½V @ 225mA. Voltage can be altered by changing zener. Not working, but only minor faults **£1.**

All prices include VAT and postage. SAE list, enquiries. Computers, equipment and components always wanted for cash.

GREENWELD ELECTRONICS (PE3)

Head office, mail-order dept, Wholesale/Retail shop: **51 SHIRLEY PARK RD., SOUTHAMPTON SO1 4FX. Tel. (0703) 772501.** Also callers welcome at 21 Deptford Broadway SE8, Tel. 01-692 2009 and 38 Lower Addiscombe Rd., Croydon. Tel. 01-688 2950.

Dimmit

range of light dimmers and lighting control systems

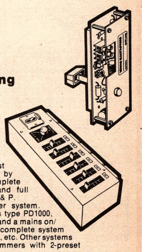

Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppressed, 60mm slider range, size 12 × 5 × 4cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studio, etc. Complete with scale plate, fixing screws and full instructions. **£7·25** inc. VAT and P. & P.

Illustrated is the DD61 dimmer system. Contains: six 1000W slider dimmers type PD1000, six outlet sockets, a master control and a mains on/off switch. Size 59 × 22 × 12cm. A complete system in one unit for stage or disco lighting, etc. Other systems available with 1000W or 2000W dimmers with 2-preset and master controls.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for industrial heating applications, etc. Rotary and slider control versions. Ratings: 1000W; 2000W; 3000W; 110V and 240V.

Model SL800 sound to light converter. Modulates the light in time with sound. Built in microphone. Just place unit near any sound source—radio, hi-fi, TV, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800W. Complete with full instructions.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Personal callers welcome, visit our showroom for a demonstration of any of the modules or systems.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN. Tel. 01-267 0201

SUPERSOUND 13 HI-FI MONO AMPLIFIER

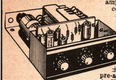

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power out-put transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz ±3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high × 6" wide × 7½" deep. AC 200/250V. PRICE **£12·50.** P. & P. 50p.

DE LUXE STEREO AMPLIFIER

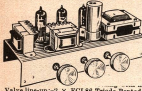

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate ..egligible hum. Valve line-up:–2 × ECL86 Triode Pentodes. 1 × EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11"w × 4"d. Overall height including valves 5". Ready built and tested to a high standard. **£10·75.** P. & P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7½v. and 9v. and 12v. at 1 amp on lead.
Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" × 3½" × 2½". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. Price **£5·20.** P. & P. 35p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price **£1·30** yd. length. P. & P. 15p per yd. (min. 1·yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully solated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.
P. & P. 40p. BARGAIN PRICE **£4·20**

FEW ONLY. High grade mains transformer with grain orientated lamination. Primary 200/240. Secondary 18·5 volts at 0·6 amps and 4·6 volts at 0·3 amps. Size 2in. long × 2¼in. wide × 2in. deep overall. **£1·35** plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0–210–240v. Secondary combinations 0–5–10–15–20–25–30–35–40–60v. half wave at 1 amp. or 10–0–10, 20–0–20, 30–0–30v. at 2 amps fulls wave. Size 3in. long × 3½in. wide × 3in. deep. Price **£2·60.** P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies.
Pro. 200/240v. Sec. 9–0–9 at 500 mA. **£1·25.** P. & P. 25p.
Pri. 200/240v. Sec. 12–0–12 at 1 amp. **£1·40.** P. & P. 26p.
Pri. 200/240v. Sec. 10–0–10 at 2 amp. **£2·00.** P. & P. 35p.

3 ,VOLT RELAY. 100 m/a single pole normally closed. 2 for **60p.** P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T line 200/300v. Frequency response 15Hz—25KHz. Gain 26dB. Solid encapsulation size 1¾" × 1½" × ¾". Brand new complete with instructions. Price **£1·20.** P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY **40p.** Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristic, diode and transistor equivalents. Many thousands of up to date European types listed.
Diode Equivalents 90p. Transistor Equivalents £1. Transistor Characteristics £1·30. POST FREE
All three together **£3.**

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias **£1.** Post Free.

8 pole 3 way 2 bank low loss Yaxley type switches 1¼" sections. Standard spindle. 2 switches **64p** + 10p P. & P.

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER

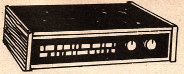

Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation, I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12¼in wide × 8in deep by 2¾in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form).

Price **£23·00.** Post and Packing 50p.

STEREO-DECODER SIZE 2" × 3" × ½"

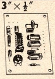

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. **£5** plus 10p P. & P.
Stereo beacon light if required 40p extra.

LATEST HI SENSITIVITY UNI-DIRECTIONAL SLIM-LINE CONDENSER MICROPHONE as used by many professionals. Very low acoustic feedback. Available Hi impedance or low impedance. State which required. **£13·50.** P. & P. 25p.

LATEST ACOS GP91/1SC mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1·46.** P. & P. 15p.
CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY **£1·75. P. & P. 15p.**
SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78.
ONLY £2·27. P. & P. 10p. Also available fited with twin Diamond T/O stylus for Stereo LP. **£2·76.** P. & P. 15p.
LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. **£1·60.** P. & P. 15p.
LATEST RONETTE T/C MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only **£1·47.** P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide × 3in deep × 6in high. Ready built and tested. PRICE **£5·50.** P. & P. 50p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE **£6·70.** P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM MkII

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16½" high × 10½" wide × 9" deep. Fitted with E.M.I. Ceramic Magnet 13" × 8" bass unit, H.F. tweeter unit and crossover (approx). AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £9·50 each. Carr. 90p.

Cabinet Available Separately £5·00. Carr. 90p.
Also available in 8 ohms with EMI 13" × 8" bass speaker with parasitic tweeter **£8·00.** Carr. 75p.

LOUDSPEAKER BARGAINS

5in. 3 ohm **£1·25,** P. & P. 15p. 7 × 4in. 3 ohm **£1·40,** P. & P. 20p. 10 × 6in. 3 or 15 ohm **£2·10,** P. & P. 30p. E.M.I. 8 × 5in. 3 ohm with high flux magnet **£1·70,** P. & P. 20p. E.M.I. 13½ × 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm **£3·50,** P. & P. 30p. E.M.I. 13 × 8in 3, 8 or 15 ohm with inbuilt tweeter and crossover network **£4·65,** P. & P. 30p.
E.M.I. tweeter. Approx. 3½". Available 3 or 8 or 15 ohms, **£1·25** + 20p, P. & P.
BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£7·50.** Guitar models: 25w. **£7·50.** 35w. **£8·50.** P. & P. 45p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11¾" × 14$\frac{11}{16}$" × 1$\frac{7}{16}$" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for details. Only **£6·60** each. P. & P. 34p.
NOW ALSO AVAILABLE 8in. 10W rms 20W peak 40Hz—20,000Hz. Overall depth 1in. Ideal for Hi-Fi or for use in cars. **£4·32.** P. & P. 25p.

SPECIAL BARGAIN OFFER!
Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge.
Brand new. ONLY £8·00 + p. & p. 60p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

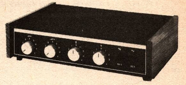

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3dB 12–30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±3dB 12–15,000 Hz. Bass, boost approx. to ±12dB. Treble cut approx. to —16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1·0 amp.
Overall Size 12"w. × 8"d. × 2¾"h.
Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT	**£12·96**	P. & P. 30p
(Magnetic input components 33p extra)		
POWER PACK KIT	**£4·32**	P. & P. 40p
CABINET	**£4·32**	P. & P. 40p

(Post Free if all units purchased at same time)
Full after sales service

Also available ready built and tested **£28·08.** Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

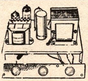

3-VALVE AUDIO AMPLIFIER HA34 MK II.
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, 7½"w. × 4"d. × 4¾"h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£6·50.** P. & P. 45p.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£5·50.** P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

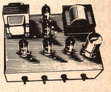

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.
Fully shrouded section wound output transformer to match 3–15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p × SAE (Free with parts). All parts sold separately. ONLY **£10·25.** P. & P. 60p. Also available ready built and tested **£14·00.** P. & P. 70p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo ¼in jack plug. Frequency response 30–15,000Hz. Matching impedance 8–16 ohms. Easily converted for Mono. PRICE **£3·50.** P. & P. 25p.

PRICES INCLUDE VAT

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday
Closed Wednesday.
Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

THE NEW NELSON-JONES FM TUNER

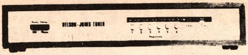

PUSH-BUTTON VARICAP DIODE TUNING (6 Position)

('WW' JUNE '73)

Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:—

MOSFET front end for excellent cross modulation performance and low noise.
3 GANG tuning for high selectivity.
VARICAP tuning diodes in back to back configuration for low distortion.
CERAMIC filters for defined IF response.
INTEGRATED circuit IF amplifiers for reliability and excellent limiting/AM rejection.

PHASE LOCKED Stereo decoder with Stereo mute, see below
LED fine tuning indicators.
PUSH BUTTON tuning (with AFC disable) over the FM band (88-104)
IC STABILISED and S/C protected power supply.
CABINET double veneered against warp.

The Nelson-Jones Tuner has **all** of these features and many more, and more importantly the design is fully **proven** not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting 0·75uV. Image rejection —70dB.I.F. Rejection —85 dB.

Basic tuner module prices start as low as **£12·31**, with **complete** kits starting at **£26·95** (mono) + P.P. 65p, and of course all components are available separately.

Our low cost **alignment service** is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

PORTUS AND HAYWOOD PHASE LOCKED DECODER (W.W. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0·05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED.
Price **£7·02** when bought with a **complete** N-J tuner kit or **£8·29** if bought separately (P.P. 21p).

PLEASE NOTE. Existing tuners are readily convertible and kits/parts are available for this purpose.

TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at **£30·78** plus P.P. 65p including Teak Sleeve.

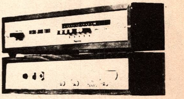

NEW LOW COST STEREO TUNER

Available as basic or complete kits

Basic stereo tuner **£15** post free.
Basic mono tuner **£12** post free.
6 position push button units with integral pots **£2·92**.

No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with **Interstation Mute,** restricted range **AFC,** single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

TYP. SPECIFICATION
2μV for 30dB S/N
Image rejection 40dB
IF rejection 65dB

VAT at 8% is included in all prices

PRICE Complete stereo kit **£28·42**
Complete mono kit **£24·19**
P. & P. 65p

Access

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106

TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES.CALLERS WELCOME.

FAST SERVICE. SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P.OVERSEAS 65P. CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays

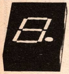

MINITRON 3015F
0-9DP £1.15 ea

LED 0.3" digit
0-9DP £1.49 ea

JUMBO LED 0.6"
0-9DP £2.25 ea

LIQUID CRYSTAL
6 digit £18

LEDS 14P.

MINI PIN SOURCE OR RED DIFFUSE LEDS.209 STYLE.NO CLIP. 14P ea

TIL209 RED LED & CLIP 17P ea

BIG ¼" RED LED & CLIP 18P ea

ORANGE & GREEN LEDS:
MINI 25P ea.BIG & CLIP 33P ea

INFRA RED LED £1.2N5777 33P.
PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

MOS INTEGRATED CIRCUITS.
AY51224 4 DIGIT CLOCK supplied with 14pin socket & data £4.25

MM5311/14 6 DIGIT CLOCK with 28 pin socket & data £7.50

3½DIGIT DVM AY53500 £7.50
4DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12·50

STEREO CASSETTE MECHANISM.

As used in imported types costing £100.Only requires a case & electronics.Heads supplied.Send for data 15p.

IC's & Semiconductors

702 OPA	69p
703 RF/IF	28p
709 TO99	21p
709 DIL 14	29p
710 DIL 14	.36p
720 Radio	£1.39
723 Regulator	67p
741 TO99	29p
741 DIL8	31p
741 DIL14	31p
747 Dual 741	89p
748 DIL 8	36p
1505 IC A/D Converter	£7
7805 1A5V	£1.59
7808 1A8V	£1.69
7812 1A12V	£1.69
7815 1A15V	£1.69
76009 ½W AF	75p
76013 6W AF	£1.39
8038 Sig Gen	£3
CA3046	69p
LM301 OPA	49p
LM307 OPA	49p
LM308 HiBoPa	95p
LM309K Reg.	£2.29
LM371 RF/IF	£2
LM372N AF/IF	£2
LM373	£3
LM377 2x2W	£2.69
LM380 2W AF	99p
LM381) 2xpre.	£2
LM382) amp	£2
LM3900 4xOPA	69p
MC1303	£1.20
MC1306	49p
MC1310 & LED	£2.69
MC1312 SQamp	£2.50
MC1330	69p
MC1339	£1
MC1350	55p
MC1351	71p
MC1352	71p
MC1357	£1
MC1358	£1
MC1375	£1.25

MFC4000 ¼W AF	35p
MFC4060	54p
MFC6030	52p
MFC6040	90p
MFC8010	£1.10
MFC8040	£1
NE531 35V/us	£2
NE536 FET OPA	£2
NE540 Driver	£1
NE546 AM Rx	£1.50
NE550 2v ref	79p
NE555 TIMER	67p
NE556 Dual"	£1.30
NE560 PLL	£3.15
NE561 PLL	£3.15
NE562 PLL	£3.19
NE565 PLL	£2.69
NE566 Gen	£2.49
NE567 code	£2.69
SN72709 709	29p
SN72741 741	31p
SN72748 748	36p
SN76131	£1.20
SN76660 FMIF	£1
SN76611 IF	£1.25
TAD 100 & IF	£2
ZN400E	£3
ZN402T	£1.75
ZN403 Servo	£2.50
ZN414 AM Rx	£1.09

74 TTL

7400 etc gates	16p
7413 schmitt	31p
7447 driver	£1.09
7470/72	32p
7473/74/76	39p
7475	48p
7490 Counter	63p
7492 Counter	69p
74121 mono	45p
74141 driver	83p

Full range in Cat..

SPECIAL OFFERS

741 29p MFC4000 35p
555 67p ZN414 £1.09

BC107,BC108,BC109 9p ea
2N3055 39p Three for £1
115W/TO3 or 90W plastic
2N3819E 16p 2N3053 17p
BFY50/51/52/53 all 18p
1A50Vrect 4p ea IN914 4p

Price each:-

AC127/128	16p	TIP2955	90p
AC187/188	19p	TIP3055	55p
AD161/162	35p	TIS43 UJT'	25p
BC107/8/9	9p	IN4001	4p
BC132/4/7	18p	IN4004	6p
BC147/8/9	10p	IN4148/914	4p
BC157/8/9	12p	2N697	13p
BC167/8/9	12p	2N706/8	10p
BC177/8/9	18p	2N2646	49p
BC182/3/4*	11p	2N2904/5	20p
BC212/3/4*	12p	2N2926royg	9p
*A or L		2N3053	17p
BCY70/1/2	15p	2N3055	39p
BD131/2	39p	2N3614	49p
BFY50/1/2	18p	2N3702/3	9p
BFY53	17p	2N3704/5	10p
BSX20	12p	2N3706/7	9p
MJE2955	95p	2N3708/9	8p
MJE3055	62p	2N3710/11	9p
MPU131put	49p	2N3563/64	16p
OA91	8p	2N3566/67	16p
TIP29A	48p	2N3638	16p
TIP30A	57p	2N3641/2	16p
TIP31A	61p	2N3819E	16p
TIP32A	73p	2N3832E	17p
TIP41A	78p	2N3904/6	14p
TIP42A	89p	2N4249	16p

BZY88 400mW
ZENERS 9p

BRIDGE RECT
1A 50V 20p

GAS SENSOR £2
GAS " KIT £5

TAG 1/400 55P
C107D1 SCR
4A/400V 55p

SC146D TRIAC
10A 400V 75p

vero

NEW LOW PRICES!

VERO PINSx36 25p.
COPPER CLAD VEROBOARD 0.1"
2½x5" 27p.2½x3¾" 24p.3¾x3¾"27p.
3¾x5" 29p.3¾x17" £1.50
DIL IC's BOARDS 6x4½" £1.50
24 way edge connector 60p
36way 90p. PLAIN 3¾"x17 £1
FACE CUTTER 43p. FEC ETCHANT

DALO pen 69p

PRINTED CIRCUIT BOARD KIT £1.69
COPPER BOARD 6x4" 40p.
DESOLDER BRAID reel 59p

HEATSINKS

5f/TO5 & 18f/TO18 5p ea.
TV4 12p.TV3/TO3 16p.4YI/TO3 29p.

CAPACITORS

22pf to 0.1uf 4p ea.ELECTROLYTIC
25V 2/10/50/100uf 6p.1000uf 20p
PRESETS VERT:5p.RESISTORS5% 1½p

POTS AB or EGIN

ROTARY:12p.SWITCH 13p.DUAL 38p.

SLIDERS:SINGLE 26p.DOUBLE 48p.

SWITCHES:SPST 18p.DPDT 25p.
MINI ¼":SPST 39p.PUSH 39p.

BENCH POWER SUPPLY 3-12V £5.

DIN PLUGS all 13p ea.Sockets 9p
TRANSFORMERS 1A 6/12V £1.34
BHA 0002 MODULE 15WATT AMP £5
EA1000 4W AF MODULE £2.49
8W/12V FLUORESCENT LIGHT £3.

DIL sockets

PROFESSIONAL
GOLD PLATED
& GREY NYLON.
8,14 or 16 PIN
ONLY 15p each.

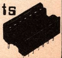

CUSTOM CABINETS

331 High Street, Rochester, Kent. Tel: Medway (0634) 404199

SPEAKER CABINETS IN KIT FORM REPRESENT HUGE SAVINGS

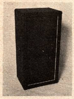

2′ x 12″ Cabinet

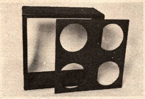

4′ x 12″ Cabinet

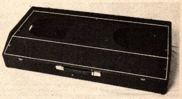

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows:-

1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and1 baffleboard with speaker cutout
2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

PRICE & TYPE LIST

Type	*Size*	*Price manufactured*	*Kit price*
2 x 12″ (illustrated above)	36″ x 18″ x 13″ x ¾	£21·45	£13·75
4 x 12″ (illustrated above)	31″ x 31″ x 13″ x ¾	£26·95	£19·25
4 x 12″ P.A. Column	48″ x 27″ x 13″ x ¾	£33·00	£23·65
1 x 18″	31″ x 31″ x 13″ x ¾	£26·95	£19·25
1 x 15″ with two top horn cutouts	36″ x 20″ x 13″ x ¾	£23·10	£14·85

SPECIAL ANNOUNCEMENT

Owing to difficulties in obtaining raw materials and labour we apologise for any inconvenience caused to our customers.

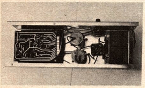

- * 100w RMS slave amp for Disco
- * 100w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £42·00 complete

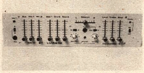

- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00

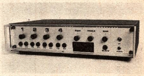

ERC 100w power amplifier
- * Electrolytic capacitors and second generation ICs
- * Fully protected against short or open circuit
- * Less than 0·1% distortion at all powers
- * Rise time 4muS-stability–Unconditional Price £66.50

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY

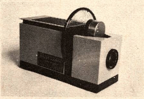

Disco imp projector 150 watt tungsten
unbeatable price
Includes liquid wheel and postage
Normally sold between £24—£27·50

OUR PRICE £19·75

TRADE AND EXPORT ENQUIRIES WELCOME

12in LONG PERSISTENCE CRT. Full spec. Price **£6·50** to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY **£6·25,** P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10·7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6·3V a.c. and use within minutes of receiving. All this for ONLY **£6·75,** P. & P. 25p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. **£8·85** each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic **15p** each, P. & P. **5p.**

Large quantity of good quality components—**NO PASSING TRADE**—so we offer 3lb of **ELECTRONIC GOODIES** for **£1·50.** Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 1 off 4 pole, 2 way, etc.), **50p,** P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft—no tiny pieces. **50p,** P. & P. 20p.

CAPACITOR PACK—50 brand new components, only **50p,** P. & P. 20p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. **25p** the lot, P. & P. 10p.

PHOTOCELL equ. OCP71, **13p each. MULLARD** OCP70, **10p each.**

DELIVERED TO YOUR DOOR, 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY **£4.**

MODERN TELEPHONES. Type 706. Two-tone grey, **£3·75** each. Two-tone green **£3·75** each. Black **£3·75** each, P. & P. 35p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding, **£1·75** each, P. & P. 35p.

HANDSETS. Complete with 2 inserts and lead, **75p** each, P. & P. 37p.

DIALS. ONLY **75p** each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. **£1·75,** post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1–9 **13p** each, P. & P. 15p; 10–99 **10p** each, P. & P. 25p; 100–999 **7p** each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** each. Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, **30p,** P. & P. 10p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—or build your own. Send for our tube list with a S.A.E.

Use Access here

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

BARCLAYCARD welcome here

CF

GIRO NO. 331 7056. Access accepted.
C.W.O. only. P. & P. 10p on orders below £5
Discount: £10–10%, £20–15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ¼W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), **£3·58** net
10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), **£3·77** net
25E12 ¼W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), **£8·19** net
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), **£8·28** net
5E12 ½W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), **£2·80** net

Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, **3½p.** 0·068μF, 0·1μF, **4½p.** 0·15μF, **4½p.** 0·22μF, **5½p.** 0·33μF, **8p.** 0·47μF, **9p.** 0·68μF, **12p.** 1μF, **15p.** 1·5μF, **23p.** 2·2μF, **26p.**

MULLARD POLYESTER CAPACITORS C296 SERIES

400V, 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½p.** 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3½p.** 0·047μF, 0·068μF, 0·1μF, **4½p.** 0·15μF, **6½p.** 0·22μF, **8½p.** 0·33μF, **12p.** 0·47μF, **14p.**
160V: 0·01μF, 0·15μF, 0·022μF, **3p.** 0·047μF, 0·068μF, **3½p.** 0·1μF, **4½p.** 0·15μF, **5p.** 0·22μF, **5½p.** 0·33μF, **6½p.** 0·47μF, **8½p.** 0·68μF, **12p.** 1μF, **14p.**

MINIATURE CERAMIC PLATE CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (μF) 0·01, 0·015, 0·022, 0·033, 0·047, **2½p.** each. 0·1, 30V, **5p.**

POLYSTYRENE CAPACITORS 160V 5%

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, **4½p.**

RESISTORS

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

W.	Type	Range	1–99	100–499	500–999	1000 +	Size mm
⅛	CF	12–1M	1	0·75	0·60	0·55	2·4x7·5
¼	CF	22–2M2	1	0·75	0·60	0·55	3·9x10·5
½	CF	22–1M	1	0·75	0·60	0·55	5·5x16
¼	MF	10–2M7	2	1·54	1·32	1·1	3x7
½	MF	10–2M2	2	1·43	1·21	0·99	4·2x10·8
1	MF	10–10M	3	1·98	1·81	1·65	6·6x13
2	MF	10–10M	4·5	3·52	3·08	2·75	8x17·5

For value mixing prices, please refer to our catalogue. (Price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS

MINIATURE 0·25W Vertical or horizontal **6p** each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0·05W Vertical, 100 Ω to 220K Ω **5p** each.

Buy it with Access

B. H. COMPONENT FACTORS LTD.

(P.E.), LEIGHTON ELECTRONICS CENTRE, 59 NORTH STREET, LEIGHTON BUZZARD, BEDS. Tel.: Leighton Buzzard 2316 (Std. Code 05253).
CATALOGUE No. 3, 20p.

Miniature Mullard Electrolytics

1·0μF	63V	6½p	68μF	16V	6½p
1·5μF	63V	6½p	68μF	63V	12p
2·2μF	63V	6½p	100μF	10V	6½p
3·3μF	63V	6½p	100μF	25V	6½p
4·0μF	40V	6½p	100μF	63V	14p
4·7μF	63V	6½p	150μF	16V	6½p
6·8μF	63V	6½p	150μF	63V	15p
8·0μF	40V	6½p	220μF	6·4V	6½p
10μF	16V	6½p	220μF	10V	6½p
10μF	25V	6½p	220μF	16V	8p
10μF	63V	6½p	220μF	63V	21p
15μF	16V	6½p	330μF	16V	12p
15μF	63V	6½p	330μF	63V	25p
16μF	40V	6½p	470μF	6·4	9p
22μF	25V	6½p	470μF	40V	20p
22μF	63V	6½p	680μF	16V	15p
32μF	10V	6½p	680μF	40V	25p
33μF	16V	6½p	1000μF	16V	20p
33μF	40V	6½p	1000μF	25V	25p
32μF	63V	6½p	1500μF	6·4V	15p
47μF	10V	6½p	1500μF	16V	25p
47μF	25V	6½p	2200μF	10V	25p
47μF	63V	8p	3300μF	6 4V	26p

VEROBOARD	0·1	0·15
2½ x 5″	36p	36p
2½ x 3¾″	33p	25p
3¾ x 5″	42p	46p
3¾ x 3¾″	36p	36p
2½ x 1″	9p	9p
2½ x 5″ (Plain)	—	19p
2½ x 3¾″ (Plain)	—	16p
5 x 3¾″ (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 25	22p	22p

TRANSISTORS

AC127	16½p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	TIS43	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, **16½p** Dual Gang **46p.** Log single with switch **26p.** Slider Pots. 10K, 100K, 500K, semi log 30mm, **34p.** 45mm, **47p.** 60mm, **55p.**

DIODES

IN4001	6½p
IN402	7½p
IN4003	9p
IN4400	9p
IN4005	12p
IN4006	14p
IN914	1p
IN916	7p
BA100	10p
OA5	42p
OA47	9p
OA81	11p
OA200	8p

PLUGS

Din 2 Pin	12p
3 Pin	13p
5 Pin 180°	16p
Std. Jack	20p
2·5mm jack	13p
Phono	6p

SOCKETS

Din 2 Pin	10p
3 Pin	10p
5 Pin 180°	12p
Std. Jack	15p
2·5mm Jack	13p
Phono	6p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
(uF/V): 1/25, 2/25, 4/25, 4·7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, **6½p.** 50/50, **8p.** 100/50, 200/25, **11p.** 250/50, **18p.** 500/10, **11p.** 500/25, **15p.** 500/50, **18p.** 1000/10, **15p.** 1000/25, **22p.** 1000/50, **40p.** 2000/10, **20p.** 1000/100, **88p.** 2000/25, **30p.** 2000/100, **93p.** 2500/25, **38p.** 2500/50, **61p.** 5000/25, **65p.** 5000/50, **£1·08.**

HI-VOLT: 4/350, **14p.** 8/350, **19p.** 100/100, **20p.** 16/350, **22p.** 16/450, **23p.** 32/350, **33p.** 50/250, **20p.** 100/250, **30p.**

METALLISED PAPER CAPACITORS
250V: 0·05μF, 0·1μF, **6p.** 0·25, **6p.** 0·5μF, **7½p.** 1μF, **9p.** 500V: 0·025, 0·05, **6p.** 0·1, **6p.** 0·25, **7½p.** 0·5, **9p.** 1000V: 0·01, **11p.** 0·022, **13p.** 0·047, 0·1, **15p.** 0·22, **23p.** 0·47, **34p.**

PLEASE NOTE OUR NEW ADDRESS. OUR NEW ELECTRONICS CENTRE IS NOW OPEN

NEW KIT
5E12 ⅛W Metal Film.
5 each value 10 Ω-1M,
total of 305 **£3·25**

MULTIMETER U4323

22 Ranges plus AF/IF Oscillator 20,000 Ω/Volt.
Vdc—0·5—1000V in 7 ranges
Vac—2·5—1000V in 6 ranges
Idc—0·05—500mA in 5 ranges
Resistance—5 Ω—1M Ω in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465KHz (A, M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE **£8·30** net P. & P. 25p.

U4323

MULTIMETER U4324

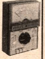

34 Ranges. High sensitivity.
20,000 Ω/Volt. Overload protected.
Vdc—0·6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0·06—3A in 6 ranges.
Iac—0·3—3A in 5 ranges.
Resistance—25 Ω—5M Ω in 5 ranges.
Accuracy—dc and R—2½% of F.S.D.
ac and db—4% of F,S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE **£9·95** net P. & P. 25p.

U4324

MULTIMETER U4341

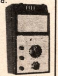

27 Ranges plus Transistor Tester.
16,700 Ω/Volt. Overload protected.
Vdc—0·3—900V in 8 ranges.
Vac—1·5—750V in 6 ranges.
Idc—0·06—600mA in 5 ranges.
Iac—0·3—300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges. Accuracy—dc—2½%.
ac—4% of F.S.D.
hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE **£11·30** net P. & P. 30p.

U 4341

MULTIMETER U4313

33 ranges. Knife edge with mirror scale.
20,000 Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1·5—600V in 9 ranges.
Vac—1·5—600V in 9 ranges.
Idc—60—120 microamps in 2
Idc—0·6—1500mA in 6 ranges.
Iac—0·6—1500mA in 6 ranges.
Resistance—1K Ω—1M Ω in 4 ranges.
db scale——10 to + 12db.
Accuracy—dc—1½%, ac—2½%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE **£13·40** net P. & P. 30p.

U4313

NEW CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V. 5 of each value: 0·01 0·022, 0·047, 0·1, 0·22μF. 2 of 0·47, 1μF. **£1·30** net.
C296 Kit—Tubular polyester, 400V. 5 of each value: 0·01, 0·022, 0·047, 0·1, 0·22μF. 2 of 0·47μF. **£1·30** net.
Ceramic Kit—square plaquette 50V. 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0·1μF. **£1·30** net.
250V Paper kit—Tubular metal case. 3 of each value: 0·05, 0·1, 0·25, 0·5, 1μF. **90p** net.
500V Paper Kit—Tubular metal case. 3 of each value: 0·025, 0·05, 0·1, 0·25, 0·5μF. **90p** net.
1000V Paper Kit—Tubular metal case. 3 each value: 0·01, 0·025, 0·05, 0·1μF. **£1·10** net.

S-DeC

S-DeC	£2·14
T-DeC	£3·92
μDeC "A"	£4·30
μDeC "B"	£7·53
2 DeC	£4·72

ANTEX

CCN240	£2·43
CN240	£2·01
X25	£2·01

MULTIMETER U435

32 ranges. High sensitivity. 20,000 Ω/Volt.
Vdc—75mV—1000V in 8 ranges
Vdc—2·5—1000V in 7 ranges.
Idc—0·001—2·5A in 6 ranges.
Iac—0·005—2·5A in 5 ranges.
Resistance—3-300K in 3 ranges
Capacitance scales 0-0·5μF.
Accuracy—dc and R—2½% of F.S.D.
ac and C—4% of F.S.D.
Size—205 x 110 x 84mm.
Complete with steel carrying case, test leads and battery.
PRICE **£9·45** net P. & P. 25p.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT
VARIABLE 0–260V All Types
SHROUDED TYPE

200 watt (1 amp) £9·00
0·5 KVA (2½ amp) (MAX) £10·00
1 KVA (5 amp) (MAX) £14·70
2 KVA (10 amp) (MAX) £28·10
3 KVA (15 amp) (MAX) £31·25
4 KVA (20 amp) (MAX) £72·50
37·5 amp (MAX) £102·50
CARRIAGE AND PACKING EXTRA
OPEN TYPE 1 amp (panel mount) **£9·00**

L.T. TRANSFORMERS

0, 10, 17, 18 Volt at 10 amp. **£7·90.** Post 60p.
0, 6, 12 Volt at 20 amp. **£9.** Post 60p.
0, 12, 24 Volt at 10 amp. **£9·20.** Post 60p.
0, 6, 12, 17, 18, 20 Volt at 20 amp. **£10·40.** Post 60p.
Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up step down

0-115/200/220/240 Volts.
At 75 watt **£2·64.** Post 36p.
150 watt **£3·18.** Post 36p.
300 watt **£6·20.** Post 50p.
500 watt **£9·20.** Post 65p.
1000 watt **£12·00.** Post 80p.

300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13·5 cm. Width 11 cm. Height 13·5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm × 130 mm × 60 mm. Price **£2.** Post 20p. (Total incl. VAT and Post **£2·38**).

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp. contacts. Fitted diecast case. Tested and in perfect condition **£4·75.** Post 25p.

COIN MECHANISM (Ex London Transport)
Unit containing, selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only **£2·50.** Post 60p.

230/250 VOLT A.C. SOLENOID

Approximately 1½lb pull. Size of feet 1⅛″×1$\frac{3}{16}$″
Price **£1·00.** Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two × approx. 1lb pull ½ inch travel. 6 × approx. 4oz. pull ½ inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price **£2·50.** Post 60p. **ABSOLUTE BARGAIN.**

'STC' 6″ RED ALARM BELL

24/48 volt DC. **Brand New.**
Price **£4.** Post 50p.

'GENTS' 6″ ALARM BELL

200/250V AC/DC. **Brand New.** Price **£5.** Post 60p.

INSULATION TESTERS *NEW!*

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. **1,000V,** 1,000 megohms, **£34.** Post 60p. **500V,** 500 megohms, **£28.** Post 60p.

600 WATT DIMMER SWITCH
Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. **£2·75.** Post 25p.

All Mail Orders—Callers—Ample Parking
Dept. PE3, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions **£6·30.** Post 30p.

INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
Approx. ¼ output of Hy-Lyght. Price **£14·00.** Post 50p.

HY-LYGHT STROBE MK III
For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. **£14.** Post 50p.

THE 'SUPER' HY-LYGHT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light. ONLY **£22.** Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector **£5·75.** Post 25p.
Super Hy-Lyght case including reflector **£8.** Post 60p.

7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price **55p.** Post 15p.

COLOUR WHEEL PROJECTOR

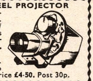

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V AC. Features extremely efficient optical system. **£20·50.** Post 50p.

6 INCH COLOUR WHEEL
As used for Disco lighting effects, etc. Price **£4·50.** Post 30p.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast is essential Price of matched ballast and bulb **£16.** Post £1. Spare bulb **£7.** Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
4ft 40 watt. Price **£5·50.** Post 30p. (4ft to Personal callers only). **2ft 20 watt, £4·25.** Post 25p. (For use in standard bi-pin. MINI. **12in 8 watt, £1·60.** Post 15p. **9in 6 watt, £1·30.** Post 15p. Complete ballast unit and holders for 9in and 12in tube, **£1·70.** Post 25p. (9in and 12in measures approx.)

U.D.I. SINGLE CHANNEL 750 WATT MANUAL/AUTO DIMMER

750W Solid State Fader, with three functions. Manual fade; Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three-position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6″ × 3″ glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE **£15.** Post 30p.

POWER RHEOSTATS ! ! !

Superior Quality Precision Made
NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/150/500/1k/ohm. **£1·70.** Post 10p.
50 WATT 1/5/10/25/50/100/250/500 1·5k/ohm **£2·10.** Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/3·5k/5k ohm **£3·30.** Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1½in. dia. brass bush. Ideal for above **22p** each.

TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS
10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146E 10 amp, 500 PIV, **£1·00.** Post 5p. (Inclusive of data and application sheet.) Suitable Diac **18p.**

All prices are subject to
8% VAT. (8p in the £)
To all orders add 8% VAT to total value of goods including carriage packaging.

SERVICE TRADING CO.

LED READOUTS

7 series, L/H d.p. one-third high character. 14 pin D.I.L. Available in RED or GREEN. Price **£1·65.** Post 10p.
4 for £6. Post paid.

RELAYS SIEMENS, PLESSEY. Etc, MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
Col. (2)	52	4–8	2 c/o	**70p**
Working	58	5–9	6 c/o	**80p**
d.c. volts	185	8–12	6M	**60p***
Col. 3	230	9–18	2 c/o	**70p**
Contracts	308	9–14	4 c/o	**75p***
	430	15–24	4 c/o	**80p**
Col. (4)	700	16–24	4M 2B	**60p***
Price	700	16–24	4 c/o	**80p***
HD =	2,500	31–43	2 c/o HD	**60p***
Heavy duty	2,500	36–45	6M	**60p**
	9,000	40–70	2 c/o	**60p***
	15k	85–110	6M	**60p***

*Incl. Base All prices incl. P. & P.

OPEN TYPE RELAYS
6 VOLT D.C. 1 make contacts **35p.** Post 10p.
9 VOLT D.C. RELAY
3 c/o 5 amp contacts. 70 ohm coil. **75p.** Post 10p.
12 VOLT D.C. RELAY
3 c/o 5 amp contacts. 120 ohm coil. **75p.** Post 10p.
24 VOLT D.C. 3 c/o **75p.** Post 10p.
2 HD c/o 700 ohm coil. **75p.** Post 10p.
4 c/o 300 ohm coil. **85p.** Post 10p.
100 VOLT A.C. 2 c/o sealed type, octal base **75p.** Post 10p.

ENCLOSED TYPE RELAYS
24 VOLT A.C. 3 h.d. c/o. **65p.** Post 10p. Base 15p.
24 VOLT A.C. Mfg. by ITT.2 h.d. c/o contacts. **55p.** Post 10p.
240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Price **75p.** Post 10p. Octal plug in base 15p extra.
230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price **£1.** Post 10p.
220/240 VOLT A.C. RELAY
3 c/o 5 amp contacts. Sealed. **£1·25.** Post 10p. 11-pin base 15p extra.
CLARE-ELLIOTT TYPE RP7641 G8
Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. **70p** post paid.
110V. 2 c/o. 20 amp contacts. **£1·25.** Post 10p.
Many others from stock—phone for details.

VERY SPECIAL OFFER

MINIATURE ROLLER MICRO SWITCH. 5 amp. c/o contacts. NEW. Price 10 for **£1·50.** Post 10p. (Min. order 10). As above less roller/leaver) 20 for **£2.** Post 10p. (Min. order 20).
Ditto press to make, 20 for **£1·50.** Post 10p.
Ditto press to break, 20 for **£1.50.** Post 10p.

230/240 VOLT A.C. MINIATURE MOTOR. 20 R.P.M. Price **£1.** Post 10p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in. **Reversible** 1/70th h.p. cycle 0·38 amp. **(Type 2) 28 r.p.m.** torque 20 lb. in **Reversible** 1/80th h.p. 50 cycle 0·28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for **230/240v A.C. input.**
Price, either type **£6·25.** Post 50p or less transformer **£3·75.** Post 40p.

'FRACMO' 240 VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

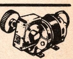

33 r.p.m. 30 lb. ins. Reversible. Fitted with mounting feet. Brand New. **£14.** Post 60p. (Total price incl. VAT **£15·77**).

230V FAN ASSEMBLY

Continuously rated, removable aluminium blades. Price **£1.** Post 20p.

PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Heavy Duty continuously rated, smooth running, 230/240V a.c. motor. Size: 16 × 14cm (case only). OAL 15cm. Aperture 6 × 6cm. **£6·50.** Post 50p.

230/240 VOLT A.C. EXTRACTOR FAN KIT

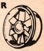

Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price **£1·75.** Post 25p. (Total incl. VAT and Post **£2·16**).

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR

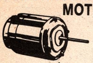

Type SS15. Thes fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give d.c. to winding for a maximum holding torque of 300oz/in with 35V at 0·35A through winding. For a.c. (synchronous) operation at 120r., 50Hz. Speed 60r.p.m. at 60Hz, 72r.p.m. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0·1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4in, body length $4\frac{3}{4}$in, spindle length $2\frac{1}{4}$in × $\frac{5}{16}$in dia. Weight $6\frac{1}{2}$lb. BRAND NEW in maker's packing. Offered at less than half maker's price.

OUR PRICE ONLY £15. P. & P. £1

MAGNETIC DEVICES SOLENOID

240V a.c. 50 P.C. rated 18lb pull, $1\frac{1}{2}$in travel push or pull. Shackle both ends, length overall 4in plus 3in travel arm × $2\frac{3}{4}$in × $3\frac{1}{4}$in high.
Brand new **£5·25** plus 60p P. & P. or ex-equipment **£3** plus 60p P. & P.

CARTER ELECTRIC

Similar to above with alloy gear case. 60r.p.m. This item is ex-equipment but perfect. **£1·95.** P. & P. 30p.

SHADED POLE MAINS MOTOR

A quality shaded pole motor. Open frame. 3in high × $2\frac{1}{2}$in × 2in. Spindle 1in × $\frac{3}{16}$in, 1,420r.p.m. **£1·95.** P. & P. 20p.

"LABGEAR ELIMINAC"

P.S.U. 200–250V, 40/60Hz. Alternative outputs fully variable (variac Incorporated). Output 1, 12V at 5A d.c. fully smoothed. Output 2, 12V at 8A d.c. with ripple content. Output 3, 20V at 10A a.c. $2\frac{1}{2}$in × $2\frac{1}{4}$in flush 0·20V d.c. m/c motor. In attractive grey hammer finish case. In maker's carton. **£27·50.** Carr. & Pkg. £1·50.

SPECIAL OFFER
LIGHT DEPENDENT RESISTORS

Matched pairs Pioneer Type 174 similar to OPR 12. Resistance 1kΩ to 4kΩ. Dia. $\frac{3}{8}$in with $\frac{1}{2}$in flanges.
£1·50 for two pair (minimum) 10 or more pairs 50p. per pair incl. P. & P.

MAINS SOLENOID

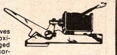

This little unit gives vertical lift of approximately 1in through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, $2\frac{1}{2}$in 240V a.c. Pull at coil is approximately 1lb. **£1.** FREE P. & P. Special quote for quantities.

SOLENOIDS by WESTOOL

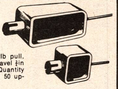

240 a.c. type, MM6 3lb pull, $2\frac{3}{4}$in × 1in × $1\frac{1}{4}$in. Travel 1in **90p** each. P. & P. 10p.
240 a.c. type MM4. 2lb pull, $1\frac{1}{2}$in × $1\frac{3}{4}$in × 1in. Travel $\frac{3}{4}$in **70p** each. P. & P. 10p. Quantity discounts: 10–50 10%, 50 upwards 25%.

OPEN FRAME shaded pole GEARED MOTORS

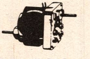

(Dural gear case) 240 a.c. 28r.p.m. NEW HIGH TORQUE, approx. overall size: $3\frac{1}{2}$in × $3\frac{1}{4}$in × $2\frac{3}{4}$in + spindle $\frac{1}{4}$in dia. as illustrated, **£2·70** plus 30p P. & P.
110r.p.m. with pressed steel gear case (similar to above but slightly smaller). **£2·70** plus 30p P. & P.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3A at 120V, $1\frac{1}{2}$A at 240V. Size: (approx.) $1\frac{7}{16}$in long × $\frac{1}{2}$in dia. Ideal for burglar alarms, security systems, etc., and wherever non-mechanical switching is required. 10 for **£2·10;** P. & P. 15p. 50 for **£8·80;** 100 for **£15·50.** FREE P. & P. over 10.

AMPEX 7·5V D.C. MOTOR

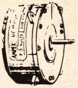

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500mA. Draws 60mA on run. 600r.p.m. ± speed adjustment. Internal AF/RF suppression, $\frac{1}{4}$in dia. × 1in spindle motor 3in dia. × $1\frac{3}{8}$in. Original cost **£16·50.** OUR PRICE **£4·25.** P. & P. 25p. Quantity available. Mu-metal enclosure available **75p** each. FREE P. & P.

FAN/BLOWER

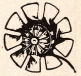

Precision built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60mA on run. Size: $5\frac{1}{4}$in dia. × $2\frac{1}{4}$in deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at **£3** plus 40p P. & P.

ALL PRICES INCLUDE VAT

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under **£5**. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317 EDGWARE ROAD
LONDON, W.2
Tel: 01-723 5667, 01-402 5580

★ ELECTRONIC PIANO KIT
★ SYNTHESISER KIT
★ ELECTRONIC ORGAN KITS

There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, **£145·29.** ★ Console organ with 5 octave keyboard, **£250·93.** ★ Console organ with 2 × 4 octave keyboards and 13 note pedal board, **£470·65.** ★ Console organ with 2 × 5 octave keyboards and 32 note pedal board, **£680.** ★ Console organ with 3 × 5 octave keyboards and 32 note pedal board, **£960.** ★ W/W Sound Synthesiser Kit, **£130.** ★ W/W Touch Sensitive Electronic Piano, **£100.**

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 50p for catalogue which includes 5 × 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

Elvins Electronic Musical Instruments

12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455);
8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949);
40a/42a Dalston Lane, Dalston Junction, London E8 (Tel 01-249 5624).

Business hours: Open 10 a.m. to 7 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.

---

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB35, P.O. BOX 156, JERSEY

NAME : ____________________
ADDRESS : ____________________
____________________ BLOCK CAPS please

Marshall's

Everything you need is in our New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Call in and see us 9–5.30 Mon–Fri
9–5.00 Sat
Trade and export enquiries welcome

Popular Semiconductors

2N456	0·80
2N456A	0·85
2N457A	1·20
2N490	3·16
2N491	3·58
2N492	3·99
2N493	4·20
2N696	0·22
2N697	0·16
2N698	0·40
2N699	0·45
2N706	0·14
2N706A	0·16
2N708	0·17
2N709	0·42
2N711	0·50
2N718	0·23
2N718A	0·28
2N720	0·50
2N721	0·55
2N914	0·22
2N916	0·28
2N918	0·32
2N929	0·30
2N1302	0·19
2N1303	0·19
2N1304	0·24
2N1305	0·24
2N1306	0·31
2N1307	0·22
2N1308	0·40
2N1309	0·36
2N1671	1·44
2N1671A	1·54
2N1671B	1·72
2N1671C	4·32
2N1711	0·45
2N1907	5·50
2N2102	0·50
2N2147	0·78
2N2148	0·94
2N2160	0·90
2N2192	0·40
2N2192A	0·40
2N2193	0·58
2N2193A	0·61
2N2194	0·73
2N2194A	0·30
2N2218A	0·22
2N2219	0·24
2N2219A	0·26
2N2220	0·25
2N2221	0·18
2N2221A	0·21
2N2222	0·20
2N222A	0·25
2N2368	0·25
2N2369	0·37
2N2369A	0·41
2N2646	0·55
2N2647	1·12
2N2904	0·22
2N2904A	0·24
2N2905	0·24
2N2905A	0·26
2N2906	0·19
2N2906A	0·21
2N2907	0·22
2N2907A	0·24
2N2924	0·14
2N2925	0·17
2N2926	
Green	0·12
Yellow	0·11
Orange	0·11
2N3053	0·25
2N3054	0·60
2N3055	0·75
2N3390	0·26
2N3391	0·23
2N3391A	0·29
2N3392	0·13
2N3393	0·13
2N3394	0·13
2N3402	0·18
2N3403	0·19
2N3440	0·59
2N3441	0·59
2N3442	1·69
2N3414	0·20
2N3415	0·21
2N3416	0·34
2N3417	0·24
2N3638	0·15
2N3638A	0·15
2N3639	0·27
2N3641	0·17
2N3702	0·12
2N3703	0·13
2N3704	0·14
2N3705	0·12
2N3706	0·12
2N3707	0·13
2N3708	0·10
2N3709	0·11
2N3710	0·12
2N3711	0·11
2N3712	0·96
2N3713	1·20
2N3714	1·33
2N3715	1·50
2N3716	1·80
2N3771	2·20
2N3772	1·80
2N3773	3·20
2N3789	2·06
2N3790	2·40
2N3791	2·35
2N3792	2·69
2N3794	0·24
2N3819	0·37
2N3820	0·64
2N3823	0·78
2N3900	0·28
2N3901	0·32
2N3903	0·24
2N3904	0·27
2N3905	0·24
2N3906	0·27
2N4036	0·63
2N4037	0·42
2N4058	0·16
2N4059	0·09
2N4060	0·11
2N4061	0·11
2N4062	0·11
2N4126	0·20
2N4289	0·34
2N4919	0·84
2N4920	0·99
2N4921	0·73
2N4922	0·84
2N4923	0·83
2N5172	0·12
2N5174	0·22
2N5175	0·26
2N5176	0·32
2N5190	0·92
2N5191	0·95
2N5192	1·24
2N5195	1·46
2N5245	0·43
2N5457	0·49
2N5458	0·46
2N5459	0·49
40361	0·48
40362	0·50
40363	0·88
40389	0·46
40394	0·56
40395	0·65
40406	0·44
40407	0·33
40498	0·50
40409	0·52
40410	0·52
40411	2·00
40414	3·55
40430	0·85
40583	0·23
40601	0·67
40602	0·46
40603	0·53
40604	0·56
40636	1·10
40669	1·00
40673	0·73
AC107	0·51
AC113	0·16
AC117	0·20
AC126	0·20
AC127	0·20
AC128	0·20
AC151V	0·25
AC152V	0·17
AC153	0·25
AC153K	0·33
AC154	0·20
AC176	0·23
AC176K	0·33
AC187K	0·23
AC188K	0·34
ACY18	0·24
ACY19	0·27
ACY20	0·22
ACY21	0·26
ACY28	0·20
ACY30	0·58
AD142	0·59
AD143	0·60
AD149	1·20
AD150	1·15
AD161	0·50
AD162	0·50
AD161	1·20
AD162	1·20
AF109R	0·40
AF115	0·24
AF116	0·25
AF117	0·20
AF118	0·55
AF124	0·30
AF125	0·30
AF126	0·28
AF127	0·28
AF139	0·39
AF170	0·25
AF172	0·25
AF178	0·55
AF179	0·65
AF180	0·58
AF186	0·46
AF200	0·35
AF239	0·51
AF240	0·72
AF279	0·54
AF280	0·54
AL102	1·00
AL103	0·70
BC107	0·16
BC108	0·15
BC109	0·19
BC113	0·15
BC115	0·17
BC116	0·17
BC116A	0·18
BC117	0·21
BC118	0·11
BC119	0·29
BC121	0·23
BC125	0·16
BC126	0·23
BC132	0·30
BC134	0·13
BC135	0·13
BC136	0·17
BC137	0·17
BC138	0·24
BC140	0·34
BC141	0·29
BC142	0·23
BC143	0·25
BC145	0·21
BC147	0·12
BC148	0·13
BC149	0·12
BC153	0·18
BC154	0·18
BC157	0·14
BC158	0·13
BC159	0·14
BC160	0·37
BC167B	0·13
BC168B	0·13
BC168C	0·11
BC169B	0·13
BC169C	0·13
BC170A	0·11
BC171	0·13
BC172	0·11
BC182	0·12
BY182L	0·12
BC183	0·12
BC183L	0·12
BC184	0·13
BC184L	0·13
BC186	0·25
BC187	0·27
BC207	0·12
BC208	0·11
BC212K	0·16
BC212L	0·16
BC214L	0·16
BC237	0·13
BC238	0·13
BC239	0·13
BC251	0·20
BC252	0·18
BC253	0·23
BC257	0·14
BC258	0·13
BC259	0·14
BC261	0·20
BC262	0·18
BC263	0·23
BC300	0·36
BC301	0·34
BC302	0·29
BC303	0·54
BC307	0·11
BC307A	0·10
BC308	0·12
BC308A	0·12
BC308B	0·09
BC309	0·10
BC309A	0·10
BC309B	0·10
BC237	0·21
BC238	0·19
BC337	0·19
BC338	0·19
BCY30	0·64
BCY31	0·64
BCY32	1·15
BCY33	0·45
BCY34	0·49
BCY38	0·55
BCY39	1·50
BCY40	0·87
BCY42	0·28
BCY58	0·21
BCY59	0·22
BCY70	0·17
BCY71	0·22
BCY72	0·13
BCY87	3·54
BCY88	2·42
BCY89	0·97
BD115	0·75
BD116	1·00
BD121	1·00
BD123	0·82
BD124	0·67
BD131	0·40
BD132	0·50
BD135	0·43
BD136	0·49
BD137	0·55
BD138	0·63
BD139	0·71
BD140	0·87
BDY20	1·05
BF115	0·25
BF116	0·23
BF117	0·43
BF119	0·58
BF121	0·25
BF123	0·27
BF125	0·25
BF152	0·20
BF153	0·21
BF154	0·20
BF158	0·23
BF159	0·27
BF160	0·23
BF161	0·42
BF163	0·32
BF166	0·32
BF167	0·21
BF173	0·24
BF177	0·29
BF178	0·35
BF179	0·43
BF180	0·35
BF181	0·34
BF182	0·40
BF183	0·40
BF184	0·30
BF185	0·30
BF194	0·12
BF195	0·12
BF196	0·13
BF197	0·15
BF198	0·18
BF199	0·18
BF200	0·40
BF225J	0·19
BF237	0·22
BF238	0·22
BF244	0·21
BF245	0·33
BF246	0·58
BF247	0·49
BF254	6·16
BF255	0·17
BF257	0·46
BF258	0·59
BF259	0·55
BFS21A	2·30
BFS28	0·92
BFS61	0·27
BFS98	0·25
BFX29	0·30
BFX30	0·27
BFX44	0·33
BFX63	2·48
BFX68	0·30
BFX84	0·24
BFX85	0·30
BFX87	0·28
BFX88	0·25
BFX89	0·45
BFY18	0·52
BFY19	0·62
BFY20	0·50
BFY29	0·40
BFY50	0·23
BFY51	0·23
BFY52	0·21
BFY53	0·18
BFY90	0·75
BRY39	0·48
BU104	2·00
BU105	2·25
C106A	0·46
C106B	0·55
C106D	0·65
C106E	0·43
CA3020A	1·80
CA3046	0·70
CA3048	2·11
CA3089E	1·96
CA3090Q	4·23
CD4000	0·51
CD4001	0·51
CD4002	0·51
CD4009	1·07
CD4010	1·07
CD4011	0·51
CD4015	2·66
CD4016	1·02
CD4017	2·66
CD4020	2·96
CD4023	0·51
CD4024	1·90
CD4027	1·56
CD4028	2·34
CD4029	3·79
CD4041	2·11
CD4044	2·11
CD4047	1·65
CD4049	0·90
CD4050	0·90
LM301A	0·48
LM304A	2·03
LM309K	1·88
LM702C	0·75
LM709	
TO99	0·48
8DIL	0·38
14DIL	0·40
LM723C	0·90
LM741	
TO99	0·40
8DIL	0·40
14DIL	0·38
LM747	1·00
LM748	
8DIL	0·60
14DIL	0·73
LM7805	2·00
MC1303P	1·26
MC1310	2·92
MC1458CP1	0·79
MJ480	0·90
MJ481	1·14
MJ490	0·98
MJ491	1·38
MJE340	0·45
MJE2955	1·12
MJE3055	0·68
MP8111	0·32
MP8112	0·40
MP8113	0·47
MPF102	0·39
MPSA05	0·25
MPSA06	0·26
MPSA55	0·26
MPSA56	0·27
NE555V	0·70
NE560	4·48
NE561	4·80
NE565A	4·48
OC23	1·35
OC28	0·76
OC35	0·60
OC42	0·50
OC45	0·32
OC71	0·20
OC72	0·25
OC81	0·25
OC83	0·24
ORP12	0·55
R53	1·80
RL54	0·15
SC35D	1·68
SC36D	1·46
SC40D	1·89
SC41D	1·32
SC45D	1·89
SC45D	1·96
SC50D	2·60
SC51D	2·39
SL414A	1·80
SL623	4·59
TAA263	1·00
TAA350	2·10
TAA621	2·03
TAA661B	1·32
TAD100	1·50
Filter	0·70
TBA271	0·64
TBA641B	2·25
TBA800	1·50
TBA810	1·50
TIL209	0·30
TIP29A	0·49
TIP30A	0·58
TIP31A	0·62
TIP32A	0·74
TIP33A	1·01
TIP34A	1·51
TIP35A	2·09
TIP36A	3·70
TIP41A	0·79
TIP42A	0·90
TIP2955	0·98
TIP3055	0·60
ZTX300	0·13
ZTX302	0·20
ZTX500	0·15
ZTX502	0·18
ZTX530	0·21

PW TELETENNIS KIT

As featured on BBC Nationwide and in the Daily Mail 2 Oct. '74. Ideal game for whole family. No need to modify your TV set, just plugs in to aerial socket.

Parts list as follows: A Resistor Pack £1 P. & P. 20p; B Potentiometer Pack £1·25 P. & P. 20p; C Capacitor Pack £3·10 P. & P. 20p; D Semiconductor Pack £14·50 P. & P. 20p; E IC Sockets £4 P. & P. 20p; F Transformer £1·15 P. & P. 25p; G PCB's £7·50 P. & P. 20p; H Switches £4·50 P. & P. 20p; 1 UHF Modular Kit £7·50 P. & P. 20p.

Special Prices—complete kit excluding case £42 P. & P. 50p. Sections A–F incl. £23·50 P. & P. 30p. Assembly instructions with complete kit or 75p on request.

P.C. Marker Pen Dalo 33PC
Price 87p

Zeners 400MW 2·7V–43V **11p.** 1W 3·3V–120V **17p.**

IC Sockets 8 DIL **16p.** 14 DIL **17p.** 16 DIL **20p.**

Liquid Crystals—£13

Ex-stock S.A.E. for details of CMOS battery operated clock kit using LCD's.

Scorpio Car Ignition Kit—£11·50 + VAT

IMF440V £1·10.
BSTB0246 £1·05. Transformer £2·75.
Minitron £1·55.
DL707 £2·25 *or* 4 for £8.

Resistors / Tant Beads

Resistors W	Tol	Price	Tant Beads Value	Price
⅛	5%	1p	0·1/35	14p
¼	5%	1½p	0·22/35	14p
½	5%	2p	0·47/35	14p
1	10%	2½p	2·2/35	14p
2	10%	6p	4·7/35	18p
2½	5%	7p	10/16V	18p
5	5%	9p	47/6·3V	20p
10	5%	10p	100/3V	20p

Veroboard

	Copper 0·1	Copper 0·15	Plain 0·1	Plain 0·15
2·5 × 3¾in	36p	26p	—	17p
2·5 × 5in	40p	40p	—	19p
3¾ × 3¾in	40p	42p	—	—
3¾ × 5in	45p	47p	—	32p
3¾ × 17in	£1·61	£1·26	£1·00	92p
Pins × 36	30p		30p	
× 200	£1·16		£1·16	

Trade and Retail supplied.

Integrated Circuits—TTL Reductions!

SN7400	0·16
SN7401	0·16
SN7401AN	0·38
SN7402	0·16
SN7403	0·16
SN7404	0·24
SN7405	0·24
SN7406	0·45
SN7407	0·45
SN7408	0·25
SN7409	0·33
SN7410	0·16
SN7411	0·25
SN7412	0·28
SN7413	0·50
SN7416	0·45
SN7417	0·30
SN7420	0·20
SN7423	0·37
SN7425	0·37
SN7427	0·45
SN7430	0·16
SN7432	0·45
SN7437	0·35
SN7438	0·35
SN7440	0·16
SN7441	0·85
SN7442	0·85
SN7445	1·59
SN7446	2·00
SN7447	1·30
SN7448	1·50
SN7450	0·16
SN7451	0·16
SN7453	0·16
SN7454	0·16
SN7460	0·16
SN7470	0·30
SN7472	0·38
SN7473	0·44
SN7474	0·48
SN7475	0·59
SN7476	0·45
SN7480	0·75
SN7481	1·25
SN7482	0·87
SN7483	1·20
SN7484	0·95
SN7485	1·58
SN7486	0·45
SN7490	0·65
SN7491	1·10
SN7492	0·75
SN7493	0·65
SN7494	0·85
SN7495	0·80
SN7496	1·00
SN74100	2.16
SN74107	0·43
SN74118	1·00
SN74119	1·92
SN74121	0·57
SN74122	0·80
SN74123	0·72
SN74141	1·00
SN74145	1·44
SN74150	1·44
SN74151	1·10
SN74153	1·09
SN74154	1·66
SN74155	1·55
SN74157	1·09
SN74160	1·58
SN74161	1·58
SN74162	1·58
SN74164	2·01
SN74165	2·01
SN74167	4·10
SN74174	1·80
SN74175	1·29
SN74176	1·44
SN64180	1·44
SN74181	5·18
SN74190	1·95
SN74191	1·95
SN74192	2·05
SN74193	2·30
SN74196	1·58
SN74197	1·58
SN74198	3·16
SN74100	2·88

Potentiometers

Linear or Log	Single	Double
Rotary Pots	20p	45p
Rotary Switched	30p	—
Sliders	50p	80p

Full range of capacitors stocked. See catalogue for details

Presets—Horizontal or Vertical
0·1W **8p** 0·25W **10p**

Diodes and Rectifiers

PIV	50	100	200	400	600	800	1000
1·5	15p	17p	20p	22p	25p	27p	30p
3	15p	17p	20p	22p	25p	27p	30p
10	—	35p	40p	47p	56p	—	—
35	84p	92p	1·18	2·15	2·52	3·65	4·20

Cathode Stud Only IN3766 (35A 800pv) £3·65 IN3786 (35A 1000pv) £4·20

IN34A	10p
IN914	7p
IN916	7p
AA119	7p
AA129	15p
BA100	15p
BA102	25p
BA110	25p
BA115	7p
BA141	17p
BA142	17p
BA144	12p
BA145	17p
BA154	12p
BY100	15p
BY126	15p
BY127	17½p
BY140	£1
BY237	12½p
BYZ10	35p
BYZ11	32p
BYZ12	30p
OA9	10p
OA10	20p
OA47	7½p
OA70	7½p
OA73	10p
OA79	7p
OA81	8p
OA85	10p
OA90	7p
OA91	7p
OA95	7p
OA200	7p
OA202	10p
OA210	27p

OPTO & LED's

Red, green and yellow
0·16 diameter **31p**
0·20 diameter **33p**
DL707 **£2·35** or 4 for **£8**
Minitron **£1·55**

Bridge Rectifiers

Plastic	1A	2A	4A	6A
50	0·24	0·32	0·60	0·62
100	0·26	0·37	0·70	0·75
200	0·30	0·41	0·75	0·80
400	0·36	0·45	0·85	1·10
600	0·40	0·52	0·95	1·25
SCR's	100V	200V	400V	600V
½A	0·43	0·44	—	—
1A	0·45	0·50	0·60	—
1·2A	0·38	0·42	0·53	0·75
3A	0·47	0·53	0·60	0·90
4A	0·50	0·55	0·65	—

Construction Kits

AV7 Aerial Amps	£2·04
UHS70 Transmitter	£2·79
MUE7 Receiver for above	£3·22
EW18 Electronics dice	£6·53
EX20 Electronic Dice + Sensor	£7·79

Mail Order

VAT All prices exclusive P. & P., 20p

TRY OUR NEW GLASGOW SHOP

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

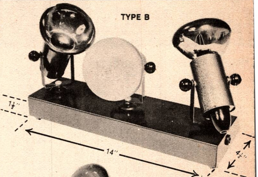

TYPE B 3-BANK UNIT

Has two brackets to accept P/C Board. Transformers. Also has holes in ends for Potentiometers, Jack Socket, Cable, etc. Ideal for making Sound to Light and Strobes. Base Cover included. Less Lamps, only

£6·50

inc. VAT. P. & P. 40p.

SOUND TO LIGHT

Three channel, using Type B unit. Ideal for small disco's and home entertainment. Complete with Lamps. Ready wired,

£25

inc. VAT. P. & P. 40p.

STROBE UNIT

Using Type B unit. Adjustable frequency. Single knob control. Complete with Lamps, just plug into mains—*that's it.*

£25

complete, inc. VAT. P. & P. 40p.

100 WATT SPOT LAMPS

Red, Pink, Green, Yellow, Blue, Violet, Clear. Only

80p

each **Minimum 3 Lamps** = **£2·40** inc. VAT, P. & P. 25p pe

TYPE A

ONLY

£1·50

inc. VAT
Less Lamp
Plus 25p P. & P.
each

TRAFALGAR SUPPLIES

Dept H.T. · Standish Street · Burnley · Lancs

SCOOP!! CALCULATOR I.C.

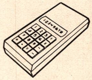

THURLBY

ELECTRONICS

XE 202 FULL 4 FUNCTION + CONSTANT CALCULATOR CHIP **£2.95** +VAT

For only £2.95 you get a brand new, tested full four function calculator chip, with the following features:

8 DIGIT DISPLAY CAPABILITY
FULLY FLOATING DECIMAL POINT
ALGEBRAIC LOGIC DATA ENTRY
KEYED CONSTANT ON ALL FOUR FUNCTIONS
TRAILING ZERO SUPPRESSION
DIRECT SEGMENT DRIVE
ENORMOUS EXPONENT RANGE: 10^{-20} to 10^{+79}
SINGLE 'STROBE' LINE FOR SIMPLE KEYBOARD CONSTRUCTION

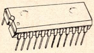

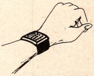

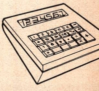

By the addition of a display and a few discrete components you can construct a powerful machine capable of handling advanced calculations.
The XE202 is supplied with full circuit diagrams and wiring details covering the use of different types of displays and keyboards (including a low cost single digit display and rapidly constructed stylus keyboard), and with instructions for realising the full computing powers of this chip to calculate advanced functions such as roots, sines, logs, etc.

Full money back guarantee.
Cash with order. Postage and packing 20p per order.
Please add 8% VAT to total order value.

ALSO AVAILABLE AT SPECIAL PRICES FOR PURCHASERS OF THE XE202 CHIP:

Specially designed display driving interface chip at £0.75

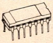

8 digit magnified LED display at £3.95

TO
THURLBY ELECTRONICS,
Church Farm House,
Church End,
Over,
Cambs. CB4 5NH

PLEASE SUPPLY__________

____

____

FOR WHICH I ENCLOSE CASH/CHEQUE/PO F

£_____ INCLUDING VAT & POSTAGE

NAME__________

ADDRESS__________

____

ALL MAIL ORDER BY
RETURN. C.O.D. SERVICE
WELCOME

C. T. ELECTRONICS

VAT
Unless otherwise stated all prices are EXCLUSIVE of VAT. Please add 8% to all orders. Carriage: orders under £5 plus 20p. Over £5 post free.

All mail order and enquiries to 270 Acton Lane, Chiswick W4 5DG. Tel. 01-994 6275

SEMICONDUCTORS

AC107	35p
AC125	25p
AC126	25p
AC127	27p
AC128	25p
AC176	25p
AC188	30p
ACY17	25p
ACY18	30p
ACY19	30p
ACY20	25p
ACY21	30p
AD140	60p
AD142	50p
AD149	60p
AD161	44p
AD162	44p
AF114	25p
AF115	25p
AF116	25p
AF117	25p
AF118	60p
ASZ21	60p
ASY28	30p
BA102	33p
BA112	50p
BA114	16p
BA156	15p
BC107	12p
BC108	12p
BC109	14p
BC113	15p
BC115	15p
BC116	16p
BC117	20p
BC118	12p
BC147	11p
BC148	11p
BC149	12p
BC153	15p
BC157	14p
BC158	15p
BC169	15p
BC182	12p
BC183	12p
BC184	14p
BC186	25p
BC212	14p
BC212L	16p
BC213	14p
BC214	14p
BC301	25p
BC302	25p
BC303	40p
BCY30	40p
BCY31	55p
BCY32	95p
BCY34	60p
BCY38	65p
BCY39	£1·00
BCY55	£1·50
BCY70	22p
BCY71	22p
BCY72	22p
BD121	75p
BD123	75p
BD124	65p
BD131	40p
BD132	50p
BD153	75p
BD156	75p
BDY11	£1·40
BDY17	£1·60
BDY19	£1·95
BDY20	£1·40
BF152	20p
BF194	14p
BF195	15p
BF196	15p
BF197	20p
BF200	30p
BF224J	30p
BFX29	30p
BFX34	30p
BFX85	30p
BFX86	30p
BFX88	30p
BFY10	35p
BFY44	50p
BFY50	25p
BFY51	25p
BFY52	25p
BFY53	25p
BFY90	65p
BSW63	65p
BSW68	80p
BY127	20p
BY134	65p
IS100	15p
IS103	15p
MJ340	50p
MJ481	95p
MJ2801	£1·25
MJ2901	£1·95
MJE340	50p
MJE370	75p
MJE371	90p
MJE520	65p
MJE2955	£1·20
MJE3055	75p
MM1613	45p
MM1712	60p
MPF102	45p
MPF103 (2N5457)	35p
MPF104 (2N5458)	35p
MPF105 (2N5459)	40p
OA47	10p
OA70	10p
OA79	10p
OA81	10p
OA90	10p
OA91	10p
OA200	10p
OA202	10p
OA210	35p
OA211	35p
OC16	90p
OC19	85p
OC22	55p
OC26	65p
OC28	60p
OC35	60p
OC36	65p
OC42	40p
OC44	20p
OC45	25p
OC70	15p
OC71	12p
OC72	20p
OC75	25p
OC76	25p
OC77	40p
OC81	25p
OC83	25p
OC84	25p
OC139	30p
OC170	25p
OC171	30p
OC200	60p
OC201	60p
OC202	75p
TIP29A	45p
TIP30	55p
TIP31A	57p
TIP32A	69p
TIP33A	£1·00
TIP34A	£1·40
TIP35A	£3·20
TIP36A	£3·50
TIP41A	70p
TIP42A	85p
TIP29B	54p
TIP30B	60p
TIP31B	65p
TIP32B	77p
TIP33B	£1·06
TIP34B	£1·62
TIP35B	£2·71
TIP36B	£3·50
TIP41B	78p
TIP42B	95p
TIP29C	68p
TIP30C	72p
TIP31C	80p
TIP32C	£1·00
TIP33C	£1·20
TIP34C	£1·80
TIP35C	£3·00
TIP36C	£3·75
TIP41C	90p
TIP42C	£1·00
TIS50	40p
ZTX107	15p
ZTX300	15p
ZTX500	16p
ZTX501	20p
ZTX504	50p
ZTX531	30p
ZTX550	25p
IN659	8p
IN914	8p
IN916	8p
IN4001	8p
IN4002	9p
IN4003	9p
IN4004	10p
IN4005	12p
IN4006	14p
IN4007	16p
IN4148	7p
2N696	25p
2N697	20p
2N698	25p
2N706	12p
2N706A	15p
2N708	15p
2N930	20p
2N1132	25p
2N1302	16p
2N1303	16p
2N1304	25p
2N1305	25p
2N1306	25p
2N1307	25p
2N1308	25p
2N1309	25p
2N1613	25p
2N1711	25p
2N2147	70p
2N2160	65p
2N2217	25p
2N2218	25p
2N2219	25p
2N2222	20p
2N2222A	25p
2N2306	70p
2N2477	30p
2N2640	50p
2N2846	£1·50
2N2904	25p
2N2906	25p
2N2907	25p
2N2926	12p
2N3053	25p
2N3054	65p
2N3055	50p
2N3232	70p
2N3525	95p
2N3643	30p
2N3702	14p
2N3703	12p
2N3704	12p
2N3705	12p
2N3706	12p
2N3707	12p
2N3708	12p
2N3709	12p
2N3771	£1·70
2N3772	£2·00
2N3773	£2·50
2N3819	35p
2N3320	55p
2N3866	85p
2N3904	22p
2N3905	25p
2N4058	12p
2N4059	12p
2N4060	12p
2N4061	12p
2N4126	17p
2N4286	15p
2N4287	15p
2N4288	15p
2N4289	15p
2N4290	15p
2N4444	£1·90
2N4871	35p
2N4903	£1·10
2N5069	£1·10
2N5191	96p
2N5194	£1·10
40360	50p
40361	50p
40362	50p
40669	90p
40673	70p
D5151 Microwave Diode	£1·00

QTY. DISCOUNTS: 12 + 10%; 25 + 15%; 100 + 20%

S.C.R.s

CRS1/05	40p
CRS1/10	56p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS3/10	62p
CRS3/20	62p
CRS3/40	90p
CRS7/400	£1·00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1·60
C106B	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	£1·90
BT10/500A	90p

BRIDGE RECTIFIERS

W02 1A 200V	38p
BY164 1·4A 200V	57p
MDA952/2 6A 100V	80p

ZENER DIODES

BZY88 Series 400mW 3·3V–33V, 5%	11p
1·5W range	25p
10W range	45p

L.E.D.

TIL209	38p
HP5082	28p
MA2082R	20p

L.D.R.

ORP12	60p

NE555 Timer	80p

TRIACS

TXL228B 8A 400V	85p
SC40D	£1·40
SC40E	£1·65
SC45D	£1·70
SC45E	£2·10
SC50D	£2·42
SC50E	£2·70
DIAC	25p

LINEAR I.C.s

LM309K 5V 1A Voltage Reg	£2·10
LM723C 2·37V 150mA Voltage Reg.	£1·05
MFC4000 250mW Audio	75p
TBA800 5 Watt Audio	£1·50
709C Op Amp D.I.L./TO99	45p
741C Op Amp 8/14 D.I.L./TO99	35p
748C Op Amp D.I.L.	75p
747C Dual OP Amp	£1·20
ZN414 Radio I.C.	£1·25
TAD100 Radio I.C. inc. Filter	£1·90
CA3014	£1·55
CA3018	£1·00
CA3028	£1·20
CA3036	£1·00
CA3046	95p
CA3048	£2·35
CA3075	£1·60
CA3090Q	£4·85
MC1303L	£2·20
MC1310P	£2·80

TO3 VOLTAGE REGULATORS

L005 5V 650mA
L036 12V 500mA
L037 15V 450mA £1·60 each

★★SPECIAL OFFERS★★

MINIATURE MAINS TRANSFORMER. PRI 240V SEC, 12V 100MA Manuf.: Hinchley. Size: 36 × 45 × 40mm F.C. 53mm. Price 1—**65p.** 100—**60p ea.** 1,000—**50p ea.** 10,000—**40p ea.**

3 CORE PVC INSULATED MAINS CABLE, GREY ML6650, 3 × 7/0·2mm. Price 100m—**£4·50.** 1,000m—**£35.** 10,000m—**£330.**

0·47mfd. 50V MYLAR FILM CAPACITOR. Size 1in × 0·35in × 0·65in P.C. Mount. Price 100—**4p ea.** 1,000—**3p ea.**

240V A.C. SOLENOID. Reversible operation; twin coil. Size approx. 2¾in × 1½in × 1¾in **90p ea.**

30 unmarked OC71 transistors	£1·00
25 Unmarked 250mW Zenerdiode, 4·7V, 5·1V, 6·2V, 7·5V, 9·1V, 10V. Measured and tested	£1·00

Please state voltage required

50 GE Diode OA47 equivalent	£1·00

TRANSFORMER: DOUGLAS PRI, 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2½A, **£4·50** + **50p p.p.**

TRANSFORMER
PRI, 0, 115, 160, 205, 225, 245. SEC. 35-0-35, 1·2A **£4·50 + 50p p.p.**

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)

Type 092	0·8-2·2p	
801	0·8-2·2p	Price **10p ea.**
991	0·5-1·3p	

QUANTITY DISCOUNTS PLEASE TELEPHONE

1,000pF Feedthrough capacitor	**5p ea.**
Miniature tubular P.C. trimmers 3·5-13pF 6-30pF	**10p ea.**
4p c/o Varley 700Ω relay	**50p ea.**

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE AND P.K. screws

	Length	Width	Height	
AB7	2¾in	5¼in	1½in	55p
AB8	4in	4in	1½in	55p
AB9	4in	2¾in	1½in	55p
AB10	4in	5¼in	1½in	55p
AB11	4in	2½in	2in	65p
AB12	3in	2in	1in	50p
AB13	6in	4in	2in	77p
AB14	7in	5in	2½in	90p
AB15	8in	6in	3in	£1·16
AB16	10in	7in	3in	£1·32
AB17	10in	4½in	3in	£1·10
AB18	12in	5in	3in	£1·32
AB19	12in	8in	3in	£1·80

ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20 8in Long 9in Wide 3½in High at back 2in High at front 6in Slope to front With P.K. Screws	£2·20
AB21 As above but 10in long	£2·40
AB22 As above but 12in long	£2·60

VEROBOARD

	0·1	0·15
2½ × 3¾	32p	23p
2½ × 5	35p	35p
3¾ × 3¾	35p	35p
3¾ × 5	40p	41p
17 × 2½	£1·05	79p
17 × 3¾	£1·43	£1·12
17 × 5	£1·84	—
PIN INS. TOOL	72p	72p
SP.F. CUTTER	52p	52p
100 PINS SS	30p	30p
100 PINS DS	30p	30p
500 PINS SS	£1·20	£1·20
500 PINS DS	£1·20	£1·20

DIGITAL INTEGRATED CIRCUITS

SN7400	18p
SN7401	18p
SN7402	20p
SN7403	20p
SN7404	20p
SN7405	20p
SN7406	30p
SN7407	30p
SN7408	20p
SN7409	40p
SN7410	18p
SN7411	23p
SN7412	22p
SN7413	40p
SN7416	30p
SN7417	30p
SN7420	20p
SN7422	38p
SN7423	38p
SN7425	38p
SN7427	42p
SN7428	50p
SN7430	20p
SN7432	42p
SN7433	70p
SN7437	50p
SN7438	50p
SN7440	20p
SN7441AN	75p
SN7442	75p
SN7443	£1·00
SN7445	£1·70
SN7446	£2·00
SN7447	£1·50
SN7448	£1·75
SN7450	20p
SN7451	20p
SN4753	20p
SN7454	20p
SN7460	20p
SN7470	30p
SN7472	30p
SN7473	40p
SN7474	40p
SN7475	55p
SN7476	45p
SN7480	80p
SN7481	£1·25
SN7482	87p
SN7483	£1·00
SN7484	90p
SN7486	45p
SN7490	75p
SN7491AN	£1·00
SN7492	75p
SN7493	75p
SN7494	80p
SN7495	80p
SN7496	£1·00
SN7497	£2·25
SN74100	£2·00
SN74104	£1·45
SN74105	£1·00
SN74107	55p
SN74110	80p
SN74118	£1·90
SN74119	£1·90
SN74121	65p
SN74122	£1·35
SN74123	£2·00
SN74141	£1·00
SN74145	£1·50
SN74150	£1·35
SN74151	£1·10
SN74153	£1·35
SN74154	£2·00
SN74155	£1·55
SN74156	£1·55
SN74157	£1·80
SN74160	£1·60
SN74161	£1·60
SN74162	£1·60
SN74163	£3·40
SN74164	£2·75
SN74165	£2·00
SN74166	£4·00
SN74167	£4·25
SN74170	£4·10
SN74174	£2·00
SN74175	£1·35
SN74176	£1·60
SN74177	£1·60
SN74180	£1·55
SN74181	£6·00
SN74182	£2·00
SN74184	£2·45
SN74185A	£2·40
SN74190	£1·95
SN74191	£1·95
SN74192	£2·00
SN74193	£2·00
SN74194	£2·50
SN74195	£1·85
SN74196	£1·50
SN74197	£1·50
SN74198	£3·00
SN74199	£2·60

ALSO STOCKED

Electrolytic Capacitors Mullard, Sprague, Lorlin etc. Polyester, Polystyrene, Silver Mica Capacitors, etc. Resistors ½W-10Watt.

Potentiometers; carbon, wirewound, Preset, Rectilinear multiturn. Antex Soldering Irons, switches, rotary, slide, toggle. etc. Cable, veroboard.

Potentiometers

Linear or Log	Single	Double
Rotary Pots	15p	42p
Rotary Switched	25p	—

ELECTRONIC COMPONENTS

BARGAIN COMPONENT PACKS
ALL COMPONENTS NEW AND UNUSED

£1 plus 25p p.p. per pack, **£5** for 5 packs p/free.

Pack No.

1 500 Carbon resistors, ¼, ½, 1, 2W.
2 100 Electrolytic Condensers.
3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
4 250 Polyester, Polycarbonate, paper, etc., Condensers.
5 25 Potentiometers, assorted.
6 250 High-stab. 1%, 2%, 5% resistors.
7 50 Assorted Tagstrips.
8 1lb. Assorted nuts, bolts, washers, spacers, etc.
9 25 Assorted switches, rotary, lever, micro, toggled, etc.
10 50 Preset Potentiometers.
11 Trial mixed component pack **£1.**
12 Jumbo mixed pack **£5.**

★ ★ SPECIAL OFFERS ★ ★

MULTICORE CABLE. 25-way, individually screened, 14/0076. **£1·00** per yard + VAT. Postage by weight.

IMHOF 19in RACKING CABINETS. 13½in high, 22in wide, 13in deep. Brand new. **£10·00** each + VAT. Carriage £1·00.

SIEMENS CONTACTORS. Over 1,000 in stock. All types. Phone or write for details.

METAL OXIDE RESISTORS TR4/5/6 in stock. All Values. 1-off price **3p** each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Painton, etc. All values in stock. **50p** each. Discount on quantity.

9-WAY FULLY STABILISED BATTERY CHARGERS. 24in L, 7½in H, 7in D. Price **£14·00** each. Carriage £1·00 + VAT.

DEAC RECHARGEABLE BATTERY CASSETTES. 13·4V (nom.). Type B/SA 80351/108. Heavy duty encapsulated DEAC supply. Size 3½in × 2½in × 1½in. Price **£5·00** + VAT.

8-WAY BATTERY CHARGER. Type CC 999. Charges up to 8 of the above battery cassettes. Price **£14·00** + VAT.

12-WAY BATTERY CHARGER. Type CC 999. Charges up to 12 of 13·4V DEAC batteries. Metered battery condition check. Price **£25·00** + VAT.

We are open from 9.30 a.m.—6.00 p.m. Monday–Saturday

We have the largest retail selection of components available. Phone or write if you are in difficulties obtaining a particular component.

C.O.D. service welcome. All mail order by return. Official orders welcome by Government establishments, Education authorities, etc.
Tel. 01-994 6275

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER
STEREO & MONO

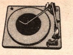

Plays 12″, 10″ or 7″ records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13½ × 11¼in.
Above motor board 3¾in. Below motor board 2½in.
with STEREO and MONO XTAL **£7·95** Post 45p.

PORTABLE PLAYER CABINET
Modern design. Rexine covered. Large front grille. Lift-up Lid. Chrome fittings. Approx. size 17in × 15in × 7in. Few only in red and black rexine. Motor board cut for Garrard deck **£4·50** Post 50p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono compatible cartridge. **£4.95** Post 25p

R.C.S. DISCO DECK
SINGLE RECORD PLAYER
Fitted with auto stop. Stereo/mono cartridge. Baseplate. Size 11in × 8½in. Turntable. Size 7in diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

£5·50 Post 25p

SOLID MAHOGANY PLINTH
Post 45p
With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Size 12½ × 14¾ × 7½in. **£6·50**

COMPACT PORTABLE STEREO HI-FI
Two full size loudspeakers 13¾ × 10 × 3¾in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¾ × 10 × 8½in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V AC Mains.

W.

Attractive Teak finish Weight 13 lb.

Bargain Price **£25** 85p Carriage

SPECIAL OFFER!
SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES

Single pole two-way Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4·50. Brand new and fully guaranteed.
OUR PRICE **£2·20** Post 25p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in sides 6 × 4in 45p; 8 × 6in 53p; 10 × 7in 65p; 12 × 8in 85p; 14 × 9in 90p; 16 × 6in 90p; 12 × 3in 50p; 16 × 10in £1.
ALUMINIUM BOXES 3 × 3 × 3in 60p; 4 × 4 × 4in 70p; 6 × 4 × 4in 80p; 9 × 4 × 4in £1; 12 × 4 × 4in £1·30.
ALUMINIUM PANELS 18 s.w.g. 6 × 4in 12p; 8 × 6 in 19p; 14 × 3in 20p; 10 × 7in 24p; 12 × 5in 25p; 12 × 8in 34p; 16 × 6in 34p; 14 × 9in 40p; 12 × 12in 47p; 16 × 10in 60p.
PAXOLIN PANEL 10 × 8in 30p.
1¼ inch DIAMETER WAVECHANGE SWITCHES, 45p ea.
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way.
1 p.1. 2-way, or 4 p. 2-way, or 4 p. 3-way.
TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

BRITISH FM/VHF TUNING HEART
88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10·7 Mc/s I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3·95** Post 20p
SUITABLE I.F. STRIP £4·95. DECODER £4·95

R.C.S. STABILISED POWER PACK KITS
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less
PLEASE STATE VOLTAGE REQUIRED. **£2·20** Post 20p
Details S.A.E. Size 3½ × 1½ × 1⅝in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE
Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¾ x 1¼ x ¾ in. Response 25 c/s to 25 kc/s, 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. **£1·25** Post 10p

R.C.S. POWER PACK KIT
12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. **£2·95** Post 25p
12 VOLT 300mA KIT, £2·75. 9 VOLT 1 AMP KIT, £2·95.

NEW TUBULAR	ELECTROLYTICS			CAN TYPES	
2/350V	14p	250/25V	14p	50 + 50/300V	50p
4/350V	14p	500/25V	20p	32 + 32/350V	35p
8/350V	22p	100 + 100/275V	65p	32 + 32/450V	60p
16/350V	30p	150 + 200/275V	70p	350 + 50/325V	55p
32/500V	50p	8 + 8/450V	22p	16 + 16 + 16/275V	45p
25/25V	10p	8 + 16/450V	25p	32 + 32 + 32/350V	65p
50/50V	10p	16 + 16/450V	40p	900/350V	95p
100/25V	10p	32 + 32/350V	40p	4700/63V	95p

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0·01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0·1 7p; 0·5 18p; 1mF 15p; 2mF 150V 15p.
500V-0·001 to 0·05 4p; 0·1 10p; 0·25 8p; 0·47 25p.
TWIN GANG. "0-0" 208pF + 176pF, £1.10p.
Slow motion drive 365pF + 365pF with 25pF + 25pF, 50p;
Twin 500pF 75p. Twin 410pF 50p. Twin 120pF 50p.
SHORT WAVE SINGLE. 25pF, 45p; 50pF, 55p.
NEON PANEL INDICATORS 250V AC/DC. Amber 30p.
RESISTORS. ¼W, ½W, 1W, 20% 1p; 2W, 5p. 10Ω to 10M.
HIGH STABILITY. ½W 2% 10 ohms to 6 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each.
TAPE OSCILLATOR COIL Valve type 35p.
FERRITE ROD 8 × ⅜in 20p; 6 × ⅜in 20p; 3 × ⅜in 10p.

MAINS TRANSFORMERS
ALL POST 25p each

250-0-250 80mA. 6·3V 2 amp .... £2·50
250-0-250 80 mA. 6·3V 3·5A 6·3V 1A or 5V 2A .... £4·00
350-0-350 80 mA 6·3V 3·5A, 6·3V 1A or 5V 2A .... £5·00
300-0-300V 120mA, 6·3V 4A C.T.; 6·3V 2A ...... £6·00
MINIATURE 200V 20mA, 6·3V 1A 2½ × 2½ × 2in 75p
MIDGET 220V 45mA, 6·3V 2A 2¾ × 2½ × 2in 90p
HEATER TRANS. 6·3V ½ amp 85p, 3 amp £1.20p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £4·00
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4·00
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6·00
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9·75
12, 36, 48V 2 amp. £2.20; 20V 3 amp £2. 3, 5, 8, 10, 13 or 5-0-5V 5 amp. £1·50; 6-0-6V 500mA 90p; 9V 1 amp 95p; 12V 300mA 75p; 12V 500mA 85p; 12V 750mA 95p. 40V 3 amp. £2·50; 22-0-22V 4 amp. £3; 16V ½ amp. 95p; 16V 2 amp. £1·85; 0.5V, 8V, 10V, 16V ½ amp. £1·60.
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £4·00; 500W £7·50; 750W £15; 1000W £18.
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1½ amp £2·00; 2 amp £2·50; 4 amp £4·00
BATTERY CHARGERS. Ready built with leads and clips 1½ amp £2; 4 amp £4; 5 amp. £4·50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1½ amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER
Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make (Value £19) OUR PRICE **£12** Carr. 95p
Can be used as 800 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK
£1·50 Post 50p

VOLUME CONTROLS
Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p.

80 Ohm Coax 5p yd.
BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd £2·00; 60 yd £3·00.
FRINGE LOW LOSS Ideal 625 and colour. **10p** per yd

Wire Wound controls 1¼in diam. 3 Watts. 10 ohms to 100K British Made with long spindles ¼in dia. 85p each.
DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3¼in; outer spindle 2¼in 75p.

E.M.I. 13½ × 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£4·50** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. **£2·75**
State 3 or 8 or 15 ohm. Post 25p
13 × 8in Bass unit 20 watt rubber cone surround 15 ohm £5·

LOUDSPEAKER FRONT GRILLE
Teakwood strips mounted on cloth backing, easily glued to baffle to modernise cabinets.
Size 18½ in × 10½in. **75p** Or size 10½in × 7⅞in. **45**

E.M.I. 6½in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. **£4**
Suitable Cabinet 12 × 8 × 6 £4 Suitable Tweeter £2

ELAC CONE TWEETER

The moving coil diaphragm gives a go radiation pattern to the higher frequenc and a smooth extension of total respo from 1,000 c/s to 18,000 c/s. Size 3½ 3½ × 2in deep. Rating 10W, 3 ohm.
Crossover £1·25 **£1·90** Post 2

GOODMANS 8 in. WOOFER

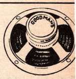

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. Ideal bass unit for Hi-Fi system. **£3·75**

SPECIAL OFFER LOUDSPEAKERS
3 ohm, 2½in; 2⅝in; 3½in; 5in.
8 ohm, 2¼in; 2¾in; 5in × 3in; 3in; 4in; 5in.
15 ohm, 3½in; 5in; 6 × 4in; 5 × 3in; 7 × 4in; 8 × 5in.
25 ohm, 2½in; 5 × 3in; 5in.
35 ohm, 3in; 5in.
80 ohm, 2¼in; 2¾in. 120 ohm 3in.
£1 EAC

LOUDSPEAKERS P.M. 3 OHMS. 7 × 4in £1·25; 6½in £1·5 8 × 5in £1·60; 8in £1·75; 10 × 6in £1·90; 10in £2·
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 diameter 4W £2·50, 10 in diameter 5W £2·95; Post 2 12in diameter, 6W, £3·50; 3 or 8 or 15 ohm models.
SPEAKER COVERING MATERIALS. Samples Large S.A.
Horn Tweeters 2-16Kc/s. 8W 8 ohm or 15 ohm £2·
De Luxe Horn Tweeters 2-18Kc/s, 15W, 15 ohm £4·
TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm £1·

CASSETTE MACHINE MOTOR. 6 Volt. Will replace many types £1·25.

R.C.S. 3 WAY CROSSOVER
Complete with 12 ft. twin lead fitted with din speaker plu Ready assembled with leads for speakers, bass, mid a tweeter. Crossover frequencies—950 cps and 3,000 cps. **£1·9**

VALVE OUTPUT TRANSFORMER 50p.
MIKE TRANSFORMER MU metal 100-1 £1·25.
PUSH-PULL VALVE OUTPUT TRANSFORMERS.
50 watt .... £12·50 100 watt .... £15·

ELECTRO MAGNETIC PENDULUM MECHANISM
1·5V d.c. operation over 200 hours continuous on S battery, fully adjustable swing and speed. Ideal displa teaching electro magnetism or for metronome, strobe, etc. **95p** Po 20

R.C.S. RECORD PLAYER AMPLIFIER
2 stage triode pentode valve. 3 watts output. Volume on/ and tone controls. Printed circuit A.C. mains complete and tested. **£4·50** Po 35
Complete with speaker.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 1
OUTLET BOXES, SURFACE MOUNTING 40p.
BALANCED TWIN RIBBON FEEDER 300 ohms, 7p y
JACK SOCKET Std. open-circuit 14p. closed circuit 23
Chrome Lead Socket 45p. Phono Plugs 7p. Phono Socket
JACK PLUGS Std. Chrome 20p; 3·5mm Chrome 15p D
SOCKETS Chassis 3-pin 10p; 5-pin 10p DIN SOCKE
Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 2
VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

ALL PRICES INCLUDE VAT ● 20p MINIMUM POST AND PACKING ● CALLERS WELCOME

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

.M.I. WOOFER AND TWEETER KIT

5·75 THE PAIR, Post 45p. (Available separately. Woofer £4·25; Tweeter £1·90)

mprising a fine example of a Woofer ¾ × 6½in with a massive Ceramic ignet, 44oz Gauss 13,000 lines. uminium Cone centre to improve ddle and top response. Also the E.M.I. veeter 3½in square has a special htweight paper cone and magnet flux ,000 lines. Crossover condenser and ll instructions supplied.

ipedance Standard	8 ohms
iximum power	12 watts
eful Response	35 to 18,000 cps
iss Resonance	45 cps

ITABLE ENCLOSURE 20 × 13 × 9in. ODERN DESIGN. TEAK WOOD FINISH. **£10·50** Post 75p

ANOTHER R.C.S. BARGAIN !

ELAC 9 × 5in. HI-FI SPEAKER TYPE 59RM

This famous unit now available, 10 watts, 8 ohm.

Price **£2·95** Post 25p

8″ or 10″ x 6″ ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50–16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts. **£3·75**

)in round £4·50.

EAK VENEER HI-FI SPEAKER CABINETS luted Wood Fronts

ODEL "A". 20 × 13 × 9in or 12 in. dia. or)in speaker. **£10·50** Post 75p

ODEL "B". 16 × 10 × 7in or 13 × 8in. or in. speaker **£6·60** Post 45p

ODEL "4C". 30 × 20 × 12in. eflex cabinet will accept 1–12in. iss unit, 1–5in. mid range, 1–3in. veeter. Teak finish. Grooved ont **£18·50** Carr. £2

OUDSPEAKER CABINET VADDING 18in wide, 20p ft.

DECCA DOME TWEETER

3½in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3·30**

ARGAIN 4 CHANNEL RANSISTOR MONO IXER. Add musical ghlights and sound effects recordings. Will mix icrophone, records, tape id tuner with separate ntrols into single output. volt battery erated. **£4·50**

TEREO VERSION OF ABOVE £5·95.

ARGAIN 3 WATT AMPLIFIER. 4 Transistor ish-Pull Ready built with volume, treble and iss controls. 18 volt battery operated. **£3·95**

HE "INSTANT" BULK TAPE RASER & HEAD DEMAGNETISER. iitable for cassettes, and all sizes of pe reels. A.C. mains 200/250V. eaflet S.A.E. **£3·75** Post 20p

VAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and lrying applications in the home, garage, greenhouse actory (available in manufacturing quantities). Approx ize 10⅞ × 8¼ × 1/16in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in sbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.

deal for home handymen and experimenters. Suitable or Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, tc., to make efficient clothes dryers, towel rails—ideal for iring cupboards. Ideal for anti-frost device for the garage —preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. nvaluable aid for bird houses, incubators, etc., etc. Can e used in series for lower heat. Or in parallel for higher eat applications.

ONLY **40p** EACH (FOUR FOR **£1·50**)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12″ £8·50

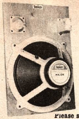

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10·95**

Please state 3 or 8 or 15 ohms.

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups.
Useful response 30-13,000 cps.
Bass Resonance 55 cps.

GROUP "25"
12in 25 watt
3, 8 or 15 ohms. **£7·75**

GROUP "35"
12in 35 watt
3, 8 or 15 ohms. **£8·50**

GROUP "50"
15in. 50 watt
8 or 15 ohms. **£17·80**

50 watt 12in VERSION £12·95

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised.
Ideal for Groups, Disco and P.A.
4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains.
Separate treble and bass controls.
Guaranteed. Details S.A.E. **£49** Carr. £1·00

NEW MODEL MAJOR 50 WATT

4 inputs, 2 way mixing, £39·95. Carr. £1. Ideal disco amp

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. **£69**

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered ¾in thick wood cabinet. Size 18½in × 18½in × 8½in. Weight 23lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6½in Woofer. £7.50. Carr. 85p.
Rosewood Version £8·50. Carr. 85p.

Baffle could be cut for larger speaker.

SPECIAL OFFER 95p. Post 25p.
100 Ohm 20 watt Rheostat 2½in dia. Ceramic Former.
Screw Terminals ¼in. dia. spindle.

R.C.S. STEREO DECODER

British made. Ready aligned and tested. Complete with instructions. Size 3in × 2in. **£4·95**

WEYRAD COILS

P50/2CC	40p	RA2W	85p
P50/1AC	60p	OPT1	65p
P50/3CC	40p	LFDT4	65p
PCA1	85p	Twin gang	£1·10

DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle 1¼in × 7/32in, size 3½in × 3in. As illustrated. 240V a.c. mains. **£2·25** Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2⅞ × 2¼ × 2¼in. **£1·00** Post 25p

BAKER HI-FI SPEAKERS

HIGH QUALITY—BRITISH MADE

REGENT

12in. 15 watts

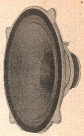

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance	45cps
Flux Density	12,000 gauss
Useful response	45-13,000cps

3 or 8 or 15 ohm models.

£7·75

DE-LUXE Mk II

12in. 15 watts

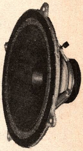

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance	30cps
Flux Density	14,000 gauss
Useful response	25-16,000cps

8 or 15 ohms models.

£9·75

SUPERB

12in. 20 watts

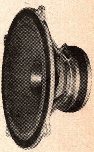

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance	25cps
Flux Density	16,500 gauss
Useful response	20-17,000cps

8 or 15 ohms models.

£13·80

AUDITORIUM

12in. 25 watts

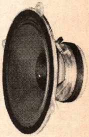

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs, Ideal for Hi-Fi and Discotheques.

Bass Resonance	35cps
Flux Density	15,000 gauss
Useful response	25-16,000cps

8 or 15 ohms models.

£12·95

AUDITORIUM

15in 35 watts

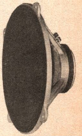

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance	35cps
Flux Density	15,000 gauss
Useful response	20-14,000cps

8 or 15 ohms models.

£17·80

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 63p.

USTOMERS FREE CAR PARK • OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

Export: Remit cash and extra postage.) *Buses 50, 68, 159. Rail Selhurst* **Telephone 01-684-1665**

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm

Supplied complete with Fixing Bracket and Control Switch. **£7·50** plus 25p P. & P.

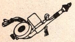

"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT This fantastic little box approx. 4" × 3" × 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier.
A Bargain at **£7·50** plus 10p.

MINIATURE RELAYS

Brand new range of British made relays, size: 1¼in × 1in × ¾in. All two changeovers with 250V 1·5A contacts and suitable for fitting on 0·1m veroboard.

Type	Volts	Current	Ohms	
27/A	12V	17M/A	700	**All**
21/A	12V	28M/A	430	**£1·30**
12/A	6V	33M/A	185	**each**

200/250V Mains Relay

Heavy duty contacts 2,500 ohm coil. All new and unused D.P.D.T. mains relays **50p,** Carr. free. Special quantity **£40** per 100 off.

MIDGET MAINS TRANSFORMER

Varnish Impregnated

Size 45mm × 36mm × 31mm

PRI 240V

Sec	3.0·3	100mA
Sec	6·0·6	100mA
Sec	9·0·9	100mA
Sec	12·0·12	100mA
Sec	20·0·20	100mA

£1·23 10p P. & P.

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, **£15;** Wheel, **£5;** Total **£20.** Plus 75p carr.

7in × 4in LOUDSPEAKER

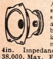

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in × 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1·60.** Free postage on this item.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U . BUILD . IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE

170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE

Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY

Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. **£25,** carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

12–0–12V 500M/A

240V primary transformer bargain. Approx. size: 60mm × 40mm × 50mm; fixing centres: 75mm. Our price **£1·20.**

18V 500M/A

240V primary. Approx. size: 60mm × 40mm × 50mm; fixing centres: 75mm. Our Price **£1** each

BARGAIN BOX

Loud buzzer mounted in a metal box complete with two U2 battery size holder.
Designed and can be used as a fire alarm but is ideal as a door or morse code practise buzzer.
Approx. size: 2¾in × 6½in × 1½in.
OUR PRICE 50p

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm × 73mm × 45mm **51p;** 1006, 150mm × 75mm × 47mm **66p;** 1007, 184mm × 124mm × 60mm **96p;** 1021, 106mm × 74mm × 45mm (sloping front) **50p.**

BARGAIN BOARDS

Components galore for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards **£1.**

2in. PANEL METERS

Size 59mm × 46mm

0·50μA —ME6	0·100mA—ME13
0·100μA—ME7	0·500mA—ME14
0·500μA—ME8	0·1A —ME15
0·1mA —ME9	0·50V a.c. —ME16
0·5mA —ME10	0·300V a.c.—ME17
0·10mA—ME11	S meter —ME18
0·50mA—ME12	V.U. meter—ME19

£3 each. 10p P. & P.

POWER PACKS

PP1 Switched 3-6-7½-9V 400M/A Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, **£5·25** each.
PP2 Switched 6-7½-9V Battery Eliminator. Approx. size 2¾in × 2¼in × 3¼in. Ideal for cassette recorders, **£3·25** each.
PP3 Car converter. From 12V Pos. or Neg. to = 6-7½-9V. Easy to fit and transistor regulated, **£3·90.**

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

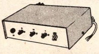

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)

£18·50 plus 38p P. & P.

MINI LOUDSPEAKERS

2¼in 80 ohm, **50p;** 2¼in 40 ohm, **50p.** Please include 5p P. & P. on each L.S.

U.K. CARRIAGE	VAT	SEND 20p FOR A
15p UNLESS OTHERWISE STATED	8% VAT TO BE ADDED TO ALL ORDERS	CRESCENT CATALOGUE

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	P & P £	p
07	20	1	8	7·0 × 6·0 × 6·0	2·55	38
149	60	3	12	9·9 × 7·7 × 8·6	3·98	45
150	100	5	8	9·9 × 8·9 × 8·6	4·45	45
151	200	8	0	12·1 × 9·3 × 10·2	7·39	53
152	250	13	12	12·1 × 11·8 × 10·2	8·93	73
153	350	15	0	14·0 × 10·8 × 11·8	10·80	73
154	500	19	8	14·0 × 13·4 × 11·8	12·41	91
155	750	29	0	17·2 × 14·0 × 14·0	18·65	*
156	1000	38	0	17·2 × 16·6 × 14·0	26.50	*
157	1500	46	0	21·6 × 13·4 × 18·1	30·23	*
158	2000	60	0	21·6 × 15·3 × 18·1	33·70	*

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	Auto Taps	P & P £	p
113	20	1	0	5·8 × 5·1 × 4·5	0-115-210-240	1·52	30
64	75	2	4	7·0 × 6·7 × 6·1	0-115-210-240	2·64	38
4	150	3	4	8·9 × 7·7 × 7·7	0-115-200-220-240	3·75	45
66	300	6	4	9·9 × 9·6 × 8·6	,, ,,	5·29	53
67	500	12	8	12·1 × 11·2 × 10·2	,, ,,	8·02	67
84	1000	19	8	14·0 × 13·4 × 14·3	,, ,,	12·44	91
93	1500	30	4	14·0 × 15·9 × 14·3	,, ,,	16·65	*
95	2000	32	0	17·2 × 16·6 × 14·0	,, ,,	22·00	*
73	3000	40	0	21·6 × 13·4 × 18·1	,, ,,	31·90	*

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets, 20VA **£2·85,** P & P 38p. 500VA **£9·50,** P & P 80p. 1000VA **£15·92,** via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps. 12V	24V	Weight lb	oz	Size cm.	Secondary Windings	P & P £	p
111	0·5	0·25		8	4·8 × 2·9 × 3·5	0-12V at 0·25A ×2	1·34	23
213	1·0	0·5	1	4	6·1 × 5·8 × 4·8	0-12V at 0·5A ×2	1·58	30
71	2	1	1	12	7·0 × 6·4 × 6·1	0-12V at 1A ×2	2·09	38
18	4	2	2	12	8·3 × 7·7 × 7·0	0-12V at 2A ×2	2·60	38
70	6	3	3	8	8·9 × 8·0 × 7·7	0-12V at 3A ×2	3·75	45
108	8	4	5	8	9·9 × 8·9 × 8·6	0-12V at 4A ×2	4·15	45
72	10	5	6	4	9·9 × 9·6 × 8·6	0-12V at 5A ×2	4·67	53
116	12	6	6	12	9·9 × 10·2 × 8·6	0-12V at 5A ×2	5·02	53
17	16	8	8	12	12·1 × 9·9 × 10·2	0-12V at 8A ×2	6·62	60
115	20	10	11	8	14·0 × 9·6 × 11·8	0-12V at 10A ×2	9·45	73
187	30	15	15	8	14·0 × 12·1 × 11·8	0-12V at 15A ×2	12·29	85
226	60	30	32	0	17·2 × 15·3 × 14·0	0·12V at 30A ×2	15·30	*

30 VOLT RANGE

Ref. No.	Amps	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
112	0·5	1	4	6·1 × 5·8 × 4·8	0-12-15-20-24-30V	1·65	30
79	1·0	2	4	7·0 × 6·7 × 6·1	,, ,,	2·18	38
3	2·0	3	4	8·9 × 7·7 × 7·7	,, ,,	3·18	38
20	3·0	4	8	9·9 × 8·3 × 8·6	,, ,,	4·12	45
21	4·0	6	4	9·9 × 9·6 × 8·6	,, ,,	4·67	53
51	5·0	6	12	12·1 × 8·6 × 10·2	,, ,,	5·83	53
117	6·0	8	0	12·1 × 9·3 × 10·2	,, ,,	6·51	60
88	8·0	12	0	12·1 × 11·8 × 10·2	,, ,,	9·00	67
89	10·0	13	12	14·0 × 10·2 × 11·8	,, ,,	8·97	73

50 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
102	0·5	1	12	7·0 × 6·4 × 6·1	0-19-25-33-40-50V	2·35	30
103	1·0	2	12	8·3 × 7·4 × 7·0	,, ,,	3·08	38
104	2·0	5	8	7·9 × 8·9 × 8·6	,, ,,	4·26	45
105	3·0	6	12	9·9 × 10·2 × 8·6	,, ,,	5·28	53
106	4·0	10	0	12·1 × 10·5 × 10·2	,, ,,	6·91	67
107	6·0	12	0	14·0 × 10·2 × 11·8	,, ,,	11·00	67
118	8·0	18	0	14·0 × 12·7 × 11·8	,, ,,	11·80	85
119	10·0	25	0	17·2 × 12·7 × 14·0	,, ,,	15·45	*

60 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
124	0·5	2	4	7·0 × 6·7 × 6·1	0-24-30-40-48-60V	2·12	38
126	1·0	3	4	8·9 × 7·7 × 7·7	,, ,,	3·10	38
127	2·0	6	4	9·9 × 9·6 × 8·6	,, ,,	4·62	45
125	3·0	8	12	12·1 × 9·9 × 10·2	,, ,,	6·84	60
123	4·0	13	12	12·1 × 11·8 × 10·2	,, ,,	7·96	67
40	5·0	12	00	14·0 × 10·2 × 11·8	,, ,,	8·87	73
120	6·0	15	8	14·0 × 12·1 × 11·8	,, ,,	10·27	85
121	8·0	25	00	14·0 × 14·7 × 11·8	,, ,,	13·64	*
122	10·0	25	0	17·2 × 12·7 × 14·0	,, ,,	15·93	*
189	12·0	29	00	17·2 × 14·0 × 14·0	,, ,,	18·16	*

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb	oz	Size cm.	Volts	P & P £	p
238	200		2	2·8 × 2·6 × 2·0	3-0-3	1·40	10
212	1A, 1A	1	4	6·1 × 5·8 × 4·8	0-6, 0-6	1·67	30
13	100		4	3·9 × 2·6 × 2·9	9-0-9	1·28	13
235	330, 330		4	4·8 × 2·9 × 3·5	0-9, 0-9	1·42	19
207	500, 500	1	00	6·1 × 5·4 × 4·8	0-8-9, 0-8-9	1·75	30
208	1A, !A	1	12	7·0 × 6·4 × 6·1	0-8-9, 0-8-9	3·00	38
236	200,200		4	4·8 × 2·9 × 3·5	0-15, 0-15	1·30	19
214	300, 300	1	4	6·1 × 5·8 × 4·8	0-20, 0-20	1·76	30
221	700 (d.c.)	1	8	7·0 × 6·1 × 6·1	20-12-0-12-20	1·98	38
206	1A, 1A	2	12	8·3 × 7·7 × 7·0	0-15-20, 0-15-20	3·15	38
203	500,500	2	4	8·3 × 7·0 × 7·0	0-15-27, 0-15-27	2·73	38
204	1A, 1A	3	4	8·9 × 7·7 × 7·7	0-15-27, 0-15-27	3·50	38

*Carriage via B.R.S.

PLEASE ADD 8% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

HROMASONIC electronics

Dept. 2. 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

RECTIFIERS

1A		3A		6A		12A	
IN4001	6½p	IN5400	15½p			BYX61 - 50	£3.21
IN4002	7½p	IN5401	16½p			BYX61 -100	£3.48
IN4003	9p	IN5402	17½p	BYZ13	58p	BYX61 -200	£3.76
IN4004	9p	IN5404	22p	BYZ12	66p	BYX61 -400	£4.29
IN4005	11p	IN5406	26p	BYZ11	73p	BYX62 -600	£4.29
IN4006	13½p	IN5407	28p	BYZ10	85p		
IN4007	16½p	IN5408	31p				

BRIDGES

V	1A	2A	6A
50	20p	35p	75p
100	20p	40p	78p
200	22p	45p	90p
400	25p	50p	£1.05
600	25p		£1.20
1000	38p		

TRIACS

	4A	
25v	2N6068	45p
50v	2N6069	52p
100v	2N6070	58p
200v	2N6071	63p
400v	2N6073	68p
600v	2N6075	£1.49

SOLDERING

Desolder Braid
Reel 64p

Multicore

18 swg size 5	32p
22 swg size 15	36½p
carton size 1	50p
" " 12	£1.57

Adcola Invader

L706 19 watt ⅓" bit £2.88
L646 20 watt " bit £3.13

DIN CONNECTORS

Pins	Plugs	Sockets	Line Couplers
2	9p	7p	11p
3	10p	7p	11p
4	11p	7p	11p
5 (180)	11p	8p	11p
5 (240)	11p	8p	11p
6	11p	9p	11p
7	13p	9p	11p

4mm.

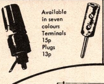

Available in seven colours
Terminals 15p
Plugs 13p

HEAT SINKS

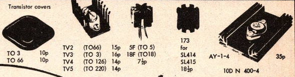

Transistor covers

TO 3	10p
TO 66	10p

TV2	(TO66)	15p
TV3	(TO 3)	16p
TV4	(TO 126)	14p
TV5	(TO 220)	14p

5F (TO 5)
18F (TO18)
7½p

173
for
SL414
SL415
18½p

AY-1-4 35p

10D N 400-4

U1(TBA800)	16p
U1(TBA810S)	16p
U2(TBA810AS)	16p
U2(TCA940)	16p
U3(TDA2020)	35p

47½

CO~AXIAL

Plug - Screened 11p
- Plastic 9p

Sockets

Chassis 10½p

Surface 11p

Coupler 25p

AUDIO I.C.'S

A brand New Audio I.C. Leaflet with Circuits and pin connections for ALL the I.C.'s listed below FREE with orders over £1.00 or 10p without

PHONO

Sockets

1 way	5p
2 way	7p
3 way	7p
4 way	8p

Plugs:

Plastic Moulded	7½p
Chrome Screened	12½p
Coupler screened	15p

JACK

	Plugs	Sockets
2.5mm *	20p	12p
3.5mm*	20p	12p
standard *	25p	15p
stereo *	27p	21p
side entry standard	48p	

* screened

I.C. SOCKETS

TO5 Style

8 pin	31p
10 "	35p

Dual-in Line

8 pin	13p
14 pin	15p
16 pin	15p
24 pin	26p
28 pin	30p
36 pin	39p
40 pin	44p

I.C. PIN SOCKETS

I.C. pins in strips of 100. Just snip off what you need. 65p per strip

P.C. CONNECTORS

0-1" pin centres 24 way + key supplied with ends 64p

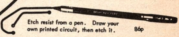

Etch resist from a pen. Draw your own printed circuit, then etch it. 86p

SWITCHES

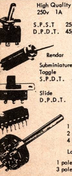

High Quality
250v 1A

S.P.S.T 25p
D.P.D.T. 45p

Rotary 2A
Mains
Switches

35p

Bulgin

push-to-make
25p

Rendar

Subminiature
Toggle
S.P.D.T. 48p

Slide
D.P.D.T. 12p

Erg Dil Switches

1 pole	8 way	99p
2 pole	4 way	85p
4 pole	2 way	£1.24

Lorlin Water Switches 27p

1 pole 12 way; 4 pole 2 way
3 pole 4 way; 4 pole 3 way

POWER OUTPUT WATTS	Supply Volts	Load Ohms	Style	Power I.C. Amplifiers	Price	Pre-Amplifiers	Supply Volts	Style		
0.25	9	16	C	MFC4000B	78p	Dual Low Noise	±24	A	LM381	£2.16
0.5	9	8	E	MC1306P	68p	Dual Low Noise	± 14	A	LM382	£2.19
1	9	8	F	TAA300	£1.76	Dual Pre-Amp	± 13	A	MC1303L	£1.59
2	12	8	G	TBA820	74p	Dual Low Noise	± 12	A	MC1339P	£1.31
2	18	8	A	LM380	£1.08	Dual Low Noise	± 15	A	TBA231	88p
2½ + 2½	18	8	A	LM377	£2.91	General				
3	18	8	J	SL414	£1.72	D.C. Controlled attenuator			MFC6040	83p
5	24	16	J	SL415	£2.24	3 stage G.P. amp.		B	TAA263	80p
5	24	8	H	TBA800	96p	Tape Pre-Amp		F	TAA310	£1.34
7	16	4	H	TBA810S	£1.07	Bi-Fet		B	TAA320	97p
7	16	4	K	TBA810AS	£1.07	Hear/Aid Amp 1.3v		I	TAA370	£5.05
10	20	4	M	TCA940	£1.94	PPL stereo decoder(i)		A	MC1310	£2.14
15	30	3	O	BHA0002	£2.60	4 channel SQ " (ii)		A	MC1312	£2.42
35 driver	25	8	F	NE540L	£1.08	4 " pre-amp (ii)		16	MC1314	£4.05
20	±15	4	N	TDA2020	TBA	CBS SQ Logic (ii)		16	MC1315	£5.37

(i) & (ii) Separate leaflets available free only with purchases over £1

MAINS TRANSFORMERS

secondaries

6-0-6v, 100mA 97p ; 20-0-20v 1A £4.55
9-0-9v, 100mA 97p ; 24-0-24v ½A £2.48
12-0-12v, 100mA 97p ; 28-0-28 1A £6.18
18-0-18v, 200mA plus 0-24v 40mA 97p

	1A	2A	4A
0-9-17v	£1.95	£2.27	£2.64
0-12-15-20-24-30v	£2.48	£4.15	-
0-24-30-40-48-60v	£5.18	£7.02	-
	½A	1A	2A
0-19-25-33-40-50	£2.70	£3.40	£4.53

RENDAR INSTA~POWER

safe; inexpensive; quick, A.C. mains connector. A 13 amp plug top containing snap connectors
£1.75

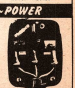

VAT INCLUSIVE PRICES AT 8%

OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
P&P On U K Orders 15p Overseas Orders at Cost

Phoenix Electronics (Portsmouth) Ltd.

139–141 Havant Road,
Drayton, Portsmouth, Hants
PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

THIS MONTH'S BARGAIN OFFER!

Rectifier kit. 4 each 1N4148, AA144, 1N4004, 1N4006, 1N5402, 1N5406, SCR 0·6A/200V, Bridge 1A/400V, Triac 2·5A/100V, plus 4 voltages of 400mW Zeners—catalogue value £10·60. Bargain pack PEP/4A—**£6·50.**

Please send your catalogue—free!

Name ....

Address ....

.... PEP/1A

NEW PE SCORPIO Mk. 2

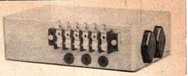

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- Now with added R.F.I. suppression.
- Fully machined and painted die-cast case with AMP termination connector block.
- Custom wound transformer.
- NOW AVAILABLE IN 6V. and 12V.
- Suitable for all types of Cars, Boats, Go-Karts, etc.
- Promotes easier starting—even under sub-zero conditions.
- Improves acceleration, gives better high speed performance and quicker engine warm up.
- Eliminates excessive contact breaker burning and pitting.
- PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board. —Uses original plugs, points and coil.—No special parts or extras required. (Case size: 7¼in × 4½in × 2in)

- All components available separately.—S.A.E. with enquiries.

- Construction manual available separately 25p.

Cost **£11·78** incl. carr. and ins. or ready built and tested **£14·49**

Conversion kit from Mk. I to Mk. 2. For constructors already possessing Mk. I Kits.—Miniature P.C. assembly **£1** incl. carr. and ins. With full conversion instructions.

PLEASE ADD VAT TO ALL U.K. ORDERS

(Carriage at cost outside U.K. — Export enquiries welcome.)

DABAR ELECTRONIC PRODUCTS
98 LICHFIELD STREET
WALSALL, Staffs WS1 1UZ

Buy it with Access

BARCLAYCARD

TTL I.C.s

7400	**14p**	7441	**75p**	7476	**37p**
7401	**15p**	7442	**70p**	7480	**65p**
7402	**15p**	7447	**95p**	7486	**41p**
7404	**18p**	7448	**90p**	7489	**340p**
7408	**20p**	7450	**22p**	7490	**45p**
7410	**15p**	7454	**22p**	7492	**68p**
7413	**30p**	7460	**22p**	7493	**48p**
7414	**72p**	7470	**30p**	74107	**45p**
7416	**33p**	7472	**30p**	74121	**34p**
7420	**15p**	7473	**36p**	74122	**76p**
7430	**15p**	7474	**34p**	74123	**110p**
		7475	**52p**	74141	**85p**

ACCESSORIES DIL SOCKETS (L.P.)
8 pin **12p,** 14 pin **13p,** 16 pin **14p.**
Mica + bushes for TO3 and TO66 8p.

5314 Clock Chip 24 pin DIL **650p.**

Alarm Clock Chip 40 pin DIL (similar MM5316) **750p.**

5001 12 Digit Calculator Chip 28 pin DIL **485p.**

(All above supplied with full data; data separately **25p** each + S.A.E.)

PC Keyboard (0–9, decimal, 4 function, C, K, keys). Size: 2·36 × 3·76″ × 0·45″ **400p.**

Popular Op Amps

ML709	OPA with ext. comp.	**28p**
ML710	Diff. comparator	**35p**
ML741	OPA with int. comp. (8 pin DIL)	**25p**
ML747	Dual 741	**70p**
ML748	OPA with ext. comp.	**38p**

LINEAR ICs

CA3046	Transistor Array	**55p**
CA3048	4 Independent Amps	**230p**
CA3089	FM. IF Amp	**250p**
CA3090	FM Stereo Decoder	**400p**
LM301	OPA with ext. comp.	**40p**
LM307	OPA with int. comp.	**50p**
MC1303	Stereo Pre-amp	**150p**
MC1307	FM Stereo Decoder	**120p**
MC1310	Coilless FM Stereo Dec.	**245p**
MC1312	SQ Quadraphonic Dec.	**220p**
MFC 4000	¼ Watt Audio Amp.	**40p**
MFC6040	Electronic Attenuator	**90p**
MFC8070	Zero Voltage Switch	**250p**
TAA570	Limiter Amp	**170p**
TBA570	AM/FM Radio receiver	**160p**
TBA800	5 Watt Audio Amp	**100p**
TBA810	7 Watt Audio Amp	**125p**
TBA820	2 Watt Audio Amps	**90p**
TCA940	10 Watt Audio Amplifier	**270p**
ZN414	Radio receiver	**110p**
NE536	FET OPA	**192p**
NE555	Timer	**50p**
NE556	Dual 555	**120p**
NE560	PLL	**285p**
NE561	PLL with AM Demod	**285p**
NE562	PLL with VCO	**285p**
NE565	Precision PLL	**285p**
NE566	Function Gen	**200p**
NE567	Tone Decoder	**250p**
SG3402N		**172p**
8038	Voltage Controlled Oscillator	**290p**

Data sheets on above ICs **10p** each.

BRIDGE RECTIFIERS

	50V	100V	400V	600V
250mA	**16p**	—	—	—
1 Amp	**20p**	**21p**	**24p**	**25p**
2 Amp	**30p**	**35p**	**45p**	**48p**
4 Amp	—	—	—	—
6 Amp	**55p**	**60p**	**78p**	**98p**

SCR—THYRISTORS

	50V	100V	400V	600V
1 Amp	**42p**	**48p**	**60p**	**78p**
3 Amp	**43p**	**49p**	**78p**	**100p**
7 Amp	—	**80p**	**84p**	**115p**
16 Amp	—	**82p**	**98p**	—

Other
C106D **45p,** 2N3525 **91p,** 2N4444 **185p**

TRIACS

	100V	400V	500V
3 Amp	**85p**	**99p**	**120p**
6 Amp	**88p**	**120p**	**150p**
10 Amp	**109p**	**154p**	**165p**
16 Amp	**145p**	**180p**	**200p**

Other
40430 **90p,** 40486 **85p,** 40669 **95p.**
DIAC ST2 for use with above triacs **21p.**

VOLTAGE REGULATORS

723
14 pin DIL **55p**
MFC4060 **70p**

1 Amp	Plastic	TO-220
7805	5V	**140p**
7812	12V	**140p**
7815	15V	**140p**
7818	18V	**140p**
7824	24V	**140p**

AC126/7	**11p**	BC212	**11p**	OC70/1/2	**11p**	2N2221/2	**20p**	MJE340	**45p**
AC128	**11p**	BC213	**10p**	OC73	**60p**	2N2369	**14p**	**UJTS**	
AC176	**11p**	BC124	**13p**	OC81/2	**12p**	2N2484	**30p**	TIS43	**25p**
AC187	**12p**	BD115	**55p**	OC83/4	**28p**	2N2905	**18p**	2N2160	**70p**
AC188	**11p**	BD124	**75p**	TIP2955	**70p**	2N2926RB	**8p**		
AD149	**43p**	BD131	**42p**	TIP41A	**68p**	2N29260	**8p**	2N2646	**35p**
AD161	**36p**	BD132	**45p**	TIP42A	**76p**	2N2926YG	**9p**	2N4871	**31p**
AD162	**36p**	BF115	**22p**	ZTX300	**14p**	2N3053	**18p**		
AF114/5	**13p**	BF167	**23p**	ZTX304	**24p**	2N3055	**40p**	**FETS**	
AF116/7	**13p**	BF173	**25p**	ZTX500	**15p**	2N3442	**140p**	BF244	**36p**
AF139	**41p**	BF184	**22p**	ZTX504	**50p**	2N3702/3/	**11p**	MPF102/3	**31p**
AF239	**44p**	BF194	**11p**	2N696	**15p**	2N3704/5	**11p**	MPF104/5	**31p**
BC107/8	**9p**	BFR39/40	**28p**	2N697	**13p**	2N3706/7	**11p**	2N3819	**20p**
BC109	**10p**	BFR41	**28p**	2N698	**30p**	2N3708/9	**9p**	2N3820	**57p**
BC147/8	**7p**	BFX29/30	**30p**	2N706	**12p**	2N3772	**161p**	2N3823	**60p**
BC149	**9p**	BFY50/1/2	**15p**	2N708	**18p**	2N3773	**220p**	2N5457	**31p**
BC157	**13p**	BRY39	**34p**	2N930	**18p**	2N3903/4	**15p**	2N5458	**31p**
BC158	**12p**	MJE2055	**95p**	2N1131/2	**18p**	2N4058	**15p**	2N5459	**31p**
BC159	**14p**	MJE3055	**65p**	2N1302/3	**17p**	2N4060	**13p**	**MOSFETS**	
BC169C	**12p**	OC26	**47p**	2N1304/5	**21p**	2N5191	**95p**	40603	**58p**
BC177	**18p**	OC28	**55p**	2N1306/7	**28p**	2N5194	**85p**	40673	**50p**
BC178	**17p**	OC35	**48p**	2N1308/9	**28p**	2N2904	**20p**	40841	**75p**
BC179	**18p**	OC36	**52p**	2N1613	**20p**	2N3054	**45p**	3N128	**75p**
BC182/3	**10p**	OC41/2	**15p**	2N1711	**20p**	40361	**36p**	3N140	**85p**
BC184	**11p**	OC44/5	**11p**	2N2219	**20p**	40362	**38p**	3N141	**75p**

C-MOS I.Cs

CD4001AE	**37p**
CD4011AE	**37p**
CD4012AE	**37p**
CD4013AE	**67p**
CD4016AE	**90p**
CD4017AE	**183p**
CD4023AE	**37p**
CD4024AE	**148p**
CD4025AE	**37p**
CD4027AE	**108p**
CD4030AE	**82p**
CD4046AE	**225p**
CD4047AE	**154p**

OPTO-ELECTRONICS
LDR ORP12 **50p,** ORP60 **60p;** Trans OCP71 **65p,** 2N5777 **45p;** LEDS TIL209 (Red) **16p,** Green/Yellow **35p.**

Seven Segment Displays

Filament			
3015F	0·354in	DIL	**120p**
All LED			
MAN–3M	0·127in	PCB	**100p**
MAN–4	0·19in	DIL	**180p**

Reflective Bar LED

LIT 704	0·33in	DIL	**135p**
LIT 707	0·33in	DIL	**135p**
LIT 747	0·63in	DIL	**250p**

3 Digit Readouts

Blisdor Lens	0·127in	DIL	**250p**
Red Lens Filter	0·127in	DIL	**185p**

RECTIFIER DIODES

500mA	
BY100	**15p**
1 Amp	
BY126	**12p**
BY127	**12p**
1N4001	**5p**
1N4004	**6p**
1N4007	**7p**
1·5 Amp	
PL4004	**10p**
3 Amp	
PL7004	**20p**
6 Amp	
BYZ10	**50p**
BYZ11	**50p**
BYZ12	**50p**
BYZ13	**50p**

SIGNAL DIODES

BA100	**10p**
OA47	**7p**
OA70	**8p**
OA79	**7p**
OA81	**7p**
OA85	**9p**
OA90	**6p**
OA91	**6p**
OA95	**7p**
OA200	**6p**
OA202	**7p**
1N914	**4p**
1N916	**6p**
1N4148	**4p**

ZENER DIODES
3·3V to 33V

400MW	**9p**
1·3W	**20p**
1·5W	**27p**
10W	**55p**

Other Diodes
TUNNEL
AEY11 **50**

VARICAP

BB103	**15**
BB104	**30**
BB105	**30**

Minimum order £2.
All prices exclusive of VAT.
P. & P. **15p.**

All goods brand new
MAIL ORDER ONLY

TECHNOMATIC LTD.

54 Sandhurst Road, London NW9. Tel. 01-204 4333

The big three from Wireless World

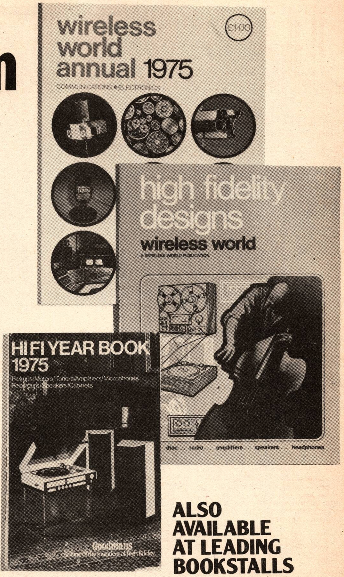
wireless world annual 1975
£1.00
COMMUNICATIONS • ELECTRONICS
BBC
high fidelity designs
wireless world
A WIRELESS WORLD PUBLICATION
disc.... radio.... amplifiers.... speakers.... headphones
HI FI YEAR BOOK 1975
Pickups/Motors/Tuners/Amplifiers/Microphones
Recorders/Speakers/Cabinets
Goodmans

WIRELESS WORLD ANNUAL 1975

The first ever Wireless World Annual contains pages of features covering all aspects of electronics and communications, including new and established techniques both practical and theoretical. Content includes constructional projects for a general purpose audio oscillator and a small boat echo sounder. There is a reference section packed with useful information.

HIGH FIDELITY DESIGNS

In response to demand for reprints of Wireless World constructional projects, we have collected fifteen of the most popular designs in one book. It covers tape, disc, radio, amplifiers, speakers and headphones. Where necessary, specifications have been updated to incorporate new components which have become available.

HI-FI YEAR BOOK 1975

This is the book that tells you everything you need to know about the hi-fi equipment on the market. Separate illustrated sections cover every major category, together giving prices and specifications of over 2,000 products. And it's got a directory of dealers/manufacturers – plus a host of articles on the latest hi-fi developments and their application.

ALSO AVAILABLE AT LEADING BOOKSTALLS

To: General Sales Department, Room 11,
Dorset House, Stamford Street, London SE1 9LU

ORDER FORM

Please send me books as indicated below (state number of copies of each):

Wireless World Annual 1975 @ £1.35 each incl. ....
High Fidelity Designs @ £1.35 each incl. ....
Hi-Fi Year Book 1975 @ £2.00 each incl. ....

I enclose remittance value £..................
(cheques payable to IPC Business Press Ltd.)

Name..
(please print)
Address...
....
....

Regd. in England No. 677128 Regd. office Dorset House, Stamford Street, London SE1 9LU

Practical Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway Hous Farringdon Street, London EC4H 4AD

RECEIVERS AND COMPONENTS

R.T. SERVICES
(MAIL ORDER ONLY)
77 Hayfield Rd., Salford 6, Lancs.

12 Volt 1 Amp Trickle Charger. £1·85 P.P.
FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½×2×1½ in with circuit, **£1·37½** inc. P.P.
Crouzet Geared Motors, 30 r.p.m. New, **£1·54** inc. P.P.
UHF TV Tuners. Transistorised, **£1·85** inc. P.P.
Panels with I.C's on **7½p** per I.C. min. order 10 I.C's.
Transformers. 7·5V+7·5V ½A, **£1** inc. P.P. 12-0-12V, 100mA, **£1·10** inc. P.P. 9-0-9V, 100mA, **£1·10** inc. P.P. 29V 50mA, **85p** inc. P.P. 6-0-6V, 100mA, **£1·10** inc. P.P.
Transformer. 24 volt, approx. 1 amp + 6·3V CT approx. 500mA, **£1·40** inc. P.P.
Transformer. 20-0-20 volt, approx. 2 amp + 6·3V, **£3** inc. P.P.
Transformer. 20 volt, 1 amp, **£1·25** P.P.
Transformer. 45 volt, 2 amp, **£3** P.P.
P.C. Board. S/S, 5½×5½in, 10 for **£1** inc. P.P.
3EG1 Scope Tubes with base and connections, **£3·30** inc. P.P.
Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, **£2** inc. P.P. Size 3″ × 2″ × 2″.
Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1250 mfd capacitors, all new **£1·40** per kit. P.P.
Electrolytic Capacitors, 4,000 MF, 50VW, 4½″ × 1¾″ **80p.** inc. P.P.
Mixed Pack of C280 series Mullard capacitors. 100 for **£1·15** inc. P.P.
4 Panels each with XN3 type Nixie tube ON **£1·85** inc. P.P. Min. order 4.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

440V AC (±10%)			63V Range	±1%	±2%	±5%
0·1µF	(1¼″×½″)	**50p**				
0·22µF	(1⅜″×⅝″)	**59p**	0·47µF	**56p**	**46p**	**36p**
0·25µF	(1⅜″×⅝″)	**62p**	1·0µF	**66p**	**56p**	**46p**
0·47µF	(1⅜″×¾″)	**71p**	2·2µF	**80p**	**65p**	**55p**
0·5µF	(1⅜″×¾″)	**75p**	4·7µF	**£1·30**	**£1·05**	**85p**
0·68µF	(2″×¾″)	**80p**	6·8µF	**£1·64**	**£1·29**	**£1·09**
1·0µF	(2″×¾″)	**91p**	10·0µF	**£2·00**	**£1·60**	**£1·40**
2·0µF	(2″×1″)	**£1·22**	15·0µF	**£2·75**	**£2·15**	**£1·90**

TANTALUM BEAD CAPACITORS—Values available: 0·1, 0·22, 0·47, 1·0, 2·2, 4·7, 6·8µF at 15V/25V or 35V; 10·0µF at 16V/20V or 25V; 22·0µF at 6V/10V or 16V; 33·0µF at 6V or 10V; 47·0µF at 3V or 6V; 100·0µF at 3V. ALL at **10p** each. 10 for **95p**, 50 for **£4**.

TRANSISTORS:					
BC107/8/9	**9p**	BC183/183L	**11p**	BFY50	**20p**
BC114	**12p**	BC184/184L	**12p**	BFY51	**20p**
BC147/8/9	**10p**	BC212/212L	**14p**	BFY52	**20p**
BC153/7/8	**12p**	BC547/558A	**12p**	AF178	**30p**
BC182/182L	**11p**	BF194	**12p**	OC71	**12p**
		BF197	**13p**	2N3055	**50p**

POPULAR DIODES—1N914 **6p**, 8 for **45p**, 18 for **90p**; 1N916 **8p**, 6 for **45p**, 14 for **90p**; 1S44 **5p**, 11 for **50p**, 24 for **£1**; 1N4148 **5p**, 6 for **27p**, 12 for **48p**; IN4001 **5½p**; IN4002 **6p**, IN4003 **6½p**; IN4004 **7p**; IN4005 **7½p**; IN4006 **8p**; IN4007 **8½p**.

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3·3V, 3·6V, 4·7V, 5·1V, 5·6V, 6·2V, 6·8V, 7·5V, 8·2V, 9·1V. 10V, 11V, 12V, 13V, 13·5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. ALL at **7p** each, 6 for **39p**, 14 for **84p**. SPECIAL OFFER: 100 Zeners for **£5·50**.

RESISTORS—High stability, low noise carbon film 5% ½W at 40°C, ⅓W at 70°C. E12 series only—from 2·2Ω to 2·2MΩ. ALL at **1p** each, **8p** for 10 of any one value, **70p** for 100 of any one value. SPECIAL PACK: 10 of each value 2·2Ω to 2·2MΩ (730 resistors) **£5.**

SILICON PLASTIC RECTIFIERS—1·5 amp, brand new wire ended DO27: 100 P.I.V. **7p** (4 for **26p**); 400 P.I.V. **8p** (4 for **30p**).

BRIDGE RECTIFIERS—2½ amp: 200V **40p**; 350V **45p**; 600V **55p.**

SUBMINIATURE VERTICAL PRESETS—0·1W only: ALL at **5p** each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2·2k Ω, 4·7kΩ, 6·8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250Ω, 680kΩ. 1MΩ, 2·5M, 5M.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS

Send S.A.E. for lists of additional ex-stock items.
Wholesale price lists available to bona fide companies.

MARCO TRADING
Dept. E.3, The Old School, Edstaston,
Nr. Wem, Shropshire
Tel.: Whixall 464/465 (STD 0948 72)
(Proprs.: Minicost Trading Ltd.)

LEDS with Data clip **1p**	dia.	0·125	0·2	D.I.L. SOCKET
	RED	**15p**	**19p**	8 pin **12p**
	GREEN	**27p**	**33p**	14 pin **13p**
	YELLOW	**27p**	**33p**	

INFRA-RED LEDs with Data | **550µW axial lead, 49p**
1·5 mW TO46, £1·10

OPTO-ISOLATORS with Data	
IL74 1·5kV, 150kHz	**£1**
4350 2·5kV, 5MHz	**£2·25**

OP. AMPS	
709 all	**25p**
741 8 pin	**29p**
748 D.I.L.	**36p**

THYRISTORS	50v	100v	400v
TO5 1A	**25p**	**27p**	**46p**
TO66 3A	**27p**	**35p**	**50p**

NE555V	**60p**
ZN414	**£1·10**
7400	**16p**
BHA 0002 15W I.C. AMP	**£2·50**

AC127	**15p**	2N2926(R)	**7p**
AC128	**15p**	2N2926(G)	**12p**
AF117	**20p**	2N3053	**15p**
BC107	**10p**	2N3055	**41p**
BC108	**10p**	2N3702	**12p**
BC109C	**14p**	2N3704	**12p**
BC169C	**12p**	TIS43	**25p**
BC182L	**11p**	MPF102	**40p**
BC184L	**11p**	2N3819	**25p**
BC212L	**12p**	2N3823	**30p**
BC213L	**11p**		
BCY70	**15p**	used OC84 10 for **50p**	
BCY71	**22p**		
BCY72	**12p**		
BFY50/51	**16p**	7805 Reg.	**£1·50**
OC71	**10p**	**Plastic 1·5 Amp**	
2N706	**10p**		
2N2904	**16p**	L129 5V reg.	
2N2906	**16p**	600mA	**£1·40**

IN914	**3p**
IN4001	**5p**
IN4002	**6p**
IN4004	**7p**
IN4148	**4p**
OA47	**6p**
OA81	**7p**
OA91	**5p**
OA95	**5p**
OA200	**6p**
OA202	**7p**

BRIDGES	
2A 50V	**30p**
2A 100V	**36p**
2A 400V	**46p**

PRICES INCLUSIVE + 10p P. & P. (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

BRAND NEW COMPONENTS BY RETURN, Electrolytics, 15V, 25V, 50V—0·47, 1, 2·2, 4·7, 10 mF, **4p;** 22, 47, **4½p;** (50V, **5p**); 100, **5½p;** (50V, **7p**); 220, **6p;** (50V, **9p**). Subminiature bead-type tantalums 0·1/35V, 0·22·/35V, 0·47/35V, 1/35V, 2·2/35V, 4·7/35V, 10/16V, 22/16V, 47/6V, 100/3V, **9p**. Mylar Film 100V 0·001, 0·002, 0·005, 0·01, 0·02, **2½p;** 0·04, 0·05, **3p**. Mullard Tubular Polyester 400V E6 series, 0·001–0·022, **3p;** 0·033–0·1, **4p.** Mullard miniature C333 ceramics E.12 series 2% 1·8pF–47pF, **2½p;** 56pF–330pF, **3p**. Polystyrene 63V. E12 series 10pF–1000pF, **2½p;** 1200pF–10000pF, **3½p**. Miniature Highstab Carbon Film Resistors ⅓W E12 series 5% 1Ω–10MΩ (10% over 1MΩ), **1p.** Postage **8p.** Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 ORN.

DRY REED INSERTS

 

Overall length 1·85″ (Body length 1·1″). Diameter 0·14″. Max. ratings 250v D.C. and 500 mA. Gold clad normally open contacts. **69p** per dozen; **£4·12** per 100; **£30·25** per 1,000; **£275** per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

BETA DEVICES
FOR BETTER PRICES

TRANSISTORS	
AC187/188 PR.	0·40
BC107/ BC108	0·09
BC109C	0·11
BC147/8/9	0·10
BCY70/71/72	0·13
BFX86/87/88	0·20
BFY50	0·18
BFY51/52	0·12
OC28	0·45
OC35	0·35
2N2646	0·30
2N3053	0·14
2N3055	0·38
2N3442	£1·40
2N3773	£2·20
TIP41A	0·74
40636	£1·00

I.C's	
709C TO.99	0·30
709C D.I.L.	0·30
741C TO.99	0·36
741C D.I.L.	0·36
723C D.I.L.	0·80
747C D.I.L.	0·85
748C D.I.L.	0·36

5Watt Audio I.C. TBA 800 **£1·50.** Data free with every order.

D.I.L. SOCKETS	
8-Pin	0·12
14-Pin	0·12
16-Pin	0·14

All prices include V.A.T.

DIODES & RECT.	
1N914	0·04
1N4148	0·04
BY127	0·14
1N4001/2	0·05
1N4003/4/5	0·06
1N4006/7	0·08
BRIDGES	
WO1 1A 100V	0·20
WO6 1A 600V	0·30
ZENERS	
BZY88 3·3–33V 5%	0·09
1 Watt 6·8–200V 5%	0·15
L.E.D.	
209—Red	0·17
L.E.D. Clip	0·02

C.W.O. PLUS P.P. 10p TO
BETA DEVICES,
263 THE RIDGEWAY, ENFIELD, MIDDX.

TTL AT LOW PRICES!
(All ex-stock. All prices include VAT.)

	1/24	25/99		1/24	25/9
SN7400	**0·15**	**0·14½**	SN7454	**0·15½**	**0·14**
SN7401	**0·15½**	**0·14½**	SN7460	**0·15½**	**0·14**
SN7402	**0·15½**	**0·14½**	SN7472	**0·29**	**0·27**
SN7403	**0·15½**	**0·14½**	SN7473	**0·33**	**0·32**
SN7404	**0·18**	**0·16½**	SN7474	**0·36**	**0·34**
SN7405	**0·18**	**0·16½**	SN7475	**0·51**	**0·50**
SN7408	**0·18**	**0·16½**	SN7476	**0·35**	**0·32**
SN7410	**0·15½**	**0·14½**	SN7480	**0·50**	**0·47**
SN7412	**0·23**	**0·21**	SN7483	**0·95**	**0·89**
SN7413	**0·33**	**0·32**	SN7486	**0·35**	**0·34**
SN7420	**0·15½**	**0·14½**	SN7489	**3·56**	**3·33**
SN7430	**0·15½**	**0·14½**	SN7490	**0·54**	**0·50**
SN7432	**0·31**	**0·29**	SN7492	**0·54**	**0·50**
SN7437	**0·31**	**0·29**	SN7493	**0·54**	**0·50**
SN7440	**0·15½**	**0·14½**	SN7495	**0·73**	**0·68**
SN7442	**0·73**	**0·68**	SN7496	**0·83**	**0·78**
SN7445	**0·99**	**0·92**	SN74107	**0·36**	**0·34**
SN7447	**0·98**	**0·98**	SN74121	**0·36**	**0·34**
SN7450	**0·15½**	**0·14½**	SN74123	**0·72**	**0·67**
SN7451	**0·15½**	**0·14½**	SN74157	**0·87**	**0·81**
SN7453	**0·15½**	**0·14½**	SN74175	**1·01**	**0·95**

DIODES: 1N4148 **4p,** 1N4001 **4½p,** 1N4002 **5p,** 1N4003 **6p** 1N4004 **6p.**
TRANSISTORS: ZTX107 **10p,** ZTX108 **8½p,** ZTX109 **11½p**
MULLARD C280 Polyester Caps (all µF): 0·01, 0·015 **3½p;** 0·022, 0·033, 0·047 **3½p;** 0·068 **4p;** 0·1, 0·15 **4½p.**
All devices full spec. by famous manufacturers. TTL MAY BE MIXED FOR 25/99 PRICES. S.A.E. for full lists 10p P. & P. on orders under £1, otherwise POST FREE.

J. C. JONES (Dept. PE3)
46 BURSTELLARS, ST. IVES
HUNTINGDON PE17 4XX
(Mail Order only)

COPPER CLAD FIBRE GLASS PANELS 12½in × 7in, **80p;** 18in × 4in, **70p.** Double sided 12½in × 7in, **90p;** 11in × 13in, **£1·30.** All post paid. **MC METERS,** 3 assorted 2-3in, **£1·30** (40p). **5 FIGURE RESETTABLE COUNTER,** 18/22V, works on 12V, **£2·25** (30p). **74 SERIES D.I.L. ICs ON PANELS,** 10 for **80p** (10p). **COPPER CLAD PAX. PANELS,** 8in × 9½in, 3 for **£1.** 12½in × 9in, 2 for **90p.** 16in × 9½in, **60p.** Double sided 12½in × 12½in, **70p.** All post paid. **22-WAY STEPPING SWITCH WITH RESET.** A.C. mains operated, **£1** (30p). **THREE TRANSISTOR AUDIO AMP** Transistors equiv. to AC128, OC72, **40p** (10p). 3 for **£1,** c.p. **VALUPAKS** P9, 100 s/mica caps **55p.** P3, 10 silicon diodes 650V 1½A, **50p.** Post 12p for one. **20p** any multiple. Send 12p stamps for full list plus computer panels, etc. Refund on purchase.

7lb ASSORTED COMPONENTS £2 c.p.

J.W.B. RADIO
2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets **Mail order only**

ALLARD ELECTRONICS
Branded Components—Full Specification

TRANSISTORS	Price each
AC125/6/7/8	**0·13**
AD140/149	**0·48**
AD161/162	**0·35**
AF114/5/6/7	**0·14**
AF118	**0·35**
BC107/8/9	**0·09**
BC147/8/9	**0·10**
BC182/3/4	**0·10**
BC212/3/4	**0·11**
BCY70/71/72	**0·12**
BD131/132	**0·35**
BF194/5/6	**0·10**
BFY50/51/52	**0·16**
BY127	**0·25**
MJE370	**0·62**
MJE371	**0·73**
2N2218	**0·19**
2N2906	**0·13**
2N2926 all	**0·11**
2N3053	**0·15**
2N3054	**0·42**
2N3055	**0·44**
2N3702/3/4	**0·10**
2N3705/6	**0·10**
2N3707/8/9	**0·08**
2N3819	**0·28**
TIL209 red (0·125″)	**0·20**
PACK OF TEN	**1·75**

SCR's	Price each
CRS1/05	**0·30**
CRS1/10	**0·56**
CRS1/20	**0·60**
CRS1/40	**0·45**
CRS3/40	**0·55**

SPECIAL
I/C OFFER
5 watt
Radio Pair
ZN414, TBA800
£2·15 pair
FREE DATA
Singly
ZN **£1·10**
TBA **£1·35**

ZENERS	
BZY88 All voltages	**0·10**
BZX61 series 1·3W	**0·17**

DIODES	Pric eac
1N914/1N4148	**0·0**
1N4001/8	**0·0**

P.W. TV TENN
SEMICON PAC
COMPLETE
2-741C, 2-BC108,
4–1N4004, 1-7805,
16-7400, 24-1N914,
12-NE555
SPECIAL PRICE
£13·55 PER PACK

FULL RANGE
Over 1,500 sem conductor types 7400 series a low prices. Verc board, pots, caps etc. etc.
Send for FRE list.
S.A.E. please

BRIDGE RECTIFIERS
Price each

p.i.v.	1A	2A	4A	6A
50V	**0·20**	**0·30**	**0·45**	**0·55**
100V	**0·20**	**0·38**	**0·48**	**0·58**
200V	**0·25**	**0·40**	**0·54**	**0·68**
400V	—	**0·43**	**0·60**	**0·75**
600V	**0·25**	**0·45**	**0·70**	**0·87**

299/301 BALLARDS LANE
LONDON N12 8NP (01-445 5188)
MAIL ORDER ONLY. Cash with order.
Orders under £3 plus 15p P. & P.
Add V.A.T. to total

N YOUR SURPLUS capacitors, transistors, into cash. Contact COLES-HARDING O., P.O. Box 5, Frome, Somerset. ediate cash settlement.

)ART ELECTRO SERVICES
24 Oaklands Park, Buckfastleigh, Devon

EC. CAPS (ITT) µF/V
)0, 2·2/63, 4·7/35, 10µF/16, **6p;** 10/63, 22/10, 47/25, /10, **7p;** 100/50, **10p;** 470/35, 220/50, **18p;** 1000/25, **24p.**

'. DISCS
1/18, 0·22/18, 0·047/12, **6p;** 0·1/30, 0·22/6, **7½p.**

;. CAPS 5%
680pF, **5½p;** 1000–10000pF, **8p.**

:. CAPS 250V
1–0·047, **5p;** 0·068–0·1, **6p;** 0·15–0·22, **8p;** 0£33–0·47, ; 0·68–1µF, **18p.**

SISTORS
5W E12CF, **1½p;** 0·5W E12CF, **1½p;** 0·5W E24MO, **4p.**

NERS
mW, **12p;** 1W, **18p.**

ANSISTORS

599	**45p**	AD161/2 MP	**95p**
1613	**25p**	BC107/8/9	**12p**
3053	**21p**	OA202	**7p**
3054	**50p**	1N914	**5p**
3055	**55p**	1N4001/2	**7p**
3702–7	**12p**	1N4003/4/5	**9p**
3773	**£2·95**	1N4006/7	**13p**
3819	**40p**	1N4148	**6p**
5459	**49p**		

I. I.Cs

709/14	**32p**	µA741/8	**38p**
709/T099	**28p**	µA723	**78p**

ease add 8% VAT and 15p Postage and Packing.

EDUCATIONAL

TELEVISION TRAINING

6 MONTHS' full-time ractical and theoretical trainig course in Radio and TV ervicing (Mono and Colour) or beginners.

3 WEEKS' full-time Colour V Servicing course. Includes)0 hours practical training. lono revision if necessary. Good ectronics background essential.

IEXT SESSION commences on pril 21st.

rospectus from London Elecronics College, Dept. A3, 20 enywern Road, London SW5 SU. Tel. 01-373 8721.

C AND G EXAMS

ake sure you succeed with an ICS home study urse for C and G Electrical Installation Work Technicians, Radio/TV/Electronics Technicians lecomms Technicians and Radio Amateurs.

OLOUR TV SERVICING

ake the most of the current boom! Learn the chniques of servicing Colour and Mono TV. s through new home study courses, approved leading manufacturers.

TECHNICAL TRAINING

ome study courses in Electronics and Electrical gineering, Maintenance, Radio, TV, Audio, mputer Engineering and programming. Also f-build radio kits. Get the qualifications you ed to succeed.

ee *details from:*

INTERNATIONAL
CORRESPONDENCE SCHOOLS
Dept. 730, Intertext House, London
SW8 4UJ
Or phone 01-622 9911 (All hours)

One of the best ways of taking A DEGREE IN ELECTRICAL or ELECTRONIC ENGINEERING and also qualifying to become a CHARTERED ELECTRICAL ENGINEER is to join the NORTH STAFFORDSHIRE POLYTECHNIC at Beaconside, Stafford.

We can introduce you to industrial firms for your practical training periods. In most cases these contacts lead to permanent staff appointment in industry upon graduation. Advice on course, accommodation and training from:

The Head of the Department of Electrical & Electronic Engineering, Room C16, North Staffordshire Polytechnic, Beaconside, Stafford. Tel.: Stafford 52331.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets, manuals, books on radios, T.V.s, etc. Service sheets **40p** plus S.A.E. Free book lists on request. Back issues of P.W., P.E., E.E., TV available **25p** plus 7p post. S.A.E. with enquiries: B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

SERVICE SHEETS for over 6000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only **30p,** plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue **20p** plus S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **20p.** S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

FOR SALE

FOR SALE back issues 1966–1973. Tel. 0283 67011.

FIBREGLASS SHEET $\frac{1}{16}$ in. thick, high strength and insulation properties, sheets 12 in. × 12 in., **45p** each. Send to: Richards, 15 Linden Lane, Kirby Muxloe, Leicester.

COMPLETE MINT COLLECTION of Practical Electronics in binders with indexes, blueprints, etc. Offers 01-435 4552.

SITUATIONS VACANT

ELECTRONIC ENGINEER

required in an expanding electronic services company in the Sultanate of Oman, specialising in commercial/industrial television and radio installations, also the installation and servicing of electronic security systems. Applicants should have a minimum of either Ordinary National Certificate or City & Guilds Final.

Salary £3,500 p.a. nett, free furnished accommodation supplied, limited free utilities, i.e. electricity and water, company car and petrol supplied free, annual paid leave of one month with air fares provided, initial contract period minimum of two years.

Applications should be made to:

P.O. Box 1000, Muscat, Sultanate of Oman

MEN! £70p.w. can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. **London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.**

After training, our exclusive appointments bureau — one of the world's leaders of its kind — introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre Y33, Oxford Hse. 9-15 Oxford St., W.1. Tel. 01-734 2874

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

'SCOPE TUBES WANTED. 1 in. type 1CP1 or DH3/91, preferably with bases and screens. Price up to **£5** according to age and condition. Cheque or P.O. by return. BARRY CHILDE, 370 Charminster Road, Bournemouth, BH8 9RX. Tel. 516565. Closed Mondays.

VINTAGE RADIOS are a fascinating and lucrative hobby. We have sets, literature, etc. from **£2–£100** and urgently need more. Write for details to VINTAGE RADIO MART, 26 Bowden Lane, Chapel-en-le-Frith, Stockport, Cheshire.

"RADIO & TV SERVICING" books wanted from 1962 edition onwards. **£2** paid per copy by return post. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, Yorks. Tel. (0423) 55885.

MISCELLANEOUS

The **PE ORION HI-FI STEREO AMPLIFIER** uses our GB1 Bec cabinet (illustrated in Jan. 1974 Practical Electronics). Special Price to readers of Practical Electronics, **£3·60** plus 45p P. & P.

Ready Punched with a self-adhesive anodised aluminium front panel, **£1·80** extra. Other sizes and types. Send S.A.E. for details.

Please add 8% VAT to total amount.

TRADE ENQUIRIES INVITED

H.M. ELECTRONICS
275a Fulwood Road
Broomhill, Sheffield S10 3BD
Tel. 669676

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 4½p stamps for catalogue. RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford on Avon. Warwicks, CV37 9NF.

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc. Guaranteed

£5·50
inc. VAT and post.
List price £7·02 inc. VAT.

SALOP ELECTRONICS **Tel. 53206**
23 Wyle Cop, Shrewsbury, Shropshire

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty P.V.C. faced steel. Hundreds of radio, electronic and hi-fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Prompt despatch. Free literature, BAZELLI, Department No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster, LA2 6LT.

FLUORESCENT LIGHT KIT

12 v
8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19
Ready built £3-78
Diffuser only 59p extra

Inc V.A.T post & packing

ALUMINIUM BOXES

Prices include lid, screws, and V.A.T.
Post and packing 10p extra on all orders.

7	5¼"	by	2¾"	by	1½"	high	39p
8	4"	by	4"	by	1½"	,,	39p
9	4"	by	2¾"	by	1½"	,,	38p
10	5¼"	by	4"	by	1½"	,,	43p
11	4"	by	2½"	by	2"	,,	38p
12	3"	by	2"	by	1"	,,	29p
13	6"	by	4"	by	2"	,,	50p
14	7"	by	5"	by	2½"	,,	65p
15	8"	by	6"	by	3"	,,	82p
16	10"	by	7"	by	3"	,,	98p

Order now to:—

ELECTRONIC DESIGN ASSOCIATES
DEPT PE
82 Bath St., Walsall, WS1 3DE. Phone 33652

LOW COST I.C. MOUNTING. 100 I.C. pin sockets **60p.** Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports **5p**/pair. (P. & P. 5p/order). LED (MLED500) **20p** each post free. Quantity rates. P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

MINI ACCUMULATORS

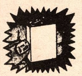

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.

Size L450—1·4" x 1·1" x 0·44". 3 for £1·85 inc. P. & P.

Size GA2—1·7" x 1.3" x 0·5". 3 for £2·35 inc. P. & P.

GARFIELDS, 269 Rye Lane, London, S.E.15

IC SOCKET PINS for low cost mounting of 8 to 40 pin DILs. **70p** (+ 5p VAT) for strip of 100, **£1·50** (+ 12p VAT), for 3 × 100, **£4** (+ 32p VAT) for 1,000. Instructions supplied—send S.A.E. for sample. 10p P. & P. for orders under £2. SINTEL, 53b Aston Street, Oxford. Tel. 0865 43203.

ENAMELLED COPPER WIRE

S.W.G.	*1lb Reel*	*½lb Reel*
10–14	**£2·05**	**£1·15**
15–19	**£2·15**	**£1·20**
20–24	**£2·20**	**£1·25**
25–29	**£2·25**	**£1·30**
30–34	**£2·35**	**£1·38**
35–40	**£2·50**	**£1·45**

All the above prices are inclusive in U.K.

COPPER SUPPLIES
102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 80p).

SEND 5" × 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
124 Colne Road, Twickenham
Middlesex TW2 6QS

THE CHIPS ARE DOWN! AY-5-1224 digital clock chip now **£3.95** inc. VAT, post free. Circuit and details S.A.E. GREENBANK ELECTRONICS, Dept. 320, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

VALVES, TRANSISTORS, STYLI. Valves 1930 to 1975. 1,500 types. Many obsolete. List **15p.** Transistors list **15p.** Styli list **10p.** S.A.E. for quotation. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel.: West Wittering 2023.

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists DOZENS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a *few* examples, there are *stacks* more!

Dazzling MINI-STROBE (pocket size)	**£2·90**
PEOPLE DETECTOR	**£3·20**
Big-Ear SOUND-CATCHER	**£3·20**
Mini DREAM LABORATORY ..	**£3·20**

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH YOU A COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey
(Mail Order U.K. only)

fibre optic supplier

MARE'S TAILS. Build a decorative display with professionally finished unit, 22in diameter with 7.0 fibres. Looks immaculate. **£9·70.**

FIBROFLEX SIZE 1. Flexible 440 strand glass light con bundle dia. 1·14mm. **40p** per metre (**£3** per 10m).

FIBROFLEX SIZE 4. 2·28mm bundle dia. **£1·50** per m (**£12** per 10m).

CROFON 1610. 64-strand plastic light conduit, bundle 1·8mm, O.D. 3·3mm. **£1·20** per metre (**£9·30** per 10m)

PLASTIC OPTICAL MONOFIBRE. For multiple illumina from one source, displays, internal illumination, eff optical coupling, etc.
FP20 (0·5mm dia.)—**50p** per 10m; **£4** per 100m.
FP40 (1mm dia.)—**£2·20** per 10m; **£14** per 100m.
FP60 (1·5mm dia.)—**£4** per 10m; **£30** per 100m.

OPTIKIT 103. Contains 2m Crofon 1610 plus 5m each F FP40, FP60 plus polishing compound. A handy pac the experimenter. **£4·70.**

LENSES AND REFLECTORS. We stock a range of 6 le and 5 reflectors for use in proximity detectors, intr detectors, batch counters, tachometers, short r optical communications.

OPTIKIT L6. 1 each of 6 lenses, **£2·50.**

OPTIKIT RR5. 1 each of 5 reflectors, **£1·50.**

CIRCULAR POLARISERS. Cut that glare. Reduce spe reflection by up to 20×—enhance contrast on crts, displays, nixies, instruments, etc. Available in red/am green/neutral. 50mm square **60p**; 75mm **£1·20**; 150mn

LINEAR POLARISERS. For light valves, stress anal type HN32. Type KN42 is for high temp. use in projec Use a pair to make a psychedelic light show. Price a circular polarisers.

LIGHT SOURCES AND DETECTORS: MV54 Minia (2mm) Red LED, **20p** (10+ **18p**); MLED500 TO92 Red **20p** (10+ **18p**); MLED92 Infra-Red Emitter, **30p** (10+ XC209-R 3mm Red LED, **20p** (10+ **18p**); XC209-Y c Yellow/Green, **30p** (10+ **27p**); 2N5777 High Sensi Photodarlington Silicon Detector, gain ×2,500, (10+ **45p**); MRD150 Silicon Phototransistor—high sp 4μs good sensitivity. **70p** (10+ **67p**).

****NEW MLS203.** Latest Motorola Light Activated High sensitivity 10mW/cm²; high current 400mA (5A p 60V. Switch small motors or relay direct from op control, up to 24W power. **£1·20** (10+ **£1·10**).

SEO5B ULTRASONIC TRANSDUCER. For remote co 40kHz. Tx/Rx pair, **£3·50.**

Please add 8% VAT to prices above
Send 9in × 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIEF
(Dept. PE), P.O. Box 702
London W10 6SL

PRINTED CIRCUIT BOARDS. Manufactur offer: PCB's for ALL "P.E. and P.V projects published after June, 1974, at O price, **70p** each. Any 5 **£2·85.** PRODUCTI SPACE available for: PCB Production, P and Electronic Design to Spec.: electroplati silk-screening, roller and electro tinning. art-work and photography undertaken. S basic circuit, P.C layout or P.C. master stat quantity required for estimate by return, phone: W.K.F. ELECTRONICS, De P.C., Welbeck Street, Whitwell, Works Notts., S80 4TW. Tel.: Whitwell (Derbys.) 6

LIGHTING MODULES AND KITS CHEAPER STILL!

SAVE POUNDS BY BUYING DIRECT

SOUND TO LIGHT: 3 × 1½ kW channels wit SENSITIVITY, DIMMING and BYPASS control Designed to be robust and reliable and simp to build. KIT FORM: **£13·99;** PRE-BUILT **£15·99.** THEATRE AND DISCO/CLUB DIM MERS OUR SPECIALITY!
Only written enquiries and Mail Order to:
SELEKTRON
21 Priors Road, Windsor, Berks. SL4 4P

AERIAL BOOSTERS £3, P. & P. 10p. make three types of boosters: **L11-VHF ra** **L12-VHF** 405 TV. Please state chan numbers. **L45-UHF-**625 TV. S.A.E. leafl LANCASHIRE MAIL ORDER, 6 Willi Street, Stubbins, Ramsbottom, Bury, Lancs

SINTEL

Add 10p P. & P. for orders unde Data, and circuits where ap priate, supplied with orders, available separately (4½p st each).

3 Digit DIP LED calculator display	**£1·35** + VAT =	£
High Quality 0·3in **LED** 7 seg. display	**95p** + VAT =	£
MK50250N Alarm Clock IC	**£6·90** + VAT =	£

Send for our new simple MK50250N circuit diagrams

Soldercon IC socket pins —	300 pins for **£1·50** + VAT =	£
	1,000 pins for **£4·00** + VAT =	£
MK50250N + 4 × DL704 0·3in LED's	**£10·20** + VAT =	£1

Complete circuits and special prices for MK50250N with LE Minitrons or SP352's.

SINTEL, 53B ASTON STREET, OXFORD. Tel (0865) 43203

FANTASTIC NEW MICROTEST 80

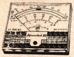

MEASURES ONLY
) × 70 × 18mm

mazing Value at £11·95

fields of measurement and 40 ranges

:s d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V :Ω/V)
:s a.c. 5 ranges: 1·5V, 10V, 50V, 250V, 1,000V (4kΩ/V).
p. d.c. 6 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A.
p. a.c. 5 ranges: 250μA, 2·5mA, 25mA, 250mA, 2·5A.
ns 4 ranges: Low Ω, Ω × 1, Ω × 10, Ω × 100 (da 1/10 fino a 5MΩ).
utput 5 ranges: 1·5V, 10V, 50V, 250V, 1,000V.
:ibels 5 ranges: +6dB, +22dB, +36dB, +50dB, 2dB.
acity 4 ranges: 25·F, 250μF, 2,500μF, 25,000μF.

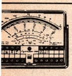

SUPERTESTER 680 R ICE

20,000 Ohm per Volt sensitivity ● Fully screened against external magnetic fields ● Scale width and small case dimensions (128 × 95 × 32mm) ● Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading ● Simplicity and ease of use and readability ● Full ranges of accessories 1,000 times overload ● Printed uit board is removable without soldering ● More ranges than any er meter. Ask for free catalogue.

£18·50
Accessories Extra

:essories (extra) available to convert Microtest 80 Supertester 680R into following SIGNAL INJECTOR, USS METER, ELECTRONIC VOLTMETER, AMPER-AMP, TRANSISTOR TESTER, TEMPERATURE OBE, PHASE SEQUENCE INDICATOR—Send for ails.

IORE RANGES FOR ESS MONEY!

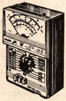

/DC Multimeter type U4324

C 0·06–3A–6 Rranges.
C 0·3–3A–5 Ranges.
C 0·6–1200 V–9 Ranges.
C 3–900 V–8 Ranges.
quency in the range of 45 to Hz. Resistance: 500 ohm to lohm—5 ranges. Decibel: −10 +12dB. Accuracy: ±2·5%. DC % AC. Dimensions: 167 × 98 33mm.

Only £8·85

ALPHANUMERIC NIXIE TUBES B7971

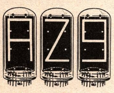

Alphanumeric IE tube has the lity to display the letters of alphabet, merals 0 thru 9 d special racters in a gle tube. m the stand-nt of both read-lity and elec-al characteris-, the Alpha-meric NIXIE tube provides many unique benefits luding ★ 170V–21mA ★ All d.c. operation ★ Uniform, ntinuous line characters of equal height ★ Memory h simple solid state drive circuits ★ Readability in h ambient light . . . 200 footlamberts brightness Long life with no loss of brightness ★ Character ght 2½in.

ses for above **60p** each.

ice only 99p each plus 16p P./P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

ra-long life, high quality, 0–9 and 2 independent deci-l points. Supply voltage 200V d.c. Current 14mA. lse duration 100μs. Character height 0·51, overall e 1·4.

and new, guaranteed. Surplus to manufacturer's uirements. Type B5853st

-25 **£1·00**; 25+ **90p**; 100+ **80p**; 000+ price on application.

Add 8% VAT to all items + 35p P. & P.

ELECTRONIC BROKERS LTD.
–53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

BUILD THE

TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC–1 & BBC–2 TV

Send s.a.e. for leaflet

Complete kit **£9·80**
P. & P. 60p + 78p VAT

Built, tested and guaranteed **£13·75**
P. & P. 60p + £1·10 VAT

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD,
LONDON E18 2AN (Mail Order Only)

METER REPAIRS. Ammeters, voltmeters multi-range meters, etc. Send to METER, REPAIRS, 21 Mount Road, Thundersley, Benfleet, Essex, SS7 1HA.

PRINTED CIRCUIT BOARDS. PCB for any PRACTICAL ELECTRONICS and PRACTICAL WIRELESS project, **50p** per board. From individual patterns **£1** plus 5p per square inch. Add VAT plus 5p P. & P. per board. Mail order only. TEC, 241 Burnt-Oak, Broadway, Middlesex.

BOOKS AND PUBLICATIONS

UFO CHARTS: Daily Flight, **50p**; Prediction, **54p**; Map, **50p**; Propulsion, **55p**; "Anti-Gravity", **55p**. TV UFO Detection (Reprint), **63p**; Circuits: Transistor Optical Detector, **66p**; Radiation/Optical, **44p**; Microdetectors (Memory, LSI), **80p**; Crystal Radiation/Counter-Timer/Stopclock, **85p**. FET Multi-meter, **£1·70**. R. & E., Highlands, Needham Market, Suffolk.

NEW IMPROVED

MAINS INTERCOM

NO BATTERIES
NO WIRES

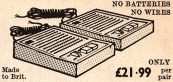

ONLY **£21·99** per pair
+VAT £1·76

Made to Brit. Safety & Telecom. Standards, Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal-clear communication from room to room. Operates over a ¾-mile range. On/Off switch, Vol. control. Useful as office intercom, baby alarm, invalids. No G.P.O. licence reqd. Full price ref. if returned in 10 days. 12 months service guarantee. P. & P. 60p.

NEW! AMERICAN TYPE CRADLE

TELEPHONE AMPLIFIER

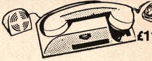

ONLY **£11·95**

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12·95.
P. & P. 48p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE3)
169 KENSINGTON HIGH STREET, LONDON, W.8

PE MINISONIC

COMPONENT KITS NOW AVAILABLE.
4½p STAMP BRINGS DETAILS.

TRANSISTORS	
BC204	11p
BC209C	11p
BC182	10p
BC184	11p
BC212	14p
BC214	16p
BC213	15p
BC213L	15p
ZTX300	15p
ZTX500	17p
2N2484	24p
2N2904	30p
2N2905	27p
2N2219	22p
2N3054	100p
High Voltage	
MPSL01	39p
MPSL51	41p
MPSU07	69p
MPSU57	85p
FETS	
2N3819	46p
2N5459	60p
DIODES	
1N5401	21p
1N914	5p
BA148	25p
1SJ50	12p
1GP7	10p
NOISE DIODES	
Z1J	60p
Z1M	120p
RECTIFIERS	
REC41A	120p
REC46	255p
REC70	40p
EA100/10	100p
MDA942A/1	210p

VOLTAGE REGULATORS	
μA7815	220p
723	180p
ARRAYS	
ML3046P	75p
CA3096AE	120p
OP. AMPS	
709/8 Dip	39p
710/TO5	39p
741	37p
748	48p
FETMOPA	450p
SPECIAL PURPOSE LINEARS	
SG3402N	174p
SG3402T	174p
SG1495D	290p
MFC6040	100p
MFC4000B	70p
T.T.L.	
7402N	38p
7410PC	24p
7420N	24p
7430PC	23p
7473N	48p
7475N	75p
7476N	49p
7489N	660p
7493PC	89p
74121J	85p
74122N	80p
74123N	144p
74150N	210p
RESISTORS	
2% METAL OXIDE	16p for 5
5% CARBON FILM	9p for 5

MINISONIC P.C.B.

118 × 295mm best quality epoxy-glass, roller tinned. Complete with over-lay details and in-structions.

£3·62 inc. VAT and U.K. postage.

V.A.T.
Please add 8% to final total of order

CONSTANTAN WIRE

0·03 ohms/cm as specified for the POWER SLAVES. 20cm lengths **10p**

INTRODUCING THE MINISONIC

C20 AUDIO CASSETTE

£1·15 Inc. VAT, P. & P.

MINISONIC COMPONENT KITS	
V.C.O. (2 required)	£3·85
V.C.F. (1 required)	£4·98
ES/V.C.A. (2 required)	£5·70
Voltage Ref.	£0·57
Ring. Mod. (1 required)	£4·14
Noise Gen. (1 required)	£1·86
Kbd. Control (1 required)	£4·16
HF Osc. and Det.	£1·93
Power Amps	£2·61

All above prices are for single kits of each type and include VAT, P. & P. Full details are included in lists.

Miscellaneous Items	
5 way 180° DIN sockets	27p
5 way 180° DIN plugs	34p
Battery connectors	9p/pair
Hook up wire, 36 colours, ½ metre of each	70p
Min. DPDT toggle switch	£1·20

VAT should be added to quoted price of miscellaneous items.

SAVE BY PURCHASING A COMPLETE SET OF KITS AS DETAILED TOGETHER WITH SWITCH, BATTERY CONNECTORS, HOOK-UP WIRE AND P.C.B.

Price inc. VAT & U.K. Postage £43

EATON AUDIO

P.O. BOX 3, ST. NEOTS
HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.

Buy it with Access

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits. **ALL ARE BRANDED, FULL SPECIFICATION** devices offered at unbeatable prices!

	1/99	100/499	500/1000
7400	£0·15	£0·125	£0·10
7401	£0·15	£0·125	£0·10
7402	£0·15	£0·125	£0·10
7403	£0·15	£0·125	£0·10
7404	£0·18	£0·15	£0·12
7405	£0·18	£0·15	£0·12
7406	£0·375	£0·312	£0·25
7407	£0·375	£0·312	£0·25
7408	£0·15	£0·125	£0·10
7409	£0·15	£0·125	£0·10
7410	£0·15	£0·125	£0·10
7412	£0·195	£0·162	£0·13
7413	£0·345	£0·287	£0·23
7416	£0·345	£0·287	£0·23
7417	£0·345	£0·287	£0·23
7420	£0·15	£0·125	£0·10
7423	£0·27	£0·225	£0·18
7425	£0·27	£0·225	£0·18
7426	£0·27	£0·225	£0·18
7427	£0·27	£0·225	£0·18
7430	£0·15	£0·125	£0·10
7432	£0·27	£0·225	£0·18
7437	£0·27	£0·225	£0·18
7438	£0·27	£0·225	£0·18
7440	£0·15	£0·125	£0·10
7441A	£0·825	£0·687	£0·55
7442	£0·645	£0·537	£0·43
7443	£1·275	£1·062	£0·85
7445	£0·855	£0·712	£0·57
7446	£1·05	£0·875	£0·70
7446A	£1·05	£0·875	£0·70
7447	£1·05	£0·875	£0·70
7447A	£1·05	£0·875	£0·70
7448	£0·855	£0·712	£0·57
7450	£0·15	£0·125	£0·10
7451	£0·15	£0·125	£0·10
7453	£0·15	£0·125	£0·10
7454	£0·15	£0·125	£0·10
7460	£0·15	£0·125	£0·10
7472	£0·255	£0·212	£0·17
7473	£0·315	£0·262	£0·21
7474	£0·315	£0·262	£0·21
7475	£0·465	£0·387	£0·31
7476	£0·315	£0·262	£0·21
7480	£0·435	£0·362	£0·29
7482	£0·75	£0·625	£0·50
7483	£0·825	£0·687	£0·55
7485	£1·275	£1·062	£0·85
7486	£0·315	£0·262	£0·21
7490	£0·465	£0·387	£0·31
7492	£0·465	£0·387	£0·31
7493	£0·465	£0·387	£0·31
7494	£0·495	£0·412	£0·33
7495	£0·63	£0·525	£0·42
7496	£0·72	£0·60	£0·48
74104	£0·315	£0·262	£0·21
74105	£0·315	£0·262	£0·21
74107	£0·315	£0·262	£0·21
74121	£0·315	£0·262	£0·21
74122	£0·45	£0·375	£0·30
74123	£0·63	£0·525	£0·42
74141	£0·75	£0·625	£0·50
74151	£0·69	£0·575	£0·46
74153	£0·69	£0·575	£0·46
74155	£0·69	£0·575	£0·46
74156	£0·69	£0·575	£0·46
74160	£1·005	£0·837	£0·67
74161	£1·005	£0·837	£0·67
74162	£1·005	£0·837	£0·67
74163	£1·005	£0·837	£0·67
74166	£1·425	£1·187	£0·95
74174	£1·20	£1·00	£0·80
74175	£0·975	£0·812	£0·65
74192	£1·275	£1·062	£0·85
74193	£1·275	£1·062	£0·85
74198	£2·10	£1·75	£1·40
74199	£2·10	£1·75	£1·40

To secure the above prices, all orders for these devices must exceed £10 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW! ! !

BRAN TUB ! ! !

- Resistors—wire-wound and carbon.
- Capacitors—silver-mica, paper, ceramic, polyester and electrolytic.
- Controls—volume, pre-set, carbon, wire.
- Diodes—silicon, germanium, zener.
- Transistors—silicon, germaniu

All the above are new and unus stock.

We have made up packs of 2lb gro weight, all are different in conten and contain a mixture of co ponents from the above list. Th is a fantastic, unrepeatable off that will enable you to get a goo stock of spares at a tiny fracti of normal price!

To make things even more interes ing—TWENTY OF THESE BAG ALSO CONTAIN A POUND NOT TWENTY CUSTOMERS WILL VERY PLEASED INDEED!

And the price that we are asking Only **£1·50** including both posta and VAT!

Rush your order now! This off is only made to reduce our surpl stock! It is unlikely that in these da of rising prices we shall ever able to repeat!

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray	£1·00
Developer and Etchant	50p

plus postage

FIBRE-GLASS COPPER LAMINATE

Single sided	75p sq.
Double sided	£1 sq.

Cut in any multiple of 6in to a maximum size of 3ft × 4f

POSTAGE 30p **NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)** **POSTAGE 30p**

SYNTHESISER
Modules by *Dewtron*®

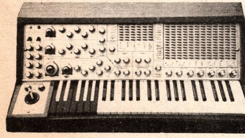

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/ps; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

P.E. ORION

Complete kit of semiconductors £9.9
High quality printed circuit £2.95

THIS GLASS FIBRE P.C.B. IS ROLLER TINNED AND SCREEN PRINTED WITH COMPONENT LOCATIONS.

FERRANTI semiconductors

BFS59	18p	ZTX304	29p	ZTX504	55p	ZS170	14p
BFS60	21p	ZTX310	12p	ZTX510	25p	ZS171	16p
BFS61	21p	ZTX311	14p	ZTX530	29p	ZS172	22p
BFS96	19p	ZTX312	14p	ZTX531	34p	ZS174	26p
BFS97	23p	ZTX313	16p	ZTX550	25p	ZS176	33p
BFS98	23p	ZTX314	17p	ZTX551	27p	ZS178	58p
ZTX107	12p	ZTX330	21p	2N3055	76p	ZS270	15p
ZTX108	9p	ZTX331	23p			ZS271	22p
ZTX109	14p	ZTX382	15p	* DIODES *		ZS272	25p
ZTX212	14p	ZTX383	19p	ZS120	15p	ZS274	29p
ZTX213	15p	ZTX384	23p	ZS121	16p	ZS276	38p
ZTX214	19p	ZTX450	23p	ZS122	19p	ZS278	61p
ZTX239	16p	ZTX451	25p	ZS123	25p		
ZTX300	16p	ZTX500	16p	ZS124	29p	* ZENERS *	
ZTX301	17p	ZTX501	17p	ZS140	26p	KSO30A to	
ZTX302	23p	ZTX502	23p	ZS141	40p	KS180A	28p
ZTX303	18p	ZTX503	18p	ZS142	39p	BZV19 series	15p

MOTOROLA BD699 **£1·10**, BD700 **£1·22**, MJE2955 **£1·30**, MJE3055 **75p.**
SIGNETICS UA748CV operational amplifier **55p** each.
RCA PRICES SLASHED! CA3090Q stereo decoder only **£3·25** each.
ZN414 THE FAMOUS FERRANTI RADIO I.C. Only **£1·32** with data.
SCORPIO Mk. II. Complete kit of semiconductors **£5·65** (State 6V or 12V).

ALL DEVICES SOLD BY US ARE TOP GRADE, BRAND NEW AND TO FULL MANUFACTURER'S SPECIFICATION. We do not sell seconds or rejects. We are specialists in FERRANTI semiconductors and can supply any device to order. S.A.E. for quote. Send S.A.E. for our free data sheet and price list for FERRANTI semiconductors.

POSTAGE AND PACKING 10p. FREE ON ORDERS OVER £3
ALL OUR PRICES INCLUDE VAT

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCS, OL2 6XJ

FREE!

Over 150 ways to ngineer a etter future

Practical Radio & Electronics Certificate course includes a learn while you build ***3 transistor radio kit.*** Everything you need to know about ***Radio & Electronics*** maintenance and repairs for a ***spare time income*** and a ***career*** for a better future.

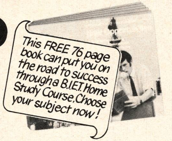
This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

t's how long it will take you to fill in the coupon. Mail it today and ll send you full details and a free book. We have successfully trained *usands* of men at home—equipped them for higher pay and better, re interesting jobs. We can do as much for YOU. A low-cost home ly course gets results fast—makes learning easier and something ook forward to. There are no books to buy and you can pay-as-you-n.

y not do the thing that really interests you? Without losing a day's . *you* could quietly turn yourself into something of an expert. nplete the coupon (or write if you prefer not to cut the page). No gation and nobody will call on you . . . but it could be the best thing ever did.

thers have done it, so can you

esterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this been the best value for money I have ever obtained. a view echoed by two eagues who recently commenced the course."—Student D.I.B.. Yorks.

ompleting your course. meant going from a job I detested to a job that I love. n unlimited prospects."—Student J.A.O.. Dublin.

y training quickly changed my earning capacity and. in the next few years. earnings increased fourfold."—Student C.C.P.. Bucks.

ND OUT FOR YOURSELF

se letters, and there are many more on file at Aldermaston College, speak e rewards that come to the man who has given himself the specialised knowemployers seek. There's no surer way of getting ahead or of opening up opportunities for yourself. It will cost you a stamp to find out how we can *you*. **Write to:**

LDERMASTON COLLEGE

Dept. TPE03, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

MECHANICAL
Society of Engineers— A.M.S.E.(Mech.) ☐
Institute of Engineers & Technicians (A.M.I.E.) ☐
CITY & GUILDS
Gen. Mech. Eng. ☐
Maintenance Eng. ☐
Welding ☐
Gen. Diesel Eng. ☐
Sheet Metal Work ☐
Eng. Inspection ☐
Eng. Metallurgy ☐

ELECTRICAL & ELECTRONIC
CITY & GUILDS
Gen. Electrical Engineering ☐
Electrical Installations ☐
Electrical Maths ☐
Computer Electronics ☐
Electronic Eng. ☐
Practical Radio & Electronics (with kit) ☐

MANAGEMENT & PRODUCTION
Institute of Cost & Management Acctnts. ☐
Computer Programming ☐
Works M'ment. ☐
Work Study ☐
Gen. Production Eng. ☐
Estimating & Planning ☐
Storekeeping ☐
Management Skills ☐
Quality Control ☐

DRAUGHTSMANSHIP
Institute of Engineering Designers (A.M.I.E.D.) ☐
General Draughtsmanship ☐
Elec. Draughtsmanship ☐
Architectural Draughtsmanship ☐
Technical Drawing ☐

RADIO & TELECOMMUNICATIONS
CITY & GUILDS
Telecoms. ☐
Gen. Radio & TV Eng. ☐
Radio Amateurs Exam ☐
Radio Servicing ☐

AUTOMOBILE & AERONAUTICAL
Institute of the Motor Industry ☐
A.M.I.I. ☐
MAA/IMI ☐
CITY & GUILDS
Auto Eng. ☐
Gen. Auto Eng. ☐
Motor Mechanics ☐
Auto Diesel Eng. ☐
Garage M'ment ☐
AEC Aero Engineering Exams ☐
Gen. Aero Eng. ☐

CONSTRUCTIONAL
Institute of Building L.I.O.B. ☐
A.B.T. Clerk of Works ☐

Construction Surveyors Institute L.C.S.I. ☐
CITY & GUILDS
General Building (all branches) ☐
Heating & Vent. ☐
Inst. Clerk of Works ☐
Site Surveying ☐
Health Engineering ☐
Road Construction ☐
Quantities Estimates ☐
Hydraulics ☐
Structural Eng. ☐

GENERAL
Agricultural Eng. ☐
Council of Eng. Institutions ☐
Farm Science ☐
Plastics ☐

Supplementary courses for Nat. Certificates.

G.C.E.
– choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, TPE03
Dept. TPE03, Reading RG7 4PF

NAME
Block Capitals Please
ADDRESS ....

.... POST CODE ....

OTHER SUBJECTS ....

.... AGE ....

Accredited by C.A.C.C. *Member of A.B.C.C.*

---

ished approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London. EC4A 4AD. Printed in England by Chapel River Press, Andover. ts. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd. isher's Subscription Rate including postage for one year, Inland £3·85, Overseas £4·70, U.S.A. and Canada $13·00. national Giro facilities Account No. 5122007. Please state reason for payment, "message to payee". tical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise osed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold red out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial er whatsoever.

Henry's Radio

LARGEST SELECTION OF ELECTRONIC
COMPONENTS AND EQUIPMENT.
LOW PRICES- MEAN LESS VAT.

You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6–ICs, 10–transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15¼in × 2¾in × 6⅝in mains operated. Free teak sleeve with every kit.

£31·00 (Carriage 50p) (also built and tested **£37·50**)

STEREO FM TUNER Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8in × 2¾in × 6⅝in. Complete kit with teak sleeve **£21·00** (Carriage 50p)

(also built and tested **£24·95**)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES
Tuners–Power Suppliers–Amplifiers

AMPLIFIERS (all single channel unless stated)

4–300	9 volt 300MW	1·75
2004	9 volt 250MW	2·70
104	9 volt 1 watt	3·10
304	9 volt 3 watt	3·95
555	12 volt 3 watt	4·10
5555ST	12 volt 1½ + 1½ watt	5·95
E1208	12 volt 5 watt	5·10
608	24 volt 10 watt	4·95
410	28 volt 10 watt	4·95
620	45 volt 30 watt	9·95
Z40	30/35 volt 15 watt	5·45
Z60	45/50 volt 25 watt	6·95
SA6817	24 volt 6 + 6	10·20

Amplifiers with controls

E1210	12 volt 2½ + 2½ watts 8 ohms	8·25
R500	Mains 5 watts 4–16 ohms	6·30
SAC 14	Mains 7 + 7 watts 8 ohms	11·75
SAC30	Mains 15 + 15 watts 8 ohms	14·95
CAO38	9 volt 1½ + 1½ watts 8 ohms	6·95
CAO68	12 volt 3 + 3 watts 8 ohms	10·50

AM/FM MODULES

Mullard LP 1186 FM tuner (front end) with data 10·7 MHZ O/P	4·85
Mullard LP 1157 AM/module	2·50
Mullard LP 1171 AM/FM module	4·50
Mullard LP 1179 AM/FM front end	4·85
Mullard LP 1185 10·7 MHZ IF unit with data	4·50

FM & AM TUNERS & DECODERS

FM5231 (TU2) 6 volt FM tuner	7·95
TU3 12 volt version (FM use with Decoder)	7·95
SD4912 Stereo Decoder for TU3 12 volt	7·95
SP62H 6 volt stereo FM tuner	11·95
A1007 9 volt MW–AM tuner	4·80
Sinclair 12/45 volt FM tuner stereo recorder for above	7·45
A1018 9 volt FM tuner in cabinet	13·95
A1005M (S) 9–12 volt Stereo decoder FM for above	7·50
1067 12V Stereo decoder gen. purpose	6·50
Gorler Permeability FM tuner (front end) 10·7 MHZ O/P	4·20

PREAMPLIFIERS

Sinclair	Stereo 60 Preamplifier	6·75
E1300	Cart/Tape Mic Inputs 9 volt	2·85
E1310	Stereo 3–30 mV mag cart 9 volt	4·75
FF3	Stereo 3 mV tape head 9 volt	4·95
3402	Stereo 5–20 mV Mag cart mains	5·95
EQ25	Mono 3–250 mV Tape/Cart/Play 9 volt	5·95

POWER SUPPLIES MAINS INPUT

(*chassis-rest cased)

470C 6/7½/9V 300MA with ad'rs	2·25
P500 9V 500 MA	3·20
HC244R 3/6/7½/9V, 400 MA stabilised	5·50
*P11 24V ½A 3·30	3·30
*P15 28V, ½A	3·30
*P1080 12V 1A 4·70	7·80
*P1081 45V 0·9A	7·80
P12 4½–12V, 0·4–1A	7·15
SE101A 3/6/9/12V 1A stabilised	12·75
P1076 3/4½/6/7½/9/12V, ½A	4·20
SE800A 1–15 VOLT 0–½A stabilised	17·50

EMI SPEAKERS SPECIAL PURCHASE

13in × 8in chassis speakers (Carr/packing 30p each or 50p pr.)

*150TC 10 watts 8 ohms twin cone **£2·20**

*450 10 watts 4, 8, 15 ohm with twin tweeters and crossover **£3·85** each

EW 15 watt 8 ohm with tweeter **£5·25**

350 20 watt 8, 15 ohm with tweeter **£7·80** each.

* Polished wood cabinet **£4·80** carr., etc. 35p each or 50p pair.

UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post/packing 25p each).

TYPE C variable tuning **£2·50**

TYPE B 4-button push-button (adjustable) **£3·50**

PA DISCOTHEQUE LIGHTING EQUIPMENT

Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request. CALL IN AND SEE FOR YOURSELF at **HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, TEL. 01-723 6963**

NOW OPEN SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains galore. Goodie bags. Components, etc.

Watch for further developments!

EP27 Low Cost Seven Segment Led. Digit Height ⅓in. **£1·35.** P. & P. 15p.
L450 rechargeable battery 2V 400mA/hr **50p.** P. & P. 15p.
Philips 12V Fluorescent Invertor for 8W fluorescent tube. Supplies with instr. and tube **£3·50.** P. & P. 30p.
STC and ITT Miniature Relays. 150R 6V 2 p.c.o.; 180R 6/12V 2 p.c.o.; 185R 12V 2 p.c.o.; 1250R 12/55 2 p.c.o.; 1700R 18/24V 2 p.c.o.; 1800R 24V 4 p.c.o.; 2500R 18/24V 2 p.c.o.; 4000R 24V 2 p.c.o.
BRAND NEW **60p.** P. & P. 15p.
10·7 MHz Miniature Ceramic IF Filter. **40p** per pair. P. & P. 15p.
SL414 Plessey 5W Power Amp I.C. **£1·65.** P. & P. 15p.
40KHz Ultrasonic Transducers. **£5·90.** P. & P. 25p. TAA 960 40KHz amp **£1·75.** P. & P. 15p.

TEST EQUIPMENT MULTIMETERS

(Carr./packing 35p)

	£ p
U4324 20kΩ/V with case	9·25
U435 20kΩ/V with steel case	8·75
U4313 20kΩ/V with steel case	12·50
U4317 20kΩ/V with case	16·50
U4341 33kΩ/V plus transistor steel case	10·50
U4323 20kΩ/V plus 1kHz OSC with case	7·70
ITI-2 20kΩ/V slim type	5·95
THL33D (L33DX) 2kΩ/V Robust	7·50
TP5SN 20kΩ/V (Case £2)	8·25
TP10S 2kΩ/V	6·25
TW20S 20kΩ/V	10·00
TW50K 50kΩ/V	11·25
EP10KN 10kΩ/V	9·95
AF105 50kΩ/V Deluxe (case £1·90)	12·50
S100TR 100kΩ/V plus transistor tester	22·50

NEW REVOLUTIONARY SUPERTESTER 680R

680R Multi-tester	18·50
†TE40 AC Multivoltmeter	19·75
†TE15 Grid dip meter 440kHz-28mHz	19·50
†TE65 28 Range valve voltmeter	22·50
†TE20D RF Generator 120kHz-500mHz	18·95
†TE22D AF Generator 20Hz-200kHz	19·95
*HM350 in circuit transistor tester	19·50
*C3025 Deluxe meter 1–300mHz	6·95
*TT145 Compact transistor tester	14·75
†G3–36 R/C osc. 20Hz-200kHz	19·75
*C3042 SWR Meter	5·75
*SE350A Deluxe signal tracer	12·95
*SE400 Mini-lab. all in one tester	15·50
C1–5 Scope 500,000kHz (carr. £1)	43·00
*C3043 5 CH F/A meter 1-300mHz	5·75
Resistance sub box {Post, etc.,	2·40
Capacitor {20p	2·10
2A variable transformers (carr. £1)	6·55
Radio activity counter 0–10r (carr. £1)	9·97
Mains unit for above (carr. 50p)	3·75

TAPE HEADS

Marriot XRSP/17 ½ Track High	2·50
Marriot XRSP/18 ½ Track Med.	3·50
Marriot XRSP/36 ¼ Track Med.	5·00
Marriot XRSP/63 ½ Track High	1·75
Marriot Erase Heads for XRSP 17/18/36 (XES11)	75
Marriot BX1ZE 343 ½ Track Erase	75
R/RPI Record/Play ½ Track	45
H/RP Single Track Rec/Play	35
Bogen Type UL290 Erase	1·50
Miniature Stereo Cassette Rec/Play	2·25

(P.P. 15p)

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8–16 ohm load. 30 volt max. d.c. operation, complete with data. Price **£1·50** each or 2 for **£2·85.** Printed Circuit Panels **50p.**

CALCULATORS

Sinclair Cambridge Kit. **£13·50**
Sinclair Cambridge (Built). **£17·50**
Sinclair Memory. **£22·50**
Sinclair Scientific. **£26·95**
Sinclair Scientific Kit. **£18·50**

VAT 8% EXTRA ON ALL ITEMS

EXTRA DISCOUNTS

Semiconductors—Any one type or mixed S Series 'IC', 12—extra 10%; 25—extra 15%; 10 extra 20%.

74 SERIES AND LINEAR

	£ p		£ p	
SN7400N	0·16	SN7485N	1·63	SN74191N
SN7401N	0·16	SN7486N	0·47	SN74192N
SN7402N	0·16	SN7489N	3·87	SN74193N
SN7403N	0·16	SN7490N	0·70	SN74194N
SN7404N	0·16	SN7491AN	1·00	SN74195N
SN7405N	0·16	SN7492N	0·70	SN74196N
SN7406N	0·42	SN7493N	0·70	SN74197N
SN7407N	0·42	SN7494N	0·80	SN74198N
SN7408N	0·28	SN7495N	0·90	SN74199N
SN7409N	0·28	SN7496N	0·95	**RCA**
SN7410N	0·16	SN7497N	3·87	CA3012
SN7411N	0·25	SN74100N	1·89	CA3014
SN7412N	0·30	SN74104N	0·58	CA3018
SN7413N	0·36	SN74105N	0·53	CA3019
SN7414N	0·72	SN74107N	0·45	CA3020
SN7416N	0·36	SN74110N	0·58	CA3022
SN7417N	0·36	SN74111N	0·88	CA3028A
SN7420N	0·16	SN74116N	1·89	CA3036
SN7421N	0·33	SN74118N	0·90	CA3046
SN7422N	0·25	SN74119N	1·68	CA3048
SN7423N	0·37	SN74120N	0·95	CA3075
SN7425N	0·37	SN74121N	0·50	CA3081
SN7426N	0·32	SN74122N	0·70	CA3089E
SN7427N	0·37	SN74123N	1·00	CA30900
SN7428N	0·40	SN74125N	0·65	**Signetics**
SN7430N	0·16	SN74132N	0·72	NE555
SN7432N	0·37	SN74141N	0·90	NE560B
SN7433N	0·37	SN74145N	1·26	NE561B
SN7437N	0·37	SN74150N	1·75	NE562B
SN7438N	0·37	SN74151N	1·00	NE567B
SN7440N	0·22	SN74153N	0·95	**Motorola**
SN7441AN	0·92	SN74154N	2·00	MC1303L
SN7442N	0·79	SN74155N	1·00	MC1304P
SN7443N	1·27	SN74156N	1·00	MC1310P
SN7444N	1·27	SN74157N	0·95	MC1458CF
SN7445N	1·60	SN74160N	1·38	MC1710CC
SN7446N	1·89	SN74161N	1·38	MFC4000P
SN7447AN	1·60	SN74162N	1·38	MFC4010P
SN7448N	1·27	SN74163N	1·38	MFC6040P
SN7450N	0·16	SN74164N	1·76	**Others**
SN7451N	0·16	SN74165N	1·76	TBA800
SN7453N	0·16	SN74166N	1·60	SN76003N
SN7454N	0·16	SN74167N	3·00	SN72741P
SN7460N	0·16	SN74170N	2·52	SN72748P
SN7470N	0·36	SN74173N	1·66	702C
SN7472N	0·38	SN74174N	1·57	709C
SN7473N	0·41	SN74175N	1·10	723C
SN7474N	0·42	SN74176N	1·26	728C
SN7475N	0·59	SN74177N	1·26	741C
SN7476N	0·45	SN74180N	1·26	747C
SN7480N	0·60	SN74181N	3·95	748C
SN7481N	1·10	SN74182N	1·26	LM309K
SN7482N	0·87	SN74184N	1·80	TAA960
SN7483N	1·10	SN74185N	1·80	**Sinclair**
SN7484N	1·00	SN74190N	2·00	IC12, 6W amp

COSMOS INTEGRATED CIRCUITS. FULL RANGE IN ST

	£ p		£ p	
AAZ13	0·12	BLY36	6·00	TIP42A
AC107	0·51	BSX20	0·13	TIS43
AC128	0·15	BU105	2·20	V405A
AC187	0·21	BY100	0·27	ZTX108
ACY17	0·40	BY127	0·12	ZTX300
ACY39	0·78	BYZ13	0·42	ZTX302
AD149	0·50	C1060	0·54	ZTX500
AD161	0·44	GET111	0·72	2N697
AD162	0·44	GET115	0·90	2N706
AF117	0·24	GET880	0·60	2N930
AF118	0·57	LM309K	2·00	2N987
AF139	0·41	MAT121	0·25	2N1132
AF186	0·48	MJE340	0·47	2N1304
AF239	0·44	MJE520	0·63	2N1613
ASY27	0·33	MJE3055	0·77	2N1671
BA115	0·10	MJE2955	1·27	2N2147
BAX13	0·05	MPF105	0·36	2N2160
BC107	0·14	NKT404	0·66	2N2926
BC108	0·13	OA5	0·72	2N3053
BC109	0·14	OA81	0·18	2N3054
BC109C	0·16	OA200	0·08	2N3055
BC113	0·15	OA202	0·06	2N3440
BC147	0·10	OC28	0·66	2N3442
BC148	0·08	OC35	0·55	2N3525
BC149	0·10	OC36	0·60	2N3614
BC169C	0·15	OC44	0·20	2N3702
BC182	0·12	OC45	0·20	2N3714
BCY32	0·85	OC71	0·18	2N3771
BCT39	1·50	OC72	0·28	2N3773
BCY55	2·64	OC77	0·54	2N3790
BCY70	0·18	OC81	0·29	2N3819
BCY71	0·22	OC83	0·27	2N3886
BCY72	0·12	OC140	1·14	2N3903
BD124	0·65	OC170	0·30	2N4002
BD131	0·42	OC200	0·54	2N4126
BF115	0·20	OC202	0·90	2N4871
BF180	0·36	OCP71	1·20	2N5457
BF194	0·10	ORP12	0·60	2S303
BFX13	0·26	ORP60	0·55	40550
BFX34	0·70	P346A	0·18	40361
BFX88	0·24	TIL209	0·20	40362
BFY50	0·21	TIP29A	0·45	40408
BFY51	0·20	TIP30A	0·57	40486
BFY64	0·36	TIP31A	0·61	40636
BFY90	0·31	TIP41A	0·74	40430

**SEND FOR FREE LIST NO. 36 FOR COMPLETE RANGE
SEMI-CONDUCTORS**

Henry's Radio

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road. London W2 1BW

Hi Fi and
Electronics
Centres Ope
9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. E.&O.E